


- ***A Better CMOS Gain Stage:***

- *No body effect issue*
- However, there are *some design issues*
- $M_n$ - $M_p$  have *same magnitude* of the *threshold voltage*:

$$V_{TN0} = |V_{TP0}|$$

- *Process transconductance parameters:*
 
$$k'_N = \mu_n C'_{ox} \quad \text{and} \quad k'_P = \mu_p C'_{ox}$$




**Circuit Schematic**


- *Oxide capacitance per unit area* ( $C'_{ox} = \epsilon_{ox} / t_{ox}$ )  
*same for both devices*, since they have *same*  
 $t_{ox}$
- However,  $\mu_n \sim 2\mu_p$  (*for Si*)
- Thus,  $k'_N = 2k'_P$
- *Ideal DC bias point* of the circuit is  $V_I = V_O = V_{DD}/2$  (yields  $V_{GSn} = |V_{GSp}|$  and  $V_{DSn} = |V_{DSp}|$ )
- Can be achieved only if the stage is *completely balanced* (*same threshold voltage magnitude* and *same device transconductance parameter*)
- Thus,  $k_N$  and  $k_P$  *need to be matched*

- *Can be achieved by making  $(W/L)_p = 2(W/L)_n$*
- If *CLM effect* is *not that important*, or if  $\lambda_n = \lambda_p$ , then this procedure works out *just fine*
- However, if  $\lambda_n \neq \lambda_p$ , then for *balancing the circuit*, the following relation *must hold* (*show!*):
 
$$k_p(1 + \lambda_p V_{DD}/2) = k_n(1 + \lambda_n V_{DD}/2)$$
- Under this condition,  $k_n \neq k_p$ , but the circuit will be *perfectly matched and balanced*
- Known as: *Stage unmatched by nature, but matched by performance*

➤ *ac Analysis:*

 

ac Midband Equivalent

 

Simplified Equivalent

➤ *By inspection:*

$$A_v = - (g_{mn} + g_{mp})R_0$$
$$= - (g_{mn} + g_{mp})/(g_{0n} + g_{0p})$$


$$R_0 = r_{0n} || r_{0p} = (g_{0n} + g_{0p})^{-1}$$

➤ *Very high  $A_v$  and  $R_0$*


➤ *Extremely popular* and *widely used circuit*

➤ Sometimes, *level shifters* are used at the *input* for *better ease* of application

- *Actively Loaded DA:*

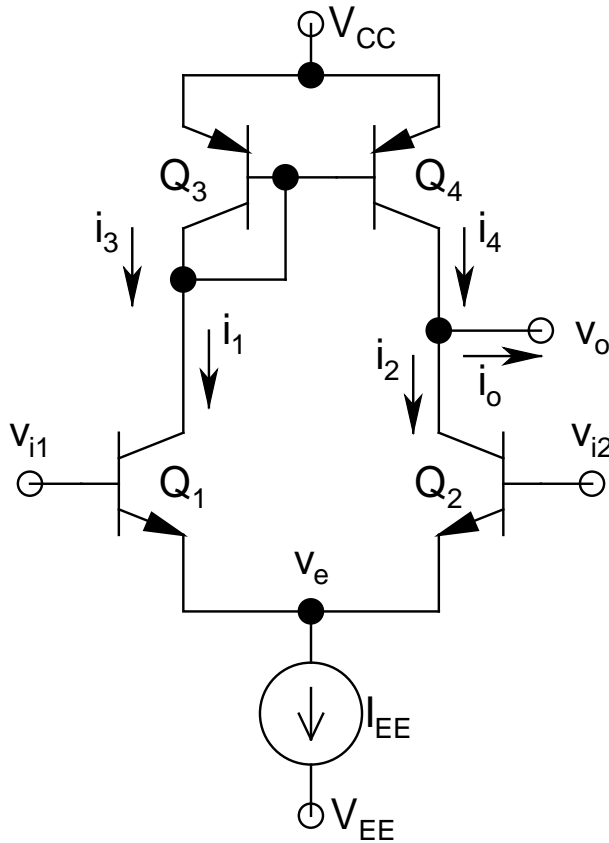

**BJT Implementation**

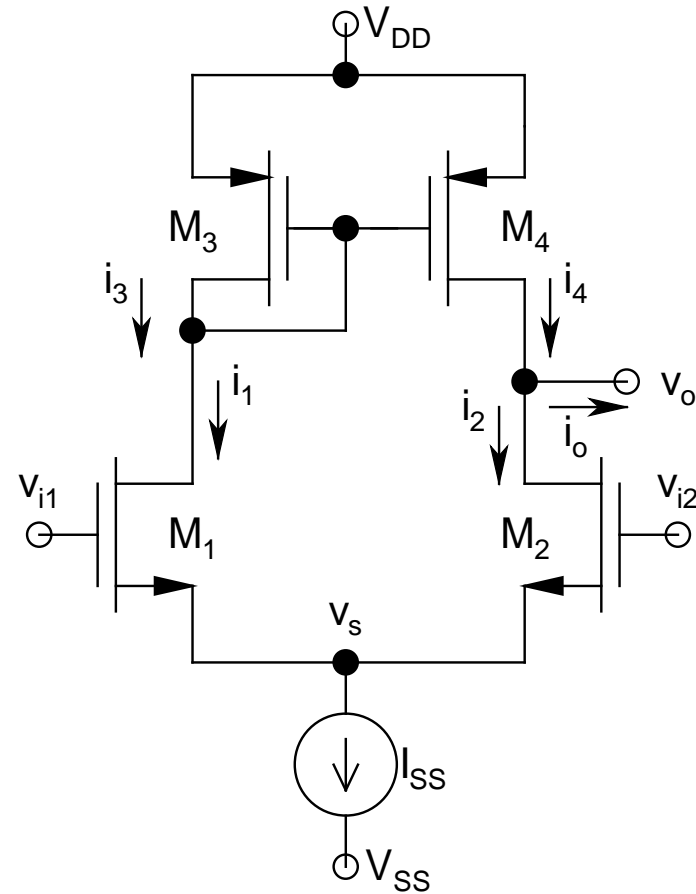

**MOS Implementation**