
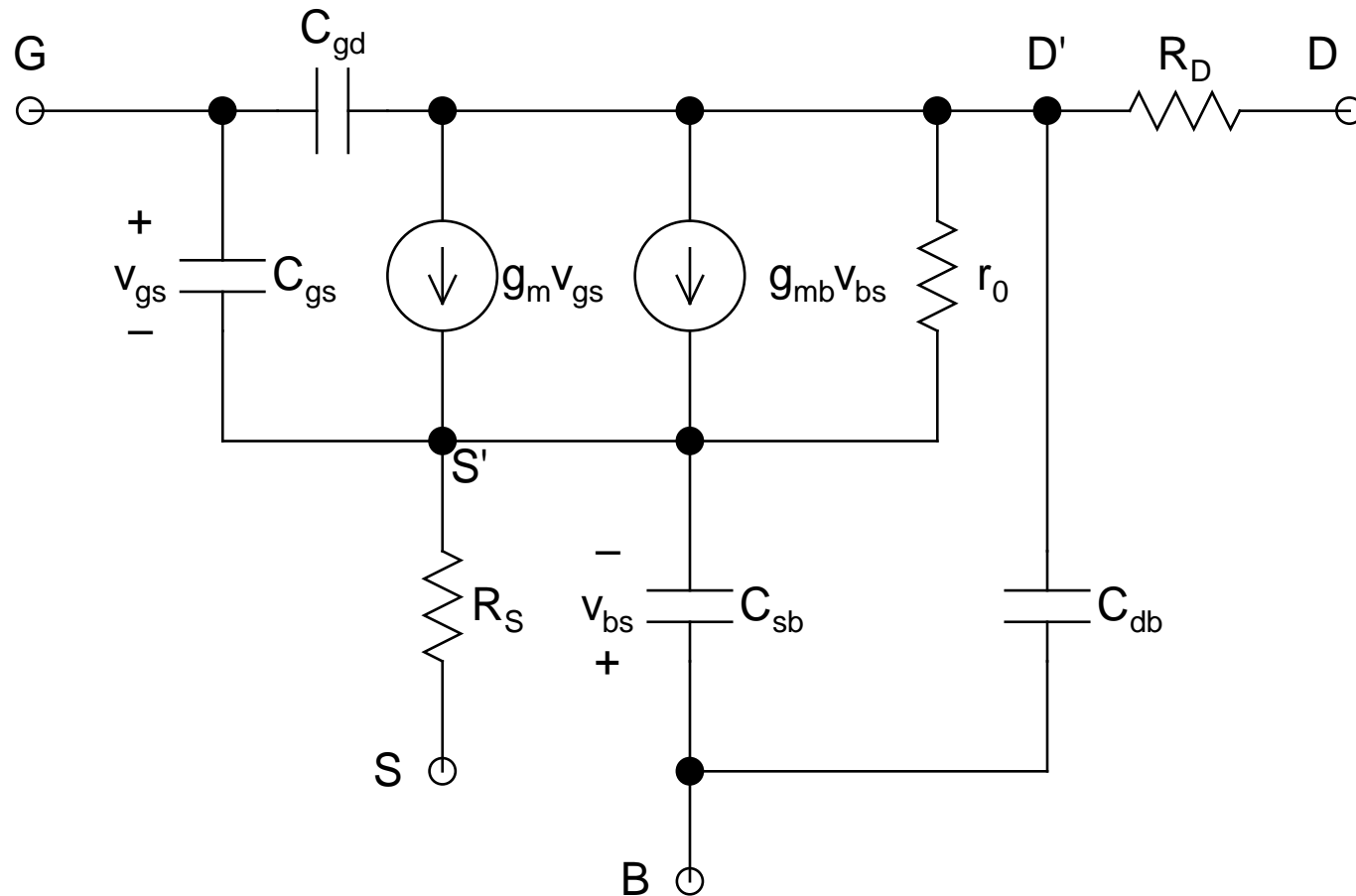


The Hybrid- π Model

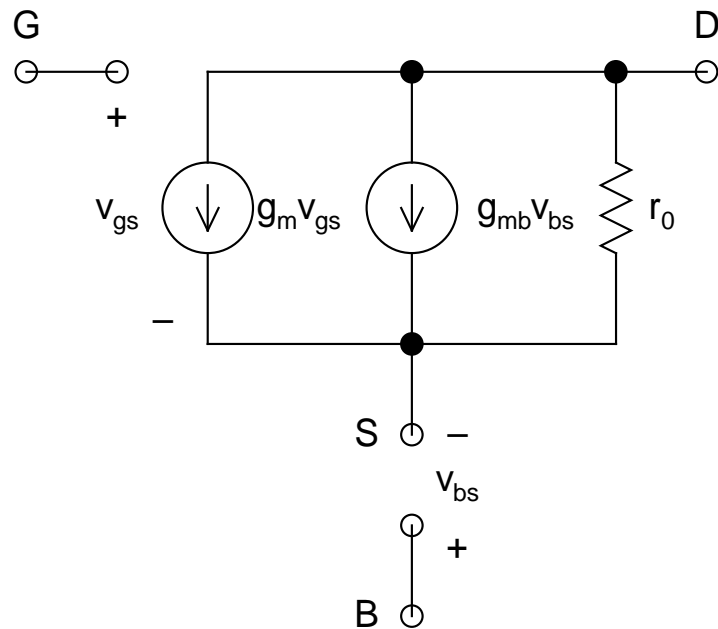


- *Simplifications:*


- R_S and R_D can be safely neglected
- For *low to moderate frequencies*, the *capacitive reactances* of all the capacitances will be *extremely large* \Rightarrow *can be neglected*
- *If both B and S are connected to fixed DC potentials*, *current source $g_{mb}v_{bs}$ disappears*
- Leads to the *Low-Frequency T-Model*, having only *two components*: $g_m v_{gs}$ and r_o
- *Simplest possible equivalent results if r_o is also neglected (ideal current source!)*



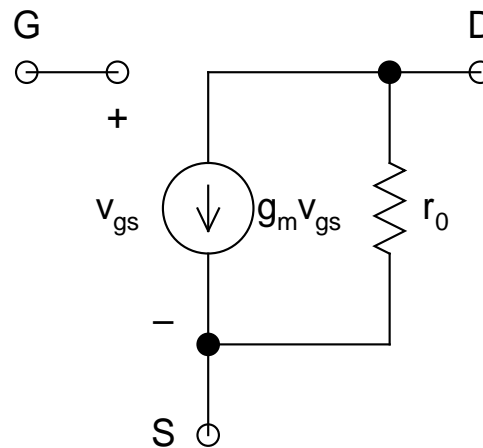**Low-Frequency T-Model
With Body Effect**




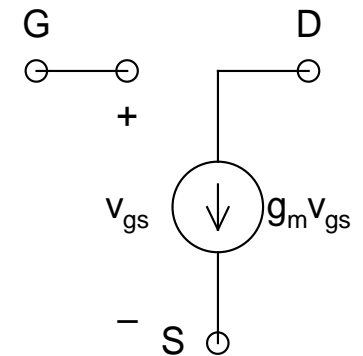
**Low-Frequency T-Model
Without Body Effect**



Without CLM

Frequency Specification of MOSFETs

- Only *Unity-Gain Frequency* (f_T)

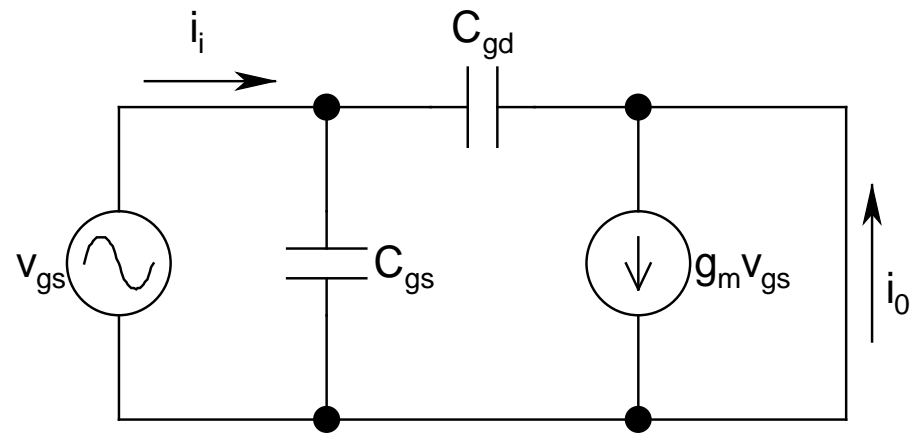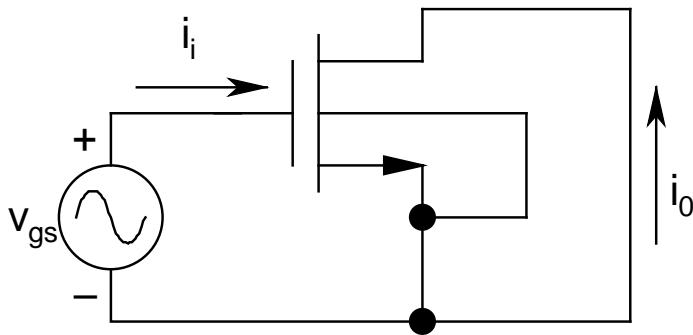

- $i_0 \approx g_m v_{gs}$ (neglecting *reverse transmission* through C_{gd})
- $i_i = j\omega(C_{gs} + C_{gd})$

$$\Rightarrow \frac{i_0(j\omega)}{i_i(j\omega)} = \frac{g_m}{j\omega(C_{gs} + C_{gd})}$$

$$\text{At } f = f_T, |i_0/i_i| = 1$$

$$\Rightarrow f_T = \frac{g_m}{2\pi(C_{gs} + C_{gd})}$$

- *Remarkable similarity with that for BJT*

- **Maximum Operable Frequency** (f_{\max}):

- *Maximum possible f_T*

- Noting that $C_{gs} \gg C_{gd}$, **neglecting C_{gst}** , and *substituting the expressions for C_{gsi} and g_m* :

$$f_{\max} = f_T \Big|_{\max} = \frac{3\mu_n V_{GT}}{4\pi L^2}$$

- $f_{\max} \propto 1/L^2$

- *Thrust towards making L as small as possible*

- $f_{\max} \propto V_{GT}$

- ***Making V_{GT} large may be detrimental!***