

DEPARTMENT OF ELECTRICAL ENGINEERING
INDIAN INSTITUTE OF TECHNOLOGY, KANPUR

EE 210

MINI-QUIZ #4A

17.2.21

Total Marks: 10

Total Time: 10 mins.

Assume $V_A = 130$ V (for both Q_1 and Q_2), and $V_0 \ll V_A$.

- Choose R such that a change in V_0 of 65 mV produces a change in I_0 of 100 nA. Assume Q_1 and Q_2 are perfectly matched, and both have very high β .
- What is the *least* value of β (*same for Q_1 and Q_2*) that you would allow such that I_0 does not deviate by more than 5% of its nominal value?
- Rework part a) if Q_1 and Q_2 are mismatched with $I_{S1} = 2I_{S2}$, but β remains very large.

