

➤ *Solving Eqs.(1) and (2):*

$$I_{c1} = I_{EE}/[1 + \exp(-V_{id}/V_T)]$$

$$I_{c2} = I_{EE}/[1 + \exp(V_{id}/V_T)]$$

➤ *Extremely interesting results:*

- *For $V_{id} = 0$, $I_{c1} = I_{c2} = I_{EE}/2$*

I_{EE} shared equally between Q_1 and Q_2


- *For positive V_{id} , $I_{c1} \uparrow$ and $I_{c2} \downarrow$*

For negative V_{id} , $I_{c1} \downarrow$ and $I_{c2} \uparrow$

But for both cases, their sum is constant and equal to I_{EE}

- *For $V_{id} > 4V_T$, $I_{c1} \rightarrow I_{EE}$ and $I_{c2} \rightarrow 0$*

For $-ve V_{id}$, with $|V_{id}| > 4V_T$, $I_{c2} \rightarrow I_{EE}$ and $I_{c1} \rightarrow 0$

 

The Current Transfer Characteristics of an npn DA

- **Linear Range** of the circuit $\sim \pm 4V_T$ ($\sim \pm 100$ mV at room temperature)
- This range is known as the **analog domain**

- *For V_{id} out of this range, either Q_1 or Q_2 carries the entire I_{EE} , with the other remaining off \Rightarrow acts as a **Current Switch***
 - This is the *digital domain*
- *For analog applications, both devices must be on and in the linear range of the I_c - V_{id} characteristic*
- *The highest linearity, which is also the region of the highest g_m ($= \partial I_c / \partial V_{id}$), occurs around $V_{id} = 0$ ($V_{i1} = V_{i2}$)*
- *This is the most preferred DC bias point*

- *At this point, $I_{C1} = I_{C2} = I_{EE}/2$, and all small-signal parameters of Q_1 and Q_2 are identical to each other*
- *This particular biasing scheme leads to a **Balanced DA**, having properties:*
 - *Q_1 - Q_2 completely matched*
 - *R_C s identically equal to each other*
 - *Both inputs connected to DC ground or to the same DC potential (ground is the best choice, obviously)*
 - *Both Q_1 and Q_2 biased at $I_{EE}/2$*
- *We will consider only **Balanced DAs***

➤ *Unbalanced DAs create anomalies in circuit operation*

➤ Now, the *output voltages*:


$$V_{o1} = V_{CC} - I_{c1}R_C \text{ and } V_{o2} = V_{CC} - I_{c2}R_C$$

➤ Define *Differential-Mode Output Voltage*:

$$V_{od} = V_{o1} - V_{o2} = I_{EE}R_C \tanh[-V_{id}/(2V_T)]$$

- V_{od} (*positive maximum*) = $I_{EE}R_C$
- V_{od} (*negative minimum*) = $-I_{EE}R_C$
- At $V_{id} = 0$, $V_{od} = 0$

 ❖ *Permits direct coupling of stages without the need of any coupling capacitor*



Linear Range = $\pm 4V_T$
($\sim \pm 100$ mV at
room temperature)

The Voltage Transfer
Characteristics
of an npn DA

➤ **DC Biasing:**

- $V_i = V_I + v_i$ (V_I : **DC bias voltage**, v_i : **ac small-signal voltage**)
- $I_c = I_C + i_c$ (I_C : **DC bias current**, i_c : **ac small-signal current**)
- *The ideal DC bias point should be $V_{I1} = V_{I2}$*
 $\Rightarrow I_{C1} = I_{C2} = I_{EE}/2$
- *Thus, any arbitrary DC voltage can be applied at the bases of Q_1 - Q_2 , provided they are same*
 \Rightarrow **Ideal choice: ground**
 \Rightarrow **Necessitates a negative power supply for proper biasing**