

**ESc201A Home Assignment 1 Aug. 05, 2019.**  
**Solutions of the HA#1 will be in copy point and Brihaspati on 09/08/19.**

Consider all voltage and current sources to be ideal.

1. Use the Node-voltage method to calculate the power delivered by the dependent voltage source of fig.1.1.

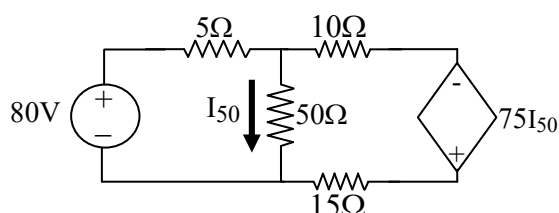


Figure 1.1

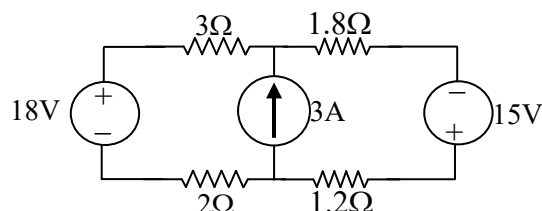


Figure 1.2

2. Use the Mesh-current method to find the total power dissipated in the circuit of fig. 1.2.
3. Use the node-voltage method to find  $V_1$  and  $V_2$  in the circuit in fig. 1.3.

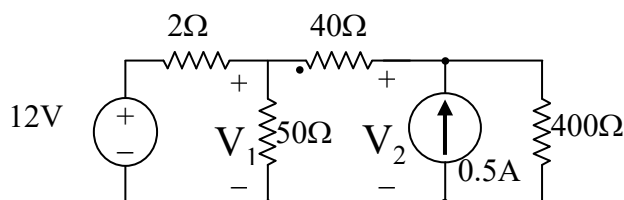


Figure 1.3

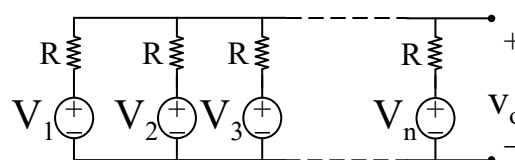


Figure 1.4

4. Use the node-voltage method to show that the output voltage  $V_o$  in the circuit in fig. 1.4 is equal to the average value of the source voltages.
5. Use the Mesh-current method to find all the branch currents of circuit in fig. 1.5. Hence show that the total power dissipated in the circuit is equal to the total power developed in the circuit.

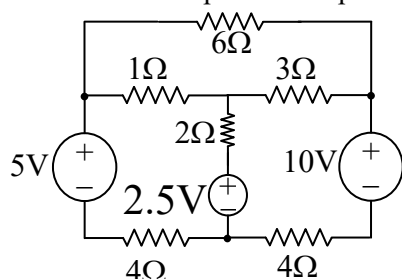


Figure 1.5

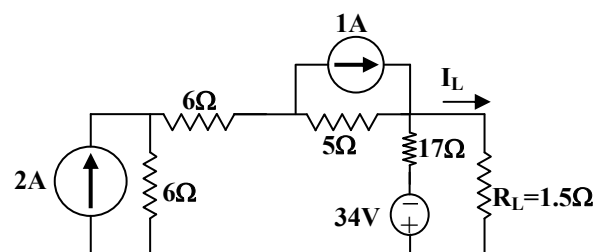


Figure 1.6

6. (a) Using mesh analysis find the current  $I_L$  in fig. 1.6. (b) Using source transformation, show that the same result can be obtained by just really one calculation.
7. Use the principle of superposition to solve for  $I_o$  and  $V_o$  in the circuit in fig. 1.7.

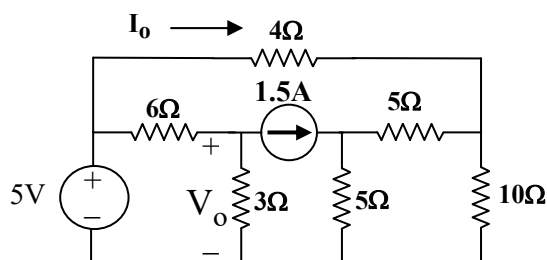


Figure 1.7

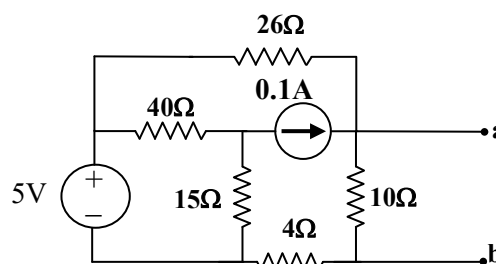


Figure 1.8

8. Find the Thevenin Equivalent of the circuit of fig. 1.8 with respect to the terminals 'a' and 'b'. Show that the  $R_{Th}$  can be obtained in this case without calculating the  $I_{sc}$ , by nulling the independent sources.
9. A Wheatstone bridge, shown in Fig. 1.9, is balanced (no Galvanometer current) when  $R_2=3k\Omega$  (This resistance come with a tolerance of 0.1%). If the galvanometer has a resistance of  $50\Omega$ , how much current will the galvanometer detect when the bridge is unbalanced, by having  $R_2$  off by 0.1%? (Hint: Find the Thevenin equivalent with respect to the galvanometer terminals when  $R'_2$  is now  $1.001 \times R_2$ .)

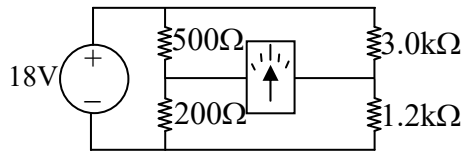


Figure 1.9

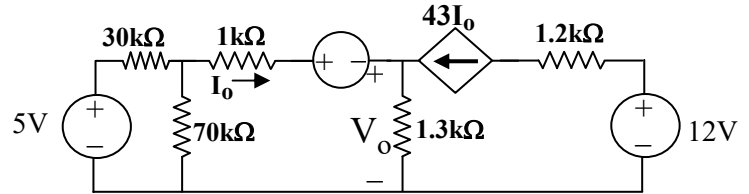


Figure 1.10

10. When a voltmeter is used to measure the voltage  $V_o$  in fig. 1.10 it reads 5.5 V. What is the resistance of the voltmeter?
11. Find the Thevenin equivalent of the circuit shown in fig. 1.11, with respect to the terminals (a, b).

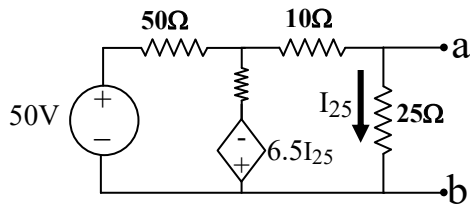


Figure 1.11

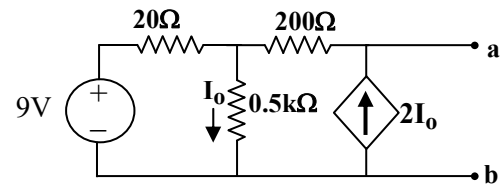


Figure 1.12

12. Find the Norton's equivalent of the circuit shown in fig. 1.12 between the terminals a,b.