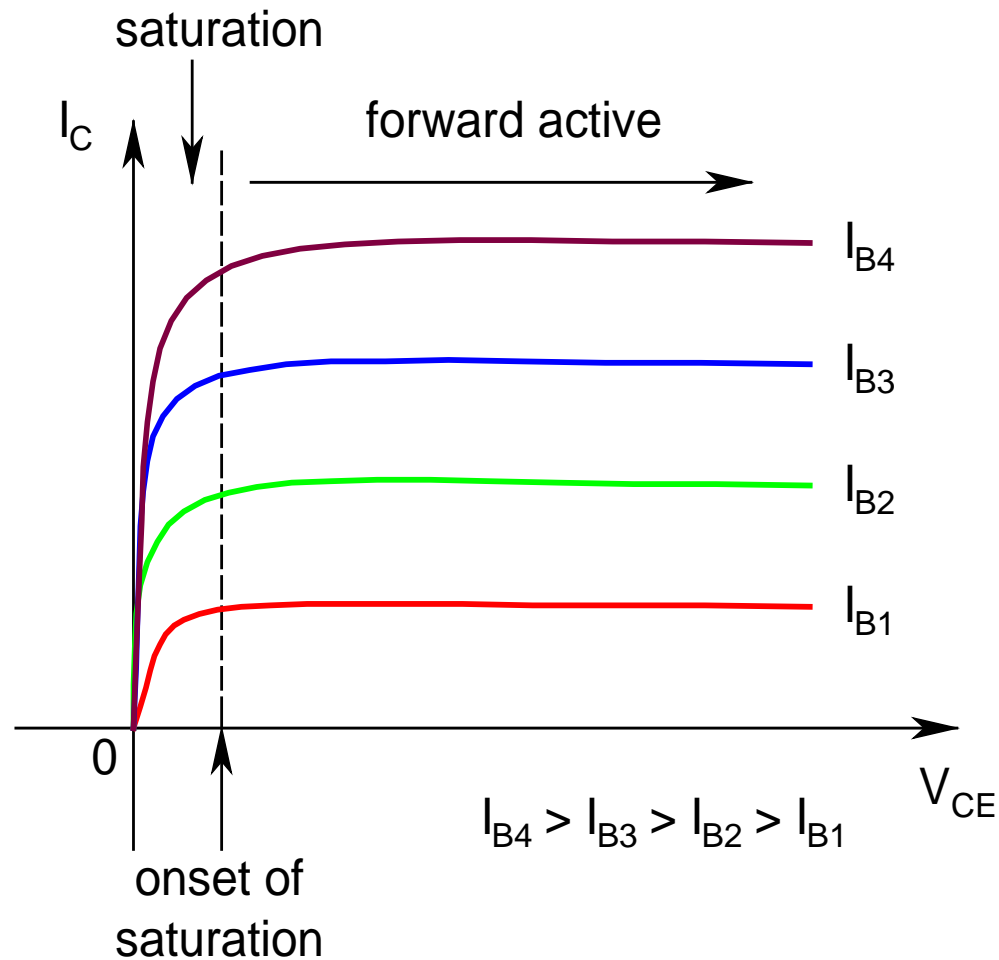


Current-Voltage Relation

- **BE junction** basically a **diode**
 - $I_E = I_{ES} \exp(V_{BE}/V_T)$ ($V_{BE} > 4V_T$)
 - I_{ES} : **Reverse Saturation Current of BE junction**
- A **fraction** α of I_E reaches **collector**
 - $I_C = \alpha I_E = I_S \exp(V_{BE}/V_T)$
 - $I_S (= \alpha I_{ES})$: **Saturation current of the BJT**
- The **difference** between I_E and I_C is I_B
 - $I_B = I_E - I_C$

Output Characteristic



- *Quick Estimate:*
 - Under *forward bias*, $V_{BE} \sim 0.7 \text{ V}$
 - *Justification:*
 - $V_{\gamma} \sim 0.6 \text{ V}$
 - 0.7 V is 100 mV above $V_{\gamma} \Rightarrow$ *junction sufficiently forward biased*
 - I_C - V_{BE} relation *exponential* \Rightarrow A *little change* in V_{BE} can cause a *large change* in I_C
 - *Heuristic estimate: not accurate*, however, *extremely useful* for a *quick hand-calculation*
- $V_{CE} = V_{BE} - V_{BC}$ (*applying chain rule*)

- Thus, for $V_{CE} > 0.7 \text{ V}$, V_{BC} *negative*
 - BC junction *reverse biased* and FA operation is *maintained*
- As $V_{CE} \rightarrow 0.7 \text{ V}$, $V_{BC} \rightarrow 0$
 - BC junction *losing its reverse bias*
- At $V_{CE} = 0.7 \text{ V}$, $V_{BC} = 0$
 - BC junction *under zero bias*
- For $V_{CE} < 0.7 \text{ V}$, V_{BC} turns *positive*
 - Both BE and BC junctions become *forward biased* \Rightarrow *saturation*

- $V_{CE} = 0.7 \text{ V}$ is known as *onset of saturation* (OS)
- *Saturation*:
 - For $V_{CE} < 0.7 \text{ V}$
 - CB junction becomes *forward biased*
 - Collector also starts to *inject* electrons to base
 - *Two effects*:
 - *Net electrons reaching collector* $\downarrow \Rightarrow I_C \downarrow$
 - *Base gets flooded with electrons*
 \Rightarrow *Recombination increases manyfold* $\Rightarrow I_B \uparrow$
 - Thus, $\beta \downarrow \Rightarrow$ Defined as $\beta_{sat} (= I_{C,sat}/I_{B,sat})$