

- *The most important property of a DA is to be able to reject common-mode signals (noise), while amplifying the difference between the two signals applied at its two inputs*
- Characterized by a parameter known as the *Common-Model Rejection Ratio (CMRR)* (*expressed in dB*):
$$\text{CMRR} = 20\log_{10}(|A_{\text{dm}}/A_{\text{cm}}|)$$
- *Ideal (Desirable) Properties:*
 - $|A_{\text{dm}}| \rightarrow \infty (\sim 10^3\text{-}10^5)$
 - $|A_{\text{cm}}| \rightarrow 0 (< 1)$
 - $\text{CMRR} \rightarrow \infty (\sim 40\text{-}120 \text{ dB})$

➤ *The circuit has two inputs and two outputs:*

⇒ *Four possible configurations:*


- *Single-ended i/p, single-ended o/p*
- *Single-ended i/p, double-ended o/p*
- *Double-ended i/p, single-ended o/p*
- *Double-ended i/p, double-ended o/p*

⇒ *Tremendous flexibility*


- *Double-ended o/p eliminates the common-mode signal completely*
- *However, at some point in the circuit, needs to be converted to a single-ended o/p*

⇒ *High CMRR is an absolute must!*

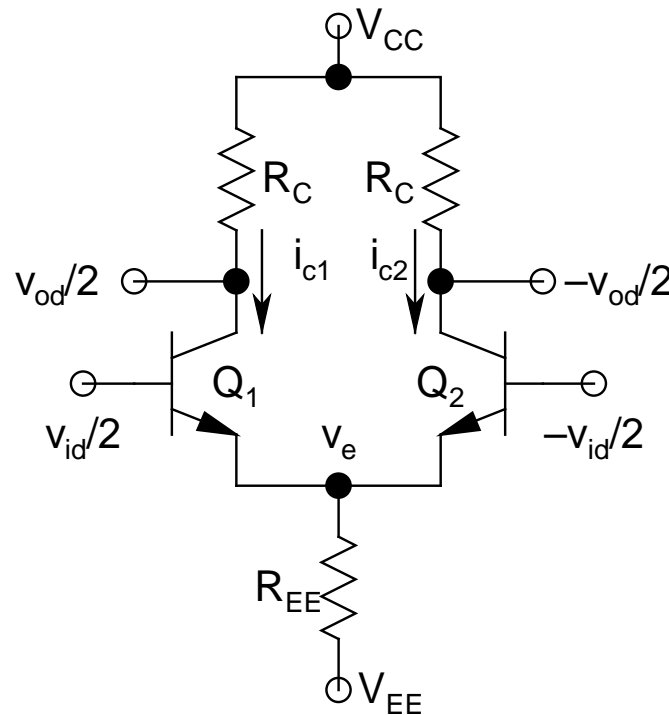➤ **Differential-Mode Half Circuit: Calculation of A_{dm} :**



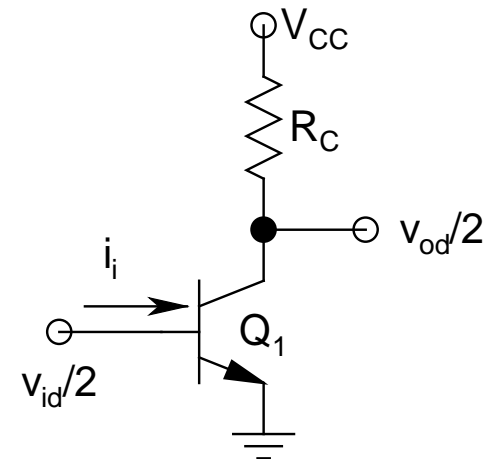**nnp DA Under Pure
Differential-Mode Input**



**Differential-Mode
Half-Circuit**

- *Can be shown that $v_e = 0$ in three ways:*
 - ❖ *From the symmetry of the circuit:*
Equal and opposite voltages applied at the bases of Q_1 and Q_2
 \Rightarrow *The emitter potential v_e got to be an average of the inputs, which is zero*
 - ❖ $i_{c1} = g_{m1}(v_{id}/2 - v_e)$ and $i_{c2} = g_{m2}(-v_{id}/2 - v_e)$
Since $g_{m1} = g_{m2}$, i_{c1} must equal $-i_{c2}$ (circulating current)
(this is again from symmetry)
 $\Rightarrow v_e = 0$
 - ❖ *Drawing the complete ac low-frequency hybrid- π model, and summing currents at the common-emitter node:*
Show that $v_e = 0$
- *Caution: $v_e = 0$ will hold true only for a balanced DA*

- *Thus, the left and right parts of the circuit become absolutely symmetrical*

⇒ *Either of the parts can be used*

⇒ *Leads to the differential-mode half-circuit*

- $g_{m1} = g_{m2} = g_m = I_{EE}/(2V_T)$, $r_{E1} = r_{E2} = r_E = 2V_T/I_{EE}$,
and $r_{\pi1} = r_{\pi2} = r_{\pi} = \beta r_E$

- *Can be easily identified to be a CE stage*

$$\Rightarrow A_{dm} = v_{od}/v_{id} = (v_{od}/2)/(v_{id}/2) = -R_C/r_E$$

- *Differential-mode input resistance:*

$$R_{id} = v_{id}/i_i = 2(v_{id}/2)/i_i = 2r_{\pi}$$

- *The simplicity of the analysis is simply mind-boggling!*