
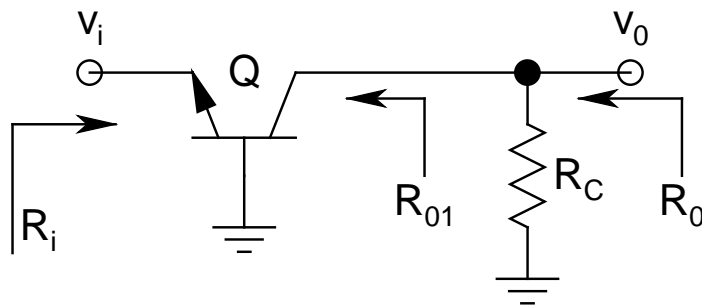


- **Common-Base (CB):**

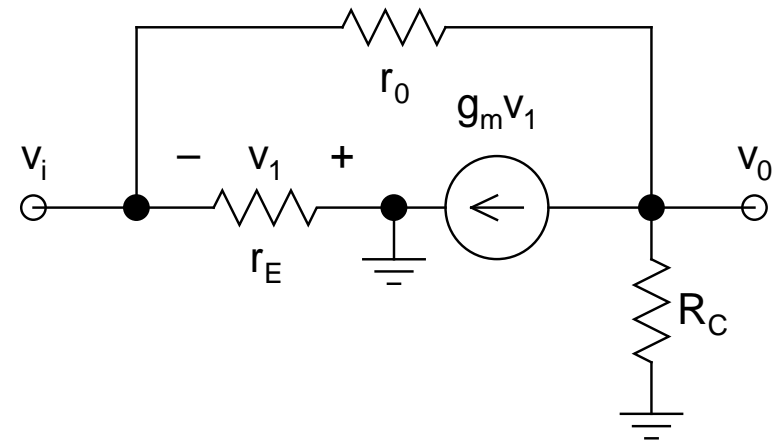

ac Schematic



ac Low-Frequency Equivalent

- Note that the **alternate hybrid- π model** appropriate for **CB circuit** has been used
- **r_0 appears between input and output**

- For now, *neglect r_o*
- Noting that $v_1 = -v_i$:

$$A_v = \frac{v_o}{v_i} = \frac{-g_m v_1 R_C}{v_i} = +g_m R_C \simeq \frac{R_C}{r_E}$$

- Note that the *expression* for A_v is *identical* to that for the *CE stage*, *without the negative sign in front*
- For this circuit, *input and output are in phase*
- $A_i = i_c/i_e = \alpha$
- $R_i = r_E$

➤ $R_0 = R_{01} \parallel R_C$

$R_{01} \rightarrow \infty$ (*Why?*)


$\Rightarrow R_0 = R_C$

➤ *Ex.: Find A_v and R_i with r_o included*


➤ *With r_o included*, the circuit shows *two different values* of R_{01} :

- *When excited by a voltage source*, $R_{01} = r_o$
- *When excited by a current source*, $R_{01} = \beta r_o$ (*Show*)
[*Hint: For this derivation, need to use $g_m r_E = \alpha$*]
- *Thus, possibility of huge R_0 under the second case, but R_C ruins it!*


- **Common-Gate (CG):**

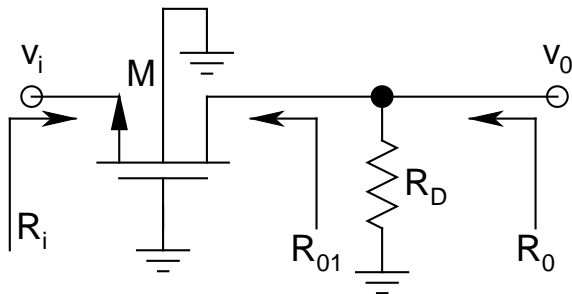


ac Schematic

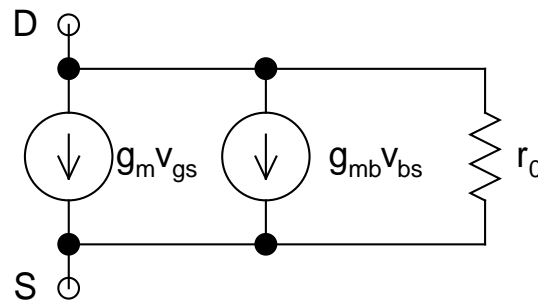


ac Low-Frequency Model for M

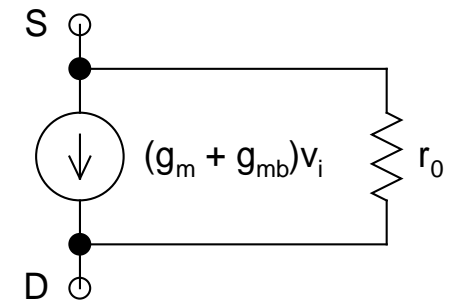

Simplified ac Low-Frequency Model for M

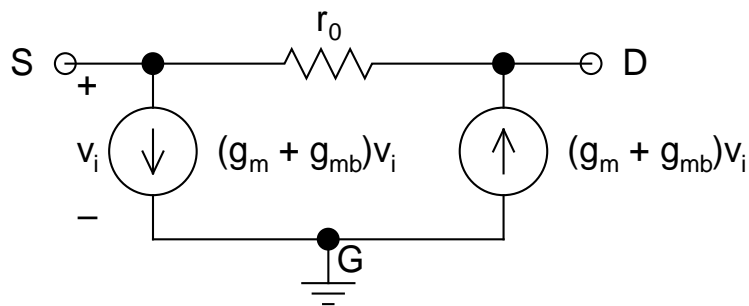

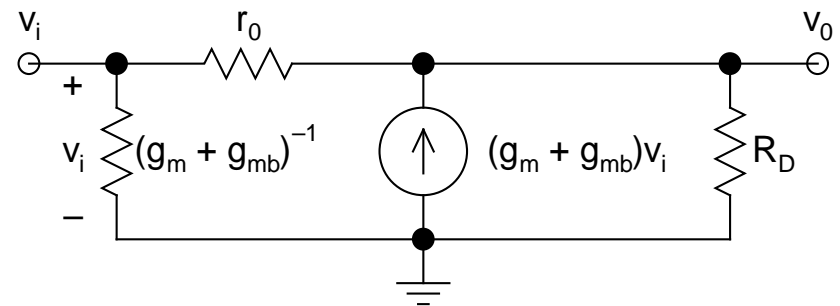Rerouting the current source between S and D to S to G and then from G to D



Final ac Low-Frequency Equivalent for CG Stage

➤ *G and B both ground:*

$$\Rightarrow V_{gs} = V_{bs} = -V_i$$

$\Rightarrow g_m V_{gs}$ and $g_{mb} V_{bs}$ can be *combined to a single current source* $(g_m + g_{mb})V_i$, *flowing from S to D*

➤ *Reroute this current source from S to G and then from G to D (the circuit remains invariant)*

\Rightarrow Leads to the *final ac low-frequency equivalent* of the CG stage

➤ *Note again that r_o appears between input and output (similar to CB stage)*