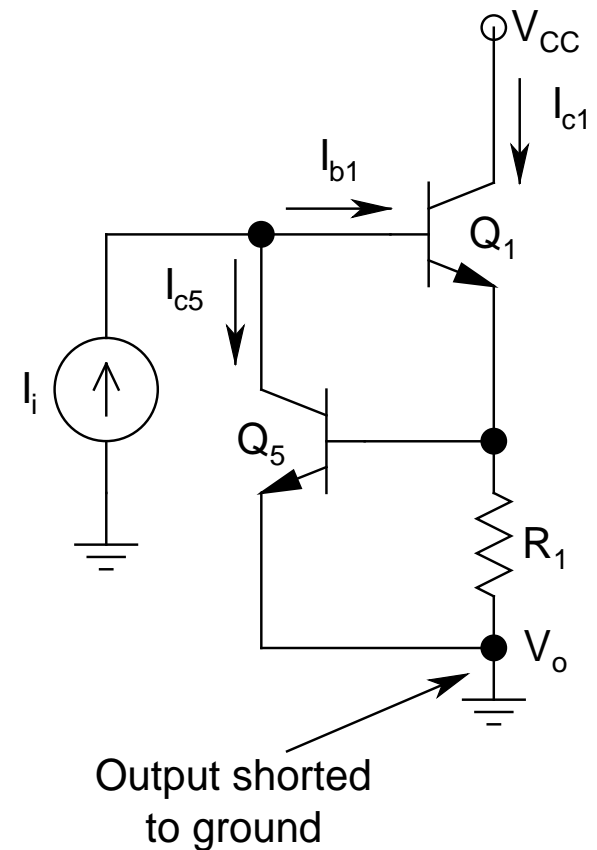


- Thus, the *current can't increase indefinitely*
- Assume  $R_1 = 30\ \Omega$  and  $V_\gamma = 0.6\text{ V}$   
 $\Rightarrow$  As soon as  $I_{c1}$  reaches about 20 mA,  $Q_5$  cuts in, shunts current away from the base of  $Q_1$ , and protects the circuit
- Due to the exponential dependence of this shunted current on  $V_{be5}$ , the maximum output current will saturate near around 20 mA itself
- Thus, under this case, if the output is accidentally shorted to ground, then  $P_1(\text{max})$  will be around 100 mW, which is well within limit, and protection will be achieved

- Similarly, for the *negative half cycle*, this job of *protection will be achieved by the  $Q_6$ - $R_2$  combination*
- The *drop across  $R_2$*  will depend on the *amount of current* being *sunk by  $Q_2$*
- Once this drop *reaches the cut-in voltage* of  $Q_6$ , it will *turn on*, and *bypass the drive current of  $Q_2$* , thus *protecting the circuit*
- This *protection circuit* is *widely used* due to its *efficacy*, and the *most popular analog building block*, the *op-amp*, *uses this protection scheme*

➤ **Quantitative Estimate of the Protection Mechanism:**


- Assume  $V_i$  positive and supplying drive current  $I_i$  to  $Q_1$
- Output shorted to ground**  
 $\Rightarrow V_o = 0$
- $I_i = I_{b1} + I_{c5}$   
 $I_{c5} = I_{S5} \exp(V_{be5}/V_T)$
- $V_{be5} = I_{c1} R_1$  (assuming  $\alpha_1 = 1$  and neglecting  $I_{b5}$ )



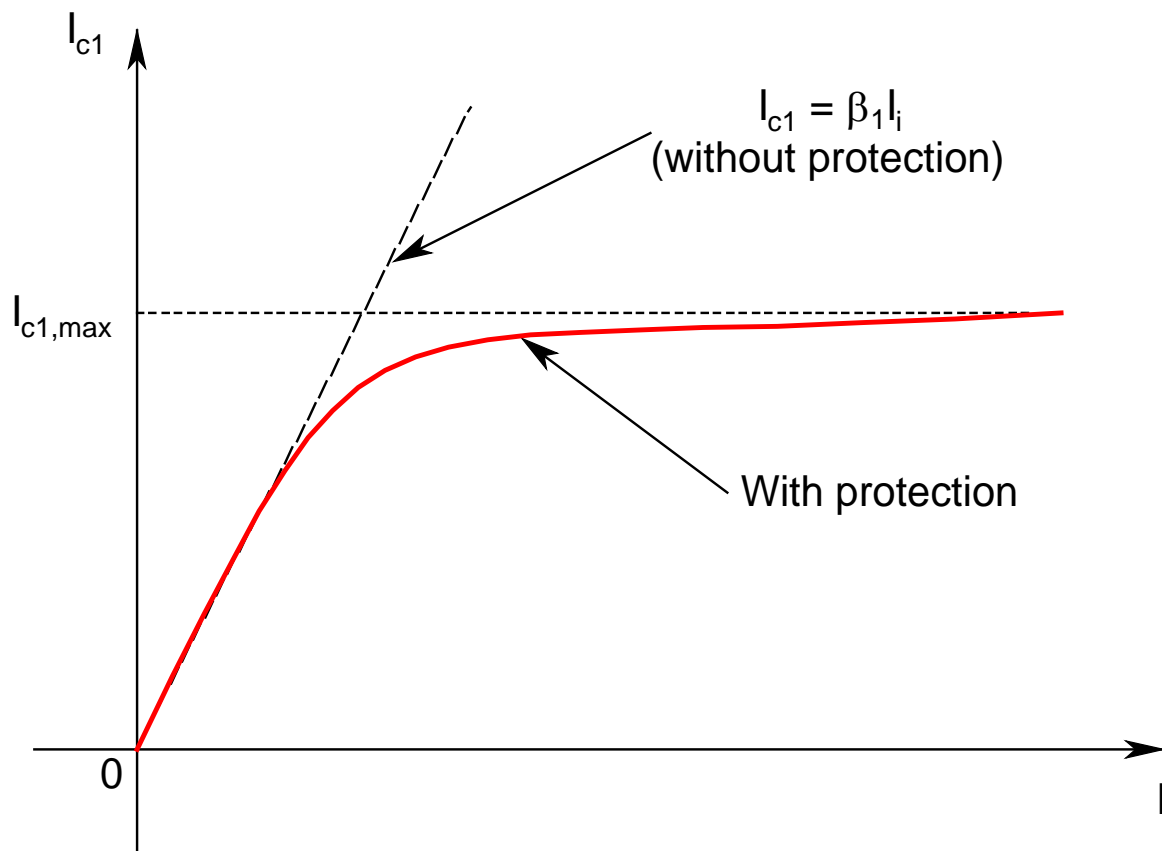**Protection Scheme**

- For *small values* of  $I_{c1}$ ,  $V_{be5}$  will be *small*, and  $I_{c5}$  will be *negligible*
- Also,  $I_{c1} = \beta_1 I_{b1} = \beta_1 (I_i - I_{c5})$   
 $\Rightarrow \beta_1 I_i = I_{c1} + \beta_1 I_{S5} \exp(I_{c1} R_1 / V_T)$
- This is the *final protection expression*
- For *small*  $I_{c1}$ , the *second term* on the *RHS* will be *negligible*  
 $\Rightarrow I_{c1}$  would follow  $I_i$  linearly with proportionality constant  $\beta_1$
- As  $I_{c1} \uparrow$ , the *second term* on the RHS *increases at a much more rapid rate* than the *first term*

- Once it starts to become *comparable* to the first term, a *very little change* in  $I_{c1}$  can *counter a large change* in  $I_i$   
 $\Rightarrow I_{c1}$  gets clamped to almost a constant value of  $I_{c1,max}$
- Note that the *protection equation* is *transcendental*  
 $\Rightarrow$  Needs numerical or iterative solution



## Protection Characteristic