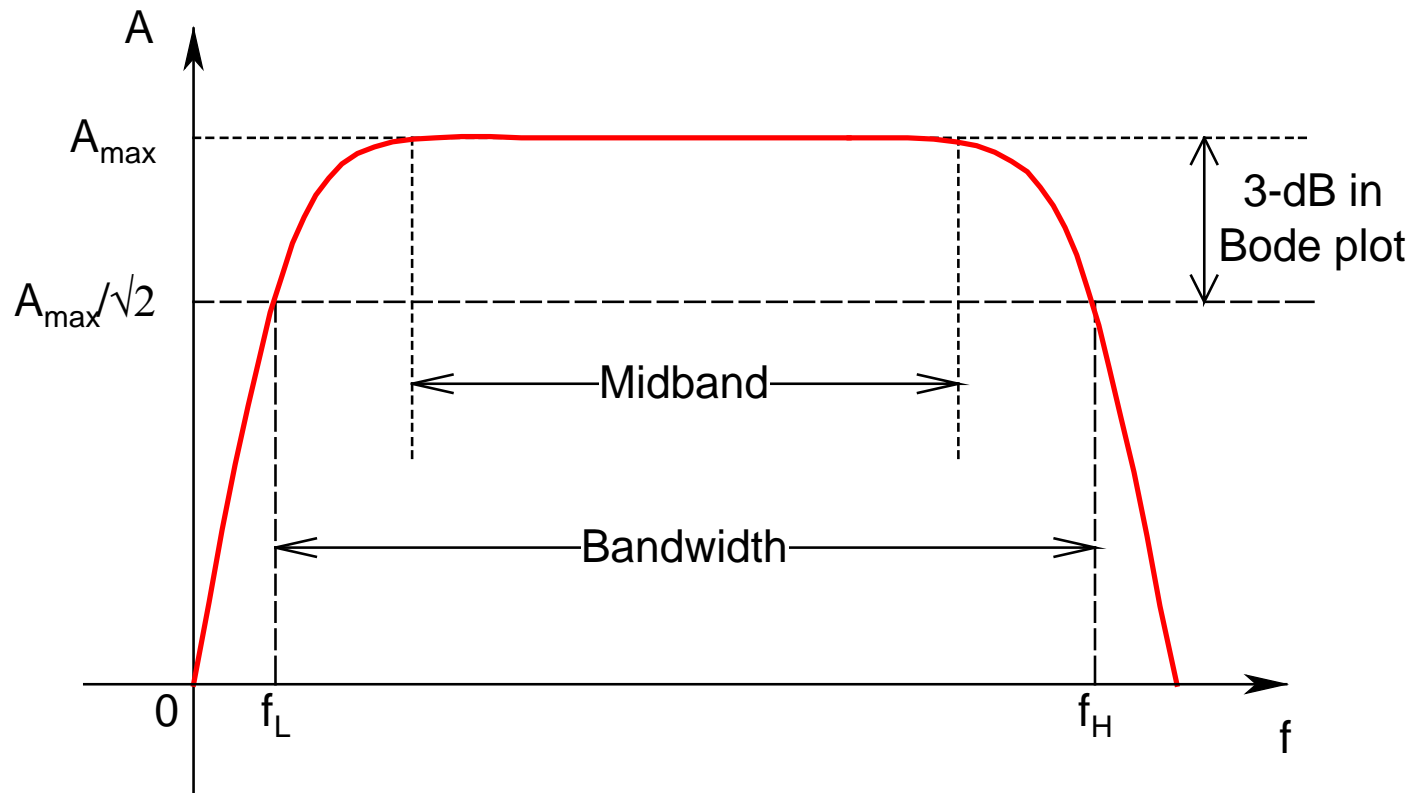


FREQUENCY RESPONSE

- So far, considered *midband analysis*, where *all capacitive effects were neglected*
 - *Voltage/current gain was independent of frequency*
- In *practical amplifier circuits*, however, the *gain would depend on frequency*
- *Characterized by:*
 - *Lower Cutoff Frequency* (f_L)
 - *Contributed by external capacitors* (C_E , C_B , C_C)

- *Upper Cutoff Frequency* (f_H)
 - *Contributed by device capacitances* (for BJT: C_π , C_μ ; *for MOSFETs*: C_{gs} , C_{gd} , C_{sb} , C_{db})
- These capacitors create *charge storage effects*, and *introduce time constants* into the circuit
- *Discrete circuits show both f_L and f_H*
- *IC stages show only f_H* , since most of them are *direct coupled* without the need for any *external capacitors*



f_L : Lower Cutoff Frequency

f_H : Upper Cutoff Frequency

$$\text{Bandwidth} = f_H - f_L$$

- *Exact analysis extremely complicated*
 - Most often, results in *very complicated expressions*, *completely hiding the physical feel of the phenomenon*
 - *Makes debugging extremely difficult*
 - For example, a circuit having *4 capacitors*, will have a *fourth-order transfer function*, which needs to be *solved* to get all the *poles and zeros* of the system
 - However, there are *techniques*, which make these *analyses* extremely *trivial*
 - *Not accurate*, but *extremely simple*, and makes *debugging easy*

- *Techniques:*
 - *Infinite-Value Time Constant (IVTC) Method*
 - *Used for obtaining f_L*
 - *Zero-Value Time Constant (ZVTC) Method*
 - *Used for obtaining f_H*
- These techniques are *extremely easy to apply*, and the results are *quite close to actuals*
- However, there is *one limitation* of these techniques