

**Department of Electrical Engineering
Indian Institute of Technology, Kanpur**

EE 210


Assignment #1

Assigned: 13.1.21


For all problems in this course, assume $T = 300\text{ K}$ (with $V_T = 26\text{ mV}$), unless otherwise stated.

1. A pn junction diode has reverse saturation current $I_0 = 10\text{ pA}$. Determine the magnitude of the diode current (along with its direction) when it is under: i) forward bias of: a) 50 mV , and b) 500 mV ; and ii) reverse bias of: a) 50 mV , and b) 500 mV .

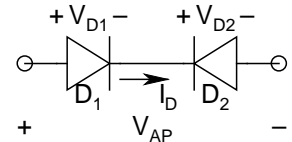2. Two diodes D_1 and D_2 are connected back to back with an applied bias of V_{AP} ($= 5\text{ V}$), as shown in the figure. Calculate the current I_D and the diode drops V_{D1} and V_{D2} . Data: $I_0(D_1) = 1\text{ pA}$, and $I_0(D_2) = 1\text{ nA}$.



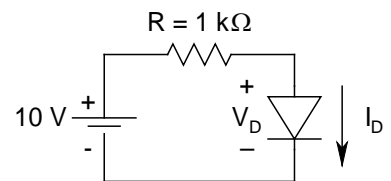3. A simple diode circuit is shown alongside. Perform a self-consistent analysis to find the diode current I_D and the diode voltage V_D . Take $I_0 = 10\text{ pA}$.



4. The measured junction capacitance C_{dep} (in μF) as a function of the applied voltage V_D (in volts) of an abrupt Si pn junction (area $= 10\text{ mm}^2$) is given by $1/C_{dep}^2 = [2.5 \times 10^5 \times (4 - 6.25V_D)]$. Determine the built-in voltage and the depletion region width at zero bias.
5. Consider Prob.3. Assuming that the junction is linearly graded, determine the small-signal parameters of the diode, and draw its small-signal equivalent circuit. Data: $V_0 = 0.8\text{ V}$, $C_{dep0} = 1\text{ pF}$, and $\tau = 1\text{ }\mu\text{sec}$.