

Consider all voltage and current sources to be ideal.

1. Find the $[Z]$ parameters for the circuit of fig. 4.1..

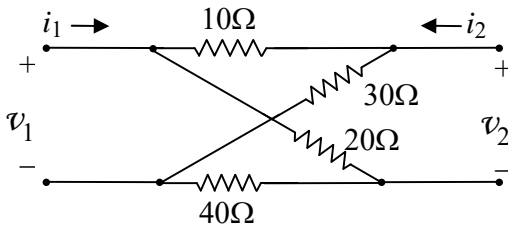


Figure 4.1

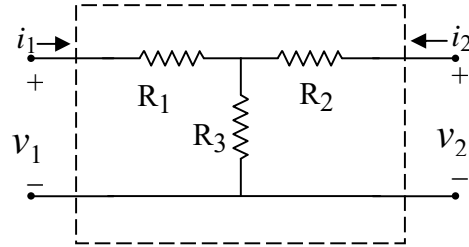


Figure 4.2

2. For the circuit shown in fig. 4.2 the $[ABCD]$ matrix is given as : $\begin{bmatrix} 1.5 & 2.75\text{k}\Omega \\ 10^{-3}\text{S} & 2.5 \end{bmatrix}$. Find the values of R_1 , R_2 , and R_3

3. Find the $[h]$ parameters of the 2-port network shown in fig. 4.3. Find R_2/R_1 for $\beta=100$.

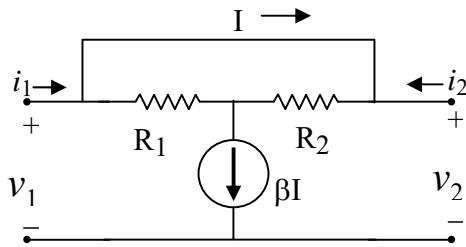


Figure 4.3

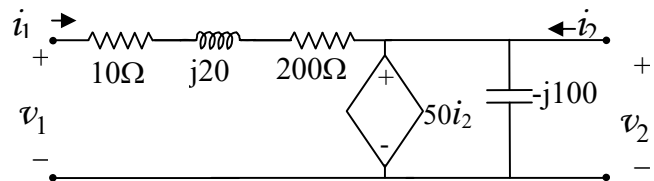


Figure 4.4

4. Find the $[h]$ parameters of the 2-port network shown in fig. 4.4.
5. In fig. 4.5 are shown two identical amplifiers connected in cascade. Each amplifier is represented by their h -parameters, $h_{11} = 1\text{k}\Omega$, $h_{12} = 1.5 \times 10^{-3}$, $h_{21} = 100$, and $h_{22} = 100\mu\text{Mhos}$. Given that $[a]$ and $[ABCD]$ parameters are exactly the same, find the voltage gain v_2/v_s .

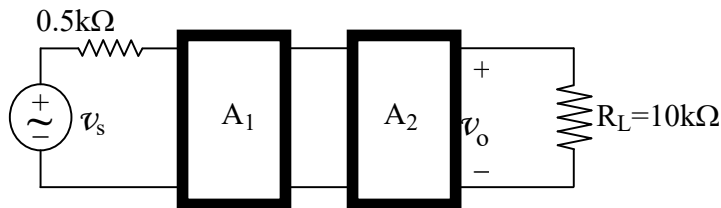


Figure 4.5

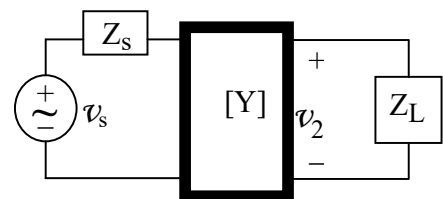


Figure 4.6

6. The $[Y]$ parameters for a 2-port network shown in fig. 4.6 are: $\begin{bmatrix} 2\text{mS} & -2\mu\text{S} \\ 100\text{mS} & -50\mu\text{S} \end{bmatrix}$. The source impedance

is $Z_s = 2.5 \text{ k}\Omega + j0 \Omega$ and the load impedance is $Z_L = 70 \text{ k}\Omega + j0 \Omega$. The ideal voltage source is $v_s = (80\sqrt{2})\cos(4000t) \text{ mV}$. Find the rms value of v_2 and the average power delivered to Z_L .

1/ The given circuit is redrawn as:


$$Z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0} = \frac{(20+40)(10+30)}{20+40+10+30} = 24\Omega$$

$$Z_{21} = \frac{V_2}{I_1} \Big|_{I_2=0}$$

$$= \frac{2i_1}{i_1} = 2\Omega$$


$$V_2^+ = \frac{i_1 \times 24}{(10+30)} \times 30$$
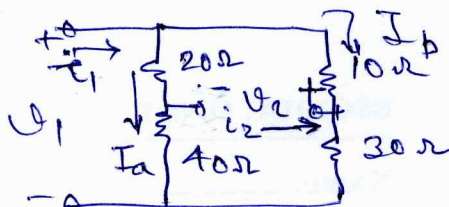
$$V_2^- = \frac{i_1 \times 24}{(20+40)} \times 40$$



$$\therefore V_2 = V_2^+ - V_2^- = 18i_1 - 16i_1 = 2i_1$$

For $i_1=0$ Need to redraw the circuit.

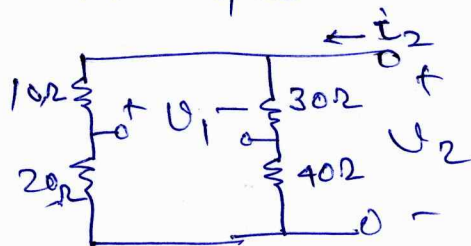

$$V_1^+ = \frac{i_2 \times \frac{30 \times 70}{100}}{10+20} \times 20 = i_2 4V$$

$$V_1^- = \frac{i_2 \times \frac{30 \times 70}{100}}{30+40} \times 40 = i_2 2V$$

$$Z_{12} = \frac{V_1}{i_2} \Big|_{i_1=0} = \frac{2i_2}{i_2} = 2\Omega \quad V_1 = V_1^+ - V_1^- = (4-2)i_2 = 2i_2$$

$$Z_{22} = \frac{V_2}{i_2} \Big|_{i_1=0} = \frac{i_2 \times \frac{30 \times 70}{100}}{i_2} = 21\Omega$$

2/ $A = \frac{V_1}{V_2} \Big|_{i_2=0}, V_2 = \frac{V_1 R_3}{R_1 + R_3} \Big|_{i_2=0}$

$$= \frac{R_1 + R_3}{R_3}$$

$$= 1 + \frac{R_1}{R_3} = 1.5 \quad \therefore \frac{R_1}{R_3} = 0.5 \quad \therefore R_3 = 2R_1$$

$$C = \frac{i_1}{V_2} \Big|_{i_2=0} \quad \left| \quad i_1 = \frac{V_1}{R_1 + R_3} \Big|_{i_2=0} \right.$$

$$= \frac{1}{R_3} = 10^{-3} \text{ V}$$

$$\text{or } R_3 = 1k\Omega$$

$$\therefore R_1 = 0.5k\Omega$$

$$ABCD \Rightarrow \begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

and from above $V_2 = \frac{V_1 R_3}{R_1 + R_3}$ or $V_1 = \frac{R_1 + R_3}{R_3} V_2$

$$= \frac{(R_1 + R_3) V_2}{R_3 (R_1 + R_3)}$$


For B & D short the V_2 voltage terminal i.e. $R_2 \parallel R_3$, current flowing in from port ① is $\frac{V_1}{R_1 + R_2 \parallel R_3} = \frac{V_1}{R_1 + \frac{R_2 R_3}{R_2 + R_3}}$

$$B = -\frac{V_1}{I_2} \Big|_{V_2=0} \quad \therefore -i_2 \text{ (the current in } R_3) = \frac{V_1}{R_2 + R_3} \times \frac{1}{R_3} = \frac{V_1}{R_3 (R_2 + R_3)}$$

$$\therefore \frac{V_1}{R_1 + R_2 \parallel R_3} = -i_2 \left(1 + \frac{R_3}{R_2}\right) \quad \therefore B = \frac{V_1}{-i_2} = \left(R_1 + \frac{R_2 R_3}{R_2 + R_3}\right) \left(1 + \frac{R_3}{R_2}\right) \frac{R_3}{R_3}$$

$$D = -\frac{i_1}{i_2} \Big|_{V_2=0} = 1 + \frac{R_2}{R_3} = 2.5 \quad \therefore \frac{R_2}{R_3} = 1.5 \text{ or } R_2 = 1.5R_3 = 1.5k\Omega$$

3/
$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix} \quad h_{11} = \frac{V_1}{I_1} \Big|_{V_2=0} \text{ \& } h_{21} = \frac{I_2}{I_1} \Big|_{V_2=0}.$$

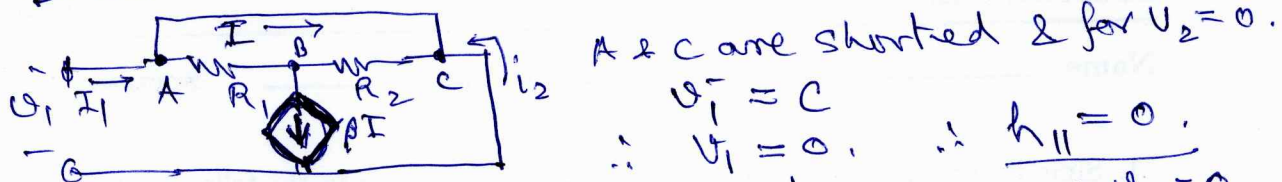

$$I_1 = I + \frac{V_{AB}}{R_1} \quad \& \quad i_2 = -I + \frac{V_{CB}}{R_2}$$


 Again $i_2 + I = I_{R_2 C \rightarrow B} = -I - \frac{(-V_{AB})}{R_2} = -I + \frac{V_{AB}}{R_2}$
 and $i_1 - I = I_{R_1 A \rightarrow B}$

and $I_{R_1 A \rightarrow B} + I_{R_2 C \rightarrow B} = \beta I = \frac{V_{AB}}{R_1} + \frac{V_{AB}}{R_2}$

$$\therefore \frac{i_2}{i_1} \Big|_{V_2=0} = \frac{-I + \frac{V_{AB}}{R_2}}{I + \frac{V_{AB}}{R_1}} = \frac{-\frac{V_{AB}}{\beta R_1} - \frac{V_{AB}}{\beta R_2} + \frac{V_{AB}}{R_2}}{\frac{V_{AB}}{\beta R_1} + \frac{V_{AB}}{\beta R_2} + \frac{V_{AB}}{R_1}}$$


$$h_{21} = \frac{\frac{\beta}{R_2} - \frac{1}{R_1} - \frac{1}{R_2}}{\frac{\beta}{R_1} + \frac{1}{R_1} + \frac{1}{R_2}}$$

for $h_{22} = \frac{I_2}{V_2} \Big|_{I_1=0}$

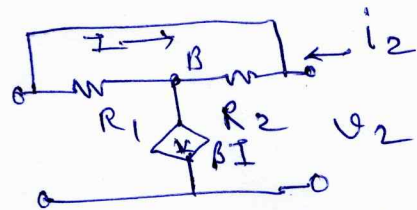

At node B $\beta I = -I + i_2 + I = i_2$
 for h_{12} Do we really need to calculate? It is shorted by the line carrying current I $\therefore V_1 = V_2$ & $h_{12} = \frac{V_1}{V_2} \Big|_{I_1=0} = 1$

Redraw:

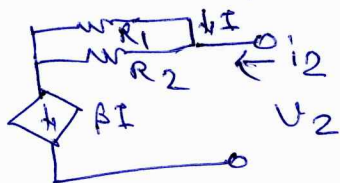

$$\therefore \beta I = 0 = i_2$$

$$\therefore i_2 = 0$$

$$\therefore h_{22} = \frac{I_2}{V_2} \Big|_{I_1=0} = 0$$


Since this is a reciprocal circuit i.e. either end could be called ① & ② ports. $\Delta h = 1$

$$\therefore |h_{12} h_{21}| = 1 \quad \text{or} \quad h_{21} = 1 \text{ also.}$$

$$\therefore \frac{\beta}{R_1} + \frac{1}{R_1} + \frac{1}{R_2} = \frac{\beta}{R_2} - \frac{1}{R_1} - \frac{1}{R_2}$$

which gives
$$\frac{R_2}{R_1} = \frac{\beta - 2}{\beta + 2} = \frac{100 - 2}{100 + 2} = \frac{98}{102} = 0.96$$

$$4/ \quad h_{11} = \frac{v_1}{i_1} \bigg|_{v_2=0} \quad h_{21} = \frac{i_2}{i_1} \bigg|_{v_2=0}$$

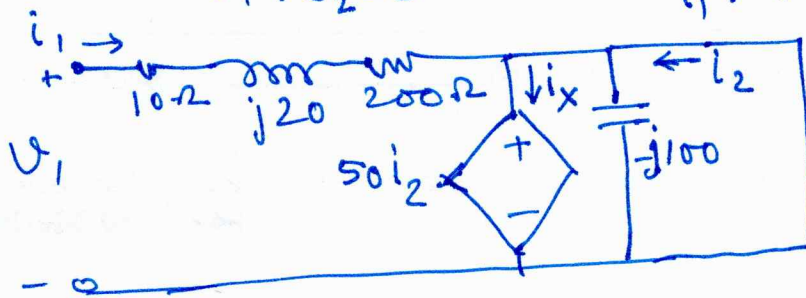

$$\therefore h_{11} = 210 + j20$$

No current flows through the capacitor. The controlled voltage source is also shorted.

$$\therefore v_1 = i_1 (210 + j20)$$


As the controlled voltage source has zero volts across it, cannot maintain the voltage across its terminals,

$$\therefore i_x = 0$$

$$\therefore i_1 = -i_2$$

$$\therefore h_{21} = -1$$

$$h_{12} = \frac{v_1}{v_2} \bigg|_{i_1=0} \quad \& \quad h_{22} = \frac{i_2}{v_2} \bigg|_{i_1=0}$$

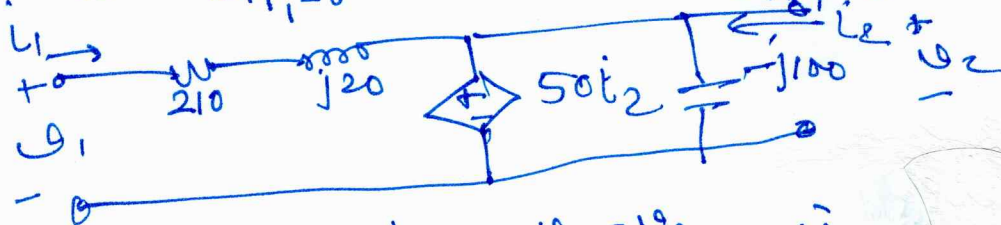

$$v_2 = 50 i_2, \quad i_1 = \frac{v_1 - v_2}{210 + j20} = 0$$

$$\therefore v_1 = v_2$$

$$\therefore h_{12} = 1$$

$$h_{12} h_{21} \neq 1 \quad ??$$

$$\text{or } \frac{i_2}{v_2} = h_{22}$$

$$\frac{i_2}{v_2} = 50^{-1} = h_{22} = 0.02$$

$$[h] = \begin{bmatrix} 210 + j20 & 1 \\ 1 & 0.02 \end{bmatrix}$$

$$6/ \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} \quad \text{But } i_2 = -\frac{V_2}{Z_L} \text{ \& } V_1 = V_s - i_1 Z_s$$

$$\therefore i_1 = y_{11}(V_s - i_1 Z_s) + y_{12} V_2 \text{ or } i_1(1 + y_{11} Z_s) = y_{11} V_s + y_{12} V_2$$

$$\therefore i_1 = \frac{y_{11} V_s + y_{12} V_2}{1 + y_{11} Z_s} \quad \downarrow$$

$$\begin{aligned} \text{Again } i_2 = -\frac{V_2}{Z_L} &= y_{21}(V_s - i_1 Z_s) + y_{22} V_2 \\ &= y_{21} V_s - y_{21} Z_s \frac{y_{11} V_s + y_{12} V_2}{1 + y_{11} Z_s} + y_{22} V_2 \end{aligned}$$

$$\begin{aligned} \approx V_2 \left(-\frac{1}{Z_L} + \frac{y_{21} y_{12} Z_s}{1 + y_{11} Z_s} - y_{22} \right) \\ = V_s \left(y_{21} - \frac{y_{21} y_{11} Z_s}{1 + y_{11} Z_s} \right) \end{aligned}$$

$$\therefore V_2 = \frac{y_{21} - \frac{y_{21} y_{11} Z_s}{1 + y_{11} Z_s}}{\frac{y_{21} y_{12} Z_s}{1 + y_{11} Z_s} - \frac{1}{Z_L} - y_{22}}$$

Multiplying by $[(1 + y_{11} Z_s) Z_L]$

$$\begin{aligned} \frac{V_2}{V_s} &= \frac{y_{21} (1 + y_{11} Z_s) Z_L - y_{21} y_{11} Z_s Z_L}{y_{21} y_{12} Z_s Z_L - (1 + y_{11} Z_s) - y_{22} (1 + y_{11} Z_s) Z_L} \\ &= \frac{y_{21} Z_L}{y_{21} y_{12} Z_s Z_L - (1 + y_{11} Z_s)(1 + y_{22} Z_L)} \end{aligned}$$

$$y_{21} Z_L = 0.1 \times 70k = 7k, \quad y_{21} y_{12} Z_s Z_L = 0.1 \times (-2 \times 10^{-6}) \times 2.5 \times 70 \times 10^6 = -35$$

$$\begin{aligned} (1 + y_{11} Z_s) &= 1 + 2 \times 10^{-3} \times 2.5 \times 10^3 = 1 + 5 = 6 \\ (1 + y_{22} Z_L) &= 1 + (-50 \times 10^{-6}) \times 70 \times 10^3 = 1 - 3.5 = -2.5 \end{aligned}$$

$$\therefore V_2 = \frac{7000}{-35 - 6 \times (-2.5)}$$

$$= -350 V_s = -350 \times 80 \sqrt{2} \angle 0^\circ$$

$$\therefore V_2|_{rms} = -350 \times 80 \angle 0^\circ \times 10^{-3} = 350 \times 80 \angle 180^\circ \times 10^{-3} = 28 \angle 180^\circ V$$

$$P = \frac{|V_2|_{rms}^2}{70k} = 11.2 \text{ mW}$$

5/ [h] parameters are not cascadeable
 \therefore one needs to convert it to [ABCD] parameters.

$$A_h = -\frac{\Delta h}{h_{21}} \quad B_h = -\frac{h_{11}}{h_{21}} \quad C_h = -\frac{h_{22}}{h_{21}} \quad \text{and} \quad D_h = -\frac{1}{h_{21}}$$

$$\Delta h = h_{11}h_{22} - h_{21}h_{12} = 1k \times 100 \times 10^{-6} - 100 \times 1.5 \times 10^{-3}$$

$$= 0.1 - 0.15 = -0.05$$

$$\therefore A_1 = \frac{0.05}{10^2} = 5 \times 10^{-2} \times 10^{-2} = 5 \times 10^{-4}$$

$$B_1 = -\frac{10^3}{100} = -10 \Omega, \quad C_1 = -\frac{10^{-4}}{100} = -10^{-6} \text{ V}, \quad D_1 = -\frac{1}{100} = -10^{-2}$$

$$[ABCD] = [ABCD]_1 \times [ABCD]_2$$

$$= \begin{bmatrix} 5 \times 10^{-4} & -10 \\ -10^{-6} & -10^{-2} \end{bmatrix} \times \begin{bmatrix} 5 \times 10^{-4} & -10 \\ -10^{-6} & -10^{-2} \end{bmatrix} = \begin{bmatrix} 25 \times 10^{-8} & -5 \times 10^{-3} \\ -5 \times 10^{-10} & 10^{-5} \end{bmatrix}$$

$$= \begin{bmatrix} 10.25 \times 10^{-6} & 0.095 \\ +95 \times 10^{-10} & 1.1 \times 10^{-4} \end{bmatrix} \quad \Delta[ABCD] = 11.275 \times 10^{-10} - 9.025 \times 10^{-10}$$

$$= 2.25 \times 10^{-10}$$

Instead of doing the calculations again we can use the derivation done in Q6 by converting the [ABCD] to [y].

$$y_{11} = \frac{D}{B}, \quad y_{12} = -\frac{\Delta(ABCD)}{B}, \quad y_{21} = -\frac{1}{B}, \quad y_{22} = \frac{A}{B}$$

$$y_{11} = \frac{1.1 \times 10^{-4}}{0.095} = 11.58 \times 10^{-4} \text{ V}$$

$$y_{12} = -\frac{2.25 \times 10^{-10}}{0.095} = -0.0024 \times 10^{-6} \text{ V}$$

$$y_{21} = -10.5325, \quad y_{22} = 1.08 \times 10^{-4} \text{ V}$$

$$\frac{V_2}{V_s} = \frac{y_{21} Z_L}{y_{21} y_{12} Z_s Z_L - (1 + y_{11} Z_s)(1 + y_{22} Z_L)}$$

$$y_{21} Z_L = -10.53 \times 10^4 = -10.53 \times 10^4$$

$$y_{21} y_{12} Z_s Z_L = (-10.53)(-0.0024 \times 10^{-6}) \times 0.5 \times 10^3 \times 10 \times 10^3$$

$$= 0.126$$

$$1 + y_{11} Z_s = 1 + 11.58 \times 10^{-4} \times 0.5 \times 10^3 = 1.58$$

$$1 + y_{22} Z_L = 1 + 1.08 \times 10^{-4} \times 10^4 = 2.08$$

$$\therefore \frac{V_2}{V_s} = \frac{-10.53 \times 10^4}{0.126 - 1.58 \times 2.08} = 33,318$$