

OUTPUT STAGES

- *Main Purpose:*
 - *To drive load with sufficient current*
- Both *BJT* and *MOS* output stages available
- *BJT* output stages preferred due to their *large current handling capability*
- *BiMOS* circuits use *MOS* devices in the *core* of the circuit, while using *BJT* devices in the *output* stage
 - *Best of both worlds!*

- **Requirements:**
 - **Sufficient drive current/power transfer to load**
 - **Low output distortion**
 - **Ideal voltage source:**
 - **Thevenin equivalent: V_0 with $R_0 \rightarrow 0$**
 - **Voltage gain A_v independent of load**
 - **Ideally unity with no phase shift**
 - **Low Standby (or Idling) Power**
 - **While not driving any load**
 - **Should not degrade frequency response**

➤ *High power conversion efficiency η*

▪ $\eta = (\text{average power delivered to load}) / (\text{average power drawn from supply})$

• *Classification:*

➤ *Depends on the conduction angle (θ)*

▪ θ : Angle over the complete cycle (360°) for which either both or one of the output transistors are/is on

➤ *Class A:*

▪ $\theta = 360^\circ$ and $\eta_{max} = 25\%$ (*large standby power*)

➤ *Class B:*

▪ θ slightly less than 180° and $\eta_{max} = 78.5\%$ (*zero standby power*)

- **Class AB:**
 - $\theta = 180^\circ$ and $\eta_{max} \approx 78.5\%$ (*very small standby power*)
- **Class C:**
 - $\theta \ll 180^\circ$ (*used in RF applications*)
- There are *other classes* also, namely **D**, **E**, **F**, **G**, and **H**
 - Used only in *special cases*, e.g., *pulse width modulated input*, *lowering of distortion*, etc.
- In this course, we shall be discussing only about **Class B** and **Class AB** output stages

- ***Class B:***

- Uses ***complementary*** set of output transistors (***npn and pnp, NMOS and PMOS***)
- One takes care of the ***positive half cycle***, while the other takes care of the ***negative half cycle***
- ***θ slightly less than 180° for each***
- ***Both output devices never ON simultaneously***
 - ***Zero standby power (significant advantage)***
- Also known as ***Push-Pull Stage***


- During *positive half cycle*, the stage *pushes current through load*
- During *negative half cycle*, the stage *pulls current away from load*
- *Very high η_{max} of 78.5%*
- However, there is a *very big limitation*, known as *Crossover Distortion*
 - Also known as *Deadband Distortion*
 - *Occurs during zero crossings of the signal*
 - *For BJT/MOS Class B stage*, the *input voltage must at least equal V_γ ($\sim 0.6\text{ V}$)/ $V_{TN}(|V_{TP}|)$ ($\sim 0.7\text{-}1\text{ V}$)* for the *output stage transistors to turn on*

- *Class AB:*
 - *Eliminates Crossover Distortion* by *prebiasing the output transistors*
 - *They remain at the verge of conduction in the standby stage*
 - *θ exactly equal to 180°*
 - *η_{max} slightly less than 78.5% due to a small amount of standby power*
 - *Extremely popular and most widely used*

- ***Class B Push-Pull Output Stage:***

- BJT Implementation:***

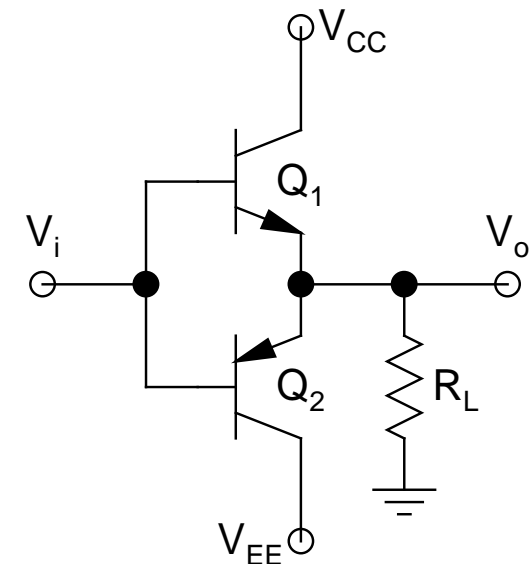
- Also known as ***Complementary Output Stage***
- ***Uses dual symmetric power supplies***
- ***Typical values used:***
 $\pm 3\text{ V}$, $\pm 5\text{ V}$, $\pm 12\text{ V}$, $\pm 15\text{ V}$
- ***Q-point:*** ***$V_i = V_o = 0$***
 $\Rightarrow V_{be1} = V_{eb2} = 0$



Circuit Schematic


- *Both Q_1 and Q_2 cutoff*
 \Rightarrow *Zero standby power*
- *Note: $V_{be1} + V_{eb2} = 0$ (always)*
- *As $V_i \uparrow$ beyond zero, $V_{be1} \uparrow$ and $V_{eb2} \downarrow$*
 \Rightarrow *Q_1 moves towards turning on and Q_2 is pushed deeper into cutoff*
- *V_i has to be at least equal to V_γ for Q_1 to conduct - till then, V_o remains zero*
- *Once V_i becomes greater than V_γ , Q_1 turns on, supplies current to the load (R_L), and V_o starts to increase*

- Similarly, *as $V_i \downarrow$ below zero, $V_{be1} \downarrow$ and $V_{eb2} \uparrow$*
 $\Rightarrow Q_2$ *moves towards turning on* and Q_1 *is pushed deeper into cutoff*
- Again, V_i *has to be at least equal to $-V_\gamma$ for Q_2 to conduct* - till then, V_o *remains zero*
- *Once V_i becomes less than $-V_\gamma$, Q_2 turns on, pulls current away from the load (R_L), and V_o starts to decrease (remains negative)*
- Thus, the name ***Push-Pull***
 - *Each transistor remains on for little less than half a cycle*

 

The Voltage Transfer Characteristic (VTC)

- Note the *deadband* ($V_o = 0$) *between* $\pm V_\gamma$
- Consider *positive* V_i :
 - *For* $V_i > V_\gamma$, V_o follows V_i with a *slope of almost unity* and *without any phase shift* (CC stage)
 - *As* $V_o \uparrow$, $V_{ce1} \downarrow$, and Q_1 starts to move towards saturation
 - \Rightarrow *Positive* $V_{o,max} = V_{CC} - V_{CE1}(HS)$
 - However, for this to happen, V_i has to be greater than V_{CC} (since there is an *extra drop of* V_{be1})
 - \Rightarrow *This point can never be reached*
- *The characteristic for negative V_i can be similarly understood*

 

Crossover Distortion

➤ **Crossover Distortion:**

- **Quantified by ϕ** (refer to the diagram)
- **Expressed as:**

$$\phi = \sin^{-1}(V_\gamma/V_M)$$

V_M : **Amplitude of the input signal**


- **Appears four times over a complete cycle**
- **Parameterized** by a term known as the **Total Crossover Distortion (TCD)**, **expressed in percent:**

$$TCD = (2\phi/\pi) \times 100\%$$

- **This distortion becomes more acute as $V_M \downarrow$**
- **For $V_M \leq V_\gamma$, no output** ($V_o = 0$ always)

- ***MOS Implementation:***

 - *Working principle absolutely similar to BJT implementation*
- *Only exception that V_γ replaced by V_{TN} and V_{TP}*
- ***Q-point:** $V_i = V_o = 0$*
- *Both devices suffer from body effect issue*



Circuit Schematic

- V_{TN} and V_{TP} function of V_o
 - ⇒ VTC significantly nonlinear
 - ⇒ Output shows more distortion
- V_i can't be more than V_{DD} or less than V_{SS}
 - ⇒ V_o can't have rail-to-rail swing
- Also, MOS devices are *inherently much poorer* than their BJT counterparts in terms of *current carrying capability*
 - ⇒ *Makes this stage quite a poor choice*
(needs extremely large W/L ratios)

- *Class AB Push-Pull Output Stage:*

- In a *Class B* stage, *Crossover Distortion* arises because the transistors are *absolutely cold* in the *standby state*, i.e., *dead off*
- If instead, these are *prebiased* at the *verge of conduction*, *but not quite turned on*, then a *slight swing* of the *input either way* can make *one of these transistors turn on* and *either supply current to the load* or *pull current away from the load*
- *This is the whole idea behind a Class AB stage*

- *Either of the output transistors remain on for complete half cycles*
- Thus, it's a *mixture of Class A and Class B operation*
- Hence, it's called *Class AB Push-Pull Stage*
- *Eliminates Crossover Distortion completely*
- *Obvious fallout:*
 - *Dissipation of standby power*
- *Extremely popular topology and widely used*
- *Efficiency drops slightly as compared to a pure Class B stage*

- **BJT Implementation:**

- *Needs additional circuitry*

(I_Q - Q_3 - Q_4)

- Q_3 - Q_4 *diode-connected*

transistors and both


are *biased by the same*

current I_Q

- This produces a *DC bias*

V_{BIAS} between the *bases*

of Q_1 - Q_2

 

Circuit Schematic

- Consider *idling condition* with R_L *open-circuited* ($I_0 = 0$)
- *Neglecting base currents* of Q_1 - Q_2 , I_Q *flows through Q_3 - Q_4* and *develops a voltage drop*:

$$V_{BIAS} = V_{BE3} + V_{BE4} = V_T \ln \left(\frac{I_Q^2}{I_{S3} I_{S4}} \right)$$

- I_Q , I_{S3} , and I_{S4} *chosen such that $V_{BIAS} \approx 2V_\gamma$*
- *Note*: V_{BIAS} *is also equal to* ($V_{BE1} + V_{EB2}$)
 \Rightarrow Q_1 - Q_2 *remain at the verge of conduction, carrying a standby (or idling) current $I_{Standby}$*

- This *extra current* of $(I_Q + I_{\text{standby}})$ causes *standby* (or *idling*) power dissipation
- Noting that:

$$V_{\text{BIAS}} = V_{\text{BE1}} + V_{\text{EB2}} = V_T \ln \left(\frac{I_{\text{Standby}}^2}{I_{S1} I_{S2}} \right)$$

$$\Rightarrow I_{\text{Standby}} = I_Q \sqrt{\frac{I_{S1} I_{S2}}{I_{S3} I_{S4}}}$$

- Now, *Q_1 - Q_2 has to supply/sink large amount of current to/from load* \Rightarrow *Their BE junction areas are made large* \Rightarrow *Large I_{S1} - I_{S2}*


➤ $I_{S1}-I_{S2}$ typically 10 times or more than $I_{S3}-I_{S4}$


⇒ $I_{standby} \geq 10I_Q$

⇒ Adds to the power overhead of the circuit

➤ Another option of prebias circuit:

 - V_{BE} -Multiplier
- $V_{BIAS} = V_{BE3} (1 + R_2/R_1)$
- Values of R_1 and R_2 chosen to give $V_{BIAS} = 2V_\gamma$



 

The Voltage Transfer Characteristic (VTC)


- *The VTC does not pass through origin*
- *Intercepts* (known as *input-output offset*):
 - $V_i = 0, V_o = +V_{EB2}$
 - $V_o = 0, V_i = -V_{EB2}$
- *For $V_i > -V_{EB2}$, $V_{be1} \uparrow$ and $V_{eb2} \downarrow$, with their sum remaining constant at V_{BIAS}*
 - ⇒ *Q_1 starts to conduct and supply current to the load (R_L), while Q_2 starts to go deeper into cutoff*
 - ⇒ *V_o starts to follow V_i with a slope ~ 1 (CC stage)*

- *V_o can rise all the way up to $[V_{CC} - V_{CE1}(HS)]$, provided that V_i can drive it that far*
- Similarly, *for $V_i < -V_{EB2}$, $V_{eb2} \uparrow$ and $V_{be1} \downarrow$, with their sum again remaining constant at V_{BIAS}*
 - \Rightarrow *Q_2 starts to conduct and pull current away from the load (R_L), while Q_1 starts to go deeper into cutoff*
 - \Rightarrow *V_o again starts to follow V_i with a slope ~ 1 , and can go down all the way to $[V_{EE} + V_{EC2}(HS)]$*

➤ *Power Output and Efficiency:*

- Refer to the figure in the next slide
 - ❖ *The constant offset of $|V_{EB2}|$ is neglected*
- *Both transistors are not ON over the entire cycle*
 - ❖ *Q_1 takes care of the positive half cycle*
 - ❖ *Q_2 takes care of the negative half cycle*
- V_{oM} : *Maximum value of V_o*
 - ❖ *Maximum possible swing between $[V_{CC} - V_{CE1}(HS)]$ and $[V_{EE} + V_{EC2}(HS)]$*
- I_{oM} : *Maximum value of load current* ($= V_{oM}/R_L$)
- *Average rms power P_L delivered to load:*
 
$$P_L = \frac{V_{oM}}{\sqrt{2}} \times \frac{I_{oM}}{\sqrt{2}} = \frac{V_{oM}^2}{2R_L}$$



- Now, we need to calculate the *power supplied to the stage by the power supplies*
- The *average current I_{supply} drawn by Q_1 from V_{CC} (happens only during the positive half cycle)*:

$$I_{supply} = \frac{1}{T} \int_0^T I_{c1}(t) dt = \frac{1}{2\pi} \int_0^\pi I_{oM} \sin \theta d\theta = \frac{I_{oM}}{\pi} = \frac{V_{oM}}{\pi R_L}$$

- *The same current will also be pushed by Q_2 to V_{EE} ($= -V_{CC}$) during the negative half cycle*
- *Thus, over a complete cycle, the average supply power P_{supply} drawn from the power supplies:*

$$P_{supply} = 2V_{CC} I_{supply} = 2V_{CC} V_{oM} / (\pi R_L)$$

- Thus, the *power conversion efficiency* (η):

$$\eta = \frac{P_L}{P_{\text{supply}}} = \frac{V_{oM}^2 / (2R_L)}{2V_{CC} V_{oM} / (\pi R_L)} = \frac{\pi V_{oM}}{4V_{CC}}$$

- η directly proportional to V_{oM} , and independent of R_L

\Rightarrow *Significant advantage*

- Also, $V_{oM}(\text{max}) \approx V_{CC}$

$\Rightarrow \eta_{\text{max}} = \pi/4 = 0.785$ (or 78.5%)


- *This value may not be attainable in practice*

❖ For $V_{oM} = -V_{CC}$, V_i has to be less than $-V_{CC}$, which *may not be practically achievable*

❖ This analysis *neglects the standby power* (quite small *though*) \Rightarrow *Inclusion of this term will reduce η_{max}*

➤ *Transistor Ratings:*

- Specified by *two parameters*:
 - ❖ *Breakdown Voltage*
 - ❖ *Maximum Power Rating*
- *Breakdown Voltage*:
 - ❖ *Maximum positive/negative V_{CE} that can be applied to an npn/pnp BJT*
 - Known as the *Collector-to-Emitter Breakdown Voltage with Base Open* (BV_{CE0})
 - ❖ *Focus on Q_1 (Q_2 will be similar)*
 - ❖ Refer to the diagram in the next slide (*Output characteristic of Q_1 along with the load line*)
 - ❖ In the analysis, the *offset in the VTC*, the *small standby current*, and $V_{CE1}(HS)$ are *neglected*

 

The Output Characteristic of Q_1 along with the Load Line

- ❖ *At Q-point: $V_o = 0 \Rightarrow V_{ce1} = V_{CC}$*
- ❖ *During positive half cycle:*
 - $V_o(max) \approx V_{CC} \Rightarrow V_{ce1} \approx 0$
 - $\Rightarrow V_{ce1}$ *ranges between 0 and V_{CC} during the positive half cycle*
- ❖ The *slope of the load line* in this part of the characteristic = $-1/R_L$
- ❖ *For negative half cycle, Q_1 cuts off (Q_2 conducts during this period)*
 - $\Rightarrow I_{c1} = 0$ *for V_o ranging between 0 and $-V_{CC}$*
 - $\Rightarrow V_{ce1}(max) = 2V_{CC}$
 - $\Rightarrow BV_{CE0} = 4V_{CC}$ [using a *Safety Factor* (or *Factor of Safety*) of 2]

■ **Maximum Power Rating:**

❖ *Same for both Q_1 and Q_2*

❖ *Average power P_L delivered by Q_1 to R_L during the positive half cycle = area covered under the load line*

$$\Rightarrow P_L = \frac{1}{2} \times V_{CC} \times \frac{V_{CC}}{R_L} = \frac{V_{CC}^2}{2R_L}$$

❖ Refer to the *constant power hyperbola* ($V_{ce1} \times I_{c1}$) shown in the figure

❖ *Maximum power dissipation of Q_1 happens when this hyperbola becomes tangent to the load line, which is right at the middle of the load line*

❖ *Proof:*

Constant power hyperbola (P_1):

$$P_1 = V_{ce1} \times I_{c1} = (V_{CC} - I_{c1} R_L) \times I_{c1} = V_{CC} I_{c1} - I_{c1}^2 R_L$$

Plug $dP_1/dI_{c1} = 0$ to get $I_{c1} = V_{CC}/(2R_L)$

This is the *mid-point of the load line*, with *coordinates* $[V_{CC}/2, V_{CC}/(2R_L)]$

$$\Rightarrow P_{\max} = \frac{V_{CC}^2}{2R_L} \text{ (using a Safety Factor of 2)}$$


❖ There is also *standby power*:

$$P_{\text{Standby}} = V_{CC} \times I_{\text{Standby}}$$

❖ In general, $P_{\max} \gg P_{\text{Standby}}$

❖ Refer to the figure in the next slide

 - o V_{ce1} *oscillates between 0 and $2V_{CC}$*
- o I_{c1} *appears only during the positive half cycle, with peak value of V_{CC}/R_L (when $V_{ce1} = 0$)*
- o $P_1 (= V_{ce1} \times I_{c1})$ *oscillates* between 0 and $V_{CC}^2/(4R_L)$ at *twice the frequency* only during the *positive half cycle*



❖ *Two Special Cases:*

- o $R_L \rightarrow \infty$ (*open-circuit*):

Load line becomes horizontal with $I_{c1} = 0$

$\Rightarrow P_1 = 0 \Rightarrow$ *no issue*

- o $R_L = 0$ (*short-circuit*):

Load line becomes vertical with $I_{c1} \rightarrow \infty$

Potentially dangerous situation

Resulting power dissipation and consequent heat generation can completely damage the device

❖ *In actual situation, I_{c1} won't reach infinite value due to:*

- o *Limited current driving capability of the driver stage*
- o *Fall of β at high current levels due to High-Level Injection or Kirk Effect*

❖ These two are *in-built self-protection mechanisms*

❖ Nevertheless, *practical output stages need short-circuit protection*

➤ **Linearity and Output Resistance:**

- *While supplying/sinking current to/from load, Q_1/Q_2 operate in CC mode*

$$\Rightarrow A_v = R_L / (R_L + r_{Ei}) \quad (i = 1, 2) \quad (r_{Ei} = V_T / I_{ci})$$

- Thus, if $R_L \gg r_{Ei}$, then $A_v \rightarrow 1$, and *very high linearity in the VTC can be achieved*
- However, r_{Ei} *is not constant* - rather *it changes with the load current*
- Thus, A_v *can depart significantly from unity*, when the *load current is very small* (*large r_{Ei}*)
- Referring to the *VTC*, the *slope of the characteristic near $\pm V_\gamma$* will be *significantly less than unity* (*Class B*)

- However, *as $V_o \uparrow$, load current \uparrow , $r_{Ei} \downarrow$* , and the *VTC starts to attain its maximum slope of unity*
- Thus, *for major part*, the *VTC is highly linear* and *produces an almost distortionless output*
- *Output Resistance:*
 - *Open R_L and look back from the output*
 - $R_o = r_{Ei}$ (*by inspection*), since *bases of Q_1 - Q_2* can be considered to be at *ac ground*
 - R_o *is variable*, but *for major part, extremely small*
- Generally, the *linearity and output resistance* are *calculated* at the *region of maximum slope* of the *VTC*


➤ *Summary:*

- *Quite small standby power*
- *Large current driving capability*
- *Almost linear VTC*
- *Very low distortion at the output*
- $A_v \sim 1$
- *No phase shift between input and output*
- *Very low output resistance*

Thus, this stage is a superb one and is highly popular!

- ***MOS Implementation:***

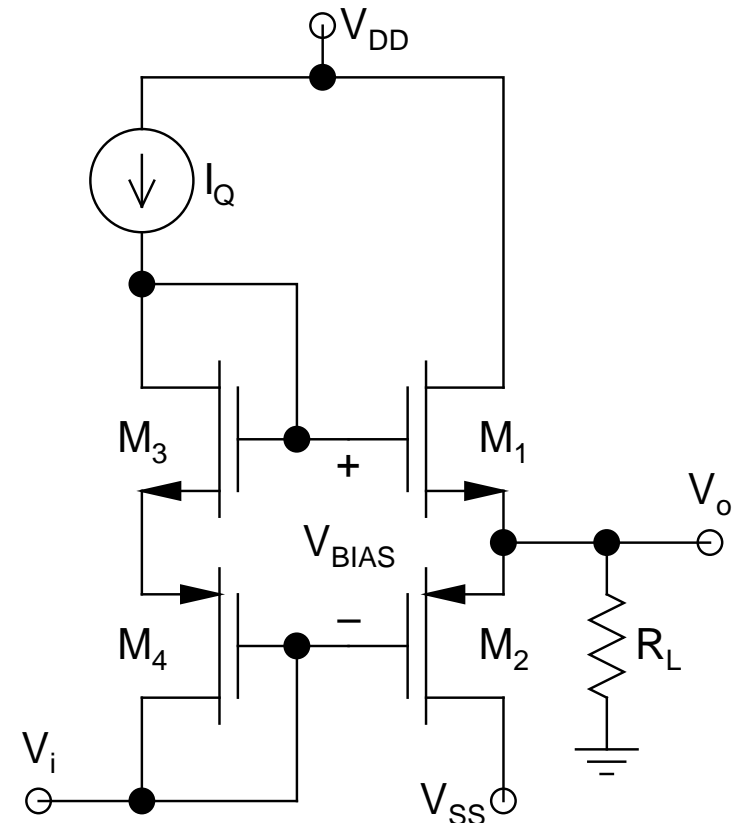- *Biased using dual symmetric power supplies V_{DD}/V_{SS}*
- *M_1 - M_2 in push-pull configuration*
 - *M_1 supplying current to load (R_L) during the positive half cycle*
 - *M_2 pulling current away from load during the negative half cycle*



Circuit Schematic

- M_1 - M_2 *prebiased* by the *series combination* of M_3 - M_4 (*both diode-connected*) *biased with I_Q*
- *Develops V_{BIAS} across the gates of M_3 - M_4* , which is *same as that between the gates of M_1 - M_2*
- *V_{BIAS} chosen to be slightly less than $(V_{TN} + |V_{TP}|)$*
- *Crossover Distortion eliminated completely*, at the cost of *introducing standby power* into the system
- *Rest of the operation of the circuit exactly similar to that of a BJT Class AB Push-Pull Output Stage*


- *All transistors suffer from body effect problem*
⇒ *More distortion at the output*
- *The linearity of the VTC is not that good*
- *Low current drive capability*
- *Biasing itself becomes tricky*, due to the *body effect of M_3 - M_4*
- The *output resistance not that low*, since *MOSFETs have lower g_m than BJTs*
- Overall, the stage *suffers from quite a few problems* and is *not used much*
- We will explore this through an assignment

- **Overload Protection:**

- *Protects the output stage from accidental short-circuits*

- *Needs 4 more components:*

 - **2 BJTs** (Q_5, Q_6)
- **2 Resistors** (R_1, R_2)
 $R_1, R_2 \sim 25\text{-}50\ \Omega$



Circuit Schematic

- During *normal operation*, these *extra circuits* play absolutely *no role*, and come *into picture* only under *accidental short-circuit* of the *output terminal to ground*
- *Numerical Example:*
 - Assume V_i at its *positive peak*, the *maximum drive current* to the base of $Q_1 = 1 \text{ mA}$, and $\beta_1 = 100$
 - Now output gets *accidentally shorted to ground* ($V_o = 0$)
 $\Rightarrow I_{c1} = 100 \text{ mA}$ and $V_{ce1} = 5 \text{ V}$
 $\Rightarrow P_1 = 500 \text{ mW}$
 - This may be *way above* the *maximum power rating* of the transistor ($\sim 100\text{-}150 \text{ mW}$) and the transistor would *burn out* \Rightarrow *potentially dangerous situation!*

➤ *Principle of Operation of the Protection Circuit:*


- Assume *positive* V_i with Q_1 *supplying current to load*
- *Q_2 is off during this time*
- As $R_L \downarrow$, $I_{c1} \uparrow$ (since $I_{c1} = V_o/R_L$)
 $\Rightarrow V_{be5} (= I_{c1}R_1)$ *also* \uparrow
- As $V_{be5} \rightarrow V_\gamma$ of Q_5 , it starts to *turn on*
 \Rightarrow A *part of base drive current* of Q_1 starts to get *shunted away* by Q_5 , and *appears at the output* almost *without any gain* ($1/\alpha_5$)
- This acts as a *limit of the rate* at which the *output current can increase*, and thus, *protects the circuit*

- Thus, the *current can't increase indefinitely*
- Assume $R_1 = 30\ \Omega$ and $V_\gamma = 0.6\text{ V}$
 - \Rightarrow As soon as I_{c1} reaches about 20 mA, Q_5 cuts in, shunts current away from the base of Q_1 , and protects the circuit
- Due to the exponential dependence of this shunted current on V_{be5} , the maximum output current will saturate near around 20 mA itself
- Thus, under this case, if the output is accidentally shorted to ground, then $P_1(\text{max})$ will be around 100 mW, which is well within limit, and protection will be achieved

- Similarly, for the *negative half cycle*, this job of *protection will be achieved by the Q_6 - R_2 combination*
- The *drop across R_2* will depend on the *amount of current* being *sunk by Q_2*
- Once this drop *reaches the cut-in voltage* of Q_6 , it will *turn on*, and *bypass the drive current of Q_2* , thus *protecting the circuit*
- This *protection circuit* is *widely used* due to its *efficacy*, and the *most popular analog building block*, the *op-amp*, *uses this protection scheme*

➤ **Quantitative Estimate of the Protection Mechanism:**

 
- Assume V_i positive and supplying drive current I_i to Q_1
- **Output shorted to ground**
 $\Rightarrow V_o = 0$
- $I_i = I_{b1} + I_{c5}$
 $I_{c5} = I_{S5} \exp(V_{be5}/V_T)$
- $V_{be5} = I_{c1} R_1$ (assuming $\alpha_1 = 1$ and neglecting I_{b5})



Protection Scheme

- For *small values* of I_{c1} , V_{be5} will be *small*, and I_{c5} will be *negligible*
- Also, $I_{c1} = \beta_1 I_{b1} = \beta_1 (I_i - I_{c5})$
 $\Rightarrow \beta_1 I_i = I_{c1} + \beta_1 I_{S5} \exp(I_{c1} R_1 / V_T)$
- This is the *final protection expression*
- For *small* I_{c1} , the *second term* on the *RHS* will be *negligible*
 $\Rightarrow I_{c1}$ would follow I_i linearly with proportionality constant β_1
- As $I_{c1} \uparrow$, the *second term* on the RHS *increases at a much more rapid rate* than the *first term*

 - Once it starts to become *comparable* to the first term, a *very little change* in I_{c1} can *counter a large change* in I_i
 $\Rightarrow I_{c1}$ gets clamped to almost a constant value of $I_{c1,max}$
- Note that the *protection equation* is *transcendental*
 \Rightarrow Needs numerical or iterative solution



Protection Characteristic