

Sinusoidal Steady-State Response

- Deals with response of circuits under *sinusoidal* (sine or cosine functions) excitations (*voltage* or *current*)
- The signals are *periodic* function of time
- There is no *transient* disturbance (all *perturbations* have settled down)
- To discuss about: *phasors*, *impedance*, *admittance*, and *response* of RC and RL circuits to *sinusoidal excitation*

- ***Sinusoidal Signals and Phasors:***

- * Sinusoidal signals can be expressed as:

$$v(t) = V_M \sin(\omega t + \phi)$$

V_M : ***Peak Value*** (also known as ***amplitude***)

ω : ***Angular Frequency*** (radians/second)


$= 2\pi f$, f : ***Cyclic Frequency*** [per second or Hertz (Hz)]

ϕ : ***Phase Angle*** (radians) (***Note***: π radians = 180°)


- * Another important term: ***Time Period*** (T) (second)

$$T = 1/f = 2\pi/\omega$$

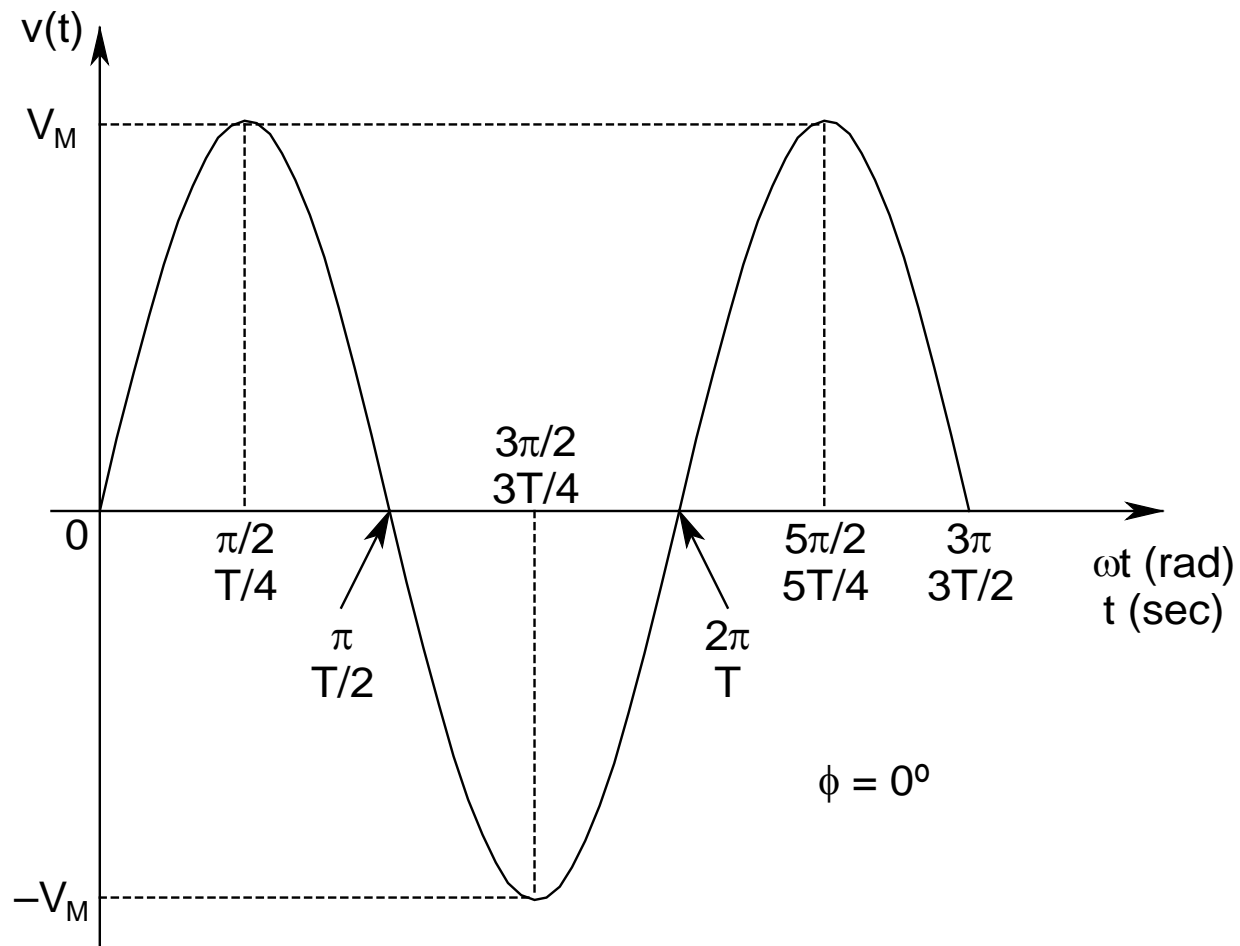- * ***Note***: During one time period, the signal sweeps an angle of 2π



Concept of Lead/Lag:

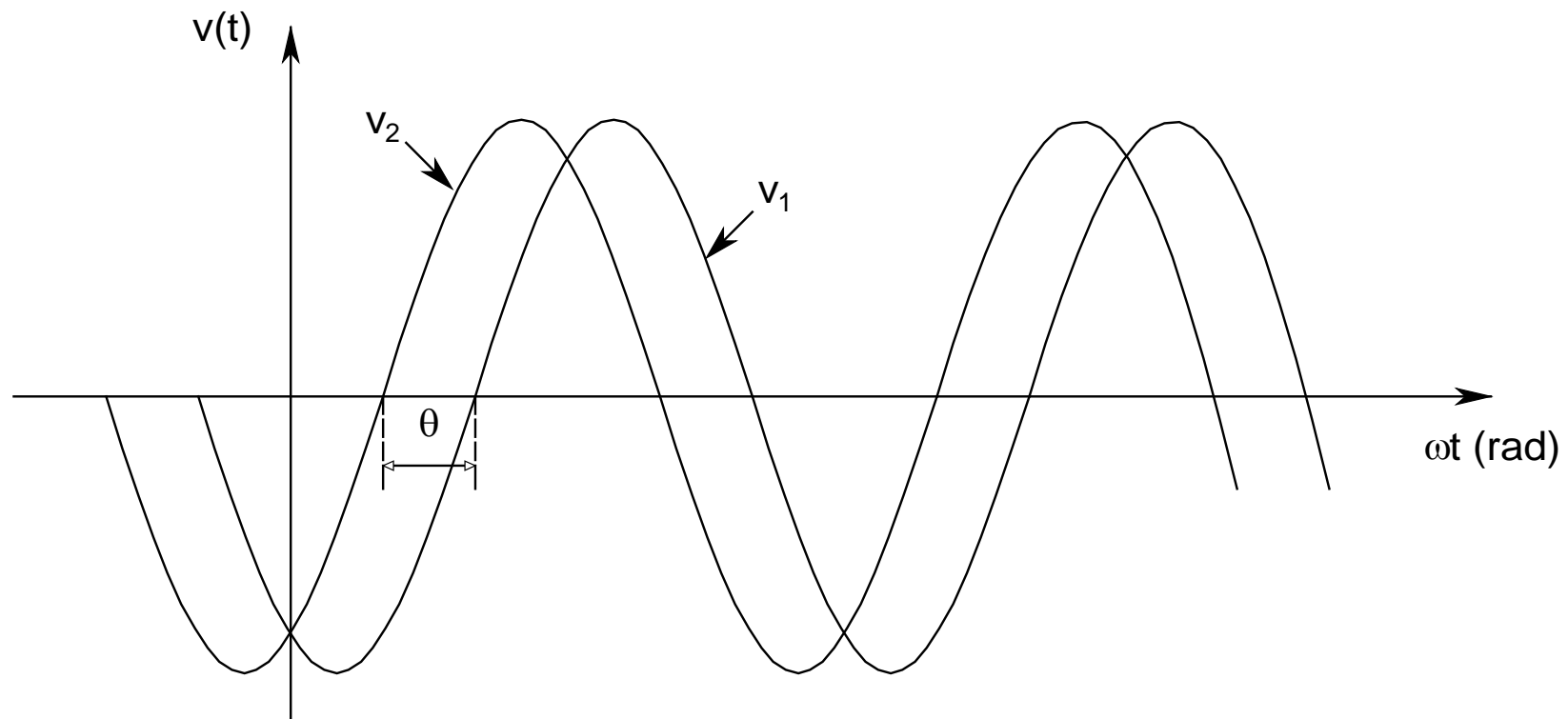

v_2 leads v_1 , or conversely, v_1 lags v_2
 θ : Phase difference between v_1 and v_2

- * Going along the time scale, the first signal encountered having a *positive* going excursion is *leading* the rest of the signals
- * *Ex:* In the figure, v_2 is leading v_1 , or conversely, v_1 is lagging v_2
- * When $\theta = 0^\circ$, signals v_1 and v_2 overlap, and are known as *in-phase* signals
- * When $\theta \neq 0^\circ$, these signals are known as *out-of-phase* signals
- * When $\theta = 180^\circ$, they are *exactly* out-of-phase

- * **Note:** The algebraic sum of two exactly equal in-phase signals is ***double*** of either of them, whereas the algebraic sum of two exactly equal and exactly out-of-phase signals is ***zero***
- * **Note:** Leading by θ also implies lagging by $(360^\circ - \theta)$
 \Rightarrow Depends on the ***Frame of Reference***
- * ***Useful trigonometric identities:***

$$\pm \sin(\omega t) = \cos\left(\omega t \mp \frac{\pi}{2}\right) \text{ and}$$

$$\pm \cos(\omega t) = \sin\left(\omega t \pm \frac{\pi}{2}\right)$$

Concept of Phasors:

- * While representing sinusoidal signals either in *angular sweep domain* or *time domain* (i.e., ωt or t respectively), confusion may arise regarding whether a given waveform is *leading* or *lagging* some other waveforms
- * This confusion can largely be eliminated by representing sinusoidal signals as *phasors*
- * **Note:** Sinusoidal signals can also be expressed as complex numbers by using *Euler's identity* :
$$\exp(j\theta) = \cos \theta + j \sin \theta$$

* ***Differential equations*** that need to be solved to obtain the response of a circuit become pure ***algebraic equations*** \Rightarrow the advantage is obvious

* ***Euler's identity*** draws out a unit circle in the ***complex plane***, since


$$|\exp(j\theta)| = \sqrt{\cos^2 \theta + \sin^2 \theta} = 1$$

$$\Rightarrow A \exp(j\theta) = A \cos \theta + jA \sin \theta = A \angle \theta$$

$A \angle \theta$: known as a ***phasor***, expressed in ***polar form***

* ***Note***: Any complex number $(a + jb)$ can be

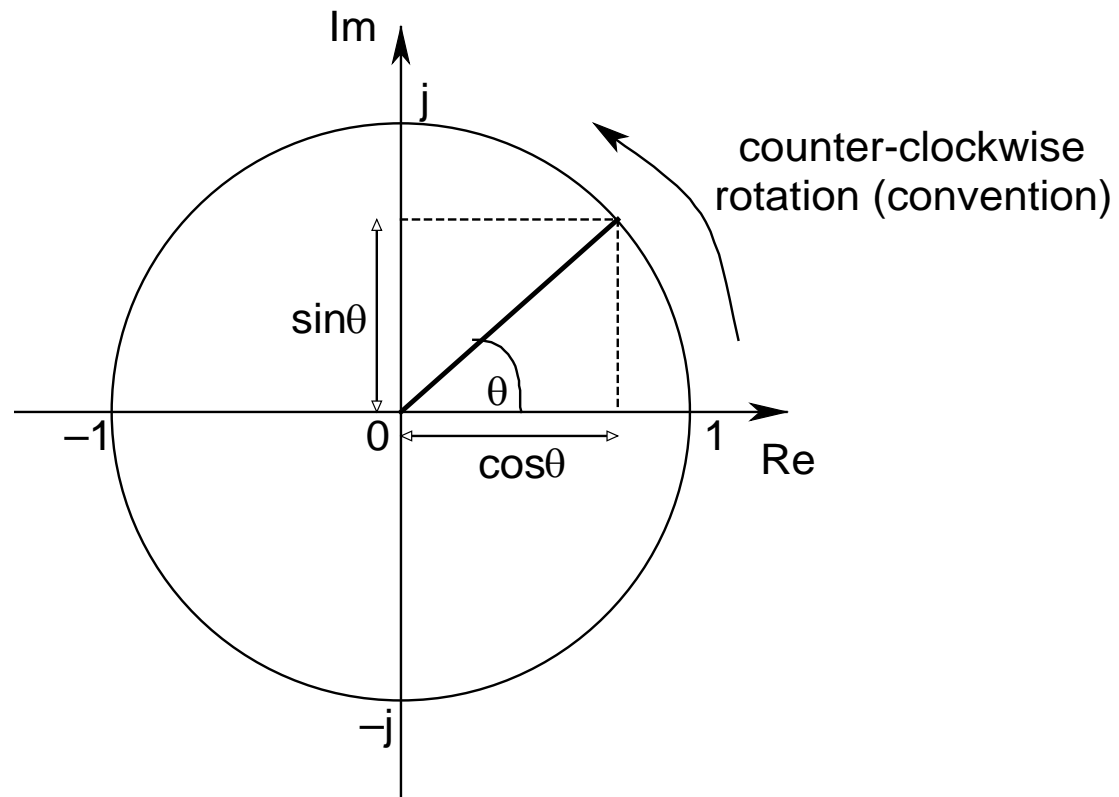expressed as $A \angle \theta$, with $A = \sqrt{a^2 + b^2}$ and $\theta = \tan^{-1}(b/a)$



Rotating Unit Phasor

- * A sinusoidal function can be expressed in ***polar form***, and thus can be represented as a ***phasor*** as:

$$A \cos(\omega t + \theta) = \mathbf{Re} \left[A \exp \{ j(\omega t + \theta) \} \right]$$

- * Thus, the ***time domain*** representation of a sinusoidal function of the form:

$$\begin{aligned} v(t) &= V_M \cos(\omega t + \theta) = \mathbf{Re} \left[V_M \exp \{ j(\omega t + \theta) \} \right] \\ &= \mathbf{Re} \left[V_M \exp(j\theta) \exp(j\omega t) \right] \end{aligned}$$

can be expressed in ***polar form*** (or in ***phasor representation***) as:

$$\bar{V}(j\omega) = V_M \exp(j\theta) = V_M \angle \theta$$

- * Note the ***bar sign*** above V , implying that it is a ***phasor***
- * This representation basically implies that the phasor \bar{V} is rotating ***anti-clockwise*** in the complex plane with an angular frequency ω , subtending an angle of θ (***referenced to a pure cosine signal***) at any given time t
- * ***Note:*** After conversion to the phasor notation, the information regarding the angular frequency ω gets ***suppressed***

* **Example:** $2\cos(50t) \Leftrightarrow 2\angle 0^\circ$

$$5\cos(100t + 30^\circ) \Leftrightarrow 5\angle 30^\circ$$

* **Note:** The two examples are for two different frequencies, however, the phasor representations *hide* this information

* That's why the LHS has the term $(j\omega)$ associated with \bar{V}


* With phasor representations, it becomes easy to visualize the *leading* or *lagging* phenomenon of various waveforms

Example: Consider two waveforms:

$$v_1 = V_{M1} \cos(\omega t + 105^\circ) \text{ and}$$

$$v_2 = V_{M2} \cos(\omega t - 45^\circ)$$

with $V_{M1} > V_{M2}$

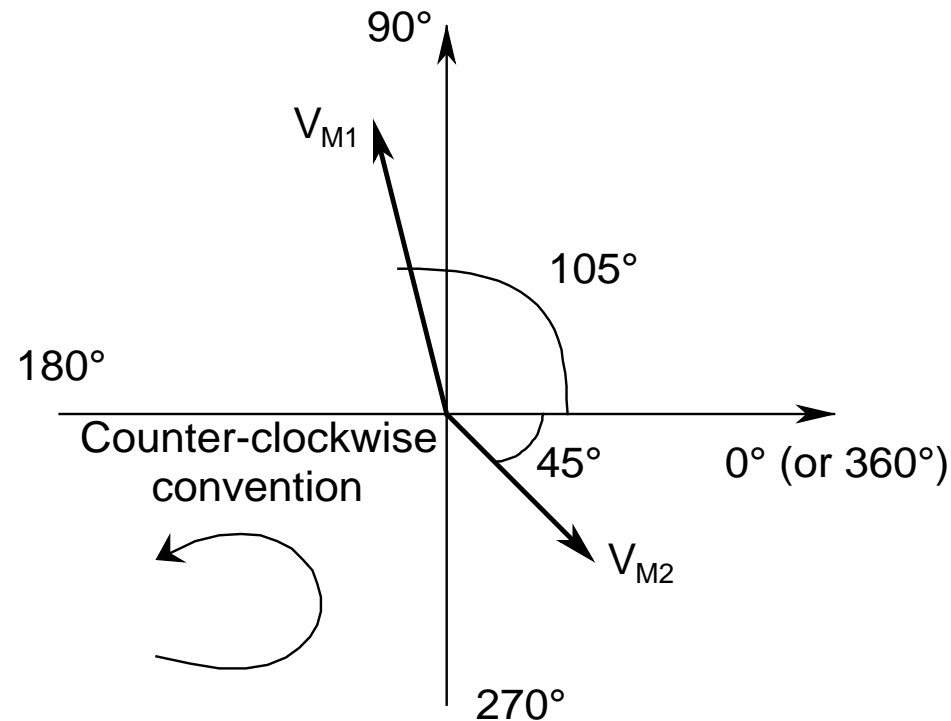

- * **Caution:** For two phasors to be plotted on the same graph, they must have the *same* angular frequency ω
- * From the plot, it can be observed that v_1 *leads* v_2 by 150° , or, equivalently, v_2 *lags* v_1 by 150°
- * It can also be conversely stated as v_2 *leads* v_1 by 210° , or, equivalently, v_1 *lags* v_2 by 210°
- * Both are technically correct, however, in general, the angle of lead or lag is generally expressed as a number that is *less* than 180°

- * Therefore, the *first* representation is the *correct* one
- * *Caution:* To convert a *sine* function to a phasor, must transform it to a *cosine* function first, using the *trigonometrical identities* given earlier
- * Phasors can be treated as *algebraic variables*
 \Rightarrow various *algebraic functions* can be performed on them

Phasor Algebra:

* Let $v_1(t) = 5\cos(\omega t + \pi/6)$ and

$$v_2(t) = 10\cos(\omega t - \pi/4)$$

* Both signals have *same frequency*, and both are in *cosine representation*

\Rightarrow *phasor algebra* can be performed on them

* $\bar{V}_1(j\omega) = 5\angle 30^\circ = 5\cos 30^\circ + j5\sin 30^\circ = 4.33 + j2.5$

$$\begin{aligned}\bar{V}_2(j\omega) &= 10\angle -45^\circ = 10\cos(-45^\circ) + j10\sin(-45^\circ) \\ &= 7.07 - j7.07\end{aligned}$$

$$\begin{aligned}
 v_1(t) + v_2(t) &= \bar{V}_1(j\omega) + \bar{V}_2(j\omega) \\
 &= 11.4 - j4.57 = 12.28 \angle -21.84^\circ \\
 &= 12.28 \cos(\omega t - 21.84^\circ)
 \end{aligned}$$

* Similarly,

$$\begin{aligned}
 v_1(t) - v_2(t) &= \bar{V}_1(j\omega) - \bar{V}_2(j\omega) \\
 &= -2.74 + j9.57 = 9.95 \angle 105.98^\circ \\
 &= 9.95 \cos(\omega t + 105.98^\circ)
 \end{aligned}$$

* Be very careful while finding the angle (θ)

Observations:

- * If both cos and sin terms are ***positive***
 \Rightarrow ***first quadrant*** and θ will be between 0° and 90°
- * If sin term is ***positive*** but cos term is ***negative***
 \Rightarrow ***second quadrant*** and θ will be between 90° and 180°
- * If both terms are ***negative***
 \Rightarrow ***third quadrant*** and θ will be between -90° and -180°
- * If cos term is ***positive*** but sin term is ***negative***
 \Rightarrow ***fourth quadrant*** and θ will be between 0° and -90°

Note:

- * Phasor algebra can be done if and only if the sinusoids are of the ***same frequency***
- * If the sinusoids have different frequencies, then phasor algebra will ***not*** be applicable
- * Under such a condition, the response of the circuit for each individual frequencies should be evaluated, and the net response will be given by a ***superposition*** of all these results
- * We will be showing this example later

Example:

Let $v_1(t) = 10 \cos(\omega t - 60^\circ)$ and

$$v_2(t) = 5 \sin(\omega t + 135^\circ)$$

Both signals have same frequency, however, while v_1 is in cos form, v_2 is in sin form

In order to apply the phasor algebra, we need to convert v_2 to cos form as well, and then proceed

$$\begin{aligned} v_1(t) + v_2(t) &= 10 \cos(\omega t - 60^\circ) + 5 \sin(\omega t + 135^\circ) \\ &= 10 \cos(\omega t - 60^\circ) + 5 \cos(\omega t + 45^\circ) \\ &= 10 \angle -60^\circ + 5 \angle 45^\circ = 8.54 - j5.12 \\ &= 9.96 \angle -30.94^\circ = 9.96 \cos(\omega t - 30.94^\circ) \end{aligned}$$

- ***Impedance:***

- The value of a pure resistance does not change with frequency (neglecting *skin effect*)
- However, for inductors and capacitors under sinusoidal excitation, the *resistance* offered by them to the current flow is *frequency dependent*
- These are *complex resistances*, and are known as *impedance* (impediment to current flow)
- Impedances are of two types: *capacitive* and *inductive* (note that both are *imaginary*)
- Both have unit of *ohm* (Ω)
- Resistors have *real* impedance, which is equal to their resistance


Resistors, Resistance, and Resistive Impedance:

$$\text{Let } v_s(t) = V_M \cos(\omega t) = v_R(t)$$

$$\text{Phasor: } \bar{V}_R(j\omega) = V_M \angle 0^\circ$$

$$i(t) = v_R(t) / R = (V_M / R) \cos(\omega t)$$
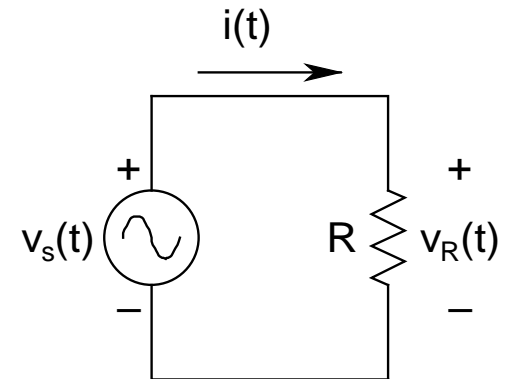
$$\text{Phasor: } \bar{I}(j\omega) = (V_M / R) \angle 0^\circ$$




Inference: The current through a resistor and the voltage across it are ***in-phase***

Voltage dropped across R $[v_R(t)]$ in phasor form:

$$\bar{V}_R(j\omega) = \bar{I}(j\omega) R$$

Resistive Impedance:
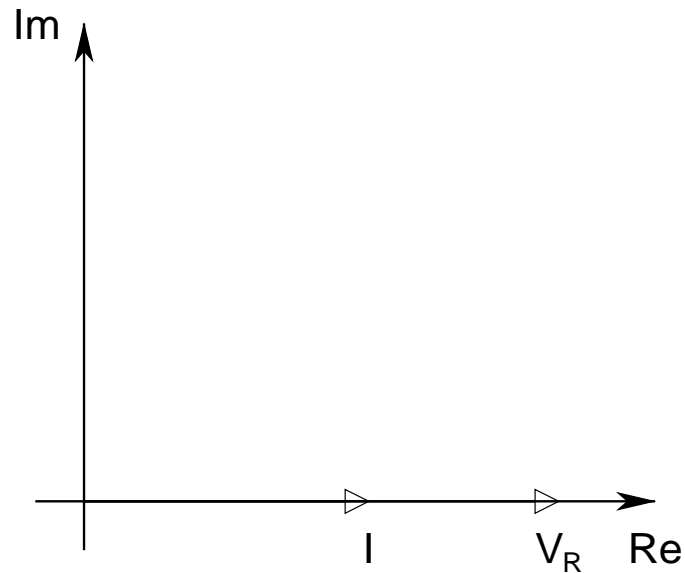
$$Z_R = \bar{V}_R(j\omega) / \bar{I}(j\omega) = R$$



Note: Both the phasors \bar{I} and \bar{V}_R are *in-phase*

Also, both of them lie on the *real* axis on the complex plane

The ratio of \bar{V}_R and \bar{I} is the *resistive impedance*,


which is *real* and is equal to the value of the resistance (R)

Inductors, Inductive Impedance, and Inductive Reactance:

$$\text{Let } v_s(t) = V_M \cos(\omega t)$$

$$v_L(t) = v_s(t) = L \frac{di(t)}{dt}$$

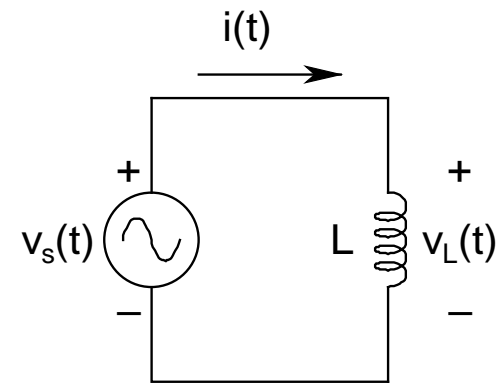
$$\begin{aligned} \Rightarrow i(t) &= \frac{1}{L} \int v_L(t) dt = \frac{V_M}{\omega L} \sin(\omega t) \\ &= \frac{V_M}{\omega L} \cos\left(\omega t - \frac{\pi}{2}\right) \end{aligned}$$



In ***phasor*** notation:

$$\bar{V}_L(j\omega) = V_M \angle 0^\circ \text{ and } \bar{I}(j\omega) = \left[V_M / (\omega L) \right] \angle -90^\circ$$

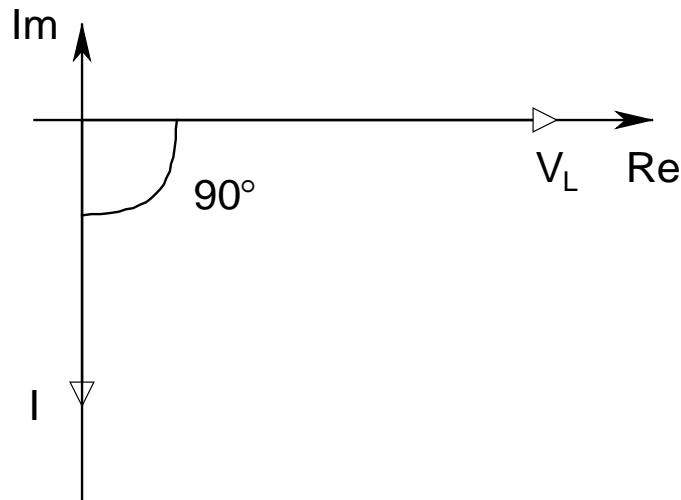Thus, the inductor current ***lags*** the inductor voltage by 90°



Note: The phasors \bar{I} and \bar{V}_L are *out-of-phase*, with \bar{I} *lagging* \bar{V}_L by 90°

$$\textbf{Inductive Impedance} = Z_L(j\omega) = \frac{\bar{V}_L(j\omega)}{\bar{I}(j\omega)} = \omega L \angle 90^\circ = j\omega L$$

where j implies a rotation of $+90^\circ$

Important Observations:

- * Inductive impedance Z_L is a ***complex*** number
- * It is a purely ***imaginary*** number, with no real part
- * It is a ***direct*** function of the angular frequency ω
- * For very low frequency, as $\omega \rightarrow 0$, $Z_L \rightarrow 0$
 \Rightarrow Thus, for ***dc***, inductors behave as ***short-circuits***


- * For very high frequency, as $\omega \rightarrow \infty$, $Z_L \rightarrow \infty$
 \Rightarrow Implies that inductors behave like *open-circuits* for *very high frequencies*
- * Z_L is also expressed as: $Z_L = jX_L$
 $X_L = \omega L \Rightarrow$ known as *inductive reactance*
- * **Note:** While Z_L is imaginary, X_L is real

Capacitors, Capacitive Impedance, and Capacitive Reactance:

$$\text{Let } v_s(t) = v_C(t) = V_M \cos(\omega t)$$

$$i(t) = C \frac{dv_C(t)}{dt} = -V_M \omega C \sin(\omega t)$$

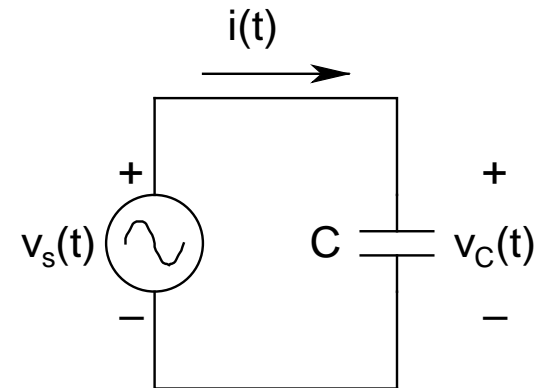
$$= V_M \omega C \cos\left(\omega t + \frac{\pi}{2}\right)$$



In *phasor* notation:

$$\bar{V}_C(j\omega) = V_M \angle 0^\circ \text{ and } \bar{I}(j\omega) = V_M \omega C \angle 90^\circ$$

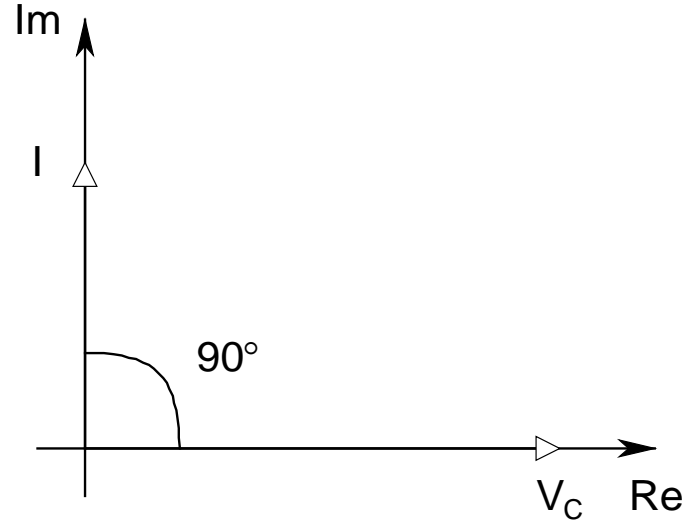Thus, the capacitor current *leads* the capacitor voltage by 90°



Note: The phasors \bar{I} and \bar{V}_C are *out-of-phase*, with \bar{I} *leading* \bar{V}_C by 90°

$$\begin{aligned} \text{Capacitive Impedance} = Z_C(j\omega) &= \frac{\bar{V}_C(j\omega)}{\bar{I}(j\omega)} = \frac{1}{\omega C} \angle -90^\circ \\ &= -\frac{j}{\omega C} = \frac{1}{j\omega C} \end{aligned}$$


Important Observations:

- * Capacitive impedance Z_C also is a ***complex*** number
- * It is also a purely ***imaginary*** number, with no real part
- * It is an ***inverse*** function of the angular frequency ω
- * For very low frequency, as $\omega \rightarrow 0$, $Z_C \rightarrow \infty$
 \Rightarrow Thus, for ***dc***, capacitors behave as ***open-circuits***

- * For very high frequency, as $\omega \rightarrow \infty$, $Z_C \rightarrow 0$
 \Rightarrow Implies that capacitors behave like *short-circuits* for *very high frequencies*
- * Z_C is also expressed as: $Z_C = -jX_C$
 $X_C = 1/(\omega C) \Rightarrow$ known as *capacitive reactance*
- * **Note:** While Z_C is imaginary, X_C is real

Complex Impedance Plane:

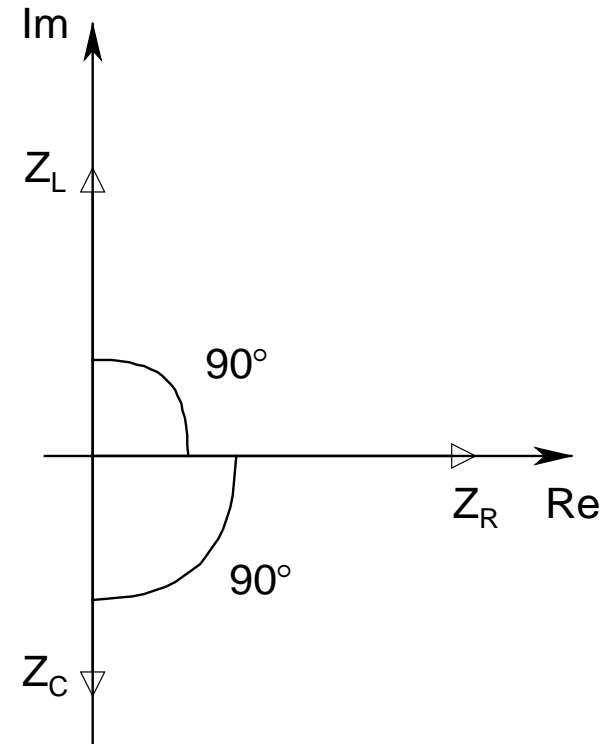- * Resistive impedance Z_R is along the *positive* real axis
- * Inductive and capacitive impedances Z_L and Z_C are along the positive and negative *imaginary* axes, respectively
- * For a pure resistance, the impedance is *real*
- * For a pure inductor or capacitor, the impedance is totally *imaginary*



- * For circuits having inductors and capacitors along with resistors, the impedance would be *complex*, having both real and imaginary parts
- * If $Z_L > |Z_C|$, then the net impedance of the circuit would be *inductive*
- * On the other hand, if $|Z_C| > Z_L$, then the net impedance of the circuit would be *capacitive*
- * If $Z_L = |Z_C|$, then the net impedance of the circuit would be purely *resistive*

* The *general form* of the impedance Z :

$$\begin{aligned} Z &= Z_R + (Z_L - |Z_C|) = R + \left(j\omega L - \frac{j}{\omega C} \right) \\ &= R + j(X_L - X_C) \end{aligned}$$

* *Note*: Z is not a phasor, but just a *complex number*

* Thus, it can be represented in the complex impedance plane by both *magnitude* and *direction*

* In general, impedances are expressed in the *polar* form: $|Z| \angle Z$

$$\text{with } |Z| = \sqrt{R^2 + (X_L - X_C)^2}$$

$$\text{and } \angle Z = \tan^{-1} \left(\frac{X_L - X_C}{R} \right)$$

* For *inductive* circuits, $X_L > X_C$ and $\angle Z$ positive

* For *capacitive* circuits, $X_C > X_L$ and $\angle Z$ negative

* For $X_L = X_C$, circuit becomes purely *resistive* and $\angle Z = 0^\circ$



Series - Parallel Combination of Impedances:

Example: To find Z ($\omega = 20$ krad/sec)

$$5\mu\text{F}: Z_C = -j/(\omega C) \\ = -j10\ \Omega$$

$$1\text{ mH}: Z_L = j\omega L \\ = j20\ \Omega$$

$$10\mu\text{F}: -j5\ \Omega$$

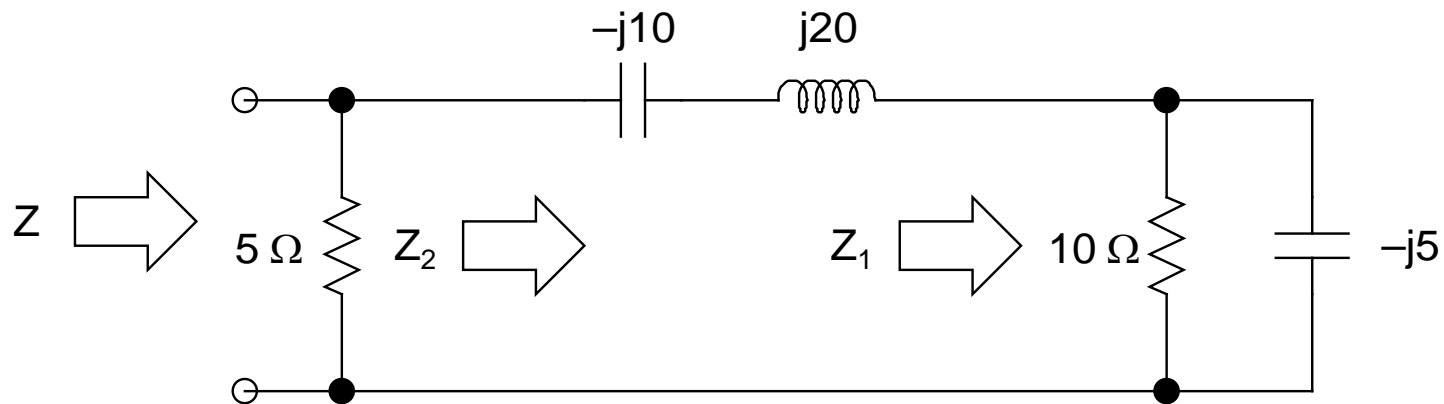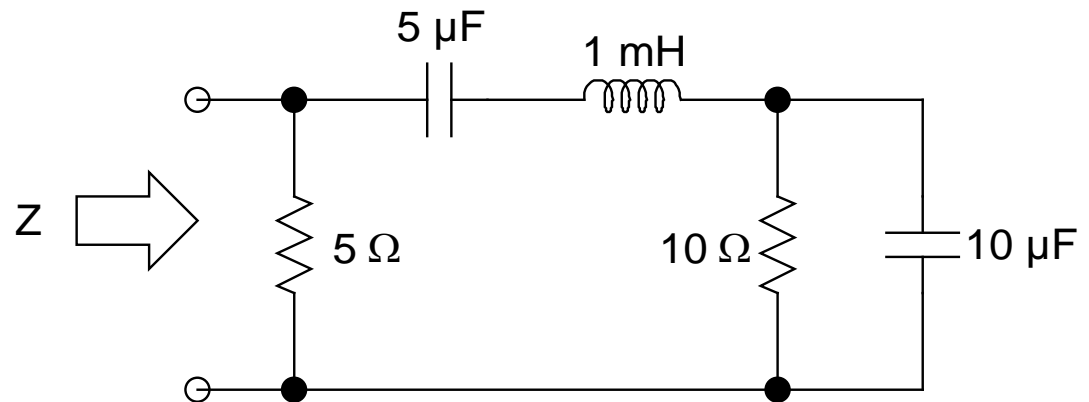

$$Z_1 = 10 \parallel (-j5) = \frac{10 \times (-j5)}{10 - j5} = \frac{50 \angle -90^\circ}{11.18 \angle -26.57^\circ}$$

$$= 4.47 \angle -63.43^\circ = 2 - j4$$

$$Z_2 = -j10 + j20 + 2 - j4 = 2 + j6 = 6.32 \angle 71.57^\circ$$

$$Z = 5 \parallel (6.32 \angle 71.57^\circ) = \frac{5 \times (6.32 \angle 71.57^\circ)}{5 + 2 + j6} = \frac{31.6 \angle 71.57^\circ}{7 + j6}$$

$$= \frac{31.6 \angle 71.57^\circ}{9.22 \angle 40.6^\circ} = 3.43 \angle 30.97^\circ = 2.94 + j1.77 \, \Omega$$

Since the imaginary component of Z is *positive*, hence, the net impedance of the circuit is *inductive* in nature

Admittance (Y):

* Y is the *dual* (or *inverse*) of Z:

$$Y = \frac{1}{Z} = \frac{\bar{I}}{\bar{V}} = G + jB$$

* Has unit of inverse ohm, known as *mho* (Ω)

* G: **Conductance** (inverse of resistance)

* B: **Susceptance** (inverse of reactance)

* **Inductor: Inductive Admittance:**

$$jB_L = 1 / Z_L = 1 / (j\omega L) = -j / (\omega L)$$

$$\Rightarrow \textbf{Inductive Susceptance } B_L = -1 / (\omega L)$$

- * **Note:** While the inductive reactance (X_L) is *positive*, the inductive susceptance (B_L) is *negative*
- * **Capacitor: Capacitive Admittance:**
$$jB_C = 1 / Z_C = j\omega C$$

$$\Rightarrow \text{Capacitive Susceptance } B_C = \omega C$$
- * Again note that while the capacitive impedance (Z_C) is *negative*, the capacitive susceptance (B_C) is *positive*

* The ***general form*** of admittance :

$$Y = G + j(B_C - |B_L|) = G + j\left(\omega C - \frac{1}{\omega L}\right)$$

* ***Caution:*** If some impedance is expressed as $Z = (R + jX)$, and its equivalent admittance representation is $Y = (G + jB)$, then $G \neq 1/R$, and $B \neq 1/X$

* ***Example:*** Let $Z = (8 - j6)$

$$\text{Then, } Y = 1/(8 - j6) = (8 + j6)/10 = 0.8 + j0.6$$

Advantage of Admittance Representation:

- * For impedances in *parallel*, their respective admittances add in *series*
- * This makes the analysis of parallel circuits using the admittance technique quite easy and straightforward

Example: Find Y ($\omega = 1$ krad/sec)


$$G = 1/R = 1/10 = 0.1 \text{ } \overline{\Omega}$$

$$\omega L = 5 \text{ } \Omega, \quad \omega C = 0.05 \text{ } \overline{\Omega}$$

$$Y = G + j \left(\omega C - \frac{1}{\omega L} \right)$$

$$= 0.1 + j \left(0.05 - \frac{1}{5} \right) = 0.1 - j0.15 \text{ } \overline{\Omega}$$
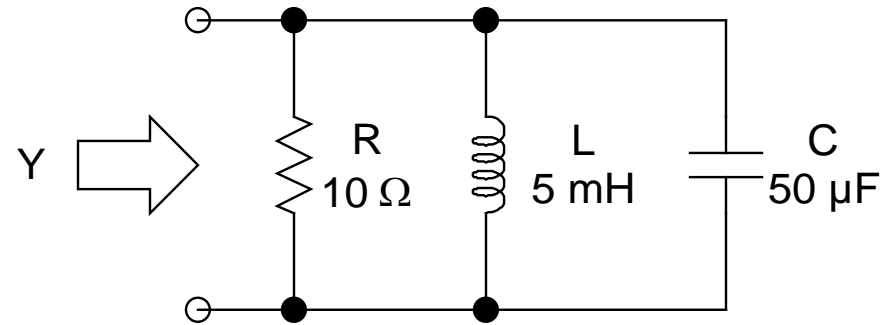
$$Z = \frac{1}{Y} = \frac{1}{0.1 - j0.15} = \frac{0.1 + j0.15}{0.18} = 0.56 + j0.83 \text{ } \Omega$$



RL Circuit:

$$\bar{V}_S = V_M \angle 0^\circ, Z_L = jX_L = j\omega L$$


$$Z = R + jX_L = |Z| \angle Z$$

$$|Z| = \sqrt{R^2 + X_L^2}, \angle Z = \tan^{-1}(X_L / R)$$

$$\bar{I} = \frac{\bar{V}_S}{Z} = \frac{V_M \angle 0^\circ}{|Z| \angle Z} = I_M \angle -\tan^{-1}(X_L / R) \text{ (phasor)}$$

$$I_M = V_M / |Z|$$
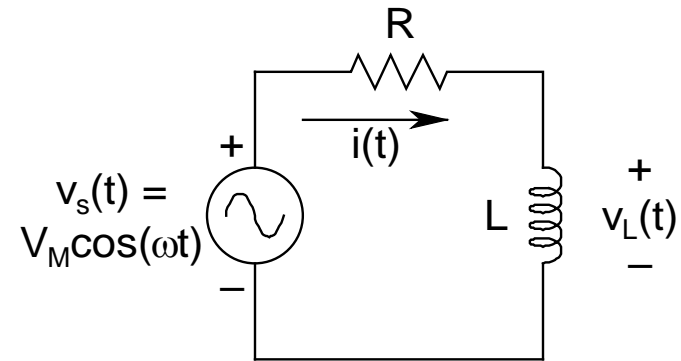
$$i(t) = I_M \cos \left[\omega t - \tan^{-1} \left(\frac{\omega L}{R} \right) \right] \text{ (sinusoidal)}$$



- * ***Caution:*** Sinusoidal and phasor representations should ***never*** be mixed up
[Ex.: $10\sin(50t)/3\angle 30^\circ \rightarrow \textbf{Invalid}$]

Observations:

- * For an inductive circuit, the current ***lags*** the excitation voltage
- * If $L = 0$, then the circuit becomes purely ***resistive***, the phase angle of the current becomes ***zero***, which makes \bar{V}_s and \bar{I} ***in-phase***

- * If $R = 0$, then the circuit turns purely *inductive*, and the phase angle of the current becomes exactly equal to -90° , which implies that the current *lags* \overline{V}_s exactly by 90°
- * For other values of R , the phase angle ranges between 0° and -90°

Another Interesting Observation:


* The voltage appearing across the inductor :

$$\begin{aligned}\bar{V}_L &= \bar{I}Z_L = \left[I_M \angle -\tan^{-1}\left(\frac{\omega L}{R}\right) \right] (\omega L) \angle 90^\circ \\ &= \omega L I_M \angle \left[90^\circ - \tan^{-1}\left(\frac{\omega L}{R}\right) \right]\end{aligned}$$

* Thus, the inductor voltage always ***leads*** the inductor current by ***90°***

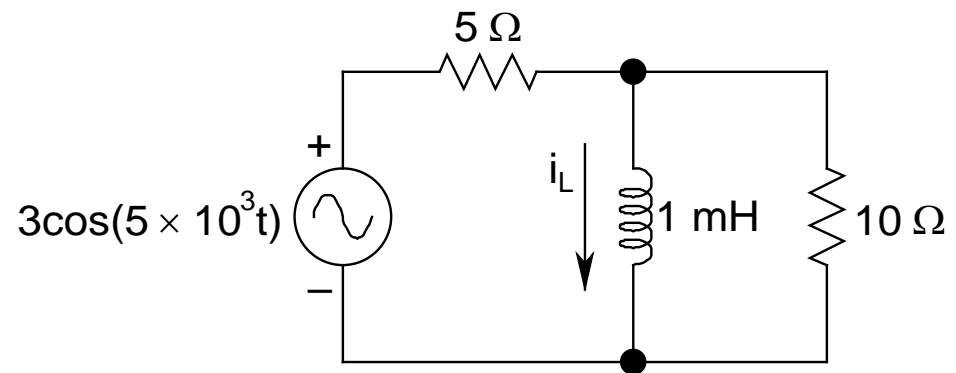Example: Find i_L , and express it in both ***phasor*** and ***sinusoidal*** representations:

First, apply Thevenin's technique by opening the inductor from the circuit and finding the open-circuit (or Thevenin) voltage V_T and the Thevenin resistance R_T appearing between these two terminals



By inspection:

$$\begin{aligned} V_T &= (10/15) \times 3 \cos(5 \times 10^3 t) \\ &= 2 \cos(5 \times 10^3 t) \end{aligned}$$

$$R_T = 5 \parallel 10 = 3.33 \, \Omega$$


$$X_L = \omega L = 5 \times 10^3 \times 10^{-3} = 5 \, \Omega$$

$$|Z| = \sqrt{R^2 + X_L^2} = \sqrt{3.33^2 + 5^2} = 6 \, \Omega$$

$$\angle Z = \tan^{-1}(X_L / R) = \tan^{-1}(5 / 3.33) = 56.34^\circ$$

$$\Rightarrow \bar{I}_L = (2/6) \angle -56.34^\circ = 0.33 \angle -56.34^\circ \text{ A } (\textit{phasor})$$
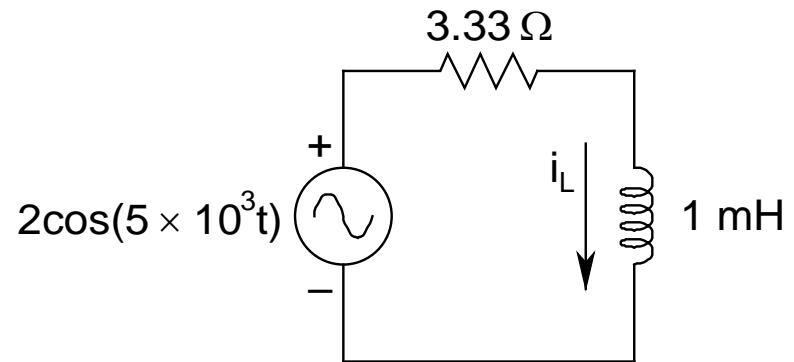
$$i_L(t) = 0.33 \cos(5 \times 10^3 t - 56.34^\circ) \text{ A } (\textit{sinusoidal})$$



RC Circuit:

$$\bar{V}_S = V_M \angle 0^\circ, Z_C = -jX_C = -j / (\omega C)$$


$$Z = R - jX_C = |Z| \angle Z$$

$$|Z| = \sqrt{R^2 + X_C^2}, \angle Z = -\tan^{-1}(X_C / R)$$

$$\bar{I} = \frac{\bar{V}_S}{Z} = \frac{V_M \angle 0^\circ}{|Z| \angle Z} = I_M \angle \tan^{-1}(X_C / R) \text{ (*phasor*)}$$

$$I_M = V_M / |Z|$$
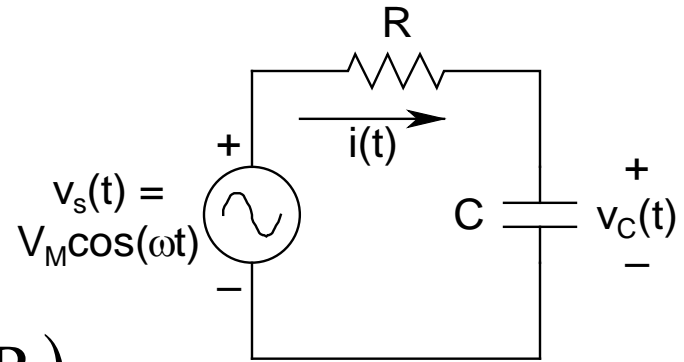
$$i(t) = I_M \cos \left[\omega t + \tan^{-1} \left(\frac{1}{\omega RC} \right) \right] \text{ (*sinusoidal*)}$$



Observations:

- * For a *capacitive* circuit, the current *leads* the excitation voltage
- * If $C \rightarrow \infty$, consequently $Z_C \rightarrow 0$, then the circuit becomes purely *resistive*, the phase angle of the current becomes *zero*, which makes \bar{V}_s and \bar{I} *in-phase*
- * If $R = 0$, then the circuit turns purely *capacitive*, and the phase angle of the current becomes *exactly* equal to 90° , which implies that the current *leads* \bar{V}_s exactly by 90°

- * For other values of R, the phase angle ranges between 0° and 90°
- * The voltage appearing across the capacitor:

$$\begin{aligned}\bar{V}_C &= \bar{I}Z_C = \left[I_M \angle \tan^{-1} \left(\frac{1}{\omega RC} \right) \right] \left(\frac{1}{\omega C} \right) \angle -90^\circ \\ &= \left(\frac{I_M}{\omega C} \right) \angle \left[\tan^{-1} \left(\frac{1}{\omega RC} \right) - 90^\circ \right]\end{aligned}$$

- * Thus, the capacitor voltage always ***lags*** the capacitor current by 90°

Phasor Analysis of AC Circuits:

All the circuit analysis techniques discussed earlier, viz. the ***node voltage method***, the ***mesh current method***, the ***superposition principle***, and the ***Thevenin and Norton techniques***, are applicable for ac circuits as well

Example: Using phasor analysis, find \bar{I}_1 , \bar{I}_2 , and \bar{I}_3 , and plot them.

$$Z_2 = \frac{10 \times (-j10)}{10 - j10} = \frac{100 \angle -90^\circ}{14.14 \angle -45^\circ}$$


$$= 7.07 \angle -45^\circ = 5 - j5 \, \Omega$$

$$Z_1 = j10 + Z_2 = 5 + j5$$

$$= 7.07 \angle 45^\circ \, \Omega$$

$$\bar{I}_1 = \frac{10 \angle 0^\circ}{7.07 \angle 45^\circ} = 1.41 \angle -45^\circ \, \text{A}$$

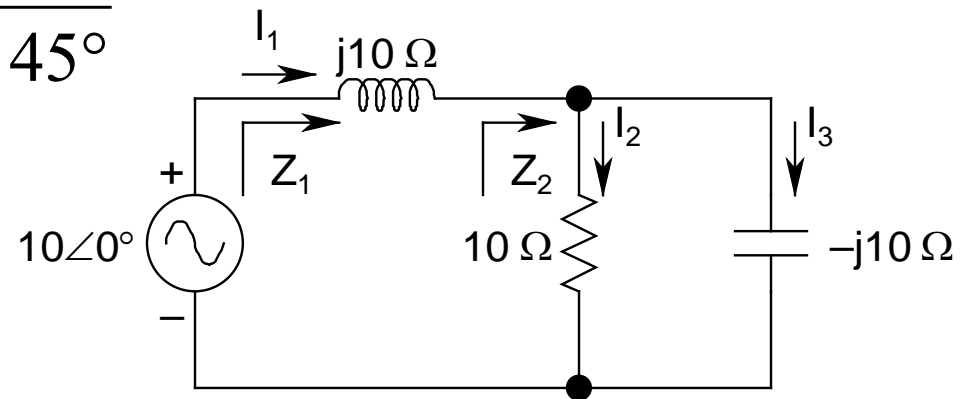
Note: \bar{I}_1 *lags* the excitation voltage \Rightarrow net impedance is *inductive* \Rightarrow corroborated by the expression of Z_1




$$\bar{I}_2 = \frac{-j10}{10 - j10} \times \bar{I}_1 = \frac{10 \angle -90^\circ}{14.14 \angle -45^\circ} \times 1.41 \angle -45^\circ = 1 \angle -90^\circ \text{ A}$$

$$\bar{I}_3 = \frac{10}{10 - j10} \times \bar{I}_1 = \frac{10 \angle 0^\circ}{14.14 \angle -45^\circ} \times 1.41 \angle -45^\circ = 1 \angle 0^\circ \text{ A}$$

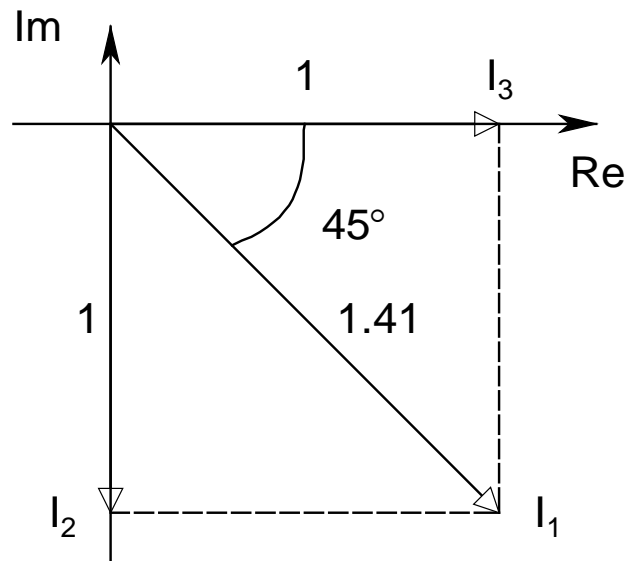Note: \bar{I}_1 is somewhat like a vector sum of \bar{I}_2 and \bar{I}_3



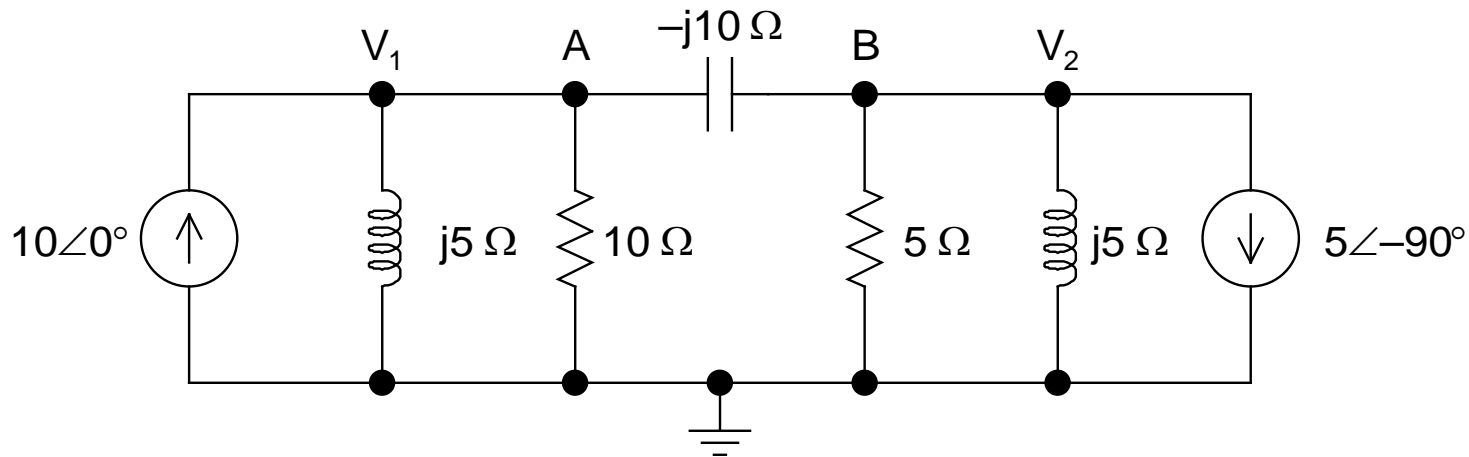Example: Using node voltage method, find \bar{V}_1 and \bar{V}_2 .



KCL at node A:

$$10\angle 0^\circ = \frac{\bar{V}_1}{j5} + \frac{\bar{V}_1}{10} + \frac{\bar{V}_1 - \bar{V}_2}{-j10}$$

$$\Rightarrow (0.1 - j0.1)\bar{V}_1 - j0.1\bar{V}_2 = 10 \quad (1)$$

KCL at node B:

$$\frac{\bar{V}_1 - \bar{V}_2}{-j10} = \frac{\bar{V}_2}{5} + \frac{\bar{V}_2}{j5} + 5\angle -90^\circ$$



$$\Rightarrow j0.1\bar{V}_1 - (0.2 - j0.1)\bar{V}_2 = -j5 \quad (2)$$

Simultaneous solution of (1) and (2) gives:

$$\bar{V}_1 = 50.3\angle 22.58^\circ = (46.44 + j19.31) \text{ V}$$

$$\bar{V}_2 = 43.9\angle 127.87^\circ = (-26.94 + j34.65) \text{ V}$$

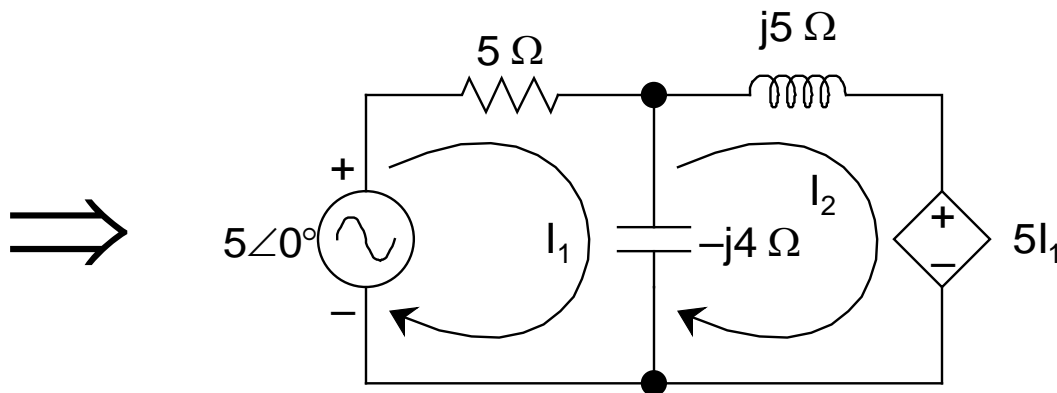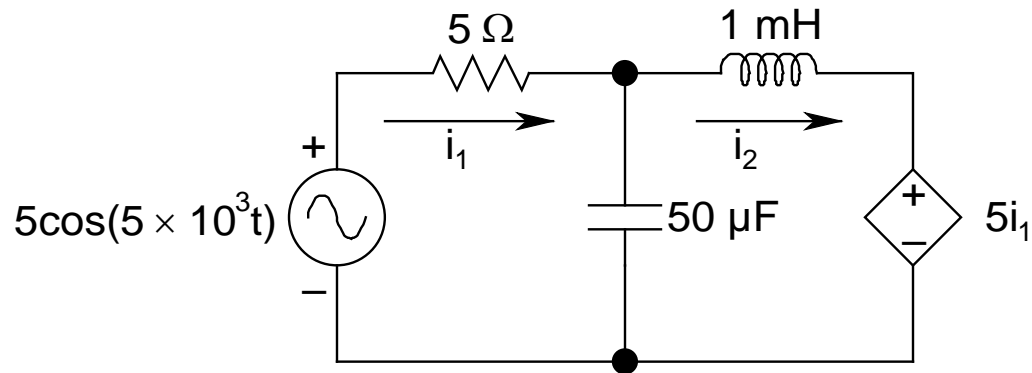Example: Using mesh current method, find the phasor representations of i_1 and i_2 ($\omega = 5$ krad/sec).



KVL in loop 1:

$$5\angle 0 = 5\bar{I}_1 - j4(\bar{I}_1 - \bar{I}_2) = (5 - j4)\bar{I}_1 + j4\bar{I}_2 \quad (1)$$



KVL in loop 2:

$$0 = -j4(\bar{I}_2 - \bar{I}_1) + j5\bar{I}_2 + 5\bar{I}_1 = (5 + j4)\bar{I}_1 + j\bar{I}_2 \quad (2)$$

Simultaneous solution of (1) and (2) gives:

$$\bar{I}_1 = 0.2\angle -143.13^\circ \text{ A} \quad \text{and} \quad \bar{I}_2 = 1.28\angle -104.47^\circ \text{ A}$$

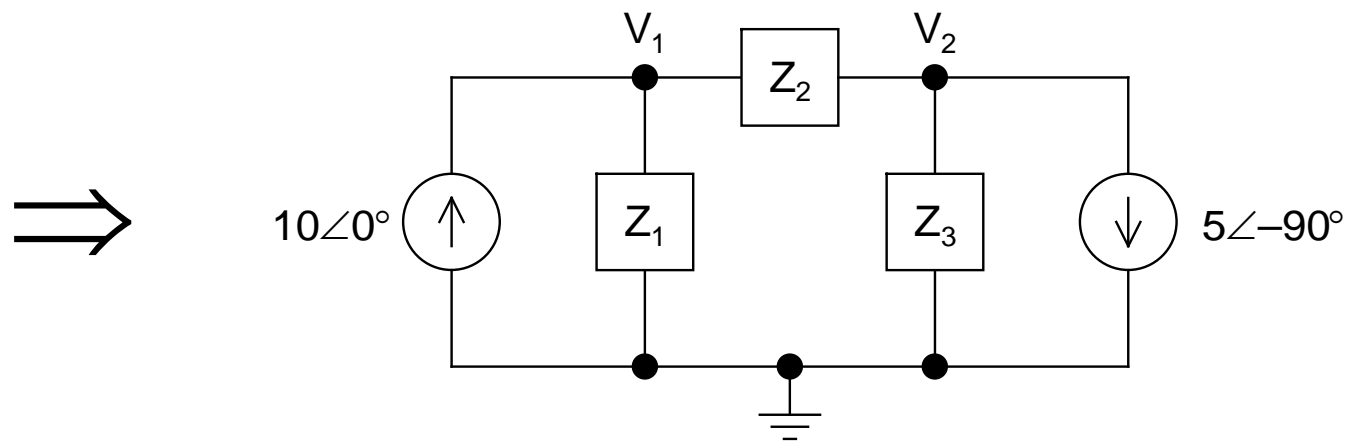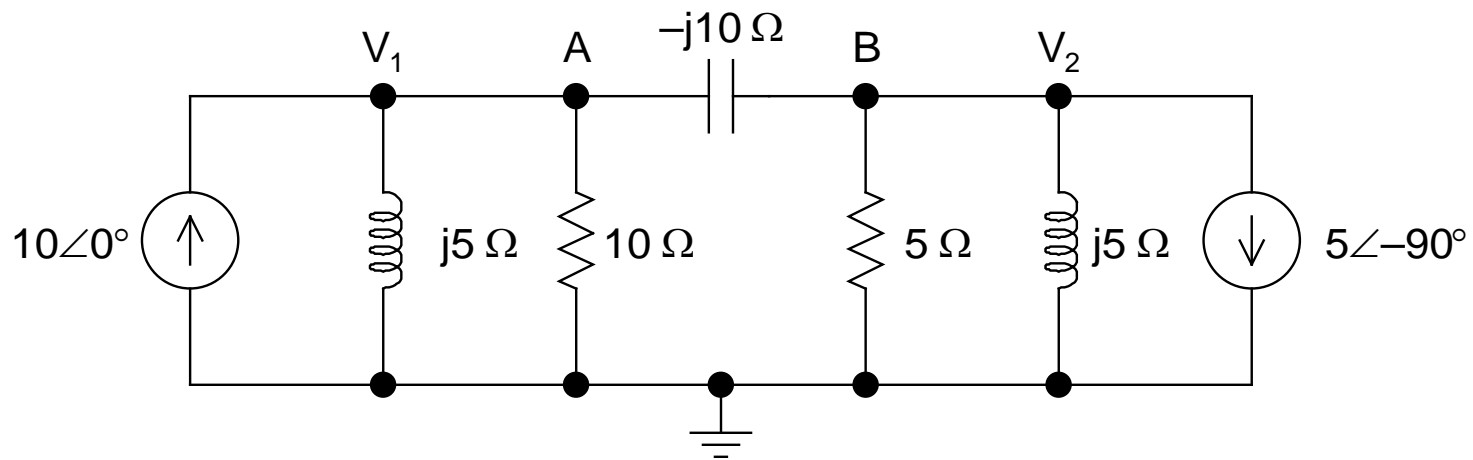Example: Using superposition principle, find \bar{V}_1 and \bar{V}_2 .



$$Z_1 = \frac{10 \times (j5)}{10 + j5} = \frac{50 \angle 90^\circ}{11.18 \angle 26.57^\circ} = 4.47 \angle 63.43^\circ \Omega$$

$$= 2 + j4 \Omega$$

$$Z_2 = -j10 \Omega$$

$$Z_3 = \frac{5 \times (j5)}{5 + j5} = \frac{25 \angle 90^\circ}{7.07 \angle 45^\circ} = 3.54 \angle 45^\circ \Omega = 2.5 + j2.5 \Omega$$

First, consider the $10 \angle 0^\circ$ source and null (open) the $5 \angle -90^\circ$ source:

$$\bar{V}_1 = \frac{Z_2 + Z_3}{Z_1 + Z_2 + Z_3} \times 10 \angle 0^\circ \times Z_1 = 62.03 \angle 29.73^\circ$$

$$= 53.87 + j30.76 \text{ V}$$

$$\begin{aligned}\bar{V}_2 &= \frac{Z_1}{Z_1 + Z_2 + Z_3} \times 10 \angle 0^\circ \times Z_3 = 27.76 \angle 146.3^\circ \\ &= -23.1 + j15.4 \text{ V}\end{aligned}$$

Next, consider the $5 \angle -90^\circ$ source and null (open) the $10 \angle 0^\circ$ source:

$$\begin{aligned}\bar{V}_1 &= \frac{Z_3}{Z_1 + Z_2 + Z_3} \times (-5 \angle -90^\circ) \times Z_1 = -13.88 \angle 56.3^\circ \\ &= -7.7 - j11.55 \text{ V}\end{aligned}$$

$$\begin{aligned}\bar{V}_2 &= \frac{Z_1 + Z_2}{Z_1 + Z_2 + Z_3} \times (-5 \angle -90^\circ) \times Z_3 \\ &= -19.63 \angle -78.7^\circ = -3.85 + j19.25 \text{ V}\end{aligned}$$

Hence, by superposition:

$$\begin{aligned}\bar{V}_1 &= 53.87 + j30.76 - 7.7 - j11.55 = 46.17 + j19.21 \\ &= 50\angle 22.6^\circ \text{ V}\end{aligned}$$

$$\begin{aligned}\bar{V}_2 &= -23.1 + j15.4 - 3.85 + j19.25 = -26.95 + j34.65 \\ &= 43.9\angle 127.88^\circ \text{ V}\end{aligned}$$

Note the exact match of the results with the previous example

Expected, since the outcome is independent of the method used

Example: Construct Thevenin and Norton Equivalents, as seen from terminals A and B:

Open the independent current source $5\angle 60^\circ$ A:


Thevenin Impedance:


$$\begin{aligned} Z_T &= (j10) \parallel (5 - j10) \\ &= 22.36\angle 26.57^\circ = 20 + j10 \Omega \end{aligned}$$

Thus, the Thevenin impedance is *inductive*



Thevenin Voltage:
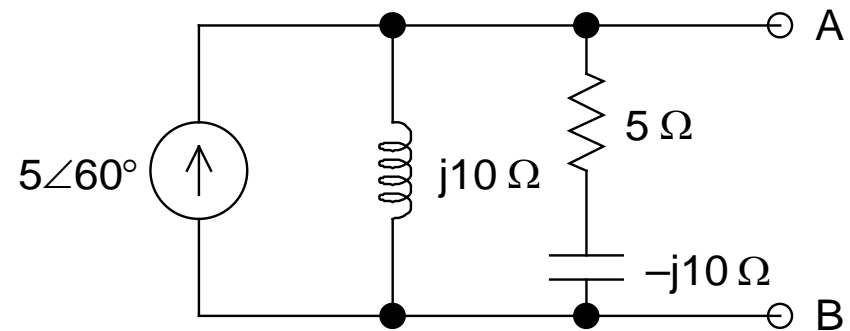
$$\begin{aligned} V_T &= (5\angle 60^\circ) \times Z_T = (5\angle 60^\circ) \times (22.36\angle 26.57^\circ) \\ &= 111.8\angle 86.87^\circ \text{ V} \end{aligned}$$



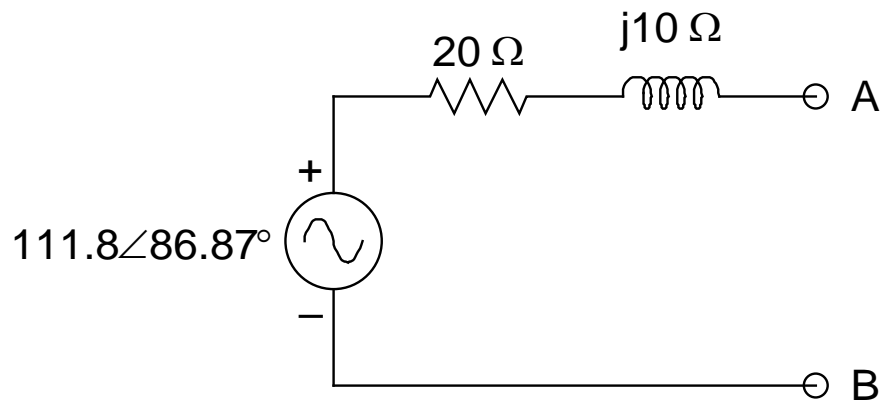

Thevenin Equivalent

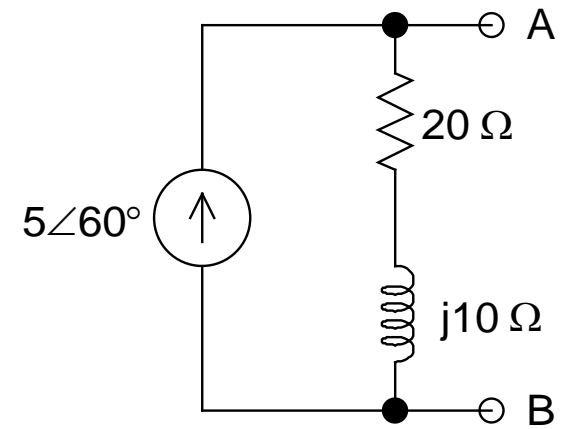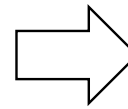


Norton Equivalent

Note: Norton Current $I_N = \frac{V_T}{Z_T} = 5\angle 60^\circ$

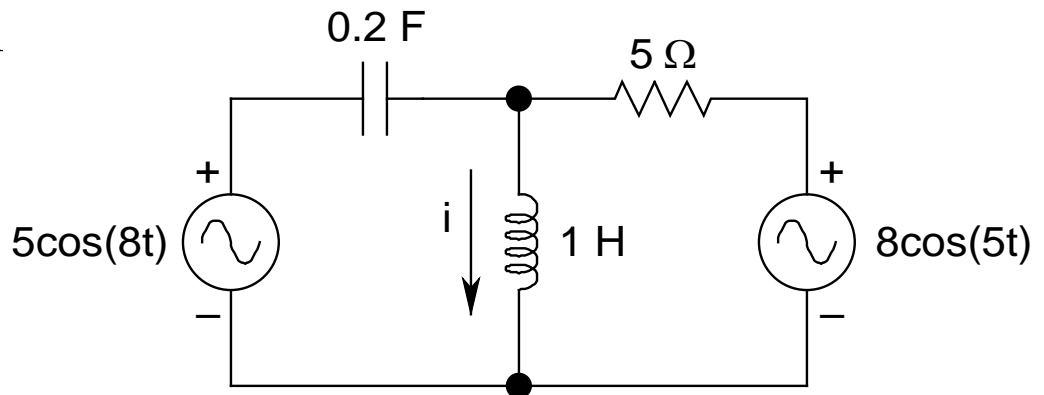Example: Sources having different frequencies.

Determine the expression for the current i .

Caution: Phasor analysis can be done for individual frequencies, but the final result can *never* be expressed in phasor form



Perform phasor analysis for each frequency, and then apply *superposition* to get the net result, which can only be expressed in *time domain*

First consider the $5\cos(8t)$ source, with $\omega = 8 \text{ rad/sec}$, and short-circuit the other independent voltage source

$$Z_1 = \frac{5 \times (j8)}{5 + j8} = \frac{40 \angle 90^\circ}{9.43 \angle 58^\circ}$$

$$= 4.24 \angle 32^\circ = 3.6 + j2.25 \Omega$$


$$Z_3 = Z_1 - j0.625 = 3.6 + j1.625$$

$$= 3.95 \angle 24.3^\circ \Omega$$

$$\Rightarrow \bar{I}_3 = (5 \angle 0^\circ) / (3.95 \angle 24.3^\circ) = 1.27 \angle -24.3^\circ \text{ A}$$

$$\Rightarrow \bar{I}_1 = \frac{5}{5 + j8} \times \bar{I}_3 = \frac{5}{9.43 \angle 58^\circ} \times 1.27 \angle -24.3^\circ = 0.67 \angle -82.3^\circ \text{ A}$$

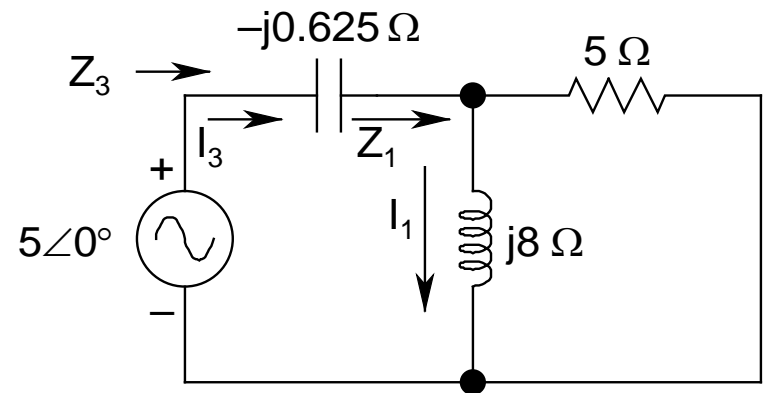In ***time domain*** representation, $i_1 = 0.67 \cos(8t - 82.3^\circ) \text{ A}$



Next, consider the $8\cos(5t)$ source, with $\omega = 5 \text{ rad/sec}$, and short-circuit the other independent voltage source


$$Z_2 = \frac{-j \times (j5)}{-j + j5} = \frac{5}{4 \angle 90^\circ}$$

$$= 1.25 \angle -90^\circ = -j1.25 \Omega$$

$$\Rightarrow Z_4 = 5 + Z_2 = 5 - j1.25$$

$$= 5.15 \angle -14.04^\circ \Omega$$
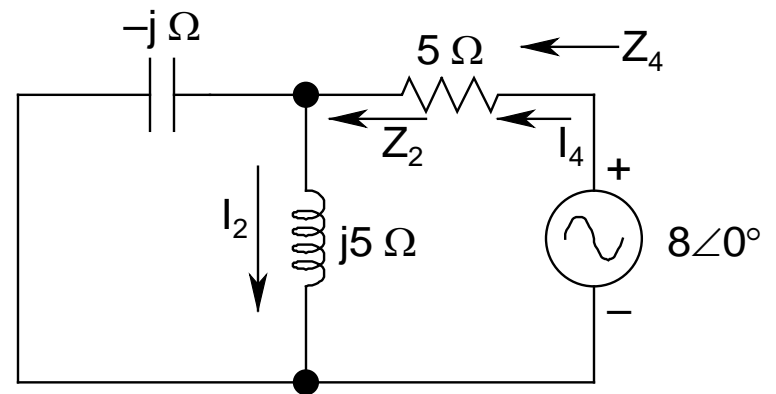
$$\Rightarrow \bar{I}_4 = (8 \angle 0^\circ) / (5.15 \angle -14.04^\circ) = 1.55 \angle 14.04^\circ \text{ A}$$



$$\Rightarrow \bar{I}_2 = \frac{-j}{-j + j5} \times \bar{I}_4 = \frac{1 \angle -90^\circ}{4 \angle 90^\circ} \times 1.55 \angle 14.04^\circ$$

$$= 0.39 \angle -165.96^\circ \text{ A}$$

In *time domain*, $i_2 = 0.39 \cos(5t - 165.96^\circ) \text{ A}$

Hence, the net current i flowing through the 1 H inductance (by *superposition*):

$$i = i_1 + i_2 = 0.67 \cos(8t - 82.3^\circ) + 0.39 \cos(5t - 165.96^\circ) \text{ A}$$