 


Circuit Schematic



ac Midband Equivalent

- *M_1 body connected to ground, M_2 - M_3 bodies connected to V_{DD}*
 - *No body effect problem for any of the devices (biggest advantage of this circuit)*

- Identify M_2 - M_3 as a *PMOS current mirror* (*perfectly matched*)
 - $\Rightarrow I_{D1} = I_{D2} = I_{D3} = I_{REF}$
- This gives the *required value* of V_I
 - \Rightarrow *DC biasing* of the circuit is *pretty straightforward*
- For *ac analysis*, we note that *node A* is *both open and short* at the same time (similar to *npn gain stage* with *pnp active load*)
 - $\Rightarrow A_v = v_o/v_i = -g_{m1}R_0$
 - $R_0 (= r_{o1} \parallel r_{o2})$: *Output resistance* of the circuit

- **Caution:** $r_{o1} \neq r_{o2}$, even though M_1 and M_2 carry the same *DC bias current*, since $\lambda_n \neq \lambda_p$ (in general)
- This circuit is *immensely useful* since it gives *extremely large voltage gain and output resistance*
- Only **problem** is that it needs a *PMOS current mirror*, thus necessitating use of an *extra PMOS*
- An **even better design** exists, which *eliminates* the need for this *extra PMOS*


- ***A Better CMOS Gain Stage:***

- *No body effect issue*
- However, there are *some design issues*
- M_n - M_p have *same magnitude* of the *threshold voltage*:

$$V_{TN0} = |V_{TP0}|$$

- *Process transconductance parameters:*
 
$$k'_N = \mu_n C'_{ox} \quad \text{and} \quad k'_P = \mu_p C'_{ox}$$



Circuit Schematic

- *Oxide capacitance per unit area* ($C'_{ox} = \epsilon_{ox} / t_{ox}$)
same for both devices, since they have *same*
 t_{ox}
- However, $\mu_n \sim 2\mu_p$ (*for Si*)
- Thus, $k'_N = 2k'_P$
- *Ideal DC bias point* of the circuit is $V_I = V_O = V_{DD}/2$ (yields $V_{GSn} = |V_{GSp}|$ and $V_{DSn} = |V_{DSp}|$)
- Can be achieved only if the stage is *completely balanced* (*same threshold voltage magnitude* and *same device transconductance parameter*)
- Thus, k_N and k_P *need to be matched*

- *Can be achieved by making $(W/L)_p = 2(W/L)_n$*
- If *CLM effect* is *not that important*, or if $\lambda_n = \lambda_p$, then this procedure works out *just fine*
- However, if $\lambda_n \neq \lambda_p$, then for *balancing the circuit*, the following relation *must hold* (*show!*):

$$k_p(1 + \lambda_p V_{DD}/2) = k_n(1 + \lambda_n V_{DD}/2)$$
- Under this condition, $k_n \neq k_p$, but the circuit will be *perfectly matched and balanced*
- Known as: *Stage unmatched by nature, but matched by performance*