
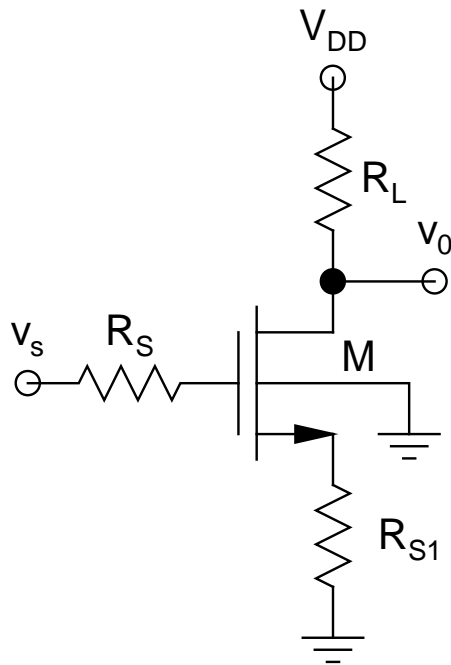


- **$CS(D)$:**

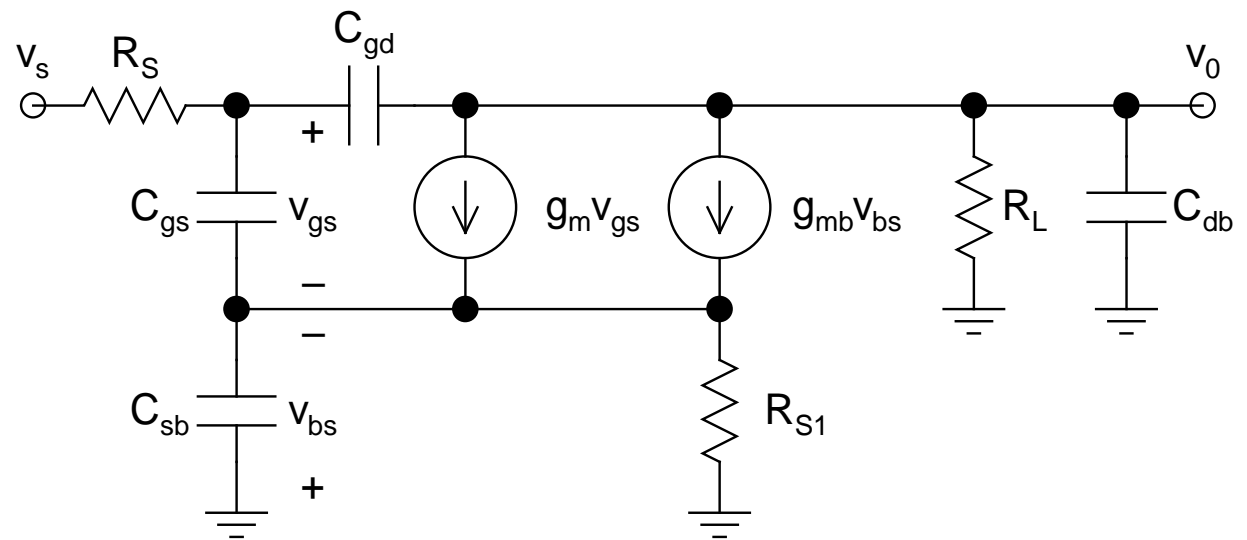


ac Schematic



High-Frequency Equivalent

- *Inarguably, the most complex module*
 - *All the capacitors will be present*
 - *None will have **Standard Form***
 - *Detailed analysis needed for each of them*

➤ C_{gs} :

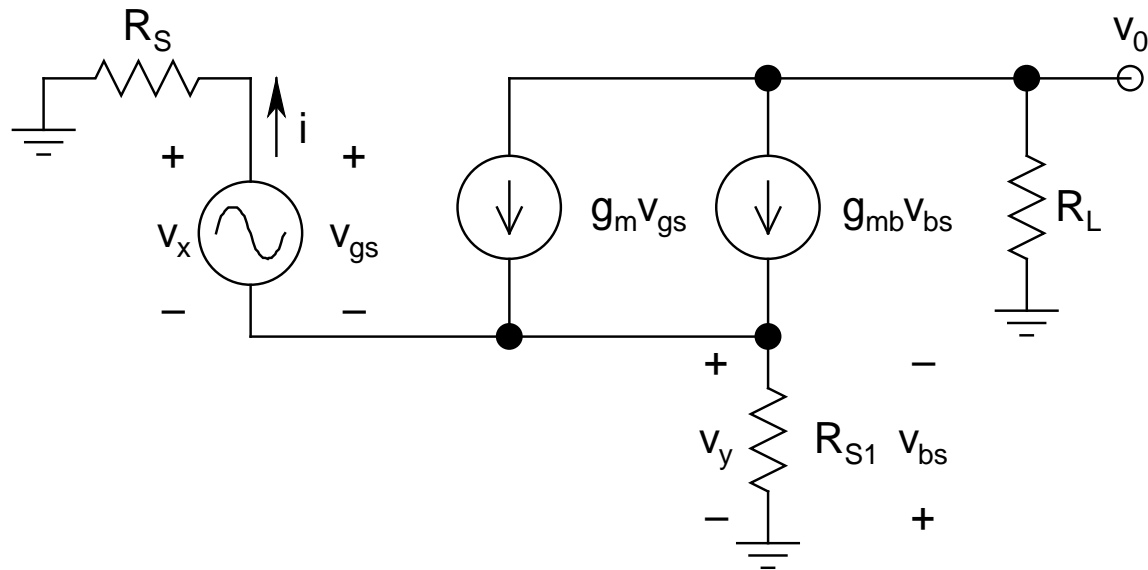

- *Open all other capacitors*
- *Replace C_{gs} by a voltage source v_x*
- $v_{gs} = v_x$ and $v_{bs} = -v_y$
- $i = (v_x + v_y)/R_S$

$$= g_m v_{gs} + g_{mb} v_{bs} - v_y/R_{S1}$$


$$= g_m v_x - g_{mb} v_y - v_y/R_{S1}$$

$$\Rightarrow v_y = [R_{S1}(g_m R_S - 1)]v_x / (R_{S1} + R_S + g_{mb} R_S R_{S1})$$

$$\Rightarrow R_{gs}^0 = \frac{v_x}{i} = \frac{R_S + R_{S1} + g_{mb} R_S R_{S1}}{1 + (g_m + g_{mb}) R_{S1}}$$

$$\Rightarrow \tau_1 = R_{gs}^0 C_{gs}$$
- Note that *if body effect is neglected* (g_{mb} ignored), then it becomes *identical to that of a CD stage*

➤ C_{gd} :

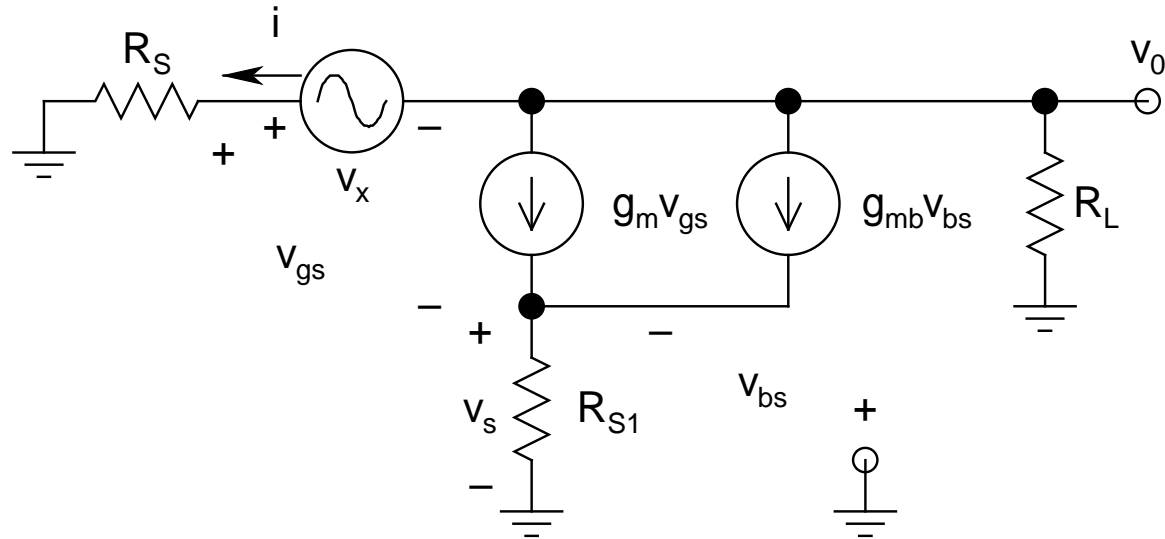

- *Open all other capacitors*
- *Replace C_{gd} by v_x*
- $v_{gs} = (v_0 + v_x - v_s)$ and $v_{bs} = -v_s$

- $i = (v_0 + v_x)/R_S$
- $v_s = (g_m v_{gs} + g_{mb} v_{bs})R_{S1}$
 $\Rightarrow v_s = g_m R_{S1}(v_0 + v_x)/[1 + (g_m + g_{mb})R_{S1}]$
- ***KCL at output node:***
 $i + g_m v_{gs} + g_{mb} v_{bs} + v_0/R_L = 0$
- ***The rest of the process involves huge amount of algebra!***
- ***Finally, if done right (check!)***

$$R_{gd}^0 = \frac{v_x}{i} = R_L \left[1 + g_m R_S + \frac{R_S}{R_L} - \frac{(g_m + g_{mb})g_m R_S R_{S1}}{1 + (g_m + g_{mb})R_{S1}} \right]$$

$$\Rightarrow \tau_2 = R_{gd}^0 C_{gd}$$

- *This is by far the most complicated calculation/expression*
- However, an *exact analysis* would have yielded a *4th-order transfer function* in ω , which had to be *solved* to get the *individual poles*
- *This is still simpler than that :)*


➤ *C_{db}*:

- *The easiest of the lot*
- *By inspection:*

$$R_{db}^0 = R_L$$

$$\Rightarrow \tau_3 = R_{db}^0 C_{db}$$

➤ C_{sb} :

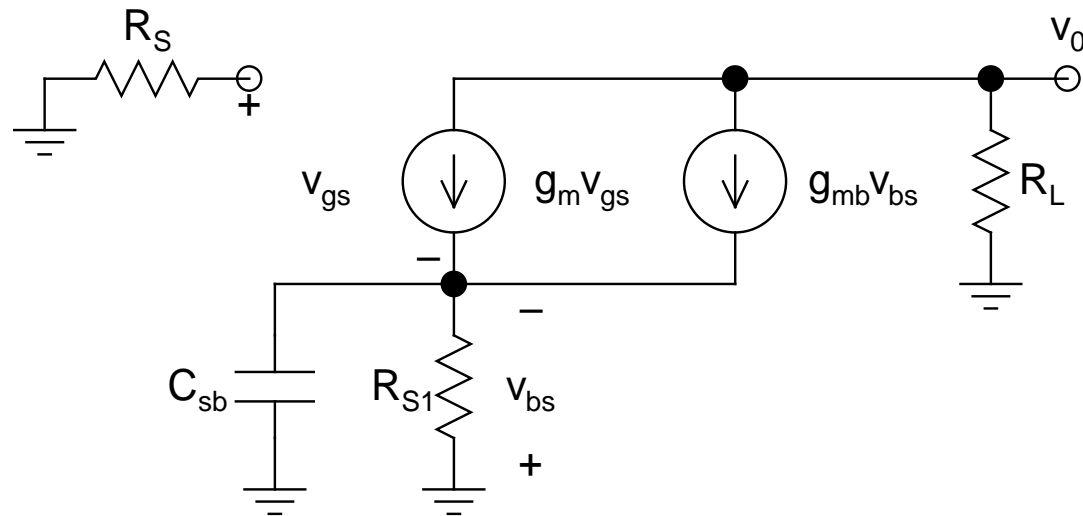

- *Analysis of this circuit is pretty straightforward*

$$R_{sb}^0 = \frac{R_{S1}}{1 + (g_m + g_{mb}) R_{S1}} \Rightarrow \tau_4 = R_{sb}^0 C_{sb}$$