

DC Bias Point Calculation

- *To find R_D for BB*


- $V_{TN0} = 1 \text{ V}$, $k'_N = 40 \mu\text{A}/\text{V}^2$,
 $W/L = 10$

- *Body terminal not shown*

➤ *Implies that it is connected
to the most negative potential available in the
circuit (**ground in this case**)*

$$\Rightarrow V_{SB} = 0 \Rightarrow V_{TN} = V_{TN0}$$

 - $I_G = 0 \Rightarrow V_{GS} = V_G = 2 \text{ V}$



- $V_{GT} = V_{GS} - V_{TN} = 1 \text{ V}$
- *Assuming saturation mode of operation and neglecting CLM:*

$$I_D = (k_N/2) V_{GT}^2 = 200 \text{ } \mu\text{A}$$
- *For BB, $V_{DS} = V_{DD}/2 = 2.5 \text{ V}$ (2-element output branch):*

$$R_D = (V_{DD} - V_{DS})/I_D = 12.5 \text{ k}\Omega$$
- $V_{DS} > V_{GT} \Rightarrow$ *Assumption of saturation mode of operation validated*
- $P_D = V_{DS} \times I_D = 0.5 \text{ mW}$


Small-Signal Model

- The *electrical equivalent* of the MOSFET at the *DC bias point*
- *Must be biased in saturation*
 - *Resembles a constant current source*
- *DC analysis must precede*, since *need the information regarding the Q-point* (I_D , V_{DS})
- *This model for NMOS and PMOS is the same (incremental model)*

Validity of the Small-Signal Model

- The *instantaneous current* (assuming $\lambda V_{DS} < 0.1$):
 
$$\begin{aligned} I_d &= \frac{k_N}{2} (V_{GT} + v_i)^2 \\ &= I_D + \frac{k_N}{2} [2V_{GT}v_i + v_i^2] \\ \Rightarrow i_d &= k_N V_{GT} v_i \left[1 + \frac{v_i}{2V_{GT}} \right] \end{aligned}$$



- Thus, for *linear relationship* between i_d and v_i , *v_i must be $\ll V_{GT}$*
- Note that $V_{GT} (\text{minimum}) = 3V_T$
- Hence, *v_i should be at least ten times less than $3V_T$*
- Recall in *BJT*, for *linear relationship* between i_c and v_i , *v_i has to be $\ll V_T$*
 - *Three times less than that for MOSFET*
 - *MOSFETs are inherently more linear device than BJTs (compare quadratic with exponential)*