

M_1 - M_2 perfectly matched. I_{SS} ideal. Neglect base current, body effect, CLM effect, and Early effect.
Other data: For M_1 - M_2 : $V_{TN0} = 1$ V, $k'_N = 40 \mu\text{A}/\text{V}^2$, $W/L = 80$; for Q_3 : $\beta = 100$.

- a) Choose R_L , R_1 , and R_2 , such that the DC levels of the voltages at nodes A and B are 2.3 V and 0 V respectively, and $I_1 = 100 \mu\text{A}$ (DC). 3
- b) What is the voltage dropped across I_{SS} ? 3
- c) Using the results of part a), find the ac small-signal midband voltage gain v_0/v_i . 6

