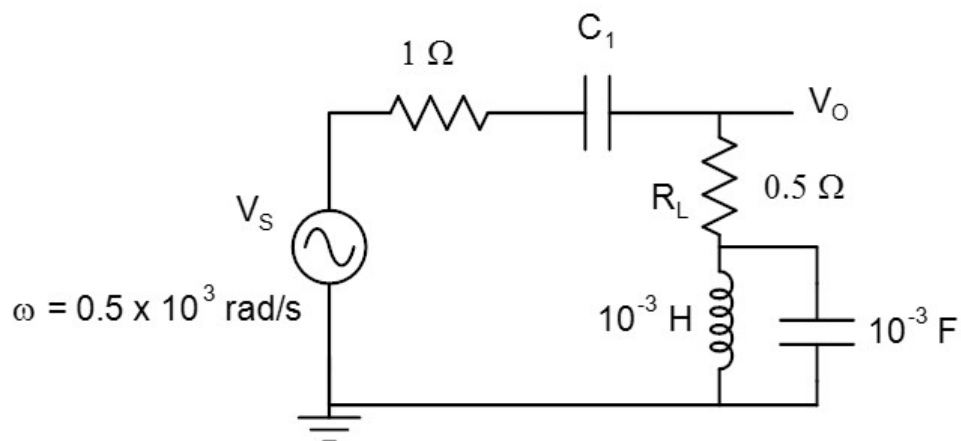


**Q.1** The value of capacitor  $C_1$  (in Milli-Farads) for which maximum power will be dissipated in the load resistor  $R_L$  is -----

(answer only as an integer)




Your answer:

3

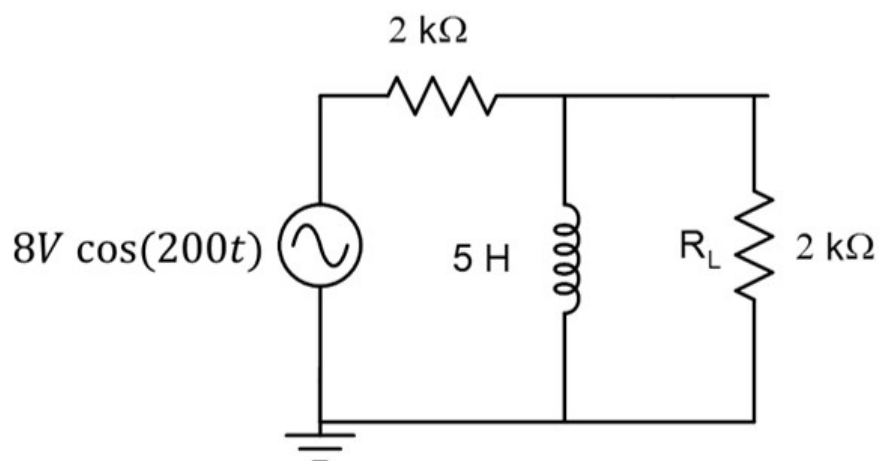**Q.2**

The power dissipated in load resistor  $R_L$  (in milli-watts ) is.....





(8V refers to peak value. Give answer as an integer)



Your answer:

2

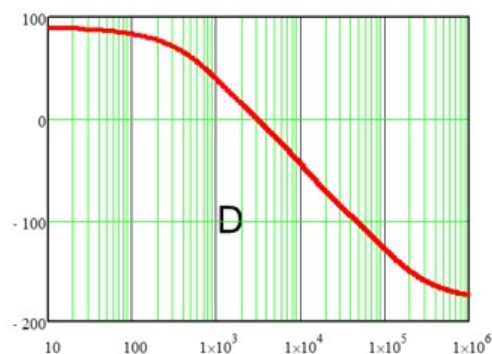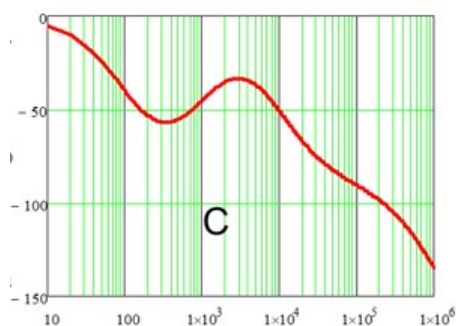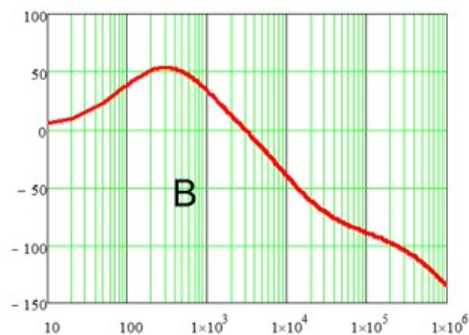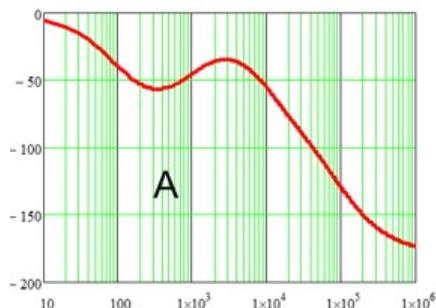**Q.3** Match the phase responses (A,B,C,D) to the transfer functions (H1,H2,H3,H4)



$$H1(\omega) = \frac{\left(j \times \frac{\omega}{10^3}\right)}{\left(1 + j \times \frac{\omega}{10^3}\right)} \times \frac{1}{\left(1 + j \times \frac{\omega}{10^4}\right)} \times \frac{1}{\left(1 + j \times \frac{\omega}{10^5}\right)}$$

$$H2(\omega) = \frac{\left(1 + j \times \frac{\omega}{10^3}\right)}{\left(1 + j \times \frac{\omega}{10^2}\right)} \times \frac{1}{\left(1 + j \times \frac{\omega}{10^4}\right)} \times \frac{1}{\left(1 + j \times \frac{\omega}{10^6}\right)}$$

$$H3(\omega) = \frac{\left(1 + j \times \frac{\omega}{10^3}\right)}{\left(1 + j \times \frac{\omega}{10^2}\right)} \times \frac{1}{\left(1 + j \times \frac{\omega}{10^4}\right)} \times \frac{1}{\left(1 + j \times \frac{\omega}{10^5}\right)}$$

$$H4(\omega) = \frac{\left(1 + j \times \frac{\omega}{10^2}\right)}{\left(1 + j \times \frac{\omega}{10^3}\right)} \times \frac{1}{\left(1 + j \times \frac{\omega}{10^4}\right)} \times \frac{1}{\left(1 + j \times \frac{\omega}{10^5}\right)}$$

$$H_1 \rightarrow D; H_2 \rightarrow A; H_3 \rightarrow C; H_4 \rightarrow B$$


$$H_1 \rightarrow B; H_2 \rightarrow A; H_3 \rightarrow C; H_4 \rightarrow D$$

$$H_1 \rightarrow D; H_2 \rightarrow C; H_3 \rightarrow A; H_4 \rightarrow B$$

$$H_1 \rightarrow B; H_2 \rightarrow C; H_3 \rightarrow A; H_4 \rightarrow D$$

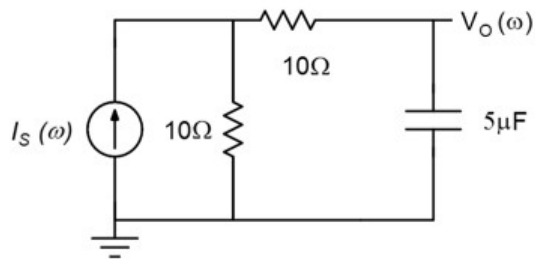Q4

For the circuit shown, the closest estimates of the magnitude of the transfer function  $\frac{V_O(\omega)}{I_S(\omega)}$  at  $\omega = 10$  and  $\omega = 10^6$  rad/s in dB are



40dB, 0dB






20dB, -40dB

0dB, -40dB

0dB, -20dB

20dB -20dB

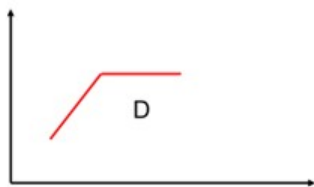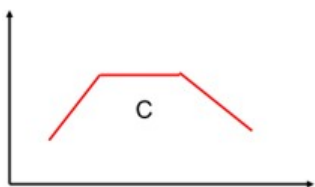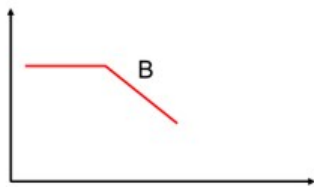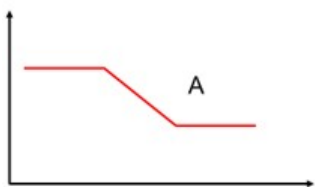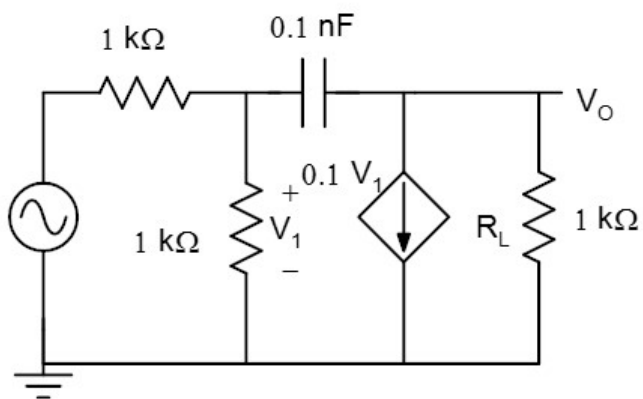output voltage  $V_O$  of the amplifier circuit shown below.



C

A

D

B

Score: Will be uploaded after end date.