

- Under *application* of an *ac signal* ( $v_i$ ), the *dynamic operating point* (DOP) will *move along the load line*
- For *positive*  $v_i$ , the DOP *will move* Q *towards saturation* ( $V_{CE} \rightarrow 0, I_C \rightarrow I_{C,max}$ )
  - The *output signal* ( $v_o$ ) will be in its *negative excursion*
  - If Q enters *saturation*, *negative peak* of  $v_o$  will get *clipped*
  - *Distorted output*

- For *negative*  $v_i$ , the DOP *will move* Q *towards cutoff* ( $V_{CE} \rightarrow V_{CC}$ ,  $I_C \rightarrow 0$ )
  - The *output signal* ( $v_o$ ) will be in its *positive excursion*
  - If Q *cuts off*, *positive peak* of  $v_o$  will get *clipped*
  - *Distorted output*
- *Golden rule of thumb for BJT biasing:*
  - *To get maximum undistorted peak-to-peak swing of  $v_o$ , Q-point must be chosen to be at the middle of the load line*

- ***Role of  $R_C$ :***

- Under ***FA mode***,  $R_C$  ***does not control  $I_C$*** , however, it ***changes  $V_{CE}$***  ( $= V_{CC} - I_C R_C$ )
- If  $R_C \uparrow$ ,  $V_{CE} \downarrow \Rightarrow Q$  moves ***towards saturation***
- If  $R_C \downarrow$ ,  $V_{CE} \uparrow \Rightarrow Q$  moves ***towards cutoff***
- Thus, ***different values of  $R_C$***  can produce ***different  $Q$ -points (in terms of  $V_{CE}$ )***

- ***DC Power Dissipation:***

- $P_D = V_{BEQ} \times I_{BQ} + V_{CEQ} \times I_{CQ}$   
 $\approx V_{CEQ} \times I_{CQ}$  (***under FA mode***)

# Some Observations

- Q should be *biased* such that it is in the *FA* mode of operation
  - Behaves like a *constant and ideal current source with infinite output resistance*, since  $I_C$  is *independent* of  $V_{CE}$
  - *Ideal region to bias a BJT*
- For *very high*  $R_C$ ,  $I_{C,max}$  *very small*
  - *Load line may not have any intersection point in the FA region at all*

- *Q-point moves to saturation region*
- *Ceases to become a constant current source*, since in *saturation*,  $I_C$  becomes a *strong function* of  $V_{CE}$
- *Disastrous way of biasing a BJT*
- *Similar situation* will arise if  $R_C$  is *very small*
  - $I_{C,max}$  will become *very large* and *Q-point will move towards cutoff*
  - *Another disastrous way of biasing a BJT*

- **Example:** Let  $V_{CC} = V_B = 5\text{ V}$ ,  $R_B = 430\text{ k}\Omega$ , and  $\beta = 100$ 
  - $I_B = (V_B - V_{BE})/R_B = (5 - 0.7)/(430\text{ k}\Omega) = 10\text{ }\mu\text{A}$  (assuming **FA** mode of operation with  $V_{BE} = 0.7\text{ V}$ )
  - $I_C = \beta I_B = 1\text{ mA}$
  - $V_{CE}$  will **depend** on our **choice** of  $R_C$
  - $R_C$  for **best biasing** (BB) ( $V_{CE}(\text{BB}) = V_{CC}/2$ ):
    - $R_C(\text{BB}) = V_{CC}/(2I_C) = 2.5\text{ k}\Omega$
  - $R_C$  that puts Q at OS ( $V_{CE}(\text{OS}) = 0.7\text{ V}$ ):
    - $R_C(\text{OS}) = [V_{CC} - V_{CE}(\text{OS})]/I_C = 4.3\text{ k}\Omega$

- *Any value of  $R_C$  higher than  $4.3\text{ k}\Omega$  would push  $Q$  in saturation*
- Choose  $R_C = 20\text{ k}\Omega$ :
  - Assuming *FA* operation is maintained,  $V_{CE}$  comes out to be  $-15\text{ V}$ !
  - *Golden rule:*
    - ❖ *Potential at any point in a circuit can never go beyond the positive and negative extremes of the power supply voltages, unless there is a power source within the circuit*
  - Thus,  $V_{CE} = -15\text{ V}$  is *absurd*
  - Hence,  $Q$  is *no more* in the *FA* mode of operation, rather it has been pushed into *saturation*