

ESc201A Home Assignment 8 Oct. 21, 2019.
Solutions of the HA#7 will be on Brihaspati on 28/10/19.

1. Obtain the truth table for the following function: $(x.y+z)(y+x.z)$ and write it as sum of products (SOP) and product of sums (POS).
2. Use Boolean identities to prove that $(w.x.z+\overline{w}.x+\overline{x}.z+\overline{y}).(y+w.x+x.z)=x.(w+y).(\overline{w}+\overline{y})+z.(x+y)$
3. Minimize the following functions using K-map:
 - (a) $F(A,B,C,D)=A.B.C.D+\overline{A}.B.C.D+\overline{A}.B.C.\overline{D}+\overline{A}.B.C.\overline{D}+\overline{A}.B.C.D+\overline{A}.B.C.\overline{D}$
 - (b) $F(X,Y,Z)=\sum m(0,1,2,3,4,5,6)$
 - (c) $F(X,Y,Z)=\prod M(0,1,2,4)$
 - (d) $F(A,B,C,D,E)=\sum (2, 6, 8, 10, 12, 14, 18, 22, 24, 26, 28, 30) .$
4. Express the function $F(A, B, C, D) = \sum(2, 3, 4, 6, 12, 14) + \sum_{\text{Don't Care}}(7, 9, 10, 11, 15)$ in the minimized Sum of Products form.
5. Express the function $F(A, B, C, D) = \sum(1, 3, 4, 6, 9, 11, 12, 14) + \sum_{\text{Don't Care}}(5, 7)$ in the minimized Products of Sum form.
6. Find a minimal expression for a Boolean function $F(A,B,C,D)$ where F is true when E is true, except when E takes X states.

| | | | | | | | | | | | | | | | | |
|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|
| A | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 |
| B | 0 | 0 | 0 | 0 | 1 | 1 | 1 | 1 | 0 | 0 | 0 | 0 | 1 | 1 | 1 | 1 |
| C | 0 | 0 | 1 | 1 | 0 | 0 | 1 | 1 | 0 | 0 | 1 | 1 | 0 | 0 | 1 | 1 |
| D | 0 | 1 | 0 | 1 | 0 | 1 | 0 | 1 | 0 | 1 | 0 | 1 | 0 | 1 | 0 | 1 |
| E | 1 | 0 | 1 | 1 | 0 | 0 | 0 | 0 | 1 | X | 1 | X | 0 | X | 0 | X |
7. Design a combinational circuit with 3 inputs and 1 output
 - (a) The output is 1 when the binary value of the inputs is less than 3. The output is 0 otherwise
 - (b) The output is 1 when the binary value of inputs is an odd number.
8. Carry out the following conversions:
 - (a) $(111011.10101)_2 = (?)_{10}$
 - (b) $(361)_{10} = (?)_2$
 - (c) $(0.90625)_{10} = (?)_2$
 - (d) $(75.4375)_{10} = (?)_2$
 - (e) $(B95C.A5)_{16} = (?)_{10}$
 - (f) $(11011011010010101.1110000111)_2 = (?)_{16}$
 - (g) $(1959)_{10} = (?)_{BCD}$
 - (h) $(1100001100010)_{BCD} = (?)_{10}$
9. Show that any Boolean expression can be implemented using either NAND or NOR gates only.
10. Perform the following arithmetic operations using 2's complement method: (Use 8-bit representation of number).
 - (a) $50 - 21$, (b) $-50 + 21$, (c) $-50 - 21$
11.
 - a) Show that a 1-bit Half adder can be implemented with an Exclusive-OR (XOR) gate and an AND gate.
 - b) Show that a 1-bit Full adder can be implemented with two Half adders and an OR gate.