
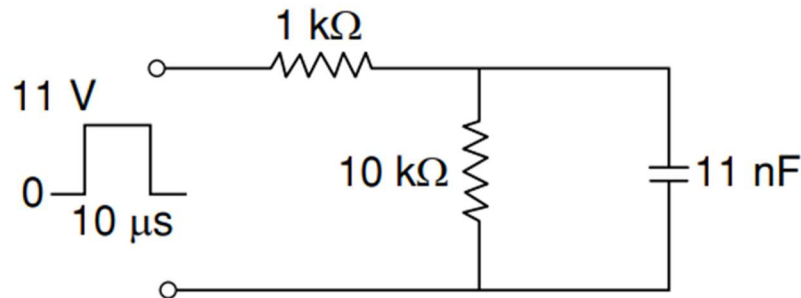


Tutorial - 4

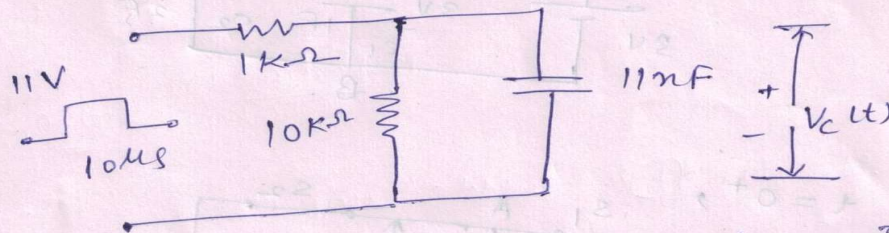1. An 11 V pulse of 10 μ s duration is applied to the circuit shown in the figure. Assuming that the capacitor is completely discharged prior to applying the pulse, the peak value of the capacitor voltage is -



Consider the figure below.



$$V_C(0) = 0V.$$

(I.V = Initial Value
F.V = Final Value.

If the input is $11u(t)$,

$$V_C(t) = I.V + (F.V - I.V)(1 - e^{-t/\tau}),$$

where, $F.V = 11 \times \frac{10}{11} = 10V,$

and $\tau = \frac{10}{11} \times 10^3 \times 11 \times 10^{-9} = 10 \mu s.$

$$V_C(t) = 10(1 - e^{-t/\tau}). \quad \text{--- (1)}$$


When we apply a pulse of 10 μ s,

$V_C(t)$ as given in (1) is true under condition $0 < t < 10 \mu s.$

∴ peak value of $V_C(t)$ occurs at $t = 10 \mu s.$

$$\text{Peak value} = 10(1 - e^{-1}) = \underline{\underline{6.32V.}}$$

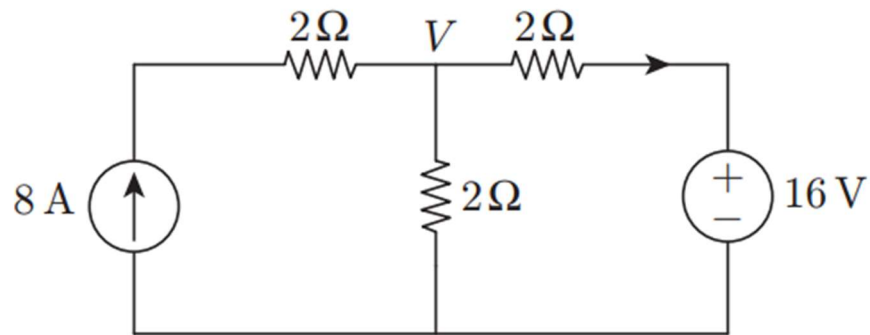2. Determine the power delivered by the 16 V source.



On nodal analysis,


$$\frac{V-16}{2} + \frac{V}{2} - 8 = 0$$

$$V = 16V$$

$P_{8A} = 32 \times 8 = 256W$ (Deliver)
 $P_{2\Omega} = 16 \times 8 = 128W$ (Absorb)
 $P_{2\Omega} = 16 \times 8 = 128W$ (Absorb)
 $P_{16V} = 0 \times 16 = 0W$

Hence, power delivered by the 16 V source is zero.

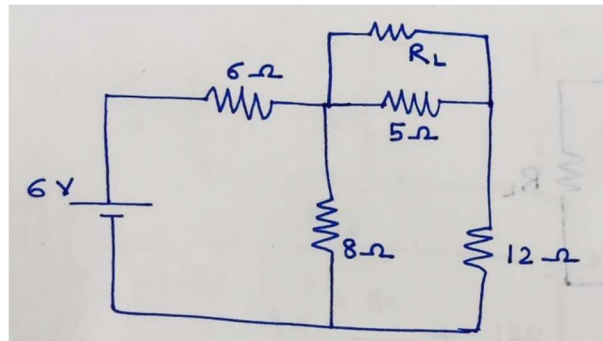3. Find the Value of R_L in the following circuit for maximum power to be transferred to it. Find the efficiency of the source voltage while delivering the maximum power to R_L .



Solution -

To find value of R_L for maximum power,

$R_{th} = 3.77 \Omega$

$V_{th} = 0.83 \text{ volts}$


\therefore For maximum power transfer,

$R_L = 3.77 \Omega$

$P_{max} = \frac{0.83^2}{4 \times 3.77} = 0.0456 \text{ watts}$

Efficiency will be 50%

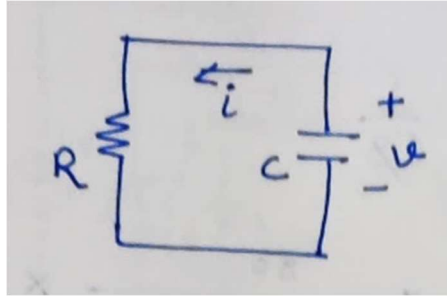4. For the following circuit, $v(t) = 10e^{-4t}$, $i(t) = 0.2e^{-4t}$. Find the values of R and C.



Solution –

$$v(t) = 10 e^{-4t} \text{ V}, \quad i(t) = 0.2 \cdot e^{-4t} \text{ Amp}, \quad t > 0$$


$$R = \frac{10}{0.2} = 50 \text{ ohm}$$

Here, $\tau = \frac{1}{4}$

$$RC = \frac{1}{4}$$

$$50 \times C = \frac{1}{4} \Rightarrow C = \frac{1}{200} = 0.5 \times 10^{-2} = 5 \text{ mF}$$

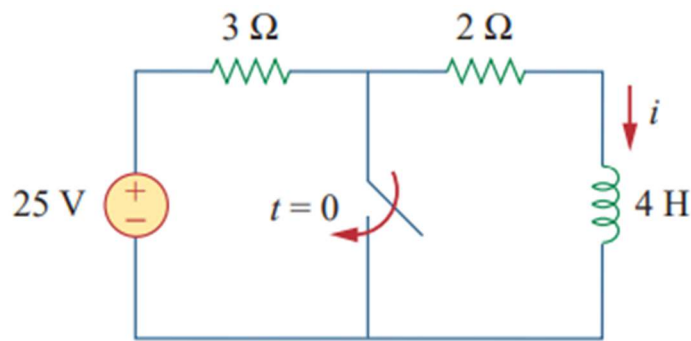5. In the circuit, the switch is closed at $t=0$ seconds. Find inductor current $i(t)$ for both $t < 0$ and $t > 0$ respectively,



Solution -

\Rightarrow For $t < 0$ time, in steady state, inductor acts as short circuit for DC. So, current, i , during $t < 0$ is given by,

$$i = \frac{25}{3+2} = 5 \text{ A}$$

\Rightarrow At $t=0$ time, switch is closed. So the energy stored in the inductor previously starts discharging. So, for $t > 0$, we have an R-L circuit as shown.




$$\Rightarrow i(t) = i(0) e^{-t/\tau};$$

$$\tau = \frac{L}{R} = \frac{4}{2} = 2; \quad i(0) = 5 \text{ A}.$$

$$\Rightarrow i(t) = 5e^{-t/2} \text{ A}.$$

$$\therefore \boxed{\begin{array}{l} i = 5 \text{ A} ; \quad t < 0 \\ i = 5e^{-t/2} \text{ A} ; \quad t > 0 \end{array}}$$

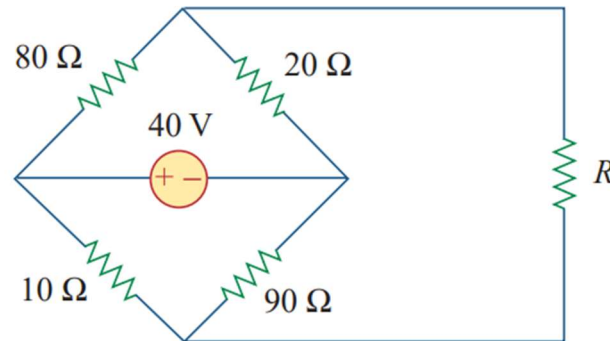6. In the circuit, R is the variable load resistance. The value of R (in ohms) at which it absorbs the maximum power from the circuit is 25 ohms. Find maximum power transferred to load resistance R in Watts?




Solution –

\Rightarrow Maximum power transferred to R , $P_{\max} = \frac{V_{th}^2}{4R_{th}}$

$\therefore R = R_{th}$, at maximum power transfer instant.

Given, $R = R_{th} = 25\ \Omega$. But, we don't know V_{th} ?

Circuit is redrawn below:

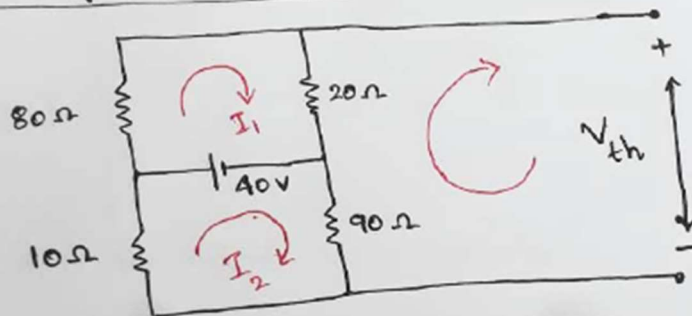

$$\begin{aligned} \rightarrow (80+20)I_1 - 40 &= 0 \rightarrow I_1 = 0.4 \\ (10+90)I_2 + 40 &= 0 \rightarrow I_2 = -0.4 \\ -90I_2 - 20I_1 + V_{th} &= 0 \rightarrow V_{th} = -28V \end{aligned}$$

$$\Rightarrow P_{\max} = \frac{V_{th}^2}{4R_{th}} = \frac{(28)^2}{4 \times 25} = \frac{784}{100} = 7.84 \text{ Watts}$$

\Rightarrow $P_{\max} = 7.84 \text{ W}$