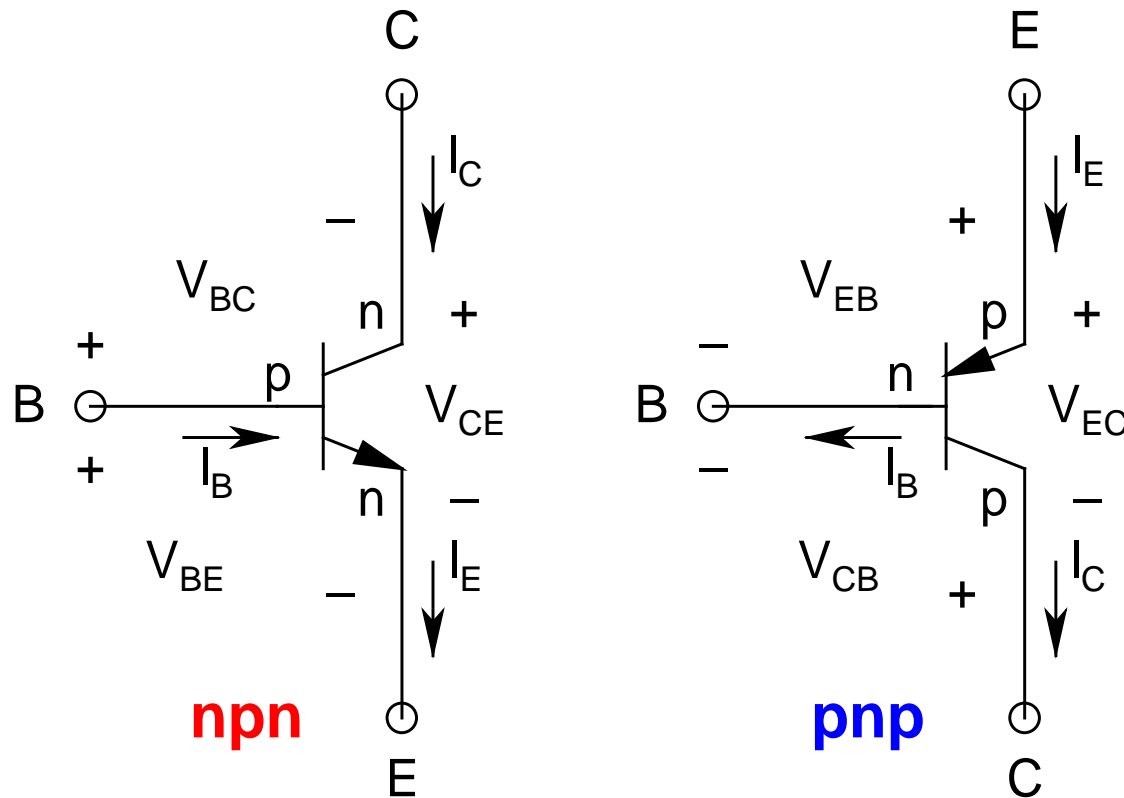


Symbols and Current-Voltage Conventions



- ***Voltage Convention:***

- ***p-side first:***

- ***Sign of the voltage*** immediately lets us know the ***biasing state*** (***forward or reverse***)

- ***nnp***: V_{BE} (***base-emitter voltage***), V_{BC} (***base-collector voltage***), and V_{CE} (***collector-emitter voltage***)

- ***npn***: V_{EB} (***emitter-base voltage***), V_{CB} (***collector-base voltage***), and V_{EC} (***emitter-collector voltage***)

- ***Note***: ***Collector-Emitter is NOT a junction***

- *Current Convention:*

- *npn:*

- I_C and I_B flow in, I_E flows out

- *pnp:*


- I_E flows in, I_C and I_B flow out

- *Applying KCL*, treating the whole BJT as a *big node*, for *both npn and pnp*:

- $I_E = I_C + I_B$

- *Extremely important KCL for the BJT*

Modes of Operation

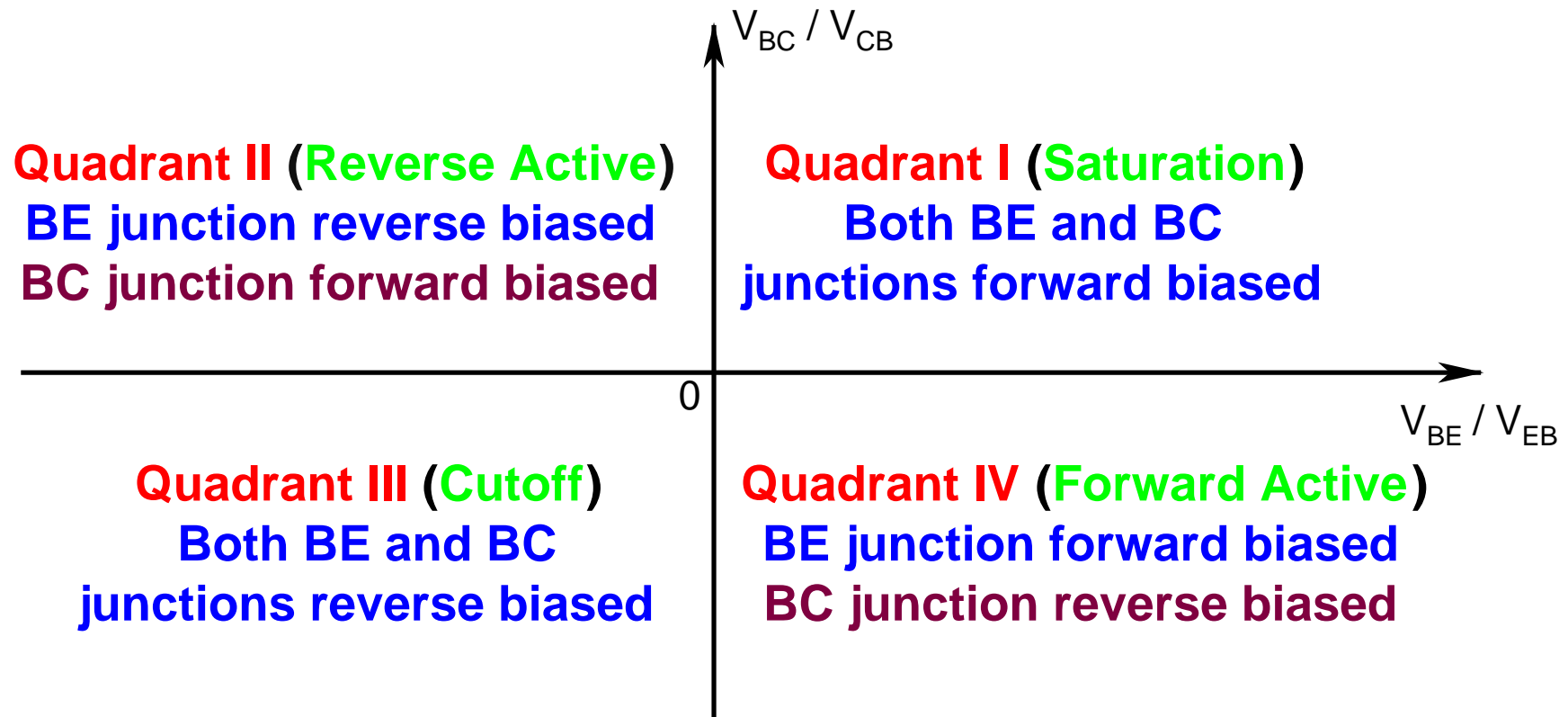


Quadrants III and IV: Analog Domain

Quadrants I and III: Digital Domain

Quadrant II: Finds use only in TTL circuits

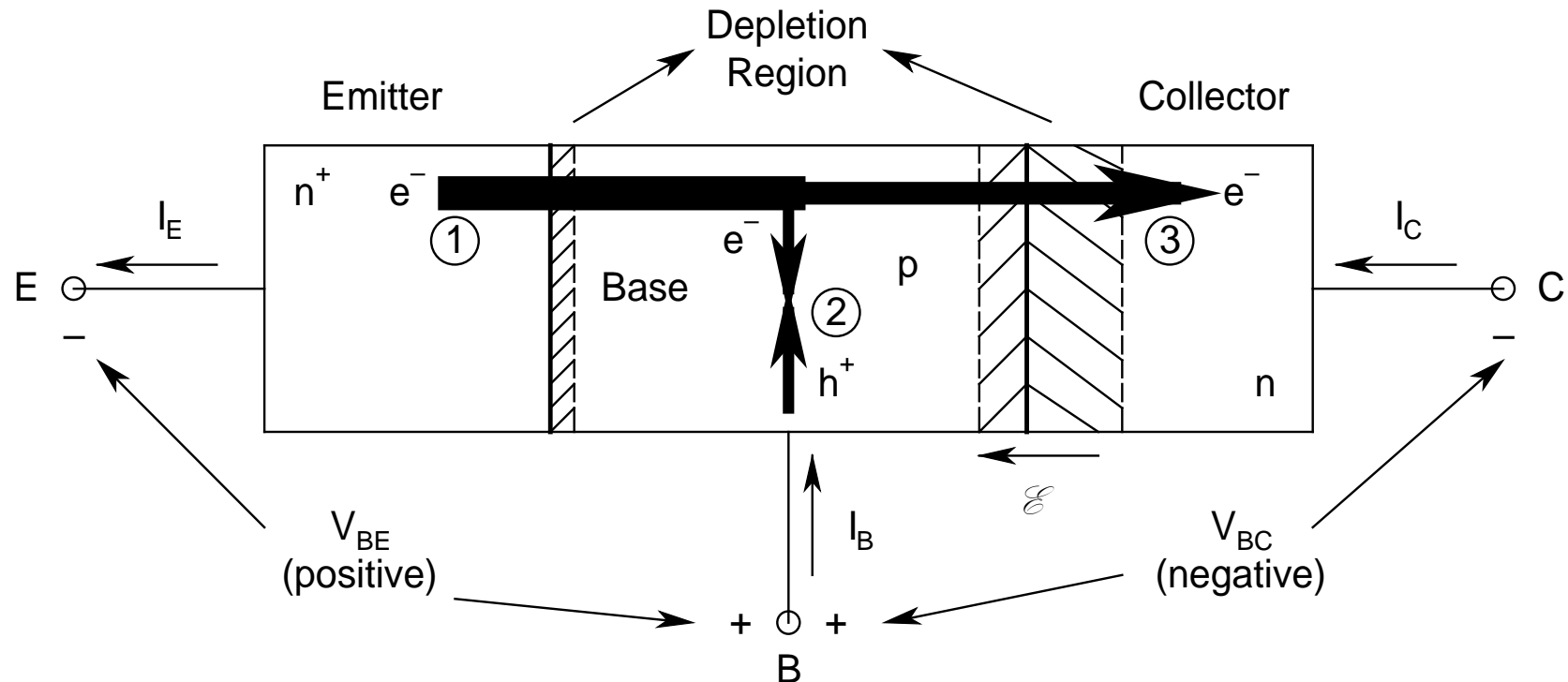Operation in the Forward Active (FA) Mode



① Injection Component, ② Recombination Component, ③ Collection Component