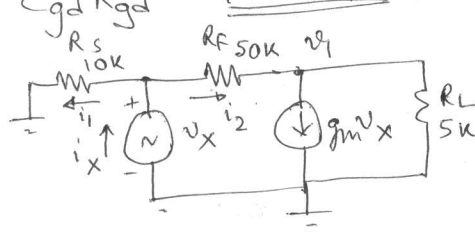


legged creature $\Rightarrow R_{eq} = R_S + R_L + g_m R_L R_S = 101.6 \text{ k}\Omega \Rightarrow R_{gd}^o = 33.5 \text{ k}\Omega \Rightarrow \tau_2 =$

$C_{gd} R_{gd}^o = 469.13 \text{ pS}$. for C_{gs} , the eqv. ckt. is not of a standard form:




$$i_1 = \frac{v_x}{R_S} \quad i_2 = \frac{v_x - v_1}{R_f} = g_m v_x + \frac{v_1}{R_L} \Rightarrow i_2 = \frac{1 + g_m R_L}{R_L + R_f} v_x$$

$$\& i_x = i_1 + i_2 \Rightarrow R_{gs}^o = R_S \parallel \frac{R_L + R_f}{1 + g_m R_L} = 3.63 \text{ k}\Omega$$

$$\Rightarrow \tau_3 = C_{gs} R_{gs}^o = 338.5 \text{ pS} \Rightarrow \Sigma \tau = 907.63 \text{ pS} \Rightarrow f_H =$$

$$\frac{1}{2\pi \Sigma \tau} = 175.35 \text{ MHz} \quad \& \quad t_{9\%} = \frac{0.35}{f_H} = 2 \text{ ns}$$

2 Neglecting R_S :


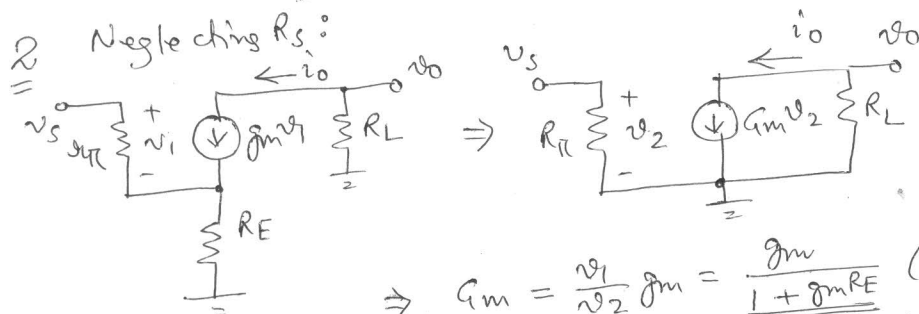


$$\Rightarrow G_m = \frac{v_1}{v_2} g_m = \frac{g_m}{1 + g_m R_E} \quad (\text{shown})$$

$$\Rightarrow G_m = \frac{v_1}{v_2} g_m = \frac{g_m}{1 + g_m R_E} \quad (\text{shown})$$

$$\text{Also, } R_{\pi} = r_{\pi} + (\beta + 1) R_E \approx r_{\pi} + g_m r_{\pi} R_E = r_{\pi} (1 + g_m R_E) \quad (\text{shown})$$

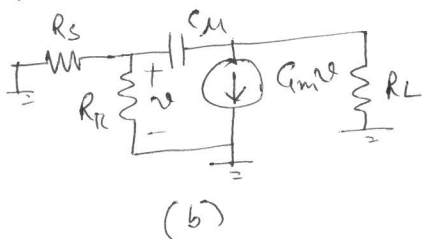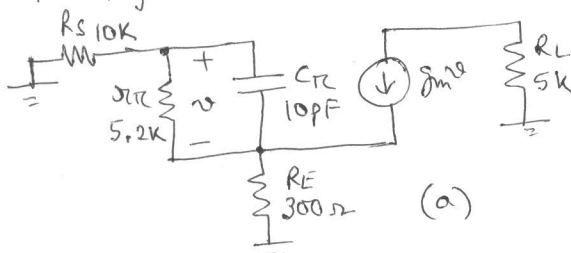Now, for the freq. resp., $r_E = 26 \Omega$, $r_{\pi} = 5.2 \text{ k}\Omega$, $C_{\mu} = 0.2 \text{ pF}$, $C_{\pi} = \frac{g_m}{2\pi f_T} - C_{\mu} = 10 \text{ pF}$



For C_{π} , refer to Fig. (a): It is a standard form, with $R_{\pi}^o = r_{\pi} \parallel \frac{R_S + R_E}{1 + g_m R_E} = 709.4 \Omega$

$$\Rightarrow \tau_1 = R_{\pi}^o C_{\pi} = 7.09 \text{ ns}$$

For C_{μ} , refer to Fig. (b), with

$$R_{\pi} = r_{\pi} (1 + g_m R_E) = 65.2 \text{ k}\Omega, \& \quad G_m = \frac{g_m}{1 + g_m R_E} = \frac{1}{326} \text{ S}, \text{ the resultant structure is a}$$

3-legged creature, with $R_{\mu}^o = R_{eq} + R_L + G_m R_{eq} R_L$, where $R_{eq} = R_S \parallel R_{\pi} = 8.67 \text{ k}\Omega \Rightarrow$

$$R_{\mu}^o = 146.65 \text{ k}\Omega \Rightarrow \tau_2 = R_{\mu}^o C_{\mu} = 29.33 \text{ ns} \Rightarrow \Sigma \tau = 36.42 \text{ ns} \Rightarrow f_H = 4.37 \text{ MHz}$$

$$\& \quad t_{9\%} = 80.1 \text{ ns} \quad [f_H = 1/(2\pi \Sigma \tau), \& \quad t_{9\%} = 0.35/f_H]$$


3 R_S plays no role in midband gain calculation, \because the gate is open-ckt.

$$g_{m1} = g_{m2} = 1.732 \text{ mS} \quad (\text{same as Prob. 1}), \& \quad g_{mb2} = \chi_2 g_{m2} = 346.4 \mu\text{S} \quad (\chi_2 = 0.2)$$

$$\text{Gain of } M_1 = - \frac{g_{m1}}{g_{m2} + g_{mb2}} = - \frac{1}{1 + \chi_2} = -0.83 \quad \& \quad \text{Gain of } M_2 = + (g_{m2} + g_{mb2}) R_L = +41.57$$

$$\therefore \text{Overall voltage gain} = -0.83 \times 41.57 = -34.5$$

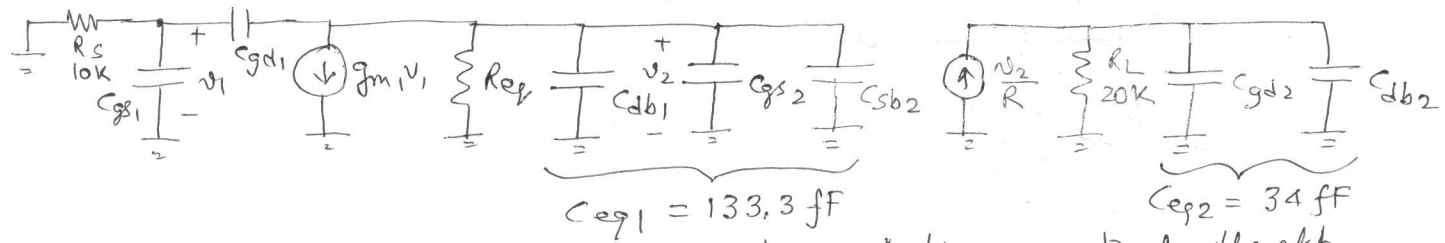Note: for freq. resp., C_{sb} would not play any role, neither capacitors would be present



After clubbing the capacitors, we would have 4 time const. for the ckt.
 $R_{gs1} = R_S = 10k \Rightarrow \tau_1 = C_{gs1} R_{gs1} = 933 pS$. $R_{gd1} = R_S + R_{eq} + g_{m1} R_S R_{eq}$, where $R_{eq} =$
 $(g_{m2} + g_{mb2})^{-1} = 481.14 \Omega \Rightarrow R_{gd1} = 18.8 k\Omega \Rightarrow \tau_2 = C_{gd1} R_{gd1} = 263.4 pS$. $R_{eq1} =$
 $R_{eq} = 481.14 \Omega \Rightarrow \tau_3 = C_{eq1} R_{eq1} = 64.14 pS$, & $R_{eq2} = R_L = 20k \Rightarrow \tau_4 = C_{eq2} R_{eq2} =$
 $680 pS \Rightarrow \Sigma \tau = 1.94 nS \Rightarrow f_H = \frac{1}{2\pi \Sigma \tau} = 82 MHz$, & $t_{cr} = \frac{0.35}{f_H} = 4.27 nS$

4 $I_{C1} = 1mA$, & with EB area of Q_2 4 times that of $Q_1 \Rightarrow I_{C2} = 4mA$. $\therefore r_{E1} = 26 \Omega$,
 $r_{E2} = 6.5 \Omega$, & $r_{\pi 2} = 1.3 k\Omega$. Q_1 is diode connected \Rightarrow the net resistance
"seen" by $i_i = r_{E1} || r_{\pi 1} || r_{\pi 2} = 26 || 5.2 k || 1.3 k = 25.37 \Omega \Rightarrow$ Voltage drop across this
 $v = 25.37 i_i$. Output current $i_o = g_{m2} v = 25.37 i_i / r_{E2} = 3.9 i_i \Rightarrow$ Midband
current gain $i_o / i_i = 3.9$, with the i/p & o/p currents in phase. For freq. resp., $C_{\pi 1} =$
 $C_{je} + \tau_F g_{m1} = 8.7 pF$, $C_{\pi 2} = 34.77 pF$. $C_{\mu 1}$ is absent (Base-Collector short), $C_{\mu 2}$ appears
bet^m i/p & o/p. $C_{\pi 1}$ & $C_{\pi 2}$ are in $||^l \Rightarrow$ net $C_{\pi} = C_{\pi 1} + C_{\pi 2} = 43.47 pF$. Now, $R_{\pi}^o =$
 $r_{E1} || r_{\pi 1} || r_{\pi 2} = 25.37 \Omega \Rightarrow \tau_1 = R_{\pi}^o C_{\pi} = 1.1 nS$. $R_{\mu 2}$ is also equal to R_{π}^o (by
inspection) $\Rightarrow \tau_2 = R_{\mu 2} C_{\mu 2} = 20.3 pS$ (note τ_2 is so much smaller than τ_1 , that
 $C_{\mu 2}$ would not play any role in determining the cutoff freq. of the ckt). $\Sigma \tau = 1.12 nS$
 $\Rightarrow f_H = 142.1 MHz$ (very large), & $t_{cr} = 2.46 nS$.

Q_{12} & Q_{13B} both saturate, then an abnormally
large resistor (R_8)