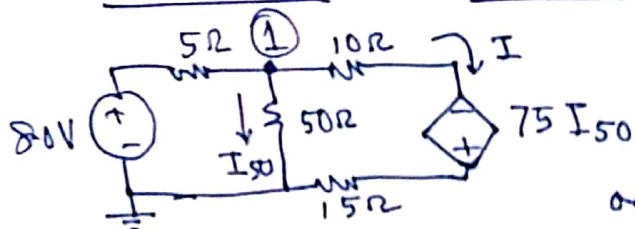


1



KCL at node 1:

$$\frac{V_1 - 80}{5} + \frac{V_1}{50} + \frac{V_1 + 75I_{50}}{10 + 15} = 0$$


$$\text{or } 0.26 V_1 + 3 \frac{V_1}{50} = \frac{80}{5}$$

$$\text{or } 0.32 V_1 = 16 \therefore V_1 = 50V. \therefore I_{50} = \frac{50}{50} = 1A$$

$$I = \frac{V_1 + 75I_{50}}{25} = \frac{50 + 75}{25} = 5A. \text{ And the power delivered}$$

$$P_{75I_{50}} = -75I_{50} \times I = -75 \times 1 \times 5 = -375W$$

2

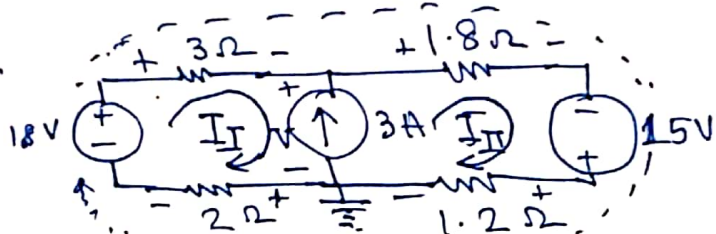

Choose mesh currents

I_I & I_{II}

$$\therefore I_{II} - I_I = 3A.$$

But voltage v is unknown.

\therefore Use a supermesh of the dotted line, which gives

$$18 = 3I_I + 1.8I_{II} - 15 + 1.2I_{II} + 2I_I.$$

$$\text{or } 33 = 5I_I + 3I_{II} \text{ or } 33 = 5I_I + 3(I_I + 3)$$

$$\therefore 33 - 9 = 8I_I \text{ or } I_I = 3A \therefore I_{II} = 6A.$$

$$V = 18 - 3I_I - 2I_{II} = 18 - 5I_I = 18 - 15 = 3V.$$

$$V_{3\Omega} + V_{2\Omega} = 18V - 3V = 15V. \therefore V_{3\Omega} = 9V \text{ \& } V_{2\Omega} = 6V. \text{ Noted}$$

$$P_{3\Omega} = 3 \times 3^2 = 27W, P_{2\Omega} = 2 \times 3^2 = 18W, P_{1.8\Omega} = 1.8 \times 6^2 = 64.8W \text{ and}$$

$$P_{1.2\Omega} = 1.2 \times 6^2 = 43.2W. \text{ Add all up and get } P_{diss} = 153W$$

Cross Check: Power Developed \rightarrow

$$P_{18V} = -18 \times 3 = -54W, P_{15V} = -15 \times 6 = -90W, P_{3A} = -3 \times 3 = -9W$$

$$\text{Total is } P_{dev} = -54 - 90 - 9 = -153W.$$

3 Apply KCL at node 1: $\frac{V_1}{50} + \frac{V_1 - 12}{2} + \frac{V_1 - V_2}{40} = 0$ or $0.515V_1 = \frac{V_2}{40} + 6$

$$\therefore V_1 = 0.046V_2 + 11.$$

Apply KCL at node 2: $\frac{V_2 - V_1}{40} + \frac{V_2}{400} - 0.5 = 0$ or $0.0275V_2 = 0.5 + \frac{V_1}{40}$

$$\therefore V_2 = \frac{0.5}{0.0275} + \frac{0.046V_2}{0.0275 \times 40} + \frac{11}{0.0275 \times 40} \text{ or } 0.958V_2 = 28.2$$


$$\therefore V_2 = 29.4V, \text{ or } V_1 = 0.046V_2 + 11 = 0.046 \times 29.4 + 11 = 12.35V$$

4

$$\frac{V_0 - V_1}{R} + \frac{V_1 - V_2}{R} + \dots + \frac{V_n - V_0}{R} = 0. \text{ or } V_0 = V_1 + V_2 + \dots + V_n$$

$$\text{or } V_0 = \frac{1}{n} \sum_{i=1}^n V_i \text{ which is the average.}$$

5

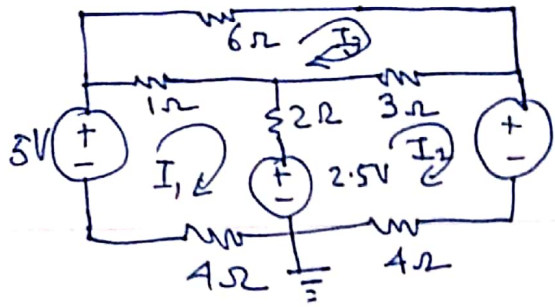

Choose mesh currents
Mesh 1: $5 + 2.5 = 1 \times (I_1 - I_3) + 2 \times (I_1 - I_2) + 4I_1$

$$\Rightarrow 2.5 = 7I_1 - 2I_2 - I_3$$

Mesh 2: $-10 + 2.5 = 4I_2 + 2(I_2 - I_1) + 3(I_2 - I_3)$

$$\Rightarrow -7.5 = -2I_1 + 9I_2 - 3I_3$$

$$\Rightarrow 7.5 = 2I_1 - 9I_2 + 3I_3$$

Mesh 3:

$$0 = 1 \times (I_3 - I_1) + 3(I_3 - I_2) + 6I_3$$

$$\Rightarrow 0 = -I_1 - 3I_2 + 10I_3$$

$$\Rightarrow 0 = I_1 + 3I_2 - 10I_3$$

$$\therefore \begin{bmatrix} 7 & -2 & -1 \\ 2 & -9 & 3 \\ 1 & 3 & -10 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 2.5 \\ 7.5 \\ 0 \end{bmatrix}$$

$$\Rightarrow [A][I] = [B]$$

$$\therefore \Delta = 7(90 - 9) + 2(-20 - 3) - 1(6 + 9) = 506$$

$$a_{11} = \begin{vmatrix} -9 & 3 \\ 3 & -10 \end{vmatrix} = 90 - 9 = 81, \quad a_{12} = \begin{vmatrix} 2 & 3 \\ 1 & -10 \end{vmatrix} = -20 - 3 = -23$$

$$a_{13} = \begin{vmatrix} 2 & -9 \\ 1 & 3 \end{vmatrix} = 6 + 9 = 15, \quad a_{21} = \begin{vmatrix} -2 & -1 \\ 3 & -10 \end{vmatrix} = 20 + 3 = 23$$

$$a_{22} = \begin{vmatrix} 7 & -1 \\ 1 & -10 \end{vmatrix} = -70 + 1 = -69, \quad a_{23} = \begin{vmatrix} 7 & -2 \\ 1 & 3 \end{vmatrix} = 21 + 2 = 23$$


$$a_{31} = \begin{vmatrix} -2 & -1 \\ -9 & 3 \end{vmatrix} = -6 - 9 = -15, \quad a_{32} = \begin{vmatrix} 7 & -1 \\ 2 & 3 \end{vmatrix} = 21 + 2 = 23$$

$$\& a_{33} = \begin{vmatrix} 7 & -2 \\ 2 & -9 \end{vmatrix} = -63 + 4 = -59$$

$$C = \begin{bmatrix} +a_{11} & -a_{12} & +a_{13} \\ -a_{21} & +a_{22} & -a_{23} \\ +a_{31} & -a_{32} & +a_{33} \end{bmatrix} \Rightarrow \begin{bmatrix} 81 & 23 & 15 \\ -23 & -69 & -23 \\ -15 & -23 & -59 \end{bmatrix}, \quad A^{-1} = \frac{1}{506} \begin{bmatrix} 81 & -23 & -15 \\ 23 & -69 & -23 \\ 15 & -23 & -59 \end{bmatrix}$$

$$\therefore \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \frac{1}{506} \begin{bmatrix} 81 & -23 & -15 \\ 23 & -69 & -23 \\ 15 & -23 & -59 \end{bmatrix} \begin{bmatrix} 2.5 \\ 7.5 \\ 0 \end{bmatrix} = \frac{1}{506} \begin{bmatrix} 30 \\ -460 \\ -135 \end{bmatrix} = \begin{bmatrix} 0.059 \\ -0.91 \\ -0.266 \end{bmatrix} A$$
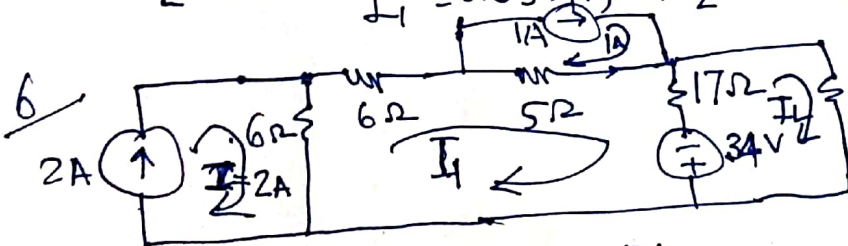
$$I_1 = 0.059 A, \quad I_2 = -0.91 A \quad \& \quad I_3 = -0.266 A$$




In the central mesh:

$$6(I_1 - 2) + 6I_1 + 5(I_1 - I_L) + 17(I_1 - I_L) - 34 = 0$$

$$\Rightarrow 34I_1 - 17I_L = 51 \quad \therefore 2I_1 - I_L = 3 \quad \& \quad I_L = 2I_1 - 3$$


In the rightmost mesh: $17(I_L - I_1) + 1.5I_L + 34 = 0$
giving $-17I_1 + 18.5I_L = -34$ or $-17I_1 + 18.5(2I_1 - 3) = -34$
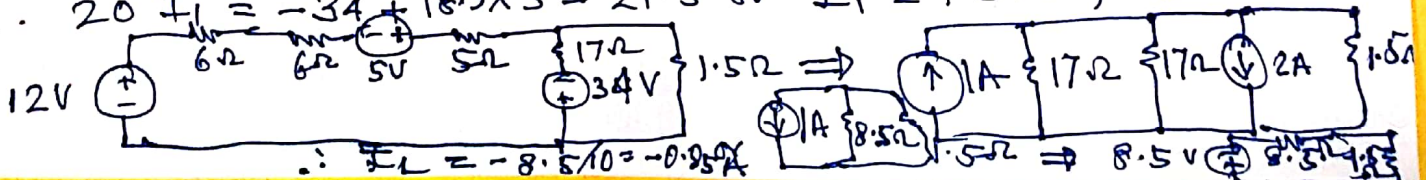
$$\therefore 20I_1 = -34 + 18.5 \times 3 = 21.5 \quad \& \quad I_1 = 1.075 A, \quad I_L = -0.85 A$$




$$\therefore I_L = -8.5/10 = -0.85 A \quad \Rightarrow \quad 8.5 V \quad \& \quad 8.5 A$$

7/

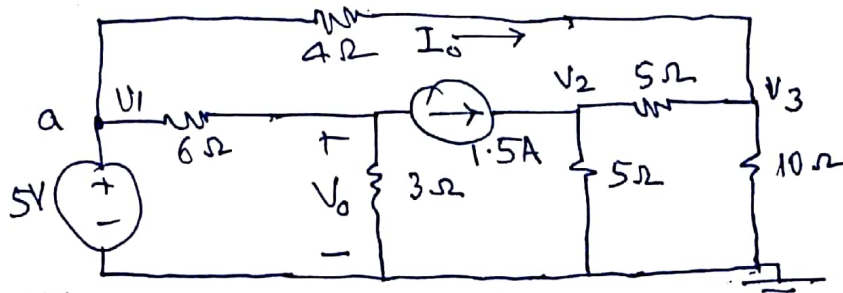

By superposition

(i) Open 1.5A Current Source:

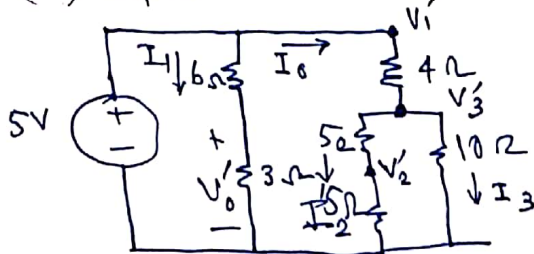


$$I_1' = \frac{5}{9} \text{ A} \quad I_0' = \frac{5}{4 + (5+5) \parallel 10}$$

$$V_1' = 5 \text{ V} \quad V_0' = \frac{15}{9} \text{ V}$$

$$V_2' = \frac{5 \times 5}{18} \text{ V} \quad V_3' = 10 \times \frac{5}{18}$$

$$\therefore I_2' = I_3' = \frac{5}{18} \text{ A}$$

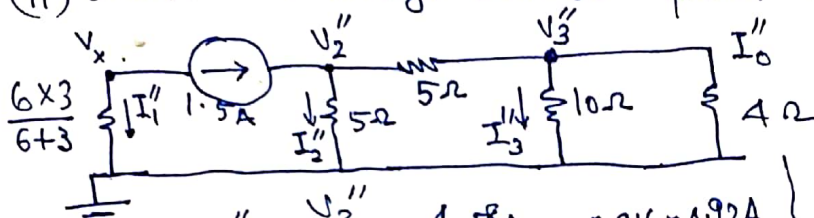(ii) Short 5V Voltage Source: point (a) is grounded i.e. $V_1'' = 0$



$$I_2'' = \frac{V_2''}{5} = \frac{4.58}{5} = 0.916 \approx 0.92 \text{ A}$$

$$\therefore I_{5\Omega} = 1.5 - 0.92 = 0.584 \text{ A}$$

$$I_0'' = \frac{1.67}{4} = 0.42 \text{ A} \quad \therefore I_3'' = \frac{1.67}{10} = 0.167 \text{ A}$$

$$\therefore V_0 = V_0' + V_0'' = \frac{15}{9} + (-1.5 \times \frac{12}{9}) = 1.67 - 2 = -0.33 \text{ V}$$

$$I_0 = I_0' + I_0'' = \frac{5}{9} + 0.42 = 0.98 \text{ A}$$

$$V_0'' = V_x = -1.5 \times \frac{12}{9} \text{ V}$$


$$V_2'' = 1.5 \times [5 \parallel (5+10 \parallel 4)]$$

$$= 1.5 \times [5 \parallel (5 + \frac{40}{14})]$$


$$= 1.5 \times (5 \parallel 7.86) = 4.58 \text{ V}$$

$$V_3'' = 0.584 \times \frac{40}{14} = 1.67 \text{ V}$$

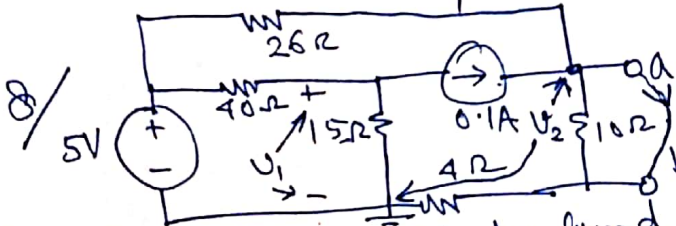Need not calculate all node voltages & currents only V_0 & I_0 needed.



Null
The independent
sources.

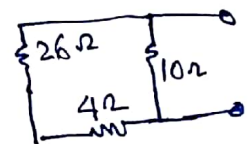

I_{sc} or V_{oc} needed to be found, & as there is a current source easier to find I_{sc} \rightarrow Nodal Equations:

$$\frac{V_2 - 5}{26} + \frac{V_2}{14} - 0.1 = 0 \rightarrow 0.11 V_2 = 0.29 \rightarrow V_2 = 2.66 \text{ V}$$

$$V_{Th} = \frac{V_2}{14} \times 10 = 1.9 \text{ V}$$


$$\text{Just for the sake of completeness find } I_{sc}$$

$$\text{again nodal equations } \frac{V_2' - 5}{26} + \frac{V_2'}{4} - 0.1 = 0 \sim 0.29 V_2' = 0.29$$

$$\text{or } V_2' = 1 \text{ V} \quad \therefore I_{sc} = \frac{V_2'}{4} = 0.25 \text{ A} \quad \text{or } R_{Th} = \frac{1.9}{0.25} = 7.6 \Omega$$

Very close to the direct method. The difference is due to rounding off errors.

9

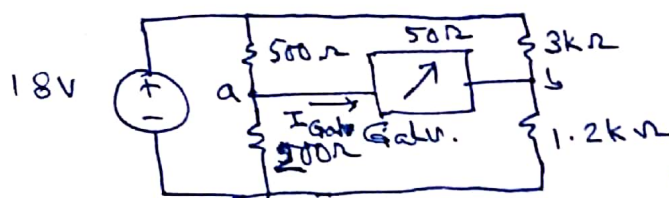

At null $V_{ab} = 0 \therefore I_{50\Omega} = 0$.
 $\therefore \frac{500}{200} = \frac{3k\Omega}{1.2k\Omega}$ Bridge is balanced.
 Now assume $3k\Omega$ is off by 0.1%
 $\text{or } 3k\Omega \rightarrow 3.003k\Omega$


$$V_{ab} = \frac{18}{700} \times 200 - \frac{18 \times 1200}{4203}$$

$$= 5.143 - 5.139 \text{ (keeping significant decimal digits here is necessary)}$$

$$= 0.00367V = 3.67mV$$


$$R_{Th} = 500 \parallel 200 + 3.003k\Omega \parallel 1.2k\Omega = 1,000.245\Omega$$
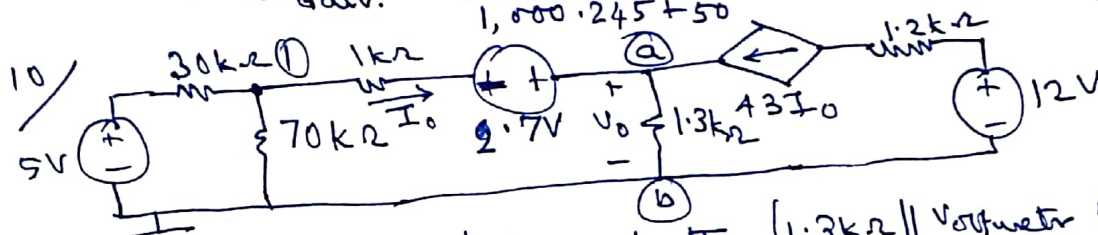
$$\therefore I_{Galv.} = \frac{3.67mV}{1,000.245 + 50} = 0.00349mA \approx 3.5\mu A$$



Does one
Need to find
the V_{Th} & R_{Th} ?

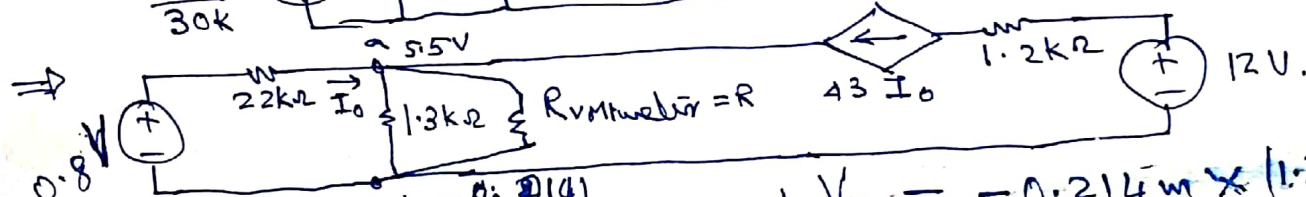
Note that the current through the $(1.3k\Omega \parallel \text{Voltmeter Resistance})$ is $43I_0$.
 and V_0 is 5.5V. Node equation at ① gives simplifying the circuit.



$$I_0 = \frac{0.8}{22k} = -0.0364mA \text{ and } V_a = -0.214mV \times (1.3k \parallel R)$$

\rightarrow voltage is negative with respect to b

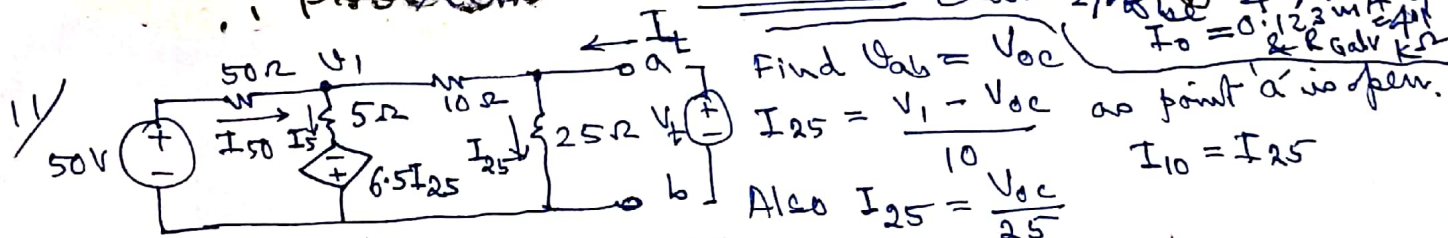\therefore Problem is incorrect. Choose 27kΩ for $R_{Galv.}$



$$\therefore V_1 = V_{oc} \left(\frac{1}{10} + \frac{1}{25} \right) \times 10 = 1.4V_{oc}$$

$$I_{50} = \frac{50 - V_1}{50} = 1 - \frac{V_1}{50} = 1 - \frac{1.4V_{oc}}{50} \text{ and } I_5 = I_{50} - I_{25}$$

$$= 1 - \frac{1.4V_{oc}}{50} - \frac{V_{oc}}{25} = 1 - 0.068V_{oc}$$

$$5I_5 - 6.5I_{25} = V_1 = 1.4V_{oc}$$

$$5 \times (1 - 0.068V_{oc}) - 6.5 \frac{V_{oc}}{25} = 1.4V_{oc} \text{ solve to get } V_{oc} = 2.87V$$

R_{Th} is easier to be found by applying a test voltage V_t at a b and nulling all independent sources.


$$\therefore I_t = \frac{V_t}{25} + \frac{V_t - V_1}{10} = 0.14V_t - 0.1V_1 \text{ and node analysis at } V_1$$

$$\text{so } \frac{V_1 - 0}{50} + \frac{V_1 + 6.5(V_t/25)}{5} + \frac{V_1 - V_t}{10} = 0 \text{ or } 0.32V_1 - 0.048V_t = 0$$

$$\therefore V_1 = \frac{0.048V_t}{0.32}$$

$$\therefore I_t = 0.14V_t - 0.1 \times \frac{0.048V_t}{0.32} = \frac{0.048V_t}{0.32} \therefore R_{Th} = \frac{V_t}{I_t} = 8\Omega$$

12/

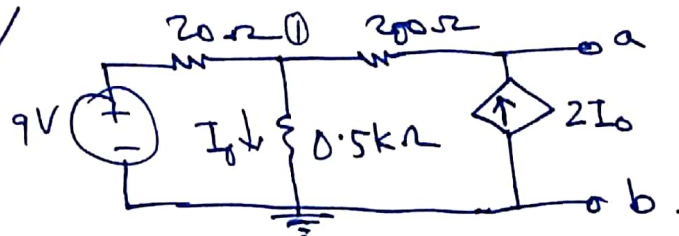Note $V_{oc} = V_{ab}$

KCL at node ① gives.

$$\frac{V_1 - 9}{20} + I_o + \frac{V_1 - V_{oc}}{200} = 0$$

$$I_o = \frac{V_1}{500}$$

$$\text{and } \frac{V_1 - V_{oc}}{200} = -2I_o = -\frac{V_1}{250}$$

$$\therefore V_{oc} = 200 \times 0.009 V_1 = 1.8 V_1$$

The KCL eqn. can now be written as $\frac{V_1}{20} + \frac{V_1}{500} + \frac{V_1}{200} - \frac{1.8 V_1}{200} = \frac{9}{20}$

$$\text{or } (0.05 + 0.002 + 0.005 - 0.009) V_1 = 0.45 \text{ or } V_1 = 9.375 \text{ V}$$

$$\therefore V_{oc} = 1.8 \times 9.375 = \underline{16.875 \text{ V}}$$

To find R_{Th} use V_t & I_t technique after shorting the 9V supply and at "a" KCL is

$$\frac{V_t - V_1}{200} - 2I_o = I_t \text{ where } I_o = \frac{V_1}{500} \text{ from node ①}$$

$$\therefore I_t = \frac{V_t}{200} - V_1 \left(\frac{1}{200} + \frac{1}{250} \right) = 0.005 V_t - V_1 (0.005 + 0.004)$$

$$= 0.005 V_t - V_1 (0.009)$$

KCL at node ① gives.

$$\frac{V_1}{20 \parallel 500} + \frac{V_1 - V_t}{200} = 0 \text{ or } 200(0.052 + 0.005) V_1 = V_t$$

$$\therefore V_1 = \frac{V_t}{11.4}$$

$$\therefore I_t = 0.005 V_t - \frac{0.009}{11.4} V_t$$

$$= 0.00421 \times V_t$$

$$\therefore R_{Th} = \frac{V_t}{I_t} = \underline{\underline{237.53 \Omega}}$$