

$$v_o = -i_o R_D \quad v_{bs} = -v_s \quad v_s = i_o R_S$$

$$KCL \text{ at } S: \frac{v_s}{R_S} + \frac{v_s - v_o}{r_o} - g_m(v_i - v_s) + g_m v_s = 0$$

$$\text{Also, } i_o = \frac{v_o - v_s}{r_o} + g_m(v_i - v_s) - g_m v_s$$

Combining the 3 expressions, after some algebra, it can be shown that $A_v = \frac{v_o}{v_i} = -\frac{i_o R_D}{v_i} = -\frac{g_m R_D}{1 + (g_m + g_{mb})R_S + R_S/r_o}$.

For R_o : We short v_i to ground, remove R_D , & excite the o/p by a test source v_t .


Note: With $v_i = 0$, $v_{gs} = v_{bs} = -v_s$.

The test current $i_t = \frac{v_t - v_s}{r_o} + (g_m + g_{mb})(-v_s)$ with $v_s = i_t R_S$.

$$\Rightarrow R_o = \frac{v_t}{i_t} = R_S + r_o [1 + (g_m + g_{mb})R_S]. \quad \text{Note: if } R_S \rightarrow \infty \quad R_o \rightarrow \infty.$$

2. In the absence of base resistance r_b , $R_i^o = r_E$, $A_v = +\frac{R_C}{r_E}$, & $R_o = R_C$.
 $I_C = 260 \mu A \Rightarrow r_E = \frac{V_T}{I_C} = 100 \Omega$, & $r_{RC} = 10 \text{ k}\Omega$. $\Rightarrow R_i = 100 \Omega$, $A_v = +100$, $R_o = 10 \text{ k}\Omega$.

With $r_b = 101 \Omega$,

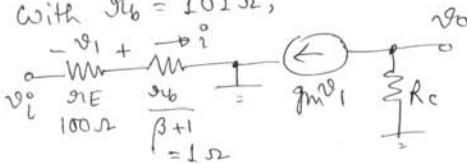

$$\Rightarrow \frac{v_o}{v_i} = + \frac{g_m R_C}{1 + \frac{r_b}{r_{RC}}} = 99.99 \quad (\text{very little effect})$$


Reason: Very small r_b as compared to r_{RC} .

Also, R_C large compared to r_b .

Large change in A_v can be observed if R_C & r_{RC} are low, & r_b is large.

$$R_i^o = r_E + \frac{r_b}{\beta + 1} = 101 \Omega. \quad R_o = R_C = 10 \text{ k}\Omega$$

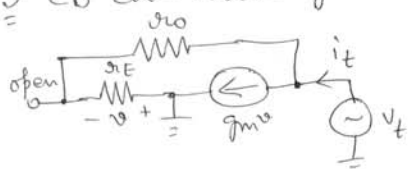3. CB ckt. excited by an ideal current source:



$$v = -\frac{v_t r_E}{r_E + r_o} \quad i_t = g_m v + \frac{v_t}{r_E + r_o}$$


$$\Rightarrow i_t = \frac{v_t (1 - g_m r_E)}{r_E + r_o} \Rightarrow R_o' = \frac{v_t}{i_t} = \frac{r_E + r_o}{1 - g_m r_E}$$

* Note: $g_m r_E = \alpha$ & if α is exactly 1, then $R_o' \rightarrow \infty$.

$$\Rightarrow R_o' \approx \frac{r_o}{1 - \alpha}$$

o.o. $r_o \gg r_E$ (in general)
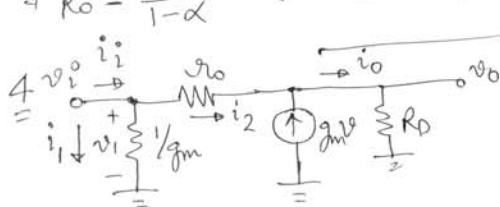
$$\& \alpha = \frac{\beta}{\beta + 1} \Rightarrow R_o' \approx r_o(\beta + 1) = \beta r_o \quad (\beta \gg 1).$$



$$v_o = i_o R_D \quad i_o = i_2 + g_m v_1 \quad v_1 = v_i$$

$$i_1 = g_m v_i \quad i_2 = i_1 + i_2 \quad i_2 = \frac{v_i - v_o}{r_o}$$


Combine all these relations to get

$$A_v = \frac{v_o}{v_i} = \frac{(1 + g_m r_o) R_D}{r_o + R_D} \quad \text{If } r_o \rightarrow \infty \quad A_v \rightarrow g_m R_D$$

$$R_i^o = \frac{v_i}{i_i} \quad \text{with } i_2 = i_1 + i_2 \quad i_1 = g_m v_i \quad \& \quad i_2 = \frac{v_i - v_o}{r_o} \quad \text{with } A_v = \frac{v_o}{v_i}$$

$$\Rightarrow R_i^o = \frac{(r_o + R_D)}{1 + g_m r_o} \quad \text{As } r_o \rightarrow \infty, R_i^o \rightarrow 1/g_m.$$

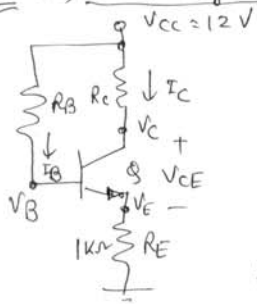
5 a) DC Analysis: Coupling & Bypass capacitors open up. (2)



Need $I_C = 1\text{mA}$ ($\beta = 200$) $\Rightarrow I_B = \frac{I_C}{\beta} = 5\mu\text{A} \Rightarrow I_E = (\beta+1)I_B = 1.005\text{mA}$
 $\Rightarrow V_E = I_E R_E = 1.005\text{V} \Rightarrow V_B = V_E + V_{BE} = 1.705\text{V}$
 $\Rightarrow R_B = \frac{V_{CC} - V_B}{I_B} = 2.06\text{M}\Omega$ for best biasing, $V_{CE} \approx \frac{V_{CC}}{3} = 4\text{V}$
 $\Rightarrow R_C = \frac{V_{CC} - V_{CE} - I_E R_E}{I_C} = 7\text{k}\Omega$

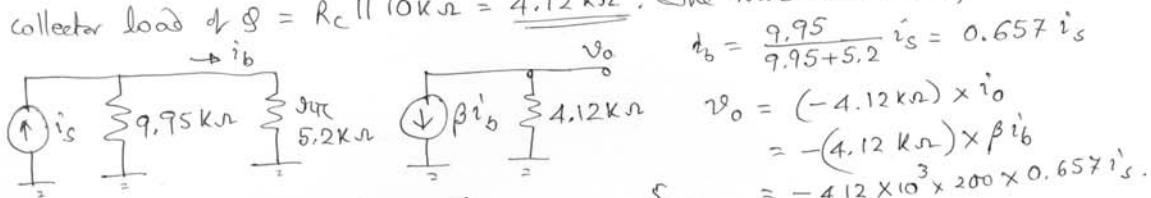b) AC Analysis: In midband, coupling & bypass capacitors short out, $\Rightarrow R_E$ gets shorted by C_2 . $R_B (= 2.06\text{M}\Omega)$ appears in \parallel with $10\text{k}\Omega$,


\Rightarrow net res. $= 9.95\text{k}\Omega$. $I_C = 1\text{mA} \Rightarrow g_{mE} = 26\Omega$ & $g_{mC} = 5.2\text{k}\Omega$. The effective collector load of $g = R_C \parallel 10\text{k}\Omega = 4.12\text{k}\Omega$. The midband ac eqv.:



\Rightarrow Midband transresistance $\frac{v_o}{i_s} = -5.4 \times 10^5 \text{V}$

6 a) DC Analysis: open capacitors C_1 & C_2 . Then, $I_E = 1\text{mA} = I_C + I_B = (\beta+1)I_B$
 $= 101 I_B \Rightarrow I_B = 9.9\mu\text{A}$. $\therefore I_C = 0.99\text{mA}$. $V_C = I_C \times 175 + 0.7 + I_B \times 100\text{k}\Omega$, &
 $V_E = I_E \times 175 \Rightarrow V_{CE} = V_C - V_E = 0.7 + (9.9\mu\text{A}) \times (100\text{k}\Omega) = 1.69\text{V}$, which is much
 larger than the value of $V_{CE}(\text{sat})$ of $0.1\text{V} \Rightarrow$ The biasing is okay.

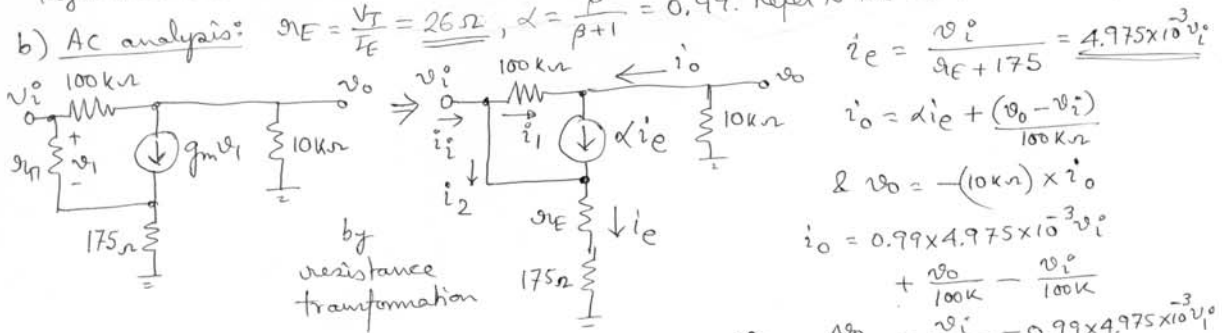b) AC analysis: $g_{mE} = \frac{V_T}{I_E} = 26\Omega$, $\alpha = \frac{\beta}{\beta+1} = 0.99$. Refer to the ac midband eqv.:



$\Rightarrow \frac{v_o}{v_i} = -\frac{4.915 \times 10^{-3}}{1.1 \times 10^{-4}} = -44.68$


$R_i = \frac{v_i}{i_i}$ with $i_i = i_1 + i_2$ $i_2 = (1-\alpha)i_e = (1-0.99) \times 4.975 \times 10^{-3} v_i = 4.975 \times 10^{-5} v_i$

& $i_1 = \frac{v_i - v_o}{100\text{k}}$ with $v_o = -44.68 v_i \Rightarrow i_1 = \frac{45.68}{100\text{k}} v_i = 4.568 \times 10^{-4} v_i$

$\Rightarrow i_1 + i_2 = 5.065 \times 10^{-4} v_i \Rightarrow R_i = \frac{v_i}{i_i} = 1.974\text{k}\Omega$.

By inspection $R_o = 100\text{k}\Omega$ (note: v_i is shorted under this condⁿ).

7 a) DC Analysis: C_1 & C_2 open up.

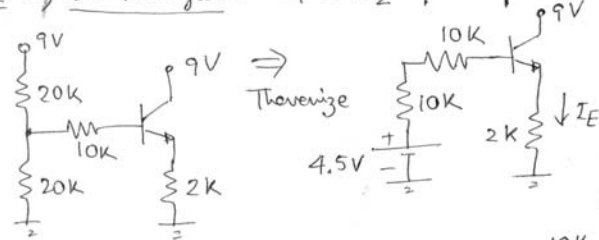


$$I_E = \frac{4.5 - 0.7}{2k + \frac{10k + 10k}{101}} = 1.73 \text{ mA} \quad (3)$$

$$I_C = \alpha I_E = 1.71 \text{ mA} \quad r_E = 15 \Omega,$$

$$r_{re} = 1.5 k\Omega, \quad g_m = 65.8 \text{ mS}.$$


b) AC Analysis: Both C_1 & C_2 shorted.

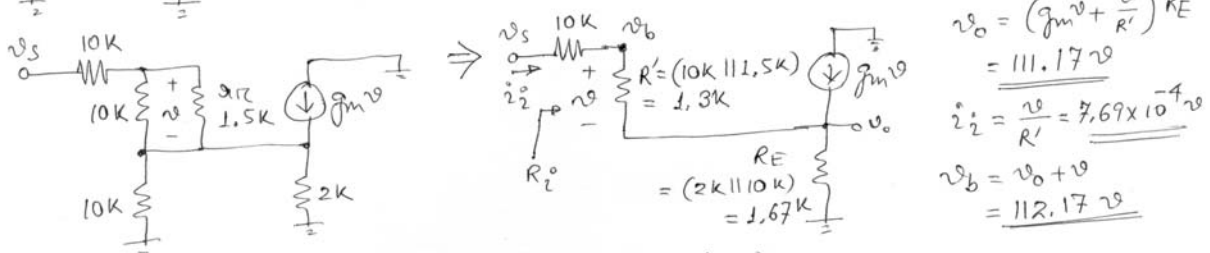

$$\Rightarrow R_i = \frac{v_b}{i_i} = \frac{112.17 \text{ V}}{7.69 \times 10^{-4} \text{ A}} = 145.86 k\Omega \quad (\text{very large}).$$

$$\frac{v_o}{v_s} = \frac{v_o}{v_b} \times \frac{v_b}{v_s} = \frac{111.17}{112.17} \times \frac{R_i}{R_i + 10k} = \frac{111.17}{112.17} \times \frac{145.86}{145.86 + 10} = 0.923 \Rightarrow \text{a perfect buffer (almost!)}$$

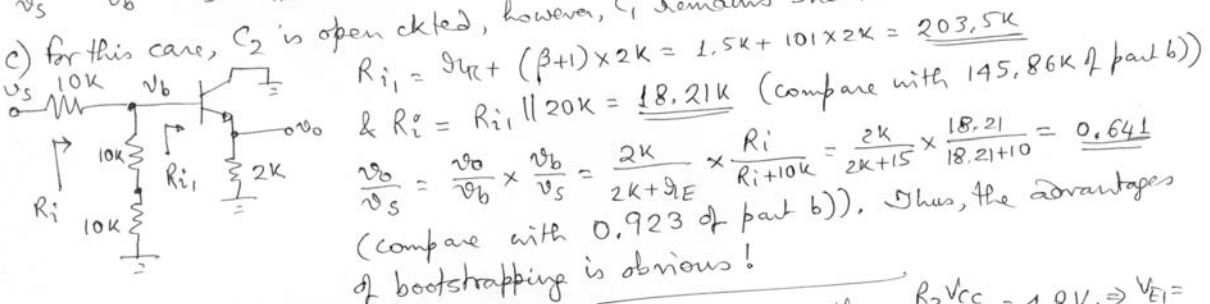c) for this case, C_2 is open ckted, however, C_1 remains shorted.



$$R_{i1} = r_{re} + (\beta + 1) \times 2k = 1.5k + 101 \times 2k = 203.5k$$

$$\& R_{i2} = R_{i1} \parallel 20k = 18.21k \quad (\text{compare with } 145.86k \text{ of part b)})$$

$$\frac{v_o}{v_s} = \frac{v_o}{v_b} \times \frac{v_b}{v_s} = \frac{2k}{2k + r_{re}} \times \frac{R_{i1}}{R_{i1} + 10k} = \frac{2k}{2k + 1.5k} \times \frac{18.21}{18.21 + 10} = 0.641$$

(compare with 0.923 of part b)). Thus, the advantages of bootstrapping is obvious!

8 a) All capacitors open up. Neglecting base current, $V_{B1} = V_{B2} = \frac{R_2 V_{CC}}{R_1 + R_2} = 4.8 \text{ V} \Rightarrow V_{E1} =$

$$V_{E2} = 4.1 \text{ V} \Rightarrow I_{C1} = I_{C2} \approx \frac{V_{E1}}{r_E} = 1.05 \text{ mA} \cdot V_{CE1} = V_{CE2} = V_{CC} - I_{C1}(R_{C1} + R_{E1}) = 3.77 \text{ V}$$

Biasing is okay $\because V_{CE} \gg 0.1 \text{ V}$, however, not the best ($\because V_{CE} (\text{best}) \approx \frac{V_{CC}}{3} = 5 \text{ V}$).

$$b) g_{m1} = g_{m2} = 40.38 \text{ mA/V}, \quad r_{E1} \approx 1/g_{m1} = 24.76 \Omega, \quad r_{re} = \beta r_{E1} = 2.48 k\Omega.$$

In midband, all coupling & bypass capacitors short out. The entire problem can be done by simple inspection.

$$i) R_{i1} = R_1 \parallel R_2 \parallel r_{re} = 2.3 k\Omega, \quad \frac{v_{b1}}{v_s} = \frac{R_{i1}}{R_{i1} + R_s} = 0.315.$$

$$ii) R_{i2} = R_{i1} = 2.3 k\Omega. \text{ Load of } Q_1, R_{L1} = R_{C1} \parallel R_{i2} = 1.72 k\Omega \Rightarrow \frac{v_{b2}}{v_{b1}} = -\frac{R_{L1}}{r_{E1}} = -69.47.$$

$$iii) \text{ Load of } Q_2, R_{L2} = R_{C2} \parallel R_L = 1.55 k\Omega \Rightarrow \frac{v_o}{v_{b2}} = -\frac{R_{L2}}{r_{E2}} = -62.6.$$

$$iv) \text{ Overall } A_v = \frac{v_o}{v_s} = \frac{v_o}{v_{b2}} \times \frac{v_{b2}}{v_{b1}} \times \frac{v_{b1}}{v_s} = +1370 \quad (\text{huge!})$$

Thus, cascading of 2 CE stages is capable of producing very large voltage gain.