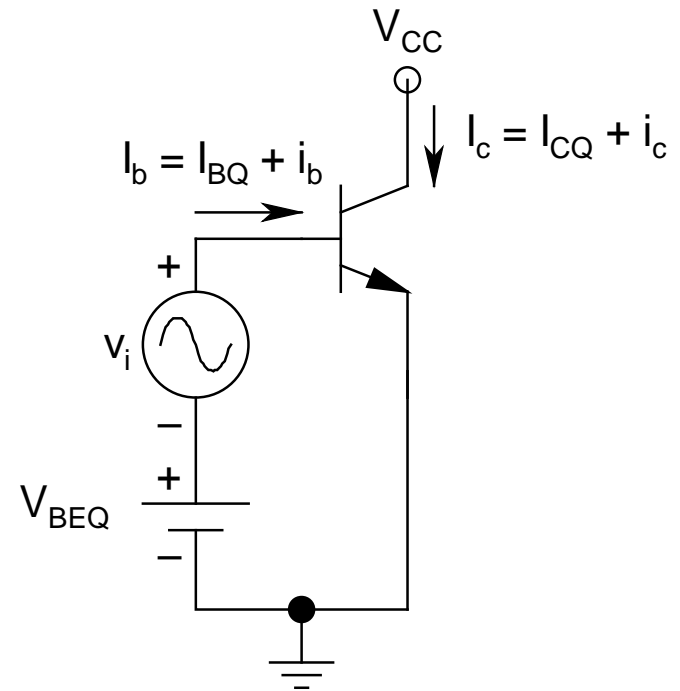


# Validity of the Small-Signal Model

- Basically *linearization* of the *operating region* around the *Q-point*
- *This linearization should not contain any higher-order terms*



- To start with, assume  $V_A \rightarrow \infty$ 
  - $I_{CQ} = I_S \exp(V_{BEQ}/V_T)$
- Thus:

$$\begin{aligned} I_c &= I_S \exp\left(\frac{V_{be}}{V_T}\right) = I_S \exp\left(\frac{V_{BEQ} + v_i}{V_T}\right) \\ &= I_S \exp\left(\frac{V_{BEQ}}{V_T}\right) \exp\left(\frac{v_i}{V_T}\right) = I_{CQ} \exp\left(\frac{v_i}{V_T}\right) \end{aligned}$$

- Expand the *exponential term* in series:

$$\blacktriangleright I_c = I_{CQ} \left[ 1 + \frac{v_i}{V_T} + \frac{1}{2!} \left( \frac{v_i}{V_T} \right)^2 + \frac{1}{3!} \left( \frac{v_i}{V_T} \right)^3 + \dots \right]$$

- Thus:

$$\blacktriangleright i_c = I_c - I_{CQ} = I_{CQ} \left[ \frac{v_i}{V_T} + \frac{1}{2!} \left( \frac{v_i}{V_T} \right)^2 + \frac{1}{3!} \left( \frac{v_i}{V_T} \right)^3 + \dots \right]$$

- *True linearization* of  $i_c$ - $v_i$  relation *can be achieved* only if *all higher-order terms* can be *neglected*  $\Rightarrow v_i$  should be  $\ll V_T$

# Small-Signal Model Parameters

- *Incremental Emitter Resistance* ( $r_E$ ):

$$r_E = \frac{V_i}{i_e} = \frac{\Delta V_{BE}}{\Delta I_E} \equiv \frac{dV_{BE}}{dI_E} = \frac{V_T}{I_E}$$

- *Transconductance* ( $g_m$ ):

$$g_m = \frac{i_c}{V_i} = \frac{\Delta I_C}{\Delta V_{BE}} \equiv \left. \frac{dI_C}{dV_{BE}} \right|_{V_{CE} \text{ constant}} = \frac{I_C}{V_T}$$

- Thus,  $g_m r_E = I_C/I_E = \alpha \approx 1$
- *A frequently used approximation:*
  - $g_m = 1/r_E$
- For  $I_C = 1 \text{ mA}$ :
  - $r_E = 26 \Omega$  and  $g_m = 1/26 \text{ A/V}$
- As  $I_C \uparrow$ :
  - $g_m \uparrow$  and  $r_E \downarrow$
  - Also  $P_D \uparrow$
- Gain =  $f(g_m)$ 
  - $\Rightarrow$  For *higher gain*, the circuit has to be fed *more power*