

- $V_{CE} = 0.7 \text{ V}$ is known as *onset of saturation* (OS)
- *Saturation*:
 - For $V_{CE} < 0.7 \text{ V}$
 - CB junction becomes *forward biased*
 - Collector also starts to *inject* electrons to base
 - *Two effects*:
 - *Net electrons reaching collector* $\downarrow \Rightarrow I_C \downarrow$
 - *Base gets flooded with electrons*
 \Rightarrow *Recombination increases manyfold* $\Rightarrow I_B \uparrow$
 - Thus, $\beta \downarrow \Rightarrow$ Defined as $\beta_{sat} (= I_{C,sat}/I_{B,sat})$

- Noting that $V_\gamma = 0.6 \text{ V}$, for $V_{BC} \leq 0.5 \text{ V}$, *injection* of electrons from *collector to base* will be *negligible*
 - It can be *assumed* that *FA operation* is *maintained* till this point, with β *retaining* its *nominal (FA) value*
 - $V_{CE} = 0.2 \text{ V}$ at this point, and is known as the *point of soft saturation* (SS)
- Beyond this point, BJT enters the *operating domain* known as *hard saturation* (HS)

- In *hard saturation*, $V_{BC} \approx 0.7$ V, and collector *injects* electrons *vigorously* into the base
- To *counter* this effect, V_{BE} automatically *increases* to about 0.8 V
- At this point, $V_{CE} = 0.1$ V, and is known as the *point of hard saturation* (HS)
- Note that all these numbers are for *quick estimates*, and *actual values* can be a *little different* from these

- ***Degree of Saturation*** (DoS):
 - $\text{DoS} = \beta/\beta_{\text{sat}} (\geq 1)$
 - Portrays how *deeply* the BJT is driven into *saturation*
- ***Commonly used values*** of *parameters* for *quick estimate*:
 - $V_{\text{BE}}(\text{FA}) = V_{\text{BE}}(\text{SS}) = 0.7 \text{ V}$
 - $V_{\text{BE}}(\text{HS}) = 0.8 \text{ V}$
 - $V_{\text{CE}}(\text{OS}) = 0.7 \text{ V}, V_{\text{CE}}(\text{SS}) = 0.2 \text{ V}$
 - $\text{DoS}(\text{FA}, \text{OS}, \text{SS}) = 1, \text{DoS}(\text{HS}) > 1$

- BJTs in *analog circuits* are used as *amplifiers*, and should *never* be pushed to *hard saturation* (*β drops significantly*)
 - *Lowest limit* of $V_{CE} = 0.2 \text{ V}$ (*soft saturation*)
- On the other hand, BJTs used in *digital circuits*, while *on*, are always pushed to *hard saturation*, since they act basically as *switches*
 - $V_{CE} = 0.1 \text{ V}$ (*hard saturation*)

Finding the Operating Point: Load Line Analysis

- *Quick estimate* in *FA mode*:
 - $I_B = (V_B - V_{BE})/R_B$
 - $V_{BE} = 0.7 \text{ V}$
 - $I_C = \beta I_B$
 - *Independent* of R_C , so long as *FA operation* is *maintained*

