
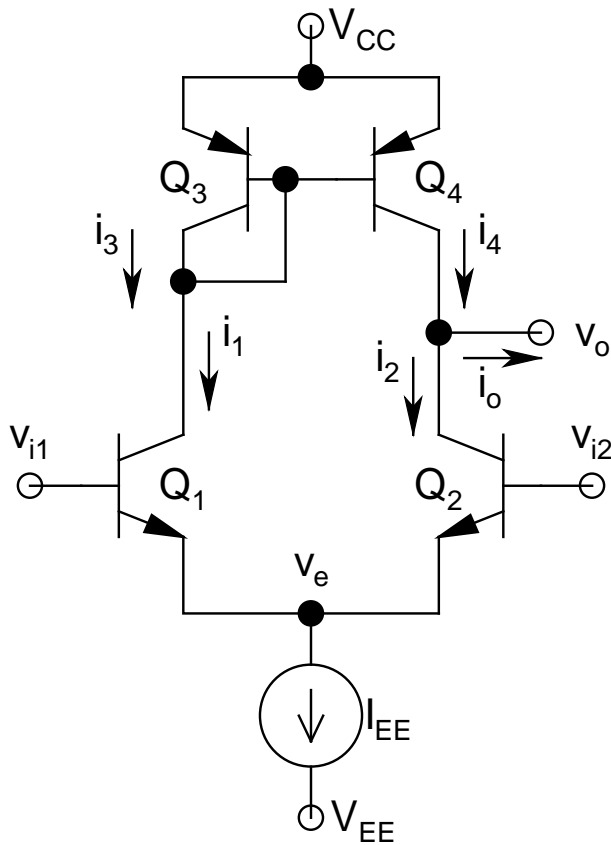


- *Actively Loaded DA:*

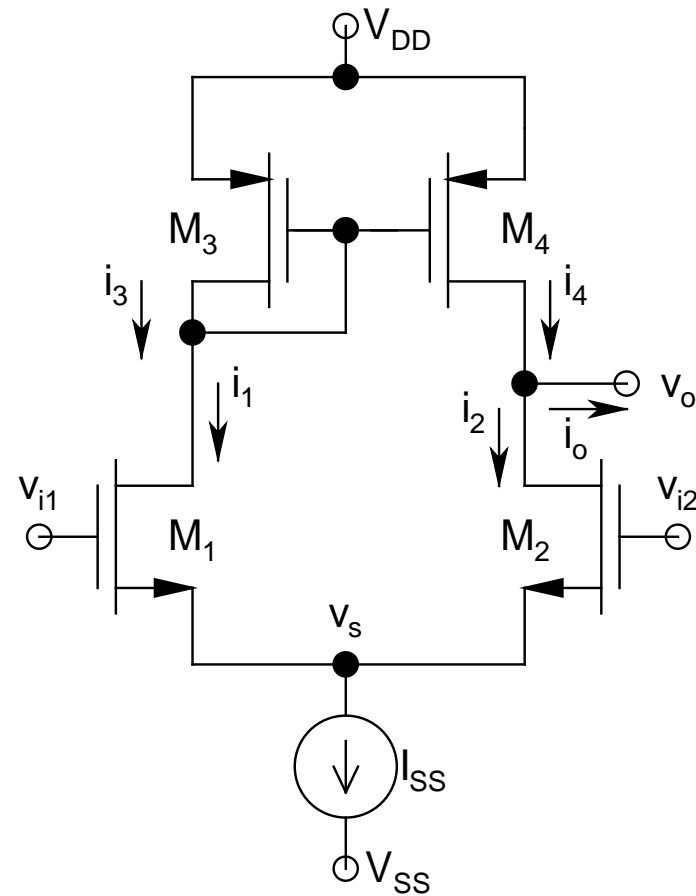

BJT Implementation



MOS Implementation

- Absolutely *similar topologies* for *both BJT and MOS implementations*
- *Produces double-ended to single-ended conversion*, i.e., *from two inputs to a single output*
- *Q_1 - Q_2 / M_1 - M_2 / Q_3 - Q_4 / M_3 - M_4 perfectly matched*
- *Output should never be taken from collector/drain of Q_1 / M_1 (Why?)*
- *DC biasing* is *absolutely straightforward* with *all branch currents equal to $I_{EE}/2$ or $I_{SS}/2$*

- **Caution:** *Half-circuit technique can't be used for this circuit*, since *collector/drain circuits of the two sides are coupled*, i.e., $i_3 = i_4$ (*always*)
- This circuit can be *analyzed by inspection*
- **Define** $v_{id} = v_{i1} - v_{i2}$
- *Apply* $+v_{id}/2$ *at the base of* Q_1 */gate of* M_1
- *Apply* $-v_{id}/2$ *at the base of* Q_2 */gate of* M_2
- From **symmetry** of the circuit *around the BE/GS loops*, the *common emitter/source node* is at **ac ground** (i.e., $v_e = v_s = 0$)

- Since $v_s = 0$, M_1 - M_2 won't have any body effect issue
- Now, $i_3 = i_4$ (*mirror*), $i_3 = i_1$ (*same branch*), and $i_2 = -i_1$ (*symmetry*)
- Also, $i_1 = g_m v_{id}/2$ and $i_2 = -g_m v_{id}/2$

$$g_m = I_{EE}/(2V_T) \text{ (BJT Implementation)}$$

$$= (k_N I_{SS})^{1/2} \text{ (MOS Implementation)}$$
- Hence, the *short-circuit output current* (with the *output terminal shorted to ground*):

$$i_o = i_4 - i_2 = i_1 - i_2 = 2i_1 = g_m v_{id}$$

- To find the **output voltage**, we need to use the **Thevenin technique**:
 - **Open-Circuit Voltage** = **Short-Circuit Current** \times **Thevenin Resistance**
- **Thevenin Resistance** (**looking from the output**):

$$R_o = r_{o2} // r_{o4}$$
- Thus, the **output voltage**:

$$v_o = i_o R_o = g_m (r_{o2} // r_{o4}) v_{id}$$
- Hence, the **differential-mode gain**:

$$A_{dm} = v_o / v_{id} = +g_m (r_{o2} // r_{o4})$$
- **$R_i = 2r_\pi$** (**BJT Implementation**)

- ***Ex.:** Prove the expressions for A_{dm} and R_i from the hybrid- π model*
- *A_{cm} for this circuit is a little difficult to evaluate*
- However, the ***CMRR can be safely approximated as:***

$$CMRR \approx 20\log_{10}(2g_m R_{EE})$$

R_{EE} : *Output resistance of the bias current source I_{EE}/I_{SS}*
- In order to ***improve CMRR***, various *current source topologies* can be used

- **Example: Simple npn CM**

- **One of the simpler choices**

- **Q_5 - Q_6 perfectly matched**


- **Neglecting base currents:**

$$I_{REF} = I_{EE} = I_{C6}$$

$$= (V_{CC} - V_{BE} - V_{EE})/R$$

- $R_{EE} = r_{06} = V_A/I_{EE}$

 - Acts as a **current source** of **magnitude I_{EE}** with a shunt **resistance R_{EE}**



- *Insights:*

- *Recall: A_{dm} independent of R_{EE} , but A_{cm} and CMRR strongly depend on R_{EE}*
- *To maximize CMRR, R_{EE} should be increased as much as possible*
- *To increase R_{EE} , other current sources discussed in class, e.g., *ratioed mirror*, *cascode*, *Widlar*, etc., can be used*
- *Note that with more advanced architectures, $V_o(min)$ increases, and may become a limiting factor!*