
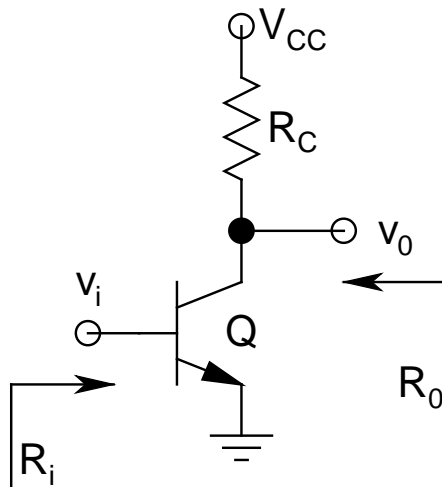


Single-Stage Amplifiers

- **Common-Emitter (CE):**

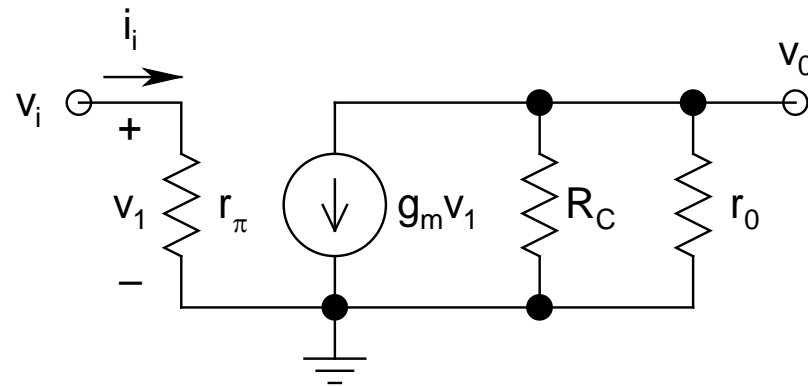

ac Schematic



ac Low-Frequency Equivalent

➤ ***Biasing circuit not shown***

- By inspection, *Voltage Gain*:

$$A_v = \frac{v_o}{v_i} = \frac{-g_m v_1 (R_C \parallel r_o)}{v_i} = -g_m (R_C \parallel r_o)$$

- The *negative sign* in front implies *180° phase shift* between v_i and v_o

- *v_i and v_o are exactly out of phase*

- For *discrete circuits*, in general, $R_C \ll r_o$

$$\Rightarrow A_v = -g_m R_C \approx -R_C/r_E \text{ (moderate to large)}$$

- On the other hand, if $r_o \ll R_C$:

$$A_v = -g_m r_o = -1/\eta = -V_A/V_T \text{ (can be huge!)}$$

- *Theoretical maximum voltage gain of this circuit*

➤ ***Current Gain:***

$$A_i = i_c/i_b = \beta \text{ (large)}$$

➤ Thus, ***Power Gain:***

$$PG = A_v \times A_i \text{ (very large)}$$

➤ Therefore, this circuit is ***designers' favorite!***

➤ Has primary use as ***audio amplifiers***

➤ ***Input Resistance:***

$$R_i = v_i/i_i = r_\pi \text{ (decent)}$$

➤ ***Output Resistance:***

$$R_o = R_C || r_o \approx R_C$$