

ESC201T: Introduction to Electronics


Users Online : 28

Discussion quiz 1

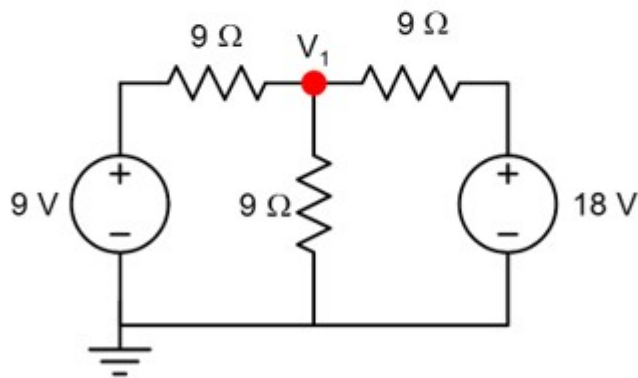Q.1

ESC201T : Introduction to Electronics
Discussion Quiz 1 (16/9/2020)

Q. Use Source transformation to determine voltage V_1 . Express your answer as an integer only without units.



Your answer:

9

Score: Will be uploaded after end date.