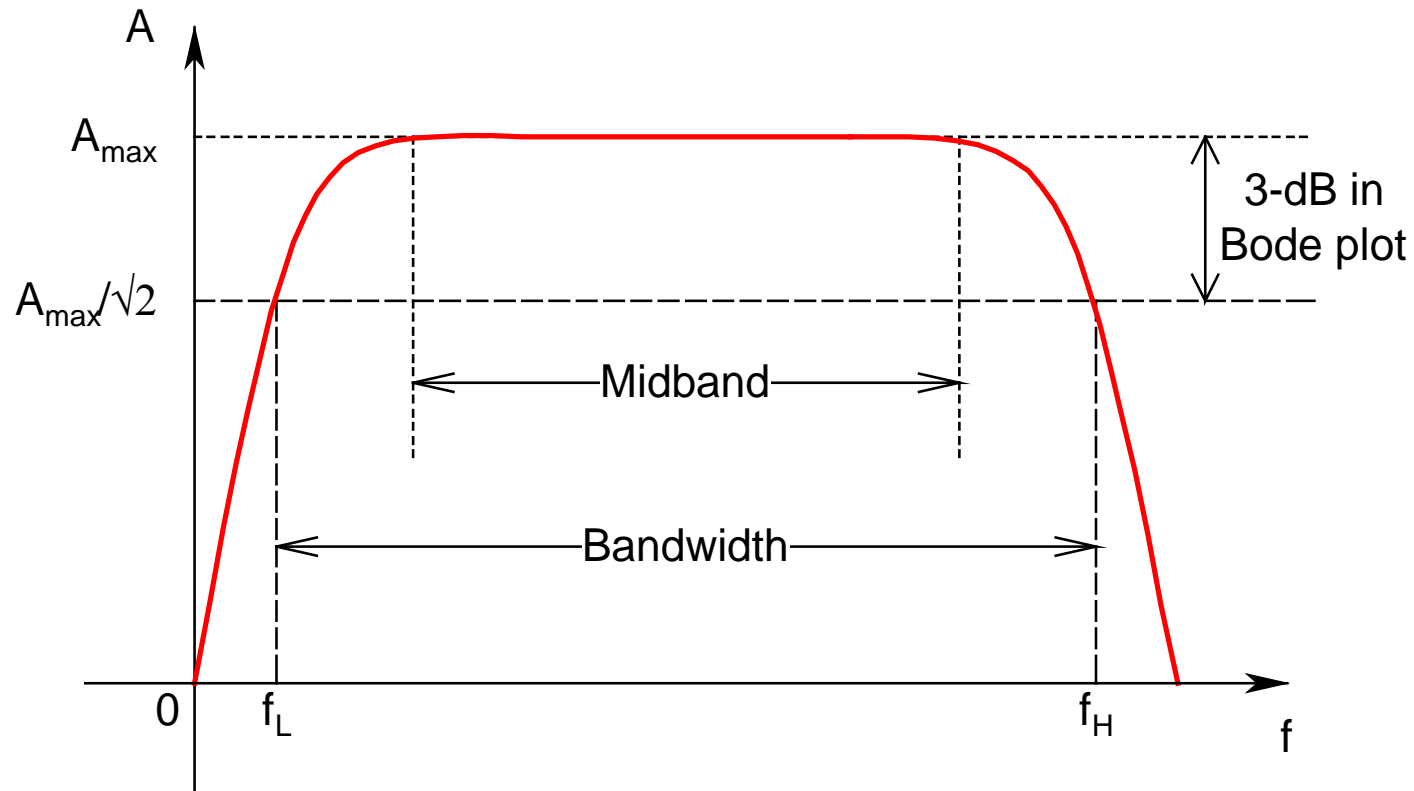


# AMPLIFIERS

# Outline

- *Amplification* of *ac signals* (*voltage*, *current*)
- *Discrete* and *IC*
- *Single-Stage* and *Multi-Stage*
- *Modular approach*
- Interested in:
  - *Voltage/Current Gain* ( $A_v/A_i$ )
  - *Input/Output Resistance* ( $R_i/R_o$ )

# Midband Analysis



$f_L$ : Lower Cutoff Frequency

$f_H$ : Upper Cutoff Frequency

$$\text{Bandwidth} = f_H - f_L$$

# Single-Stage Topologies

- **BJT:**
  - **Common-Emitter** (CE)
    - *i/p to B, o/p from C, E common to both i/p and o/p*
  - **Common-Base** (CB)
    - *i/p to E, o/p from C, B common to both i/p and o/p*
  - **Common-Collector** (CC)
    - *i/p to B, o/p from E, C common to both i/p and o/p*
  - **Common-Emitter (Degeneration)** [CE(D)]
    - *Same as CE, but now with an emitter resistance attached*

- **MOSFET:**

- **Common-Source** (CS)

- *i/p to G, o/p from D, S common to both i/p and o/p*

- **Common-Gate** (CG)

- *i/p to S, o/p from D, G common to both i/p and o/p*

- **Common-Drain** (CD)

- *i/p to G, o/p from S, D common to both i/p and o/p*

- **Common-Source (Degeneration)** [CS(D)]

- *Same as CS, but now with a source resistance attached*

- For *MOSFETs*, an *additional topology* possible: *i/p to Body*, *o/p from S/D*
  - Known as *body-driven* or *bulk-driven* stage
- Each of the *topologies* has *specific characteristics* in terms of *voltage/current gain* and *input/output resistance*
- Each of these will be treated as a *module*, and will do a *complete analysis* for each of these stages

# Multi-Stage Topologies

- Also known as *Compound Connections*
- *Combination of 2 or more stages*
  - *A module by itself*
- *Some widely used topologies:*
  - *Darlington*
  - *Cascode*
  - *Differential Amplifier/Differential Pair*  
(DA/DP)

# Basic Structure

- Consists of a *driver* and a *load*
- *Driver*: Universally *active devices*, e.g., *BJTs* or *MOSFETs*
- *Load*: Can either be *resistors* (*passive*) or *transistors* (*active*)
- Generally, *discrete stages* have *passive loads*, while *IC stages* have *active loads*



# Resistance Transformation (Only for BJTs)

- *A very useful technique*


- For *equivalence*:

$$I_b R_2 = I_e R_1$$

$$\Rightarrow R_2 = (\beta + 1)R_1$$


$$\text{or } R_1 = R_2/(\beta + 1)$$

- *Apply it freely!*

 


# Single-Stage Amplifiers

- **Common-Emitter (CE):**

 

ac Schematic

 

ac Low-Frequency Equivalent

➤ ***Biasing circuit not shown***

- By inspection, *Voltage Gain*:

$$A_v = \frac{v_o}{v_i} = \frac{-g_m v_1 (R_C \parallel r_o)}{v_i} = -g_m (R_C \parallel r_o)$$

- The *negative sign* in front implies *180° phase shift* between  $v_i$  and  $v_o$

- *$v_i$  and  $v_o$  are exactly out of phase*

- For *discrete circuits*, in general,  $R_C \ll r_o$

$$\Rightarrow A_v = -g_m R_C \approx -R_C/r_E \text{ (moderate to large)}$$

- On the other hand, if  $r_o \ll R_C$ :

$$A_v = -g_m r_o = -1/\eta = -V_A/V_T \text{ (can be huge!)}$$

- *Theoretical maximum voltage gain of this circuit*

➤ ***Current Gain:***

$$A_i = i_c/i_b = \beta \text{ (*large*)}$$

➤ Thus, ***Power Gain:***

$$PG = A_v \times A_i \text{ (*very large*)}$$

➤ Therefore, this circuit is *designers' favorite!*

➤ Has primary use as *audio amplifiers*


➤ ***Input Resistance:***

$$R_i = v_i/i_i = r_\pi \text{ (*decent*)}$$


➤ ***Output Resistance:***

$$R_o = R_C || r_o \approx R_C$$

- **Common-Source (CS):**

 

ac Schematic

 

ac Low-Frequency Equivalent

- **Biasing circuit not shown**
- **Body at ground  $\Rightarrow$  No body effect**

- By inspection, ***Voltage Gain***:

$$A_v = \frac{V_o}{V_i} = \frac{-g_m V_1 (R_D \parallel r_o)}{V_i} = -g_m (R_D \parallel r_o)$$

- The ***negative sign*** in front implies ***180° phase shift*** between  $v_i$  and  $v_o$ 
  - ***$v_i$  and  $v_o$  are exactly out of phase***
- For ***discrete circuits***, in general,  $R_D \ll r_o$   
 $\Rightarrow A_v = -g_m R_D$  (***moderate***)
- ***Input Resistance***:  $R_i \rightarrow \infty$
- ***Output Resistance***:  $R_o = R_D \parallel r_o \approx R_D$
- ***Note the remarkable similarity with CE stage***

➤ If  $R_D \gg r_0$ :

$$A_v = -g_m r_0 = -k_N V_{GT}/(\lambda I_D) = -2/[\lambda(\Delta V)]$$

(*assuming  $\lambda V_{DS} < 0.1$* )

➤ Thus, *for small  $\lambda$  and small  $\Delta V$ ,  $A_v$  can be large*

▪ Keep in mind that  $\Delta V(\min) = 3V_T$


➤ Also,  $A_v \propto 1/\sqrt{I_D}$

$\Rightarrow$  *Lower  $I_D$ , higher  $A_v$*


➤ **Recall:** For *CE stage*,  $A_v(\max)$  was *independent of  $I_C$* , and *dependent only on  $T$*

- **Common-Collector (CC):**


➤ Also known as **Emitter-Follower**

 

ac Schematic

 

ac Low-Frequency Equivalent

 

Simplified ac  
Low-Frequency Equivalent

➤ **Biasing circuit not shown**



➤ *Voltage Gain:*

$$\begin{aligned} A_v &= \frac{v_o}{v_i} = \frac{i_o (R_E \parallel r_o)}{v_1 + v_o} = \frac{(\beta + 1) i_i (R_E \parallel r_o)}{i_i r_\pi + (\beta + 1) i_i (R_E \parallel r_o)} \\ &= \frac{R_E \parallel r_o}{r_\pi / (\beta + 1) + R_E \parallel r_o} = \frac{R_E \parallel r_o}{r_E + R_E \parallel r_o} \end{aligned}$$

➤ Now, in general,  $r_o \gg R_E$

$$\Rightarrow A_v = R_E / (r_E + R_E)$$

➤ *Two important observations:*

- $A_v \leq 1$
- *No phase shift between  $v_i$  and  $v_o$*

➤ **Current Gain:**

$$A_i = i_e/i_b = \beta + 1 \text{ (large)}$$

➤ **Input Resistance:**

$$\begin{aligned} R_i &= \frac{v_i}{i_i} = \frac{i_i r_\pi + i_o (R_E \parallel r_o)}{i_i} \\ &= \frac{i_i r_\pi + (\beta + 1) i_i (R_E \parallel r_o)}{i_i} \\ &= r_\pi + (\beta + 1) (R_E \parallel r_o) \end{aligned}$$

- If  $r_o \gg R_E$ ,  $R_i = r_\pi + (\beta + 1) R_E$


- Note that this result could have been written from *inspection* from the *ac schematic* using the technique of *Resistance Transformation*

➤ ***Output Resistance:***

$$\begin{aligned} i_t &= i_0 - g_m v_1 - i_i \\ &= \frac{v_t}{R_E \parallel r_0} + g_m v_t + \frac{v_t}{r_\pi} \end{aligned}$$

$$\Rightarrow R_0 = R_E \parallel r_0 \parallel r_E \parallel r_\pi \approx r_E$$

 - Note that this expression also could have been written by *inspection*




- *Output excited by a test voltage source  $v_t$ :*
  - *The current has two parallel paths: one going through the parallel combination of  $r_o$  and  $R_E$ , and the other into the emitter of  $Q$*
- The *resistance in the base lead of  $Q$  is  $r_\pi$* , which *needs to be transformed to emitter by dividing it by  $(\beta + 1) \Rightarrow$  yields  $r_E$*
- Thus,  $R_o$  becomes a parallel combination of  $r_o$ ,  $R_E$ , and  $r_E$ , which will be *typically equal to  $r_E$* , since, in general, *it's the least among the three*
- *Understand the inspection technique, it will become immensely useful to analyze circuits*


- *Some special properties of CC Stage:*
  - $A_v \leq 1$  (by proper design, it can be made to approach unity very closely)
  - *Input and output in phase*
  - *Quite large input resistance*
  - *Very small output resistance*
- These properties are *highly desirable* to prevent *loading effect* of *cascaded stages* (to be discussed later)
- Thus, this stage is also known as *Buffer* or *Isolator* or *Impedance Matcher*

- **Common-Drain (CD):**

- Also known as *Source Follower*

 

**ac Schematic**

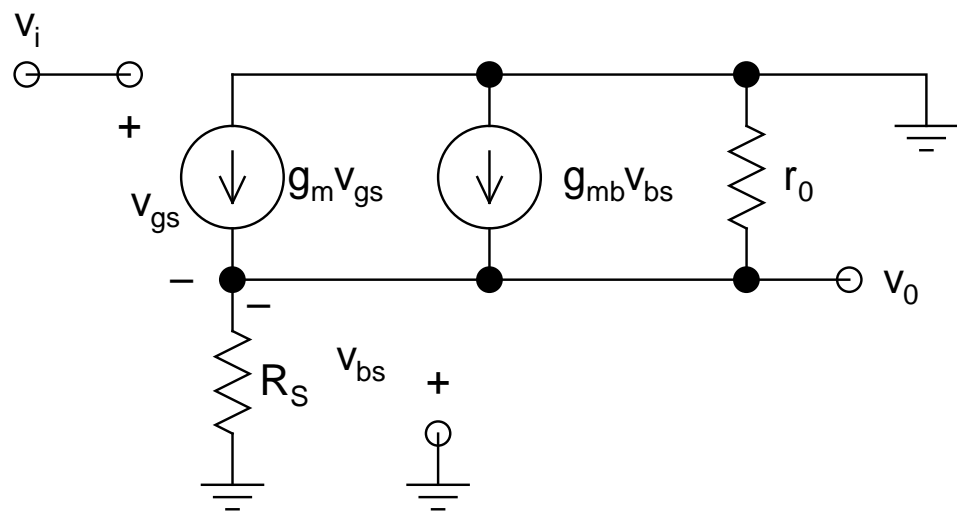

**ac Low-Frequency Equivalent**

- *Biasing circuit not shown*

- **Note:** *Body terminal at ground*, but *source is at a floating potential (it's the output terminal)*
  - ⇒ *Body effect will be very much present for M*
  - ⇒ *Can be avoided by putting M in its separate island*

➤ **Voltage Gain:**

- *KCL at output node:*

$$g_m V_{gs} + g_{mb} V_{bs} = v_o / (R_S \parallel r_o)$$

$$\text{with } v_{gs} = v_i - v_o, \text{ and } v_{bs} = -v_o$$

$$\Rightarrow A_v = \frac{v_o}{v_i} = \frac{g_m (R_S \parallel r_o)}{1 + (g_m + g_{mb})(R_S \parallel r_o)}$$

➤ *Simplification:*

- In general,  $r_0 \gg R_S$ :

$$\Rightarrow A_v \simeq \frac{g_m R_S}{1 + (g_m + g_{mb}) R_S}$$

- If *body effect is neglected*:

$$\Rightarrow A_v \simeq \frac{g_m R_S}{1 + g_m R_S} = \frac{R_S}{1/g_m + R_S}$$

*Note the remarkable similarity with CC stage*

- If  $(g_m + g_{mb}) R_S \gg 1$ :

$$\Rightarrow A_v \simeq \frac{g_m}{g_m + g_{mb}} = \frac{1}{1 + \chi}$$



▪ **Note:**

$$\chi = \frac{\gamma}{2\sqrt{2\phi_F + V_{SB}}}$$

with  $V_{SB} = V_0$  (**DC level of  $v_0$** )

- **Typical values of  $\chi \sim 0.1-0.5$**
- Thus,  **$A_v$  can depart significantly from its ideal value of unity**
- **No phase shift between input and output**

➤ **Input Resistance:**  $R_i \rightarrow \infty$

➤ **Output Resistance:** **By inspection:**

$$R_0 = (g_m + g_{mb} + g_0 + g_S)^{-1} \quad (g_0 = 1/r_0, g_S = 1/R_S)$$

- **Common-Emitter (Degeneration) [CE(D)]:**

➤ Let's attempt to analyze this circuit by *inspection*

➤  $v_0 = -i_c R_C$


$v_i = i_e (r_E + R_E)$

$\Rightarrow A_v = v_0/v_i$   
 $\approx -R_C/(r_E + R_E)$

*Piece of cake?*

➤  $A_i = i_c/i_b = \beta$

 ➤  $R_i = r_\pi + (\beta + 1)R_E = (\beta + 1)(r_E + R_E)$



➤  $R_0 = R_{01} \parallel R_C$

Can you identify  $R_{01}$  by *inspection*?

$$R_{01} = r_0[1 + g_m(r_\pi \parallel R_E)]$$

Generally,  $R_{01} \gg R_C$

$$\Rightarrow R_0 \approx R_C$$

➤ *Probe  $A_v$  further:*

$$A_v = -R_C/(r_E + R_E) \approx -g_m R_C/(1 + g_m R_E)$$

For *CE stage*,  $A_v = -g_m R_C$


For this stage,  $A_v$  is *lower* by a *factor*  $(1 + g_m R_E) \Rightarrow$  *Gain Degeneration*

- $(1 + g_m R_E)$  is known as the ***Degeneration Factor***
- $R_i$  can also be written as:  
$$R_i \approx r_\pi + \beta R_E = r_\pi (1 + g_m R_E)$$


Thus,  $R_i \uparrow$  by the ***Degeneration Factor*** as compared to the ***CE stage***
- ***Interesting to note that the loss in gain is returned by this circuit to its  $R_i$  by the same factor!***

- *Why do we sacrifice gain?*
  - Later on, we will see that this *sacrifice in gain* leads to a *commensurate increase in the bandwidth* of the circuit
- *For a given DC bias point*, the *gain-bandwidth product (GBP) of a circuit remains constant* (will be explored later)
- This is one of the *famous paradoxes* of analog circuits:
  - *To increase gain, sacrifice bandwidth, and vice versa*

 - **Common-Source (Degeneration) [CS(D)]:**



ac Schematic

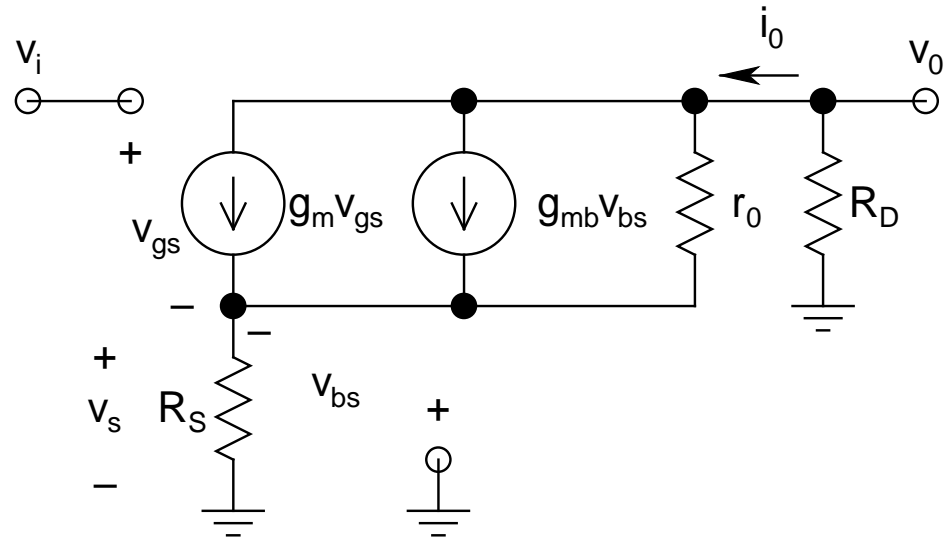

ac Low-Frequency Equivalent

➤ *Defining Relations:*

$$V_0 = -i_0 R_D$$

$$i_0 = g_m V_{gs} + g_{mb} V_{bs} + (V_0 - V_s)/r_0$$

$$V_s = i_0 R_S$$

$$V_{gs} = V_i - V_s$$

$$V_{bs} = -V_s$$

$$\Rightarrow A_v = \frac{V_0}{V_i} = -\frac{g_m R_D}{1 + (g_m + g_{mb}) R_S + (R_S + R_D)/r_0}$$

➤ Pretty *complicated* expression, however, *simplifications* can be made

- Generally,  $(R_S + R_D)/r_0$  can be *neglected*:

$$\Rightarrow A_v = \frac{V_o}{V_i} \simeq -\frac{g_m R_D}{1 + (g_m + g_{mb}) R_S}$$

- *Neglect body effect*:

$$\Rightarrow A_v \simeq -\frac{g_m R_D}{1 + g_m R_S} = -\frac{R_D}{1/g_m + R_S}$$

- Again, *remarkable similarity with CE(D) stage*


- *Golden Observation*:

- *MOS stages, in absence of body effect, is absolutely similar to BJT stages, with  $r_E$  replaced by  $1/g_m$ , and both  $\beta$  and  $r_\pi \rightarrow \infty$*




- Note that here the *Degeneracy Factor* is  $(1 + g_m R_S)$
- $R_i \rightarrow \infty$
- $R_0 = R_{01} \parallel R_D$   
 $R_{01} = r_o [1 + (g_m + g_{mb}) R_S]$  (*Show!*)
- Again *gain is sacrificed* in order to *improve the bandwidth* by the *same amount*
- The complexity of analysis of this circuit is slightly more than the others encountered so far

- **Common-Base (CB):**

 

ac Schematic

 

ac Low-Frequency Equivalent

- Note that the **alternate hybrid- $\pi$  model** appropriate for **CB circuit** has been used
- **$r_o$  appears between input and output**

➤ For now, *neglect  $r_o$*

➤ Noting that  $v_1 = -v_i$ :

$$A_v = \frac{v_o}{v_i} = \frac{-g_m v_1 R_C}{v_i} = +g_m R_C \simeq \frac{R_C}{r_E}$$

➤ Note that the *expression* for  $A_v$  is *identical* to that for the *CE stage*, *without the negative sign in front*

➤ For this circuit, *input and output are in phase*

➤  $A_i = i_c/i_e = \alpha$

➤  $R_i = r_E$

➤  $R_0 = R_{01} \parallel R_C$

$R_{01} \rightarrow \infty$  (*Why?*)


$\Rightarrow R_0 = R_C$

➤ *Ex.: Find  $A_v$  and  $R_i$  with  $r_o$  included*


➤ *With  $r_o$  included*, the circuit shows *two different values* of  $R_{01}$ :

- *When excited by a voltage source*,  $R_{01} = r_o$
- *When excited by a current source*,  $R_{01} = \beta r_o$  (*Show*)  
[*Hint: For this derivation, need to use  $g_m r_E = \alpha$* ]
- *Thus, possibility of huge  $R_0$  under the second case, but  $R_C$  ruins it!*


- **Common-Gate (CG):**

 


**ac Schematic**

 


**ac Low-Frequency Model for M**

 

 **Simplified ac Low-Frequency Model for M**



 **Rerouting the current source between S and D to S to G and then from G to D**



**Final ac Low-Frequency Equivalent for CG Stage**

➤ *G and B both ground:*

$$\Rightarrow V_{gs} = V_{bs} = -V_i$$

$\Rightarrow g_m V_{gs}$  and  $g_{mb} V_{bs}$  can be *combined to a single current source*  $(g_m + g_{mb})V_i$ , *flowing from S to D*

➤ *Reroute this current source from S to G and then from G to D (the circuit remains invariant)*

$\Rightarrow$  Leads to the *final ac low-frequency equivalent* of the CG stage

➤ *Note again that  $r_o$  appears between input and output (similar to CB stage)*

➤ *Neglect  $r_o$  for now*

➤ Noting that  $v_1 = v_i$ :

$$A_v = \frac{v_o}{v_i} = \frac{(g_m + g_{mb}) v_1 R_D}{v_i} = + (g_m + g_{mb}) R_D$$

➤ *Identical result to a CB stage, if **body effect is neglected***

➤  $R_i = (g_m + g_{mb})^{-1}$

➤  $R_o = R_{o1} || R_D$

$R_{o1} \rightarrow \infty$  (**Why?**)

$\Rightarrow R_o = R_D$

- *Ex.: Find  $A_v$  and  $R_i$  with  $r_o$  included*
- *With  $r_o$  included*, the circuit shows *three different values* of  $R_{o1}$ :
  - *When excited by a voltage source*,  $R_{o1} = r_o$
  - *When excited by an ideal current source*,  $R_{o1} \rightarrow \infty$  (*Show*)
  - *If the current source is non-ideal with shunt resistance  $R_S$* :  


$$R_{o1} = r_o[1 + (g_m + g_{mb})R_S] \text{ (*Show*)}$$




# Quick Reckoner for BJT Stages

Topology	$A_v$	$A_i$	PG	$R_i$	$R_o$
CE	Moderate to Large	Large	Large	Moderate	Moderate
CC	$\leq 1$	Large	Moderate	Large	Small
CB	Moderate to Large	$\leq 1$	Moderate	Small	Moderate
CE(D)	Moderate	Large	Moderate	Large	Moderate

 - *The RC-Coupled Amplifier:*
  - *Immensely popular*, particularly for *audio circuits*
  - Can be designed to produce *significant power gain*
  - Several such stages can be *cascaded* to produce *very large gain*
  - Can be used either with *single-supply* or *dual-supply*
  - Used primarily in *discrete designs (PCB)*




**Complete Circuit**

 


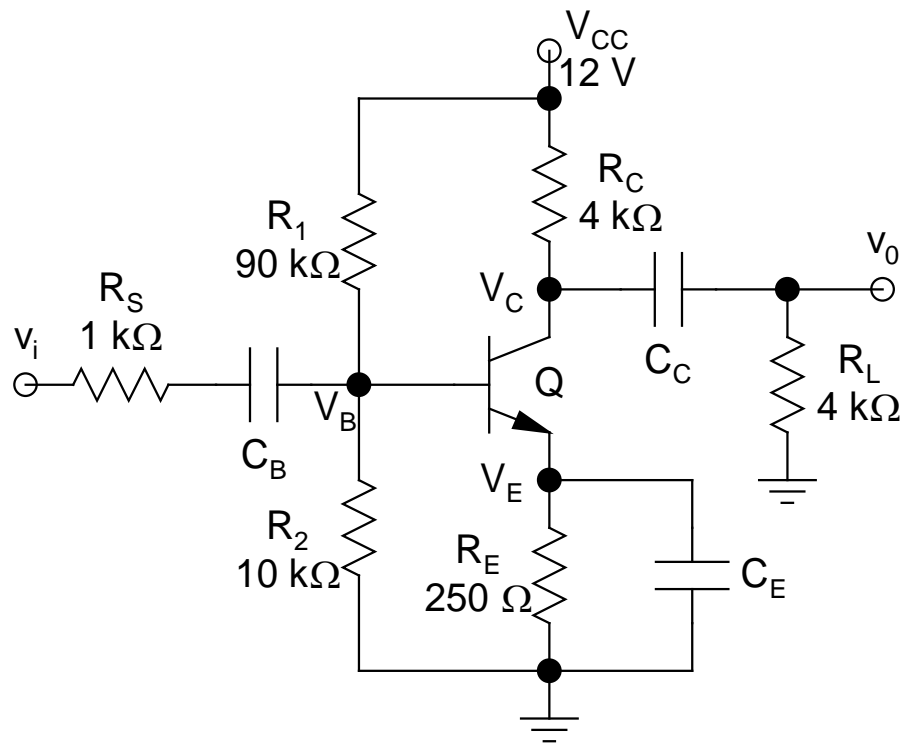**ac Schematic**

$C_B$ : **Base Blocking Capacitor** ,  $C_C$ : **Collector Coupling Capacitor**  
 $C_E$ : **Emitter Bypass Capacitor** ,  $R_S$ : **Source Resistance** ,  $R_L$ : **Load Resistance**



**Complete Circuit**

 

**ac Midband Schematic**

$C_B$ : **Base Blocking Capacitor** ,  $C_C$ : **Collector Coupling Capacitor**  
 $C_E$ : **Emitter Bypass Capacitor** ,  $R_S$ : **Source Resistance** ,  $R_L$ : **Load Resistance**

- $C_B, C_C$ : Used for *DC isolation* of the *bias circuit* from *the source and the load*
  - *DC biasing becomes independent of source and load*
- $C_E$ : *Plays no role in DC* (*opens up*), but *shorts out  $R_E$  in ac* (will see its effects later)
- These 3 capacitors dictate the *lower cutoff frequency* ( $f_L$ ) of the circuit
- Typically have values in the order of  *$\mu F$  to 100s of  $\mu F$*  in order to give  *$f_L$  as close to 0 (DC)* as possible

- First need to do the *DC analysis* to find the *operating point*
- *All capacitors open up for DC analysis*
  - *$R_S$  and  $R_L$  play no role*
- *Neglecting base current:*
$$V_B = V_{CC}R_2/(R_1 + R_2) = 1.2 \text{ V}$$
$$\Rightarrow V_E = V_B - V_{BE} = 0.5 \text{ V}$$
$$\Rightarrow I_E \approx I_C = V_E/R_E = 2 \text{ mA}$$
$$V_C = V_{CC} - I_C R_C = 4 \text{ V}$$
$$V_{CE} = 3.5 \text{ V (quite close to } V_{CC}/3)$$
- *DC bias point analysis done!*

- Now we can move on to the *ac analysis*
- *All capacitors get shorted* due to their *high values*, assuming *frequency of operation* is *beyond  $f_L$*  and *less than  $f_H$* , i.e., *midband range*
- *$C_E$  bypasses  $R_E$* 
  - ⇒ *Emitter of  $Q$  goes to ground*
  - ⇒  *$R_E$  plays no role in ac analysis*
- *Refer to the ac schematic*
  - $R_3 = R_1 || R_2 = 9 \text{ k}\Omega$
  - $R_4 = R_C || R_L = 2 \text{ k}\Omega$
- *Need  $\beta$  for ac analysis (choose 100)*

- $r_E = V_T/I_C = 13 \Omega$ , and  $r_\pi = \beta r_E = 1.3 \text{ k}\Omega$
- $R_{i1} = r_\pi = 1.3 \text{ k}\Omega$
- $R_i = R_{i1} \parallel R_3 = 1.14 \text{ k}\Omega$
- Total resistance *seen* by  $v_i = R_S + R_i = 2.14 \text{ k}\Omega$
- For calculation of *voltage gain*  $A_v$ , apply *chain rule*:

$$A_v = v_o/v_i = (v_o/v_b) \times (v_b/v_i)$$

$$v_o/v_b = -R_4/r_E = -153.85 \text{ (CE stage)}$$


$$v_b/v_i = R_i/(R_i + R_S) = 0.533$$

$$\Rightarrow A_v = -82 \text{ (Very Good Gain!)}$$



- Note that  $v_i$  and  $v_o$  are *exactly out of phase*, which is expected from a *CE stage*
- $R_0 = r_o || R_4 \approx R_4 = 2 \text{ k}\Omega$   
(since for *discrete circuits*,  $r_o$  is generally *neglected*)
- *This completes the analysis of the stage*
- *Summary:*
  - $A_v = -82$
  - $R_i = 1.14 \text{ k}\Omega$
  - Resistance *seen* by  $v_i = 2.14 \text{ k}\Omega$
  - $R_0 = 2 \text{ k}\Omega$

 - Now let's explore what happens if  $C_E$  were *absent*, i.e.,  $R_E$  *unbypassed*
- Redraw the *ac schematic*:




**ac Midband Schematic for  $R_E$  unbypassed**

- **Note:** *Degeneration Factor*  $= (1 + g_m R_E) \approx (1 + R_E/r_E) = 20.23$
- $R_{i1} = r_\pi + (\beta + 1)R_E = 26.55 \text{ k}\Omega$ 
  - *Exactly 20.23 times of the previous case* (1.3 k $\Omega$ )
- $R_i = R_{i1} \parallel R_3 = 6.72 \text{ k}\Omega$
- Total resistance *seen* by  $v_i = R_S + R_i = 7.72 \text{ k}\Omega$
- $v_o/v_b = -R_4/(r_E + R_E) = -7.6$  [*CE(D) Stage*]
  - *Reduced by exactly 20.23 times of the previous case* (– 153.85)
- $v_b/v_i = R_i/(R_i + R_S) = 0.87$ 
  - *Improvement as compared to previous case* (0.533)

- $A_v = -6.6$ 
  - *Compare with  $-82$  obtained in previous case (significant reduction)*
- $R_0 \approx R_4 = 2 \text{ k}\Omega$  (if  $r_0$  is neglected)
- *If  $r_0$  is considered, analysis becomes significantly complicated, since the Golden Rule can't be applied due to the presence of resistance (apart from  $r_\pi$ ) in the base of  $Q$*
- *Summary:*
  - $A_v = -6.6$
  - $R_i = 6.72 \text{ k}\Omega$
  - Resistance *seen* by  $v_i = 7.72 \text{ k}\Omega$
  - $R_0 = 2 \text{ k}\Omega$

 - *What if the output is taken from emitter?*
- Redraw the *ac schematic*:



**ac Midband Schematic for  
Output Taken from Emitter**

- *$R_4$  actually redundant for this case (collector of  $Q$  could have been connected to  $V_{CC}$  directly)*
- $R_{i1} = 26.55 \text{ k}\Omega$ ,  $R_i = 6.72 \text{ k}\Omega$ , and resistance *seen* by  $v_i = 7.72 \text{ k}\Omega$  (*same as before*)
- $v_o/v_b = R_E/(r_E + R_E) = 0.95$  (*CC Stage*)
- $v_b/v_i = R_i/(R_i + R_S) = 0.87$  (*same as before*)
- $A_v = 0.827$  ( $<1$ , as expected, but *could have been made closer to unity by better design!*)
- $R_o = R_E || R_{o1}$
- *Computation of  $R_{o1}$  is slightly more involved, but quite easy if the trick is understood!*

- *First, short  $v_i$  to ground*
  - $\Rightarrow R_3$  comes in parallel with  $R_S$  (call this combination  $R_5$ )
  - $\Rightarrow R_5 = R_3 || R_S = 900 \Omega$
- *$R_5$  comes in series with  $r_\pi$  (call this combination  $R_6$ )*
  - $\Rightarrow R_6 = R_5 + r_\pi = 2.2 \text{ k}\Omega$
- *Transform  $R_6$  to emitter by dividing it by  $(\beta + 1)$* 
  - $\Rightarrow R_{01} = R_6 / (\beta + 1) = 21.8 \Omega$

- Thus,  $R_0 = 20 \, \Omega$  (*Easy?*)
- *Summary:*
  - $A_v = 0.827$
  - $R_i = 6.72 \, \text{k}\Omega$
  - Resistance *seen* by  $v_i = 7.72 \, \text{k}\Omega$
  - $R_0 = 20 \, \Omega$
- Thus, this circuit has *voltage gain close to unity*, *ok input resistance*, and *very small output resistance*
  - *Ideal characteristics* needed for a *Buffer/Isolator/Impedance Matcher*



- **Loading Effect:**

- **Neglecting  $r_o$ :**


$$A_v = -g_m(R_C || R_L)$$

- $R_L$  has no role in DC biasing, but comes into picture in ac calculations

- As  $R_L \downarrow \Rightarrow |A_v| \downarrow$

- Known as **Loading Effect**

 - Similar situation happens when a **high output resistance driver** drives a **low input resistance load** (e.g., **CE stage driving a CB stage**)




- The *gain of the CE stage* will be *severely compromised* due to *low input resistance* of the *CB stage*
  - Known as *Impedance Mismatch* between *Driver and Load*
- Under such a situation, need an *Isolator/Buffer/Impedance Matcher* between the two stages
- A *CC stage perfectly fits the bill* due to its *high input resistance* and *low output resistance*, and *can be used to couple the CE stage to CB stage*
- *MOS circuits generally don't have this problem*

# Compound Connections


- *Multi-Stage*
- Have some *special properties*
- *Popular Topologies:*
  - *Darlington*
  - *Cascode*
  - *DP* (or *DA*)
- *Modules by themselves*

- *Darlington:*

 
- Cascade of a *CC* stage, followed by either a *CE* or a *CC* stage
  - *Two biggest advantages:*
    - *Extremely large  $R_i$*
    - *Extremely large  $A_i$*
  - *These two advantages are automatic for MOS stages*
- ⇒ *MOS Darlington has no special use*




**Generic Circuit**

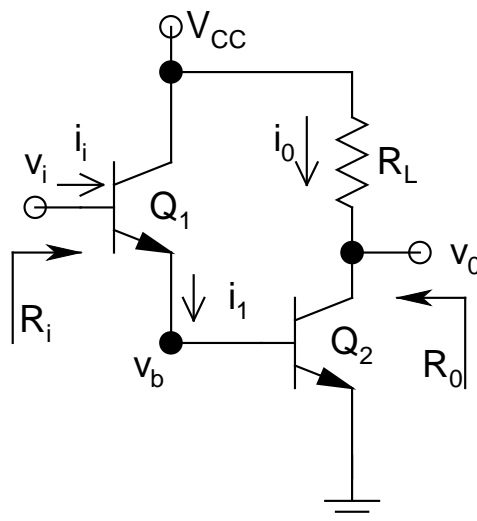

**CC-CE Stage**

 

**CC-CC Stage**

 

**Compact Representation**

➤ For ***DC biasing***:

$$I_{C2} = \beta_2 I_{B2} = \beta_2 I_{E1} \approx \beta_2 I_{C1}$$

$$\Rightarrow r_{\pi 2} = \beta_2 r_{E2} = \beta_2 V_T / I_{C2} = V_T / I_{C1} = r_{E1}$$

➤ For *ac analysis*:

*CC-CE*:

- $i_1 = (\beta_1 + 1)i_i$  and  $i_0 = \beta_2 i_1 = \beta_2(\beta_1 + 1)i_i$   
 $\Rightarrow A_i = i_0/i_i = \beta_2(\beta_1 + 1) \approx \beta^2$  (*Huge!*)
- $R_i = r_{\pi 1} + (\beta_1 + 1)r_{\pi 2} \approx 2r_{\pi 1}$   
❖  $I_{C2} \sim \text{mA}$ ,  $I_{C1} \sim 10\text{s of } \mu\text{A}$ ,  $r_{E1} \sim \text{k}\Omega$ ,  $r_{\pi 1} \sim 100\text{s of } \text{k}\Omega$  (*Huge!*)
- $v_0/v_b = -R_L/r_{E2}$  and  $v_b/v_i = r_{\pi 2}/(r_{\pi 2} + r_{E1}) = 1/2$   
 $\Rightarrow A_v = v_0/v_i = -R_L/(2r_{E2})$  (*Moderate*)
- $R_0 = R_L || r_{02} \approx R_L$  (*Moderate*)

➤ Thus, this stage has *huge  $A_i$  and  $R_i$* , and *moderate  $A_v$  and  $R_0$*

➤ For *ac analysis*:

*CC-CC*:

- $i_1 = (\beta_1 + 1)i_i$  and  $i_0 = (\beta_2 + 1)i_1 = (\beta_2 + 1)(\beta_1 + 1)i_i$   
 $\Rightarrow A_i = i_0/i_i = (\beta_2 + 1)(\beta_1 + 1) \approx \beta^2$  (*Huge!*)
- $R_i = r_{\pi 1} + (\beta_1 + 1)(\beta_2 + 1)(r_{E2} + R_L)$   
 $\approx r_{\pi 1} + \beta^2(r_{E2} + R_L)$  (*Astronomical!*)
- $R_{i1} = r_{\pi 2} + (\beta_2 + 1)R_L$
- $v_0/v_b = R_L/(R_L + r_{E2})$
- $v_b/v_i = R_{i1}/(r_{E1} + R_{i1})$
- $A_v = v_0/v_i \approx \beta_2 R_L/(2r_{E1} + \beta_2 R_L)$  (*Show!*)

➤ Thus, this stage has *extremely large  $A_i$  and  $R_i$* ,  
and  *$A_v$  is  $\leq 1$  with no phase shift*

➤  $R_0 = R_L \parallel R_{01}$

$R_{01} = r_{E2} + r_{E1}/(\beta_2 + 1)$  (*by inspection*)

$\approx 2r_{E2}$

$\Rightarrow R_0 \approx R_L \parallel (2r_{E2})$  (*Small*)

➤ Above analysis is *pretty straightforward*, and *assumes that both  $\beta_1$  and  $\beta_2$  are high*


➤ *In reality,  $Q_1$  operates with a very low value of  $I_C$  ( $\sim 10$ s of  $\mu A$ )*

$\Rightarrow \beta_1$  *would drop significantly from its nominal value*  $\Rightarrow$  *Full advantage of the circuit can't be exploited*




➤ *Need to jack up  $\beta_1$*

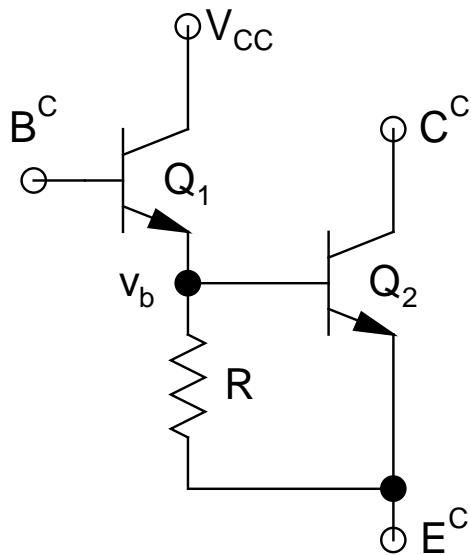
❖ *How about using a keep-alive resistor?*



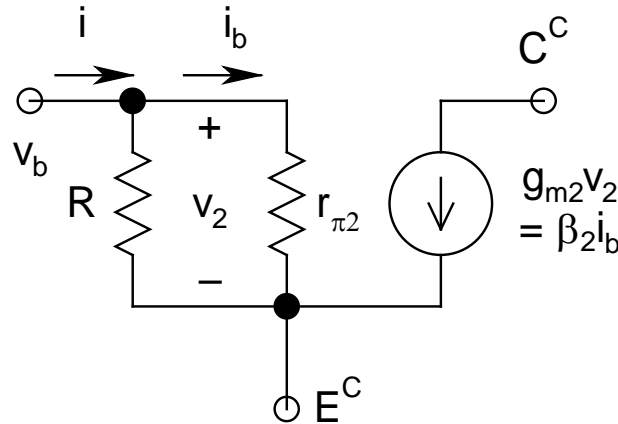**Darlington with  
Keep-Alive Resistor R**



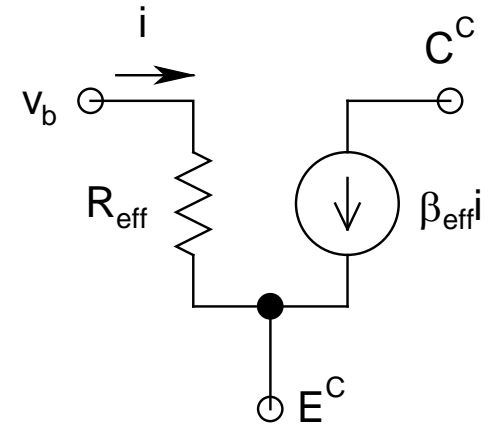**ac Midband Equivalent  
of  $Q_2$ -R Combination**



**Simplified Equivalent  
of  $Q_2$ -R Combination**

- ***R drains a constant DC current of  $\sim 0.7/R$***
- ***This current is supplied by  $Q_1$ , along with  $I_{B2}$***   
 $\Rightarrow I_{C1} \uparrow \Rightarrow \beta_1 \uparrow$
- ***However, this technique also changes  $\beta_2$***
- ***Analysis:***

$$i_b = Ri/(R + r_{\pi 2})$$


$$\begin{aligned} \Rightarrow i_c &= \beta_2 i_b = \beta_2 Ri/(R + r_{\pi 2}) = g_{m2} r_{\pi 2} Ri/(R + r_{\pi 2}) \\ &= g_{m2} (R \parallel r_{\pi 2}) i = g_{m2} R_{\text{eff}} i = \beta_{\text{eff}} i \end{aligned}$$

$$\beta_{\text{eff}} = g_{m2} R_{\text{eff}} < \beta_2 \quad (R_{\text{eff}} = R \parallel r_{\pi 2})$$

- ***Note:**  $r_{E2, \text{eff}} = R_{\text{eff}}/\beta_{\text{eff}} = 1/g_{m2} = r_{E2}$  (**unchanged**)*

- *npn Cascode:*

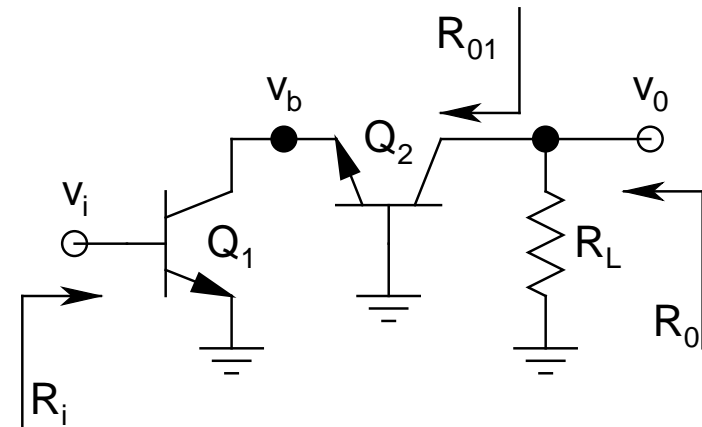- *CE*, followed by *CB*
- Known as *Wideband Amplifier*, due to its *superior frequency response characteristic*



**ac Schematic**


- *Generally, both  $Q_1$  and  $Q_2$  are biased with the same  $I_C$*
- *Assuming  $Q_1$ - $Q_2$  have same  $\beta$ :*

$$r_{E1} = r_{E2} = r_E \text{ and } r_{\pi1} = r_{\pi2} = r_{\pi}$$


- *This circuit can be analyzed by inspection*
- $R_i = r_{\pi 1}$
- $v_o/v_b = +g_{m2}R_L = R_L/r_{E2}$  (**CB Stage**)
- $v_b/v_i = -r_{E2}/r_{E1} = -1$ 
  - *CE Stage with  $R_i$  of  $Q_2 (= r_{E2})$  as its load*
- Thus,  $A_v = v_o/v_i = -R_L/r_{E2}$
- *Note that  $A_v$  is same as that for a CE stage, however, the bandwidth of this circuit is far superior than a CE stage*

- $R_0 = R_L || R_{01}$
- *If  $r_o$  is neglected*, then  $R_{01} \rightarrow \infty$
- *If  $r_o$  is included*, then  $R_{01} = \beta r_{o2}$  (*very high*)
- However, *it comes in parallel with  $R_L$*   
 $\Rightarrow$  *Overall  $R_0$  is still  $\sim R_L$*
- *Summary:*
  - *Moderate voltage gain*
  - *Moderate input resistance*
  - *Potential of having very large output resistance*
  - *Extremely large bandwidth*
  - *Preferred over a simple CE stage*

- NMOS Cascode:***

 

ac Schematic

 

ac Midband Equivalent

- ***CS***, followed by ***CG***
- ***Generally, both  $M_1$  and  $M_2$  are biased with the same  $I_D$***
- ***$M_1$  does not have body effect, but  $M_2$  has***

- *By inspection*,  $R_i \rightarrow \infty$  and  $R_0 = R_L || R_{01}$
- *With  $r_{02}$  present, the analysis becomes a little complicated  $\Rightarrow$  neglect  $r_{02} \Rightarrow R_0 = R_L$*
- *Neglecting  $r_{02}$ :*

$$V_0 = (g_{m2} + g_{mb2})V_2 R_L$$

$$V_2 = -g_{m1}V_1 / (g_{m2} + g_{mb2} + g_{01}) \quad (g_{01} = 1/r_{01})$$

$$\approx -g_{m1}V_1 / (g_{m2} + g_{mb2})$$

[since, in general,  $g_{01} \ll (g_{m2} + g_{mb2})$ ]

$$\Rightarrow A_v = V_0/V_i = -g_{m1}R_L \quad (\text{since } V_1 = V_i)$$
- *This is same as the CS stage, however, here broad-banding is happening!*

- *$A_v$  gets affected a little if  $r_{01}$  and  $r_{02}$  were included*
- *Since  $r_{01}$  comes in parallel with  $(g_{m2} + g_{mb2})^{-1}$ , its effect on  $A_v$  is less pronounced than that of  $r_{02}$*
- *By inspection:*

$$R_{01} \approx (g_{m2} + g_{mb2})r_{01}r_{02} \text{ (Show!)}$$
- *Note that if either of  $r_{01}$  or  $r_{02} \rightarrow \infty$ ,  $R_{01} \rightarrow \infty$  (Why?)*




- ***Differential Amplifier (DA)/Differential Pair (DP):***

- ***Most versatile analog building block***

- ***Immensely useful and widely used*** (particularly for ***sensing/telemetry/instrumentation*** applications)

- ***Two inputs*** ( $V_{i1}$ ,  $V_{i2}$ )/***Two outputs*** ( $V_{o1}$ ,  $V_{o2}$ )

 - ***Dual Supply*** ( $V_{CC}/V_{DD}$ ,  $V_{EE}/V_{SS}$ )




**Symbol for DA**

- ***Unique Property:***
  - *Amplifies the difference between  $V_{i1}$  and  $V_{i2}$ , while rejecting/suppressing signals common to both  $V_{i1}$  and  $V_{i2}$*
  - *Very efficient noise suppressor*
- ***The stage can be direct coupled to the next stage without the need for any coupling capacitor***
- In ***BJT technology***, known as ***Emitter-Coupled Pair (ECP)***
- In ***MOS technology***, known as ***Source-Coupled Pair (SCP)***

- ***npn DA (ECP):***

 - $Q_1$ - $Q_2$  constitute a ***matched pair***, and have their ***emitters connected together***, hence, the name
- $I_{EE}$ : ***DC bias current source***
- ***All voltages and currents*** (*apart from those used for biasing*) are ***instantaneous*** (***DC + ac***)



**npn DA Topology**

➤  $V_{be1} = V_{i1} - V_e$ , and  $V_{be2} = V_{i2} - V_e$

➤ ***KVL around  $Q_1$ - $Q_2$  BE loop:***

$$V_{i1} - V_{be1} + V_{be2} - V_{i2} = 0$$

$$\Rightarrow V_{be1} - V_{be2} = V_{i1} - V_{i2} = V_{id}$$

$V_{id}$ : ***Differential-Mode Input Voltage***

➤ ***Neglecting Early effect:***

$$V_{id} = V_T \ln(I_{c1}/I_{c2})$$

$$\Rightarrow I_{c1}/I_{c2} = \exp(V_{id}/V_T) \quad (1)$$

➤ ***Neglecting base currents:***

$$I_{c1} + I_{c2} = I_{EE} \text{ (*always!*)} \quad (2)$$

***This is because  $I_{EE}$  is an ideal current source***

➤ *Solving Eqs.(1) and (2):*

$$I_{c1} = I_{EE}/[1 + \exp(-V_{id}/V_T)]$$

$$I_{c2} = I_{EE}/[1 + \exp(V_{id}/V_T)]$$

➤ *Extremely interesting results:*

- *For  $V_{id} = 0$ ,  $I_{c1} = I_{c2} = I_{EE}/2$*

*$I_{EE}$  shared equally between  $Q_1$  and  $Q_2$*


- *For positive  $V_{id}$ ,  $I_{c1} \uparrow$  and  $I_{c2} \downarrow$*

*For negative  $V_{id}$ ,  $I_{c1} \downarrow$  and  $I_{c2} \uparrow$*

*But for both cases, their sum is constant and equal to  $I_{EE}$*

- *For  $V_{id} > 4V_T$ ,  $I_{c1} \rightarrow I_{EE}$  and  $I_{c2} \rightarrow 0$*

*For  $-ve V_{id}$ , with  $|V_{id}| > 4V_T$ ,  $I_{c2} \rightarrow I_{EE}$  and  $I_{c1} \rightarrow 0$*

 

### The Current Transfer Characteristics of an npn DA

- **Linear Range** of the circuit  $\sim \pm 4V_T$  ( $\sim \pm 100$  mV at room temperature)
- This range is known as the **analog domain**

- *For  $V_{id}$  out of this range, either  $Q_1$  or  $Q_2$  carries the entire  $I_{EE}$ , with the other remaining off  $\Rightarrow$  acts as a **Current Switch***
  - This is the *digital domain*
- *For analog applications, both devices must be on and in the linear range of the  $I_c$ - $V_{id}$  characteristic*
- *The highest linearity, which is also the region of the highest  $g_m$  ( $= \partial I_c / \partial V_{id}$ ), occurs around  $V_{id} = 0$  ( $V_{i1} = V_{i2}$ )*
- *This is the most preferred DC bias point*

- *At this point,  $I_{C1} = I_{C2} = I_{EE}/2$ , and all small-signal parameters of  $Q_1$  and  $Q_2$  are identical to each other*
- *This particular biasing scheme leads to a **Balanced DA**, having properties:*
  - *$Q_1$ - $Q_2$  completely matched*
  - *$R_C$ s identically equal to each other*
  - *Both inputs connected to DC ground or to the same DC potential (ground is the best choice, obviously)*
  - *Both  $Q_1$  and  $Q_2$  biased at  $I_{EE}/2$*
- *We will consider only **Balanced DAs***



➤ *Unbalanced DAs create anomalies in circuit operation*

➤ Now, the *output voltages*:


$$V_{o1} = V_{CC} - I_{c1}R_C \text{ and } V_{o2} = V_{CC} - I_{c2}R_C$$

➤ Define *Differential-Mode Output Voltage*:

$$V_{od} = V_{o1} - V_{o2} = I_{EE}R_C \tanh[-V_{id}/(2V_T)]$$

- $V_{od}$  (*positive maximum*) =  $I_{EE}R_C$
- $V_{od}$  (*negative minimum*) =  $-I_{EE}R_C$
- At  $V_{id} = 0$ ,  $V_{od} = 0$

 ❖ *Permits direct coupling of stages without the need of any coupling capacitor*



**Linear Range =  $\pm 4V_T$**   
**( $\sim \pm 100$  mV at**  
**room temperature)**

**The Voltage Transfer**  
**Characteristics**  
**of an npn DA**

➤ **DC Biasing:**

- $V_i = V_I + v_i$  ( $V_I$ : **DC bias voltage**,  $v_i$ : **ac small-signal voltage**)
- $I_c = I_C + i_c$  ( $I_C$ : **DC bias current**,  $i_c$ : **ac small-signal current**)
- *The ideal DC bias point should be  $V_{I1} = V_{I2}$*   
 $\Rightarrow I_{C1} = I_{C2} = I_{EE}/2$
- *Thus, any arbitrary DC voltage can be applied at the bases of  $Q_1$ - $Q_2$ , provided they are same*  
 $\Rightarrow$  **Ideal choice: ground**  
 $\Rightarrow$  **Necessitates a negative power supply for proper biasing**

- ***Under this condition:***


$$V_{01} = V_{02} = V_{CC} - I_{EE}R_C/2 \text{ and } V_{0d} = 0$$

- ***The simplest DC biasing scheme is to attach a resistor  $R_{EE}$  from the common emitter point to  $V_{EE}$ :***

$$\Rightarrow I_{EE} = (-0.7 - V_{EE})/R_{EE}$$

$$\text{and } I_{C1} = I_{C2} = I_{EE}/2$$

 - ***Both  $Q_1$  and  $Q_2$  have same  $g_m$ ,  $r_E$ ,  $r_\pi$  and  $r_o$***



**Simplest DC Biasing Scheme for npn DA**

- ***To improve performance, any of the current sources discussed earlier could be used in place of  $R_{EE}$***

- *A check is needed to see that  $Q_1$  and  $Q_2$  are biased in the forward active region*

- For this circuit, for *best biasing*:

$$V_{CE1} = V_{CE2} = (V_{CC} + |V_{EE}|)/3 \text{ (3-element o/p branch)}$$

➤ *ac Analysis:*

- *Balanced DAs have perfect symmetry around the vertical cut-line going through the middle of the circuit*
- *Can be analyzed using heuristics*
  - ❖ Known as the *Half-Circuit Technique*
- *This technique is based on an algorithm*  
*(Understand it thoroughly to get a clear grasp!)*

- ***Algorithm for the Half-Circuit Technique:***
- *Apply inputs  $v_{i1}$  and  $v_{i2}$  at the bases of  $Q_1$  and  $Q_2$  respectively*
  - *Outputs  $v_{o1}$  and  $v_{o2}$  taken from the collectors of  $Q_1$  and  $Q_2$  respectively*
  - Define  $v_{id} = (v_{i1} - v_{i2})$  as the ***pure differential-mode input***
  - Define  $v_{ic} = (v_{i1} + v_{i2})/2$  as the ***pure common-mode input***
  - Thus:  
$$v_{i1} = v_{id}/2 + v_{ic}$$
$$v_{i2} = -v_{id}/2 + v_{ic}$$

- Define  $v_{od} = (v_{o1} - v_{o2})$  as the *pure differential-mode output*
- Define  $v_{oc} = (v_{o1} + v_{o2})/2$  as the *pure common-mode output*
- Thus:  
$$v_{o1} = v_{od}/2 + v_{oc}$$
$$v_{o2} = -v_{od}/2 + v_{oc}$$
- *Now, assuming that pure differential-mode and pure common-mode signals are completely non-interacting:*
  - ❖ *Pure differential-mode output can only be caused by a pure differential-mode input*
  - ❖ *Pure common-mode output can only be caused by a pure common-mode input*

- Based on these, define:
  - ❖ *Differential-Mode Gain*:  $A_{dm} = v_{od}/v_{id}$
  - ❖ *Common-Mode Gain*:  $A_{cm} = v_{oc}/v_{ic}$
- Thus, from the *principle of superposition*:
  - ❖  $v_{o1} = (A_{dm}/2)v_{id} + A_{cm}v_{ic}$
  - ❖  $v_{o2} = -(A_{dm}/2)v_{id} + A_{cm}v_{ic}$
- Thus, *each output carries both differential- and common-mode signals*, however, the *differential-mode signals are out of phase*, whereas the *common-mode ones are in phase*
- *Hence, the difference between the two outputs carries only the differential-mode signal, with a gain double that of a single output*



- *The most important property of a DA is to be able to reject common-mode signals (noise), while amplifying the difference between the two signals applied at its two inputs*
- Characterized by a parameter known as the *Common-Model Rejection Ratio (CMRR)* (*expressed in dB*):
$$\text{CMRR} = 20\log_{10}(|A_{\text{dm}}/A_{\text{cm}}|)$$
- *Ideal (Desirable) Properties:*
  - $|A_{\text{dm}}| \rightarrow \infty (\sim 10^3\text{-}10^5)$
  - $|A_{\text{cm}}| \rightarrow 0 (< 1)$
  - $\text{CMRR} \rightarrow \infty (\sim 40\text{-}120 \text{ dB})$

➤ *The circuit has two inputs and two outputs:*

⇒ *Four possible configurations:*


- *Single-ended i/p, single-ended o/p*
- *Single-ended i/p, double-ended o/p*
- *Double-ended i/p, single-ended o/p*
- *Double-ended i/p, double-ended o/p*

⇒ *Tremendous flexibility*


- *Double-ended o/p eliminates the common-mode signal completely*
- *However, at some point in the circuit, needs to be converted to a single-ended o/p*

⇒ *High CMRR is an absolute must!*

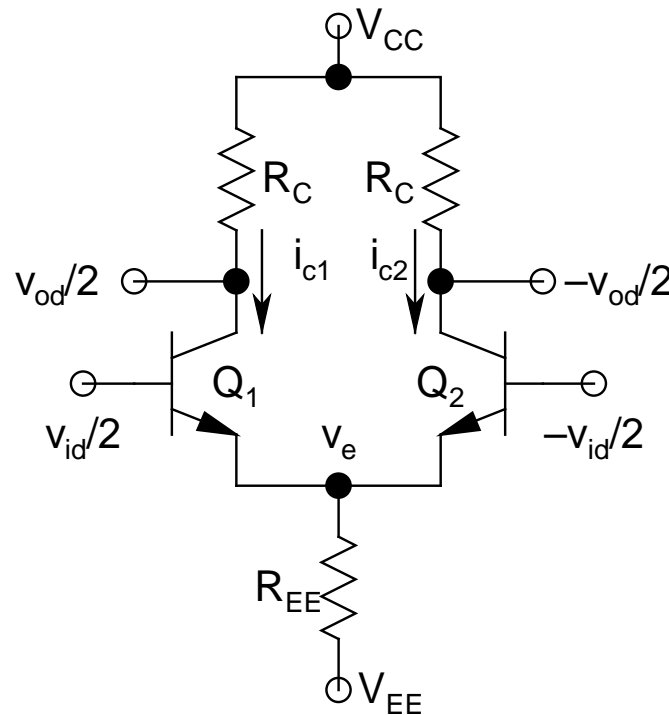➤ **Differential-Mode Half Circuit: Calculation of  $A_{dm}$ :**



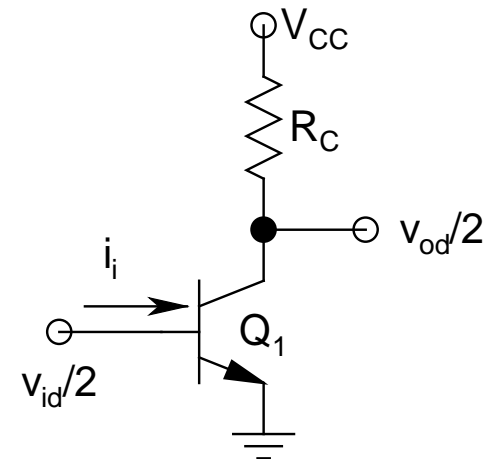**nnp DA Under Pure Differential-Mode Input**



**Differential-Mode Half-Circuit**

- *Can be shown that  $v_e = 0$  in three ways:*
  - ❖ *From the symmetry of the circuit:*  
*Equal and opposite voltages applied at the bases of  $Q_1$  and  $Q_2$*   
 $\Rightarrow$  *The emitter potential  $v_e$  got to be an average of the inputs, which is zero*
  - ❖  $i_{c1} = g_{m1}(v_{id}/2 - v_e)$  and  $i_{c2} = g_{m2}(-v_{id}/2 - v_e)$   
*Since  $g_{m1} = g_{m2}$ ,  $i_{c1}$  must equal  $-i_{c2}$  (circulating current)*  
*(this is again from symmetry)*  
 $\Rightarrow v_e = 0$
  - ❖ *Drawing the complete ac low-frequency hybrid- $\pi$  model, and summing currents at the common-emitter node:*  
*Show that  $v_e = 0$*
- *Caution:  $v_e = 0$  will hold true only for a balanced DA*

- *Thus, the left and right parts of the circuit become absolutely symmetrical*

⇒ *Either of the parts can be used*

⇒ *Leads to the differential-mode half-circuit*

- $g_{m1} = g_{m2} = g_m = I_{EE}/(2V_T)$ ,  $r_{E1} = r_{E2} = r_E = 2V_T/I_{EE}$ ,  
and  $r_{\pi1} = r_{\pi2} = r_{\pi} = \beta r_E$

- *Can be easily identified to be a CE stage*


⇒  $A_{dm} = v_{od}/v_{id} = (v_{od}/2)/(v_{id}/2) = -R_C/r_E$

- *Differential-mode input resistance:*


$$R_{id} = v_{id}/i_i = 2(v_{id}/2)/i_i = 2r_{\pi}$$

- *The simplicity of the analysis is simply mind-boggling!*

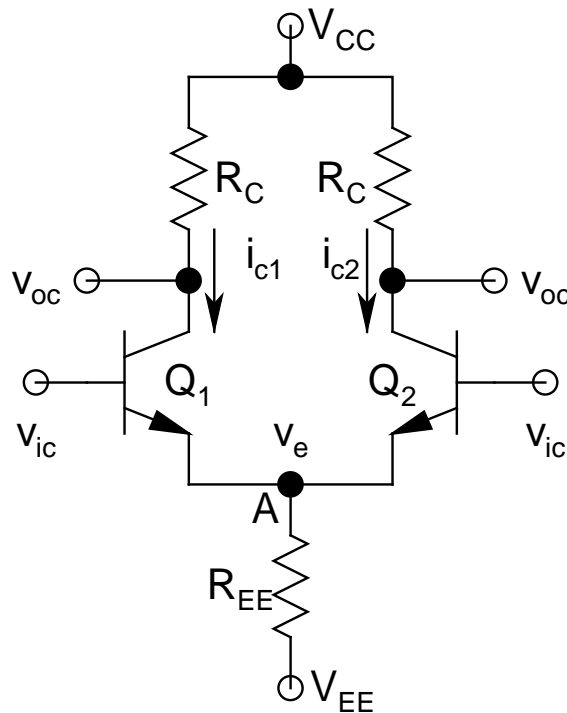➤ **Common-Mode Half-Circuit: Calculation of  $A_{cm}$ :**



 **npn DA Under Pure  
Common-Mode Input**



**Common-Mode  
Half-Circuit**

- $i_{c1} = i_{c2} = i_c = g_m(v_{ic} - v_e)$
- These two currents *sum up at node A* and *flow through  $R_{EE}$ , creating a voltage drop of  $2i_c R_{EE}$  across it*
- Thus,  *$R_{EE}$  can be split into two parts,  $2R_{EE}$  each,* and *each part put in the emitter leads of  $Q_1$  and  $Q_2$*
- *The lead connecting the two parts of  $R_{EE}$  would not carry any current, and can be removed*
- *Thus, the circuit becomes perfectly symmetric along a vertical cut-line going through the middle of the circuit, and we can consider either of them*  
 $\Rightarrow$  *Leads to the common-mode half-circuit*

- *Can be easily identified to be a CE(D) stage*  
 $\Rightarrow A_{cm} = v_{oc}/v_{ic} = -R_C/(r_E + 2R_{EE}) \approx -R_C/(2R_{EE})$   
 (since, in general,  $R_{EE} \gg r_E$ )
- *Common-mode input resistance:*  
 $R_{ic} = v_{ic}/i_i = r_\pi + (\beta + 1)2R_{EE} \approx 2\beta R_{EE}$   
 (since, in general,  $R_{EE} \gg r_\pi$ )
- *Input resistance of the npn DA:*  
 $R_i = R_{id} \parallel R_{ic} \approx R_{id} = 2r_\pi$  (*from superposition*)  
 (since, in general,  $R_{ic} \gg R_{id}$ )
- *CMRR* =  $20\log_{10}(|A_{dm}/A_{cm}|) \approx 20\log_{10}(2R_{EE}/r_E)$



➤ *Some insights:*


- $A_{dm}$  is independent of  $R_{EE}$ , however,  $A_{cm}$  is a strong function of  $R_{EE}$
- Goal is to make  $A_{cm}$  as close to zero as possible  
⇒ Make  $R_{EE}$  as large as possible
- High value of  $R_{EE}$  will automatically ensure high value of CMRR (*Highly desirable!*)
- High CMRR can also be achieved by reducing  $r_E$   
⇒ Can be obtained by increasing the DC bias current  
⇒ DC power dissipation of the circuit goes up  
⇒ Also, DC biasing may become suspect!

➤ *Increasing the Linear Range:*

- *Linear Range:  $\pm 4V_T$  ( $\sim \pm 100 \text{ mV}$  at room temperature)*
- *For some applications, this may not be enough*
- *Linear Range can be increased by attaching two identical resistors ( $R_E$ ) in the emitter branches of  $Q_1$  and  $Q_2$*
- *Increases Linear Range by  $I_{EE}R_E$  (Show!)*
- *This method decreases  $A_{dm}$  (differential-mode half-circuit becomes CE(D) topology)*
- *Has minimal effect on  $A_{cm}$*
- *CMRR suffers!  $\Rightarrow$  Not an optimal choice!*

- **NMOS DA (SCP):**

 - $M_1$ - $M_2$  constitute a *perfectly matched pair*, and have their *sources connected together*, hence, the name
- $I_{SS}$ : **DC bias current source**
- *All voltages and currents are instantaneous*



**NMOS DA Topology**

➤  $V_{gs1} = V_{i1} - V_s$ , and  $V_{gs2} = V_{i2} - V_s$

➤ ***KVL around  $M_1$ - $M_2$  GS loop:***

$$V_{i1} - V_{gs1} + V_{gs2} - V_{i2} = 0$$

$$\Rightarrow V_{gs1} - V_{gs2} = V_{i1} - V_{i2} = V_{id}$$

➤ ***Neglecting CLM Effect:***

$$I_{d1} = \frac{k'_N}{2} \left( \frac{W}{L} \right) (V_{gs1} - V_{TN1})^2 \quad \text{and}$$

$$I_{d2} = \frac{k'_N}{2} \left( \frac{W}{L} \right) (V_{gs2} - V_{TN2})^2$$

- Ran into a problem, since *both  $M_1$  and  $M_2$  would have body effect present*
  - *Both bodies connected to  $V_{SS}$ , but the common source node is at a floating potential  $V_s$*   
 *$\Rightarrow$  Analytical evaluation of  $I_{d1}$  and  $I_{d2}$  becomes pretty tedious*
- *If the CLM effect is also included, then the problem would need numerical solution!*
- To get a *first-order estimate*, *neglect body effect*  
 $\Rightarrow V_{TN1} = V_{TN2} = V_{TN0}$

➤ Thus:

$$V_{id} = \frac{\sqrt{I_{d1}} - \sqrt{I_{d2}}}{\sqrt{\frac{k'_N}{2} \left( \frac{W}{L} \right)}} \quad (1)$$

➤ Also:

$$I_{d1} + I_{d2} = I_{SS} \quad (2)$$

➤ ***Solving Eqs.(1) and (2):***

$$I_{d1} = I_{SS}/2 + \xi \quad \text{and}$$

$$I_{d2} = I_{SS}/2 - \xi$$

$$\xi = \frac{k'_N}{4} \left( \frac{W}{L} \right) V_{id} \sqrt{\frac{4I_{SS}}{k'_N (W/L)} - V_{id}^2}$$

- For  $V_{id} = 0$ ,  $\xi = 0$ , and  $I_{d1} = I_{d2} = I_{SS}/2$ 
  - *Most preferred DC bias point of the circuit*
- For  $V_{id} > 0$ ,  $I_{d1} \uparrow$  and  $I_{d2} \downarrow$
- For  $V_{id} < 0$ ,  $I_{d1} \downarrow$  and  $I_{d2} \uparrow$
- But for both cases, the *sum of  $I_{d1}$  and  $I_{d2}$  remains constant at  $I_{SS}$*
- *Linear Range* of this circuit is *defined by the values of  $V_{id}$* , which *turns either  $M_1$  or  $M_2$  off*

- To find the **Linear Range**, use **Eq.(1)** and put either  $I_{d1}$  or  $I_{d2}$  equal to  $I_{SS}$ :


$$\begin{aligned}\Rightarrow V_{id} &= \pm \sqrt{\frac{2I_{SS}}{k'_N (W/L)}} = \pm \sqrt{2} \left( \sqrt{\frac{2I_{d1}}{k'_N (W/L)}} \right) \Big|_{V_{id}=0} \\ &= \pm \sqrt{2} (\Delta V) \Big|_{V_{id}=0}\end{aligned}$$

since for  $V_{id} = 0$ ,  $I_{SS} = 2I_{d1} = 2I_{d2}$

$\Delta V$  = Gate Overdrive for  $M_1/M_2$  for  $V_{id} = 0$

 - Thus, the Linear Range is a function of  $I_{SS}$  and  $(W/L) \Rightarrow$  Tremendous flexibility!
- Recall: In **npn DA**, this Linear Range was  $\pm 4V_T$ , and depended only on temperature





## The Current Transfer Characteristics of an NMOS DA

➤ *Differential Current:*

$$\partial I_d = I_{d1} - I_{d2} = 2\xi$$

➤ *Differential-Mode Output Voltage:*

$$\begin{aligned} V_{od} &= V_{o1} - V_{o2} = (V_{DD} - I_{d1}R_D) - (V_{DD} - I_{d2}R_D) \\ &= -(\partial I_d)R_D = -2\xi R_D \end{aligned}$$

➤ *Note:*

- When  $V_{id} = 0$ ,  $\xi = 0$ ,  $\partial I_d = 0$ , and  $V_{od} = 0$
- *This is the perfect DC bias point*
- *No need for interstage coupling capacitor*
- $I_{D1} = I_{D2} = I_{SS}/2$
- $V_{Id} = 0 \Rightarrow$  *Tie both gates to ground and use a negative power supply*

➤ *ac Analysis:*

- *The procedure adopted for npn DA can be lifted verbatim*

➤ *Differential-Mode Half-Circuit: Calculation of  $A_{dm}$ :*

- *The common-source node is at ac ground (from symmetry)*


- *Body is also at ac ground*

$$\Rightarrow v_{bs} = 0 \Rightarrow g_{mb} v_{bs} = 0$$

- *Simple CS stage:*

$$\Rightarrow A_{dm} = v_{od}/v_{id} = -g_m R_D$$

$$g_m = k_N \Delta V$$

 

**Differential-Mode Half-Circuit**

➤ **Common-Mode Half-Circuit: Calculation of  $A_{cm}$ :**

- **$CS(D)$  stage**, but now **with body effect present**

$$\begin{aligned}\Rightarrow A_{cm} &= v_{oc}/v_{ic} \\ &= -g_m R_D / [1 + (g_m + g_{mb})2R_{SS}]\end{aligned}$$


➤ Thus:

$$\begin{aligned}CMRR &= 20\log_{10}(|A_{dm}/A_{cm}|) \\ &\approx 20\log_{10}[2(g_m + g_{mb})R_{SS}]\end{aligned}$$

➤ Again,  **$R_{SS}$  plays no role in**

 **$A_{dm}$** , but **determines  $A_{cm}$  and CMRR**

$\Rightarrow$  **A high value of  $R_{SS}$  highly desirable**



**Common-Mode  
Half-Circuit**

- *Actual situation is not so rosy and hunky-dory*
- *The DA can become unbalanced if there is a mismatch between the devices and/or the resistors, and our analysis would fail!*
- Gives rise to *offset voltage* (*for both npn and NMOS DA*) and *offset current* (*only for npn DA*)
- *This mismatch is caused by technology and is totally random*
- *Fortunately, the effect is not that severe, since there are technological innovations to match devices and/or resistors*


# Actively Loaded Amplifier Stages

- *Main Goal: To reduce usage of resistors as much as possible and use transistors instead as active load*
- Interesting to note that *transistors offer much higher resistance than physical resistors*, while *occupying much smaller chip area*

- *npn CE Stage With pnp Active Load:*

- $Q_1$ : *Driver*,  $Q_2$ : *Load*
- Identify  $Q_2$ - $Q_3$  as a *pnp current mirror*
- $Q_2$ - $Q_3$  constitute a *matched pair*
- *Neglecting base currents:*  
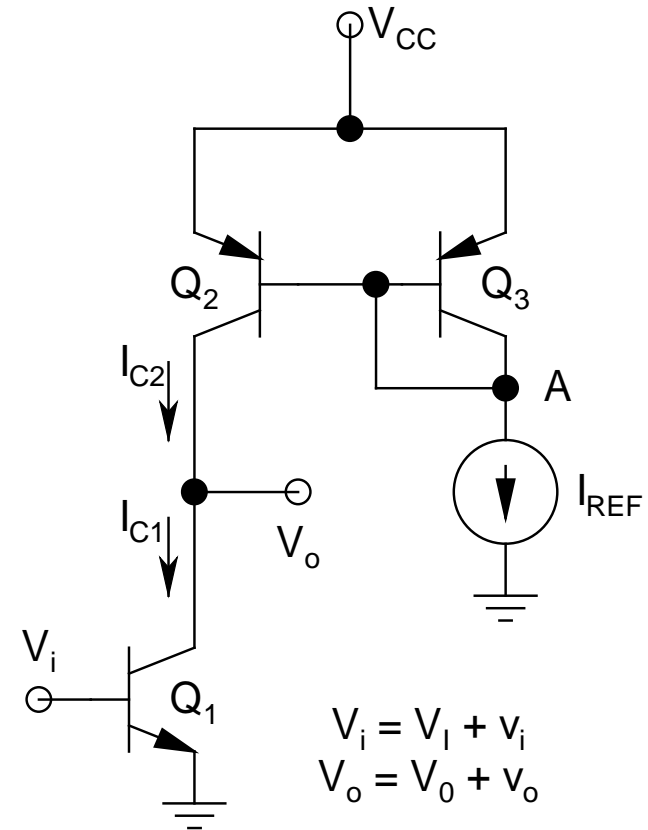
$$I_{C2} = I_{REF}$$
- *Biasing of the circuit is tricky*



**Circuit Diagram**


- There is a *trivial solution* of  $I_{C1} = I_{C2} = 0$ , and the *circuit collapses*
- For *proper biasing*,  $I_{C1}$  must equal  $I_{C2}$  ( $= I_{REF}$ )
- Thus,  $V_I$  should be properly adjusted, such that:

$$V_I = V_T \ln(I_{REF}/I_{S1})$$


- *Such a high precision in  $V_I$  may not be practically achievable*
- ⇒ *Use a resistor in series with  $V_I$  and self-consistently solve for the bias point*



➤ *ac Analysis:*

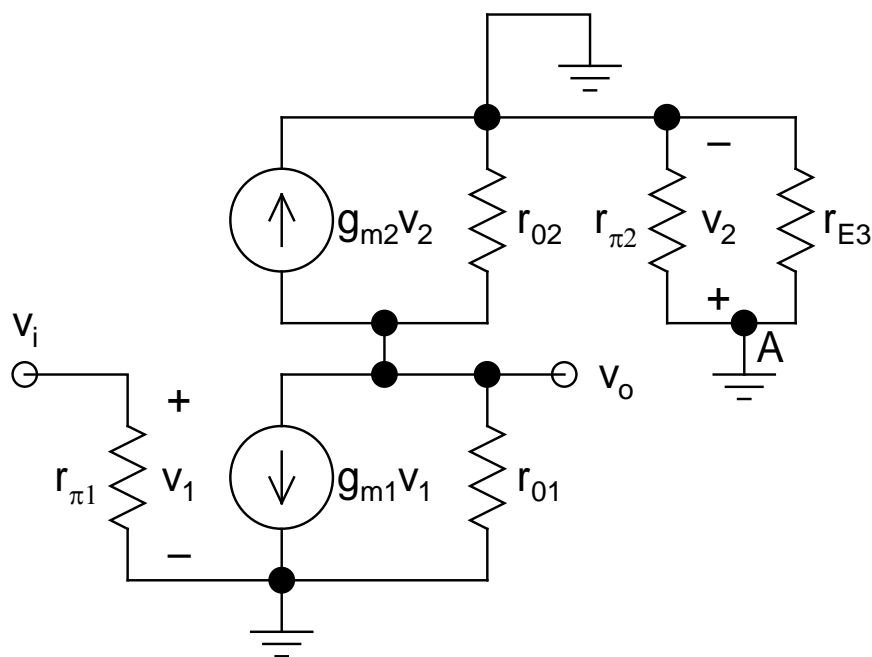

ac Midband Equivalent

 


Simplified Equivalent

- First, note that  $Q_3$  is *diode-connected* (*BC short*)  
 $\Rightarrow$  The *equivalent* of  $Q_3$  is simply a *resistor*  $r_{E3}$
- *Node A* is a peculiar one, and can be considered *open or short both*!
  - ❖ *Open because the current source  $I_{REF}$  is ideal*
  - ❖ *Short because the base of  $Q_2$ - $Q_3$  is at a fixed DC potential, and thus ac ground*
- In either case,  $v_2 = 0 \Rightarrow g_{m2}v_2$  *disappears*!  
 $\Rightarrow$  Leads to the *simplified equivalent*
- *By inspection*:  $R_i = r_{\pi1}$  and  $R_o = r_{o1} || r_{o2}$
- $A_v = v_o/v_i = -g_{m1}R_o = -1/(\eta_n + \eta_p)$   
 $\eta_n = V_T/V_{AN}$  and  $\eta_p = V_T/V_{AP}$
- *Enormously large gain possible!*
 
# p-channel MOSFET (PMOS)

- Before moving to *NMOS stages with active load*, it will be prudent to visit some details regarding *PMOS*
- *Substrate: n-type* ( $N_D$ )
  - *Bulk Potential:*
$$\phi_F = V_T \ln(N_D/n_i)$$
- *Source/Drain: p<sup>+</sup>*
- *Channel Carriers: Holes*



- **Threshold Voltage:**

$$V_{TP} = V_{TP0} - \gamma \left( \sqrt{2\phi_F + V_{BS}} - \sqrt{2\phi_F} \right)$$

$V_{TP0}$ : **Zero back-bias threshold voltage** (*negative*)

➤ **Body effect coefficient:**

$$\gamma = \frac{\sqrt{2q\epsilon_s N_D}}{C'_{ox}}$$

▪  $V_{BS} \geq 0$  (*to prevent forward biasing of SB junction*)

➤ **With back bias**,  $V_{TP}$  **becomes more negative**

➤  $V_{GS}$  **has to be less than  $V_{TP}$  to turn device on**

- **Current-Voltage Relation:**

- **Both  $V_{GS}$  and  $V_{DS}$  negative**
- **$I_D$  flows from source to drain** (the **same direction of flow as holes**)
- **In saturation** [ $|V_{DS}| > (|V_{GS}| - |V_{TP}|)$ ]:

$$I_D = \frac{k'_P}{2} \frac{W}{L} \left( |V_{GSp}| - |V_{TP}| \right)^2 \left( 1 + \lambda_p |V_{DSp}| \right)$$

- **In non-saturation** [ $|V_{DS}| < (|V_{GS}| - |V_{TP}|)$ ]:

$$I_D = k'_P \frac{W}{L} \left[ \left( |V_{GSp}| - |V_{TP}| \right) |V_{DSp}| - \frac{|V_{DSp}|^2}{2} \right]$$

$$k'_p = \mu_p C'_{ox}$$

= *Process transconductance parameter*

$\mu_p$  = *Channel hole mobility*

- *Based on the value of  $V_{TN0}$  and  $V_{TP0}$ , there are two classifications:*


- *Enhancement Mode: Normally Off (with  $V_{GS} = 0$ )*

- $V_{TN0}$  *positive* and  $V_{TP0}$  *negative*


- *Depletion Mode: Normally On (with  $V_{GS} = 0$ )*

- $V_{TN0}$  *negative* and  $V_{TP0}$  *positive*


# Symbols

 


Enhancement  
Mode NMOS

 

Enhancement  
Mode PMOS

 

Depletion  
Mode NMOS

 

Depletion  
Mode PMOS

- Note the *thick band* in the *channel region* for *depletion mode devices*, which implies that *channel is present* even *with  $V_{GS} = 0$*

- *Variants of Actively Loaded CS Stage:*
  - *Saturated Enhancement Load*
  - *Depletion Load*
  - *Complementary PMOS Load*
    - Also known as *CMOS Gain Stage*
- *The last one is the most popular*



- **Saturated Enhancement Load:**

- **Both bodies tied to ground**

- **For  $M_1$ :  $V_{SB1} = 0$**

- **For  $M_2$ :  $V_{SB2} = V_o$**

- **$M_2$  is enhancement mode**


- **$V_{TN02}$  positive**

- **$M_2$  is also diode-connected**

- **Always operates in saturation**

- **$M_2$  has a floating body effect**

 **problem:**  $V_o$  is a variable and  $V_{TN2}$  will continuously change with a change in  $V_o$




**Circuit Schematic**

- *For  $M_2$  to remain on, its  $V_{GS2}$  ( $= V_{DD} - V_o$ ) must be  $> V_{TN2}$*
- Thus, there is a *maximum possible  $V_o$* , beyond which *it cannot rise ( $M_2$  would cut off)*
- To estimate this *maximum  $V_o$* , for the time being, *neglect that  $3V_T$  cushion*
- Then:


$$V_{DD} - V_{o,max} > V_{TN2} \text{ (with } V_{SB2} = V_{o,max} \text{)}$$

$$V_{TN2} = V_{TN02} + \gamma \left( \sqrt{2\phi_F + V_{o,max}} - \sqrt{2\phi_F} \right)$$

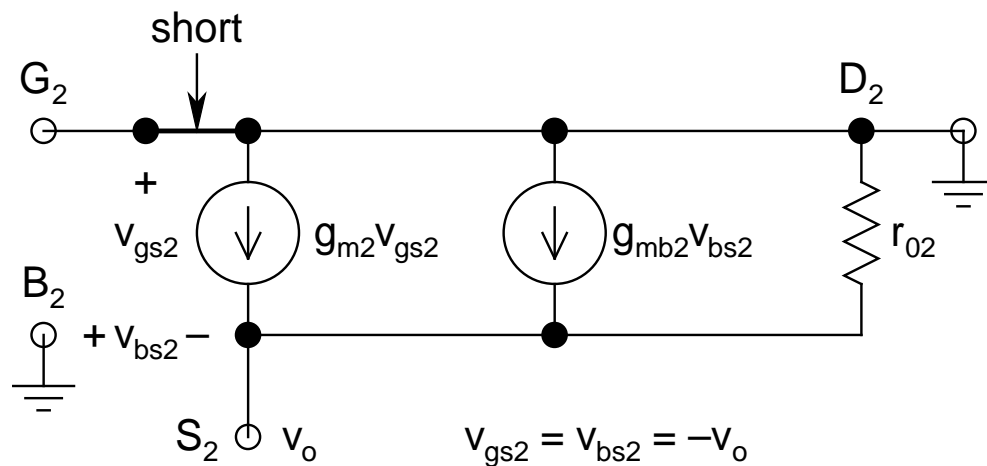- *Solution of this equation would give  $V_{o,max}$*
- *Once  $V_{o,max}$  is obtained, the best bias point would be at  $V_o = V_{o,max}/2$*
- Before doing *ac analysis*, *let's investigate  $M_2$* :



**ac Midband Equivalent of  $M_2$**

 


**Simplified Equivalent**

➤ Thus, the *complete equivalent*:

➤ *By inspection*:

$$A_v = \frac{V_o}{V_i} = -g_{m1} (r_{o1} \parallel R_{eff})$$
 
$$= - \frac{g_{m1}}{g_{m2} + g_{mb2} + g_{o1} + g_{o2}}$$



**Complete Equivalent**

➤ Now, in general,

$$(g_{m2} + g_{mb2}) \gg (g_{o1} + g_{o2})$$

$$\Rightarrow A_v \approx - \frac{g_{m1}}{g_{m2} + g_{mb2}} = - \frac{g_{m1}}{g_{m2} (1 + \chi_2)}$$

$$\chi_2 = \frac{\gamma}{2\sqrt{2\phi_F + V_{0Q}}}$$

$V_{0Q} =$  *Quiescent DC output voltage*

- Now, if  $M_2$  can be put in its *separate island*, then  $S_2$  and  $B_2$  can be *connected together*

$$\Rightarrow v_{sb2} = 0 \Rightarrow g_{mb2}v_{sb2} = 0$$

$$\Rightarrow A_v \approx -\frac{g_{m1}}{g_{m2}} = -\sqrt{\frac{(W/L)_1}{(W/L)_2}}$$


- $R_0 = (g_{m2} + g_{mb2} + g_{01} + g_{02})^{-1}$

➤ *Insights:*

- *$V_o$  doesn't go all the way to  $V_{DD}$*   
⇒ *Full rail-to-rail swing can't be achieved*
- *When  $V_o$  falls below  $\Delta V$  of  $M_1$ , it leaves the saturation region, and enters non-saturation region*  
⇒ *Distortion will set in at the output*
- *Even for a moderate voltage gain of 10, the ratio of the aspect ratios of  $M_1$  and  $M_2$  has to be 100!*
- *All these problems coupled together make this circuit highly unattractive for practical use*

- **Depletion Load:**

 - $M_2$  is *depletion mode*, having *negative*  $V_{TN0}$  (*denoted by*  $V_{TD0}$ )
- *Back bias of*  $M_2$ :  
 $V_{SB2} = V_o$
- *With*  $V_o$ ,  $V_{TD2}$  *changes*
- *Maximum*  $V_o$  *desired*  $= V_{DD}$
- *This is also the maximum back bias of*  $M_2$




 **Circuit Schematic**



- *$M_2$  has GS short  $\Rightarrow V_{GS2} = 0$*
- *Even with  $V_o = V_{SB2}(max) = V_{DD}$ ,  $V_{TD2}$  should remain negative with a cushion of at least 100 mV*
  - $\Rightarrow V_{TD2}$  with  $V_{SB2} = V_{DD}$  should be  $-100\text{ mV}$
  - $\Rightarrow V_{TD0}$  should be chosen based on this
- Now,  $V_{DS2}(min) = V_{DD} - V_o(max) = 0$
- Under this condition,  $V_{GS2} - V_{TD2} = \Delta V_2 = 100\text{ mV}$ 
  - $\Rightarrow M_2$  is in the linear region (*since  $V_{DS2} < \Delta V_2$* )



- *This has to be lived with*, and *slight distortion would appear at the output as  $V_o \rightarrow V_{DD}$*
- For *best biasing*,  $V_{oQ} = V_{DD}/2$   
 $\Rightarrow$  *Fixes the DC operating point*
- Before doing *ac analysis*, *let's investigate  $M_2$* :



ac Midband Equivalent of  $M_2$

  


Simplified Equivalent

➤ Thus, the **complete equivalent**:

➤ **By inspection**:

$$A_v = \frac{V_o}{V_i} = -g_{m1} (r_{o1} \parallel R_{\text{eff}})$$
 
$$= -\frac{g_{m1}}{g_{mb2} + g_{o1} + g_{o2}}$$



➤ Now, in general,

$$g_{mb2} \gg (g_{o1} + g_{o2})$$

$$\Rightarrow A_v \approx -\frac{g_{m1}}{g_{mb2}} = -\frac{g_{m1}}{\chi_2 g_{m2}} = -\frac{1}{\chi_2} \sqrt{\frac{(W/L)_1}{(W/L)_2}}$$

**Complete Equivalent**

$$\chi_2 = \frac{\gamma}{2\sqrt{2\phi_F + V_{DD}/2}} < 1$$

$\Rightarrow$  **Improvement** as compared to previous stage

➤ Now, if  $M_2$  can be put in its *separate island*, then  *$S_2$  and  $B_2$  can be connected together*


$$\Rightarrow v_{sb2} = 0 \Rightarrow g_{mb2}v_{sb2} = 0$$

$$\Rightarrow A_v = -\frac{g_{m1}}{g_{01} + g_{02}}$$


- Can be *very large* (*a magnitude greater than 100 is possible*)

- $R_0 = (g_{mb2} + g_{01} + g_{02})^{-1}$  (*with body effect*)
- $R_0 = (g_{01} + g_{02})^{-1}$  (*without body effect*)
- The latter case produces *very high*  $R_0$
- Thus, this circuit produces *much superior performance* as compared to the *saturated enhancement load*, in terms of:
  - *Rail-to-rail swing*
  - *With island technology:*
    - ❖ *Very large  $A_v$  and  $R_0$*
  - *Without island technology:*
    - ❖ *Moderate  $A_v$  and  $R_0$*

- ***Complementary PMOS Load:***
  - Also known as ***CMOS Gain Stage***
    - ***CMOS*** (***Complementary MOS***: ***Having both NMOS and PMOS*** in the circuit)
  - ***The Ultimate: Much superior performance*** and ***outclasses all other gain stages***
  - ***Widely used***
  - ***High  $A_v$  and  $R_0$***
  - ***Easy to bias and easy to operate***
  - ***Design also extremely simple***
  - ***Doesn't produce any anomalies***

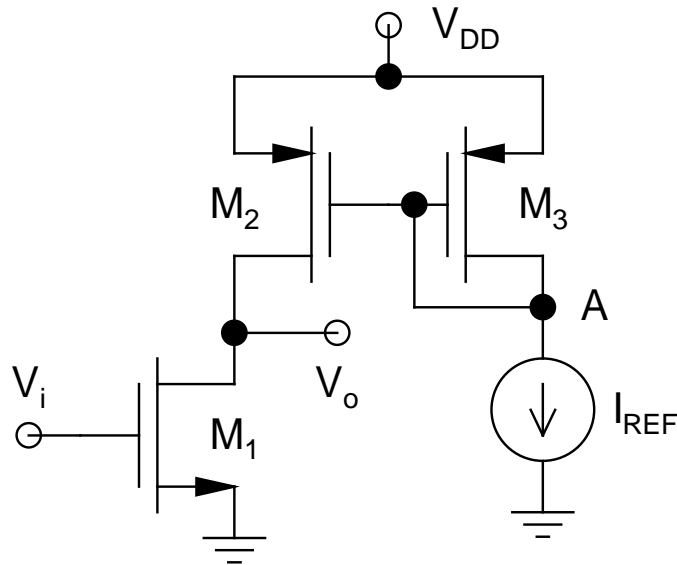

**Circuit Schematic**

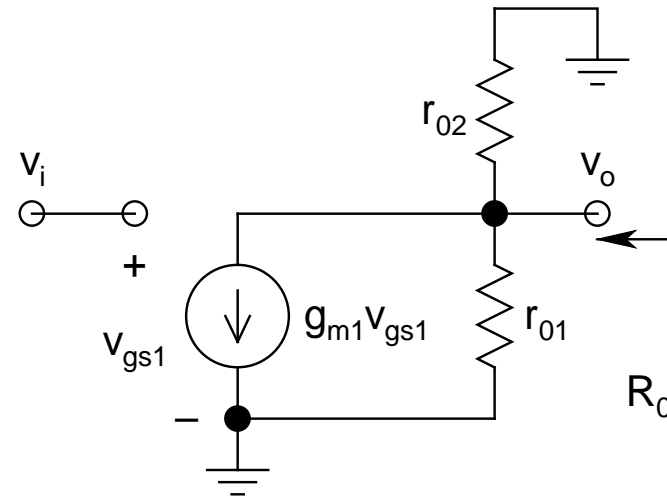

**ac Midband Equivalent**

- *$M_1$  body connected to ground,  $M_2$ - $M_3$  bodies connected to  $V_{DD}$* 
  - *No body effect problem for any of the devices (biggest advantage of this circuit)*

- Identify  $M_2$ - $M_3$  as a *PMOS current mirror* (*perfectly matched*)
  - $\Rightarrow I_{D1} = I_{D2} = I_{D3} = I_{REF}$
- This gives the *required value* of  $V_I$ 
  - $\Rightarrow$  *DC biasing* of the circuit is *pretty straightforward*
- For *ac analysis*, we note that *node A* is *both open and short* at the same time (similar to *npn gain stage* with *pnp active load*)
  - $\Rightarrow A_v = v_o/v_i = -g_{m1}R_0$
  - $R_0 (= r_{o1} \parallel r_{o2})$ : *Output resistance* of the circuit

- **Caution:**  $r_{o1} \neq r_{o2}$ , even though  $M_1$  and  $M_2$  carry the same *DC bias current*, since  $\lambda_n \neq \lambda_p$  (in general)
- This circuit is *immensely useful* since it gives *extremely large voltage gain and output resistance*
- Only *problem* is that it needs a *PMOS current mirror*, thus necessitating use of an *extra PMOS*
- An *even better design* exists, which *eliminates* the need for this *extra PMOS*




- ***A Better CMOS Gain Stage:***

- *No body effect issue*
- However, there are *some design issues*
- $M_n$ - $M_p$  have *same magnitude* of the *threshold voltage*:

$$V_{TN0} = |V_{TP0}|$$

- *Process transconductance parameters:*
 
$$k'_N = \mu_n C'_{ox} \quad \text{and} \quad k'_P = \mu_p C'_{ox}$$




**Circuit Schematic**


- *Oxide capacitance per unit area* ( $C'_{ox} = \epsilon_{ox} / t_{ox}$ )  
*same for both devices*, since they have *same*  
 $t_{ox}$
- However,  $\mu_n \sim 2\mu_p$  (*for Si*)
- Thus,  $k'_N = 2k'_P$
- *Ideal DC bias point* of the circuit is  $V_I = V_O = V_{DD}/2$  (yields  $V_{GSn} = |V_{GSp}|$  and  $V_{DSn} = |V_{DSp}|$ )
- Can be achieved only if the stage is *completely balanced* (*same threshold voltage magnitude* and *same device transconductance parameter*)
- Thus,  $k_N$  and  $k_P$  *need to be matched*

- *Can be achieved by making  $(W/L)_p = 2(W/L)_n$*
- If *CLM effect* is *not that important*, or if  $\lambda_n = \lambda_p$ , then this procedure works out *just fine*
- However, if  $\lambda_n \neq \lambda_p$ , then for *balancing the circuit*, the following relation *must hold* (*show!*):
 
$$k_p(1 + \lambda_p V_{DD}/2) = k_n(1 + \lambda_n V_{DD}/2)$$
- Under this condition,  $k_n \neq k_p$ , but the circuit will be *perfectly matched and balanced*
- Known as: *Stage unmatched by nature, but matched by performance*

➤ *ac Analysis:*

 

ac Midband Equivalent

 

Simplified Equivalent

➤ *By inspection:*

$$A_v = - (g_{mn} + g_{mp})R_0$$
$$= - (g_{mn} + g_{mp})/(g_{0n} + g_{0p})$$


$$R_0 = r_{0n} || r_{0p} = (g_{0n} + g_{0p})^{-1}$$

➤ *Very high  $A_v$  and  $R_0$*


➤ *Extremely popular* and *widely used circuit*

➤ Sometimes, *level shifters* are used at the *input* for *better ease* of application

- *Actively Loaded DA:*

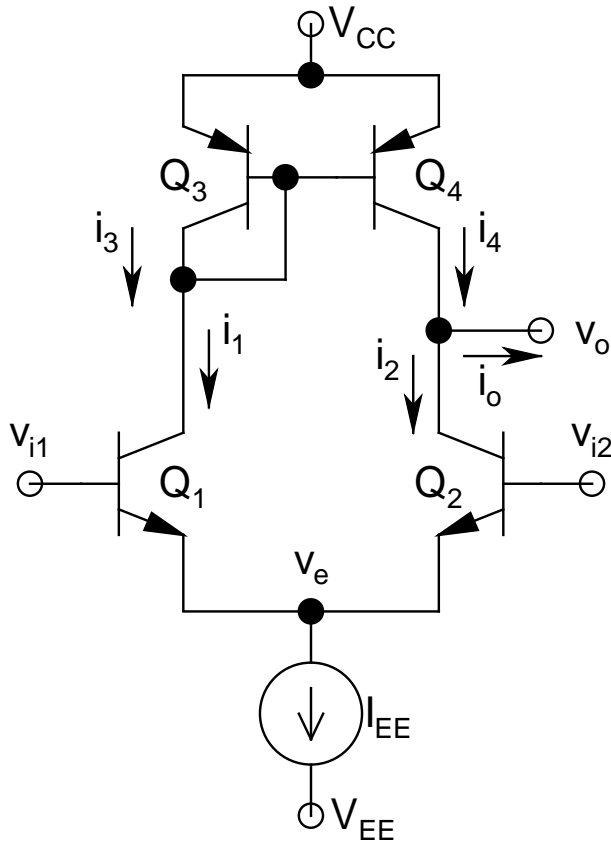

**BJT Implementation**

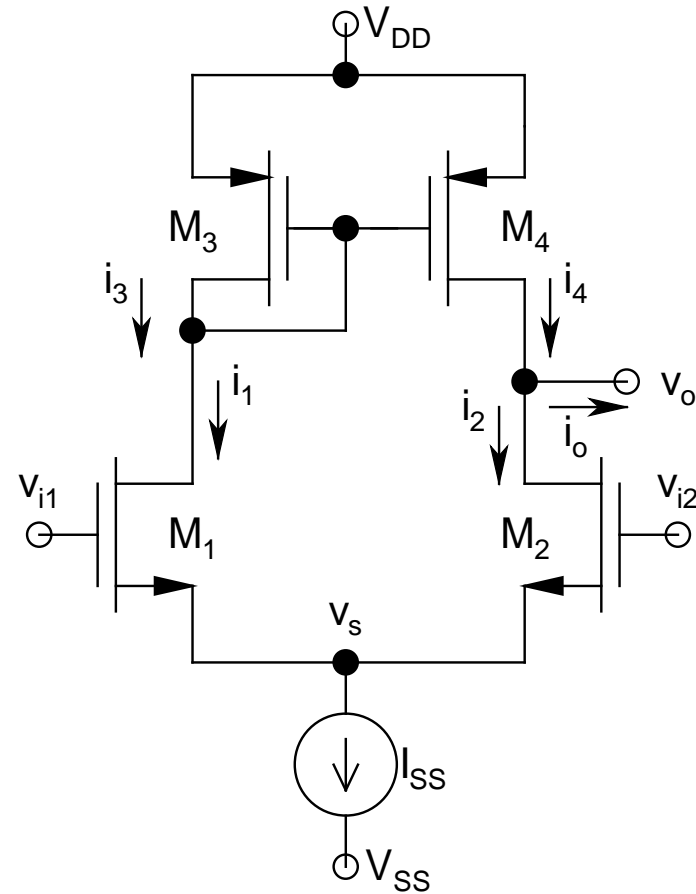

**MOS Implementation**

- Absolutely *similar topologies* for *both BJT and MOS implementations*
- *Produces double-ended to single-ended conversion*, i.e., *from two inputs to a single output*
- *$Q_1$ - $Q_2$ / $M_1$ - $M_2$ / $Q_3$ - $Q_4$ / $M_3$ - $M_4$  perfectly matched*
- *Output should never be taken from collector/drain of  $Q_1$ / $M_1$  (Why?)*
- *DC biasing* is *absolutely straightforward* with *all branch currents equal to  $I_{EE}/2$  or  $I_{SS}/2$*

- **Caution:** *Half-circuit technique can't be used for this circuit*, since *collector/drain circuits of the two sides are coupled*, i.e.,  $i_3 = i_4$  (*always*)
- This circuit can be *analyzed by inspection*
- **Define**  $v_{id} = v_{i1} - v_{i2}$
- *Apply*  $+v_{id}/2$  *at the base of*  $Q_1$  */gate of*  $M_1$
- *Apply*  $-v_{id}/2$  *at the base of*  $Q_2$  */gate of*  $M_2$
- From **symmetry** of the circuit *around the BE/GS loops*, the *common emitter/source node* is at **ac ground** (i.e.,  $v_e = v_s = 0$ )



- Since  $v_s = 0$ ,  $M_1$ - $M_2$  won't have any body effect issue
- Now,  $i_3 = i_4$  (*mirror*),  $i_3 = i_1$  (*same branch*), and  $i_2 = -i_1$  (*symmetry*)
- Also,  $i_1 = g_m v_{id}/2$  and  $i_2 = -g_m v_{id}/2$ 

$$g_m = I_{EE}/(2V_T) \text{ (BJT Implementation)}$$

$$= (k_N I_{SS})^{1/2} \text{ (MOS Implementation)}$$
- Hence, the *short-circuit output current* (with the *output terminal shorted to ground*):
 
$$i_o = i_4 - i_2 = i_1 - i_2 = 2i_1 = g_m v_{id}$$

- To find the **output voltage**, we need to use the **Thevenin technique**:
  - **Open-Circuit Voltage** = **Short-Circuit Current** × **Thevenin Resistance**
- **Thevenin Resistance** (**looking from the output**):
 
$$R_o = r_{o2} // r_{o4}$$
- Thus, the **output voltage**:
 
$$v_o = i_o R_o = g_m (r_{o2} // r_{o4}) v_{id}$$
- Hence, the **differential-mode gain**:
 
$$A_{dm} = v_o / v_{id} = +g_m (r_{o2} // r_{o4})$$
- **$R_i = 2r_\pi$**  (**BJT Implementation**)

- ***Ex.:** Prove the expressions for  $A_{dm}$  and  $R_i$  from the hybrid- $\pi$  model*
- *$A_{cm}$  for this circuit is a little difficult to evaluate*
- However, the ***CMRR can be safely approximated as:***

$$CMRR \approx 20\log_{10}(2g_m R_{EE})$$

$R_{EE}$ : *Output resistance of the bias current source  $I_{EE}/I_{SS}$*
- In order to ***improve CMRR***, various *current source topologies* can be used

- **Example: Simple npn CM**

- **One of the simpler choices**

- **$Q_5$ - $Q_6$  perfectly matched**


- **Neglecting base currents:**

$$I_{REF} = I_{EE} = I_{C6}$$

$$= (V_{CC} - V_{BE} - V_{EE})/R$$

- $R_{EE} = r_{06} = V_A/I_{EE}$

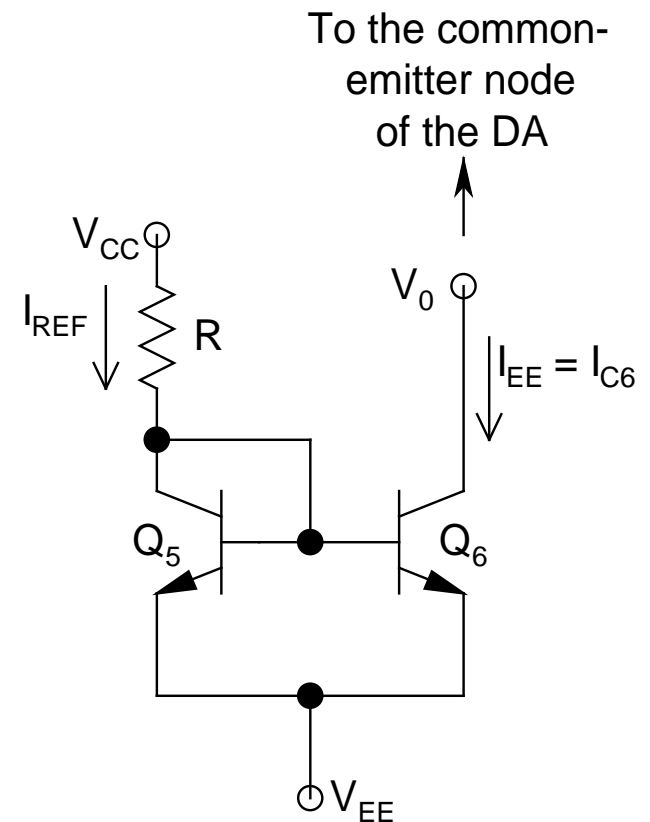- Acts as a **current source** of **magnitude  $I_{EE}$**  with a shunt **resistance  $R_{EE}$**



- *Insights:*

- *Recall:*  $A_{dm}$  independent of  $R_{EE}$ , but  $A_{cm}$  and  $CMRR$  strongly depend on  $R_{EE}$
- *To maximize  $CMRR$ ,  $R_{EE}$  should be increased as much as possible*
- *To increase  $R_{EE}$ , other current sources discussed in class, e.g., *ratioed mirror*, *cascode*, *Widlar*, etc., can be used*
- *Note that with more advanced architectures,  $V_o(min)$  increases, and may become a limiting factor!*