

Department of Electrical Engineering
Indian Institute of Technology, Kanpur

EE 210

Assignment #6

Assigned: 12.2.21

1. An n-channel MOSFET is to be designed to carry a drain current of $100\ \mu\text{A}$, remaining in the saturation region with the least value of V_{DS} equal to $100\ \text{mV}$, and at this bias point, its output resistance must equal $1\ \text{M}\Omega$. Design the values of its W and L , assuming $dX_d/dV_{DS} = 10\ \text{nm/V}$. Assume $k'_N = 40\ \mu\text{A/V}^2$, and $\lambda V_{DS} \ll 1$.
2. Determine the output current I_0 and the output resistance of the bipolar current mirror shown in Fig.1, for $V_0 = 1\ \text{V}$, $5\ \text{V}$, and $30\ \text{V}$: i) neglecting any non-idealities, and ii) including all non-idealities. For each case, find the percent change between the ideal and the non-ideal performances. All the transistors have the same emitter-base junction areas. Assume $V_A = 130\ \text{V}$ and $\beta = 50$.
3. Consider the npn ratioed current mirror shown in Fig.2, with $V_{CC} = 5\ \text{V}$ and $R_1 = 1\ \text{k}\Omega$. Choose the values of R and R_2 , such that the output resistance of the mirror is at least $10\ \text{M}\Omega$, and the circuit should operate properly for V_0 all the way down to $0.5\ \text{V}$. What is the output current I_0 ? Using the calculated value of I_{REF} , determine the value of I_0 , for which the simple approximation for the ratioed current mirror would *just* break down. What are the corresponding values of R_2 , $V_{0(\text{min})}$, and R_0 ? Neglect base currents and Early effect for the dc analysis of the circuit, and assume $V_A = 130\ \text{V}$ for ac analysis.
4. Determine the quiescent currents flowing in all the branches of the circuit shown in Fig.3, and calculate the output resistance R_0 . Neglect base currents, and assume $V_A = 130\ \text{V}$.
5. Determine the output current and the output resistance of the circuit shown in Fig.4. Neglect base currents and assume $V_A = 130\ \text{V}$.

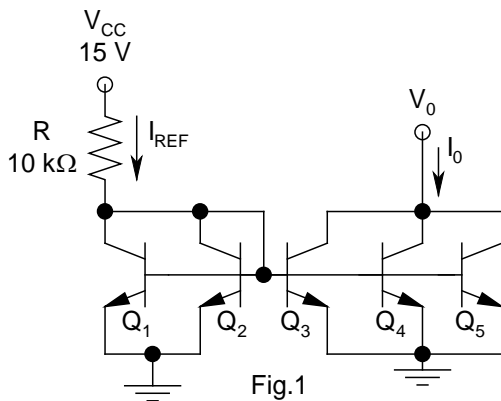


Fig.1

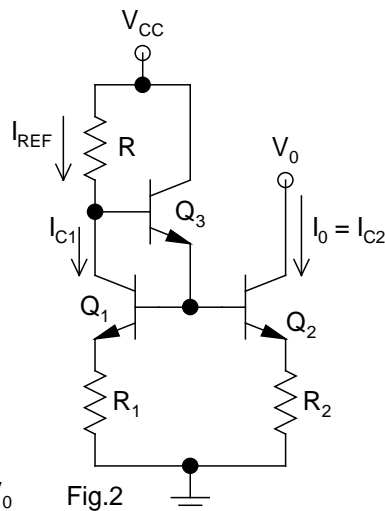


Fig.2

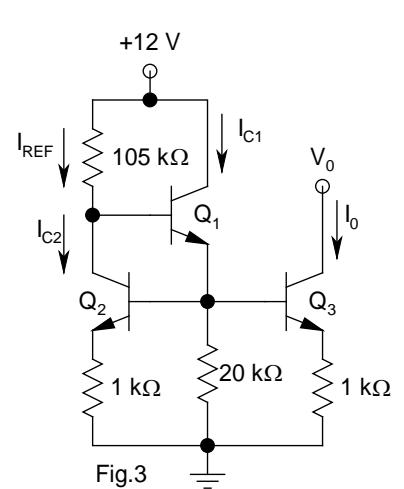


Fig.3

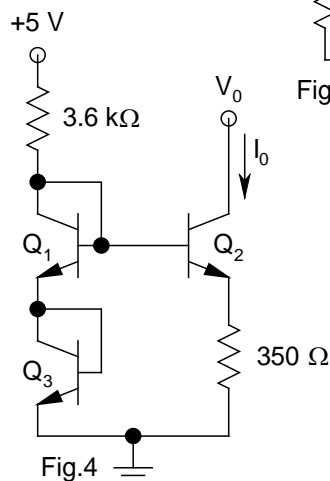


Fig.4