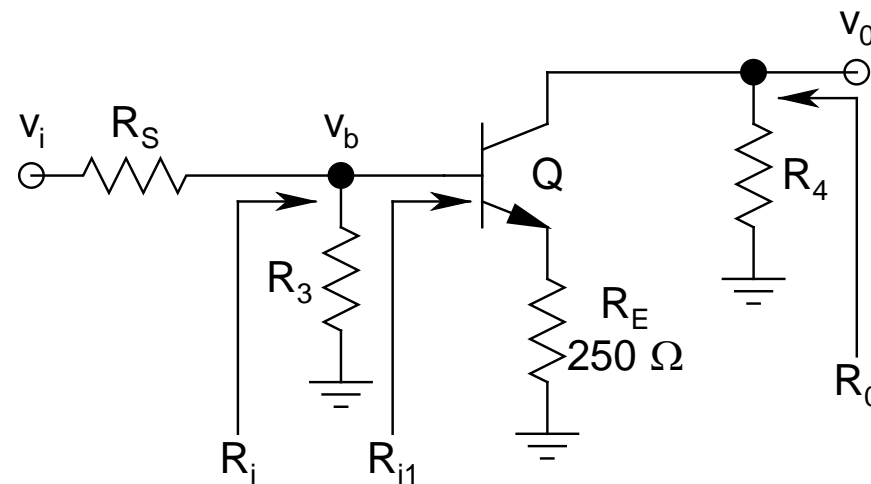


- Now let's explore what happens if C_E were *absent*, i.e., R_E *unbypassed*
- Redraw the *ac schematic*:




ac Midband Schematic for R_E unbypassed

- **Note:** *Degeneration Factor* $= (1 + g_m R_E) \approx (1 + R_E/r_E) = 20.23$
- $R_{i1} = r_\pi + (\beta + 1)R_E = 26.55 \text{ k}\Omega$
 - *Exactly 20.23 times of the previous case* (1.3 k Ω)
- $R_i = R_{i1} \parallel R_3 = 6.72 \text{ k}\Omega$
- Total resistance *seen* by $v_i = R_S + R_i = 7.72 \text{ k}\Omega$
- $v_o/v_b = -R_4/(r_E + R_E) = -7.6$ [*CE(D) Stage*]
 - *Reduced by exactly 20.23 times of the previous case* (– 153.85)
- $v_b/v_i = R_i/(R_i + R_S) = 0.87$
 - *Improvement as compared to previous case* (0.533)

- $A_v = -6.6$
 - *Compare with -82 obtained in previous case (significant reduction)*
- $R_0 \approx R_4 = 2 \text{ k}\Omega$ (if r_0 is neglected)
- *If r_0 is considered, analysis becomes significantly complicated, since the Golden Rule can't be applied due to the presence of resistance (apart from r_π) in the base of Q*
- *Summary:*
 - $A_v = -6.6$
 - $R_i = 6.72 \text{ k}\Omega$
 - Resistance *seen* by $v_i = 7.72 \text{ k}\Omega$
 - $R_0 = 2 \text{ k}\Omega$

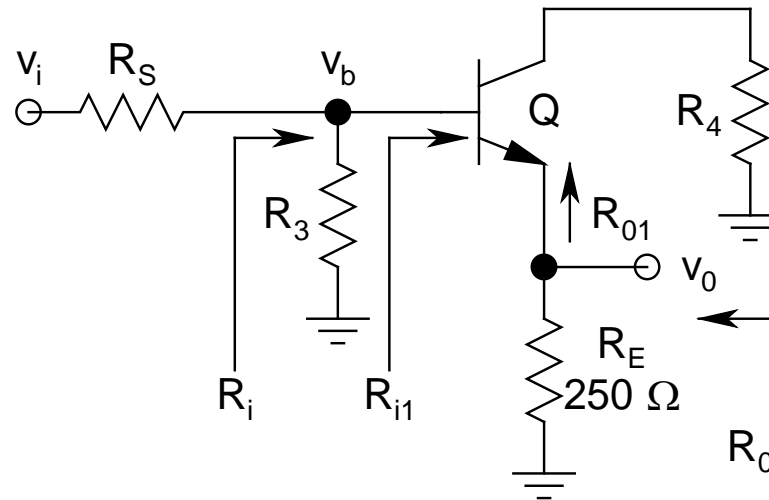- *What if the output is taken from emitter?*
- Redraw the *ac schematic*:



**ac Midband Schematic for
Output Taken from Emitter**

- *R_4 actually redundant for this case (collector of Q could have been connected to V_{CC} directly)*
- $R_{i1} = 26.55 \text{ k}\Omega$, $R_i = 6.72 \text{ k}\Omega$, and resistance *seen* by $v_i = 7.72 \text{ k}\Omega$ (*same as before*)
- $v_o/v_b = R_E/(r_E + R_E) = 0.95$ (*CC Stage*)
- $v_b/v_i = R_i/(R_i + R_S) = 0.87$ (*same as before*)
- $A_v = 0.827$ (<1 , as expected, but *could have been made closer to unity by better design!*)
- $R_o = R_E || R_{o1}$
- *Computation of R_{o1} is slightly more involved, but quite easy if the trick is understood!*