

➤ *Any value of  $R_C$  higher than  $4.3\text{ k}\Omega$  would push  $Q$  in saturation*

➤ Choose  $R_C = 20\text{ k}\Omega$ :

- Assuming *FA* operation is maintained,  $V_{CE}$  comes out to be  $-15\text{ V}$ !

- *Golden rule*:

- ❖ *Potential at any point in a circuit can never go beyond the positive and negative extremes of the power supply voltages, unless there is a power source within the circuit*

- Thus,  $V_{CE} = -15\text{ V}$  is *absurd*!


- Hence,  $Q$  is *no more* in the *FA* mode of operation, rather it has been pushed into *saturation*

- Whether it is in *soft saturation* (SS) or *hard saturation* (HS), would *depend* on the *degree of saturation* (DoS)
- *For HS, DoS must be  $\geq 2$*  ( $\beta_{\text{sat}} \leq \beta/2$ )
- Assume *HS*:  $V_{\text{BE}}(\text{HS}) = 0.8 \text{ V}$ ,  $V_{\text{CE}}(\text{HS}) = 0.1 \text{ V}$ 
  - ❖  $I_{\text{B,sat}} = [V_{\text{CC}} - V_{\text{BE}}(\text{HS})]/R_{\text{B}} = (5 - 0.8)/(430 \text{ k}\Omega) = 9.77 \text{ }\mu\text{A}$
  - ❖  $I_{\text{C,sat}} = [V_{\text{CC}} - V_{\text{CE}}(\text{HS})]/R_{\text{C}} = (5 - 0.1)/(20 \text{ k}\Omega) = 245 \text{ }\mu\text{A}$
  - ❖  $\beta_{\text{sat}} = I_{\text{C,sat}}/I_{\text{B,sat}} = 245/9.77 = 25$
  - ❖  $\text{DoS} = \beta/\beta_{\text{sat}} = 4 (> 2)$
  - ❖ *Assumption verified, and analysis is correct!*
- *Ex.*: Find the values of  $R_{\text{C}}$  that would put Q at the edge of: i) HS, and ii) SS

# Base Width Modulation Effect

- In **FA** mode, as  $|V_{BC}| \uparrow$ , BC *depletion region width*  $\uparrow \Rightarrow$  *neutral base width*  $\downarrow$ 
  - *Electrons spend less time in base*  $\Rightarrow$  *chance of recombination*  $\downarrow$
  - *More electrons make it to the collector*  $\Rightarrow I_C \uparrow$   
as  $V_{CE} \uparrow$
  - Known as the **Base Width Modulation Effect**  
(or *Early Effect*)

- The *current-voltage characteristic*, including *Early Effect*, is modeled as:
  - $I_C = I_S[\exp(V_{BE}/V_T)](1 + V_{CE}/V_A)$
  - $V_A$ : *Early Voltage* ( $\sim 130$  V for *nnp*, and  $\sim 52$  V for *pnnp*)
  - $V_A$  is a *negative number*, but taken to be a *positive quantity*
- Imparts a *positive slope* in the *output characteristics* in the *FA region*
  - Introduces an *output resistance*, and makes the current source *non-ideal*!

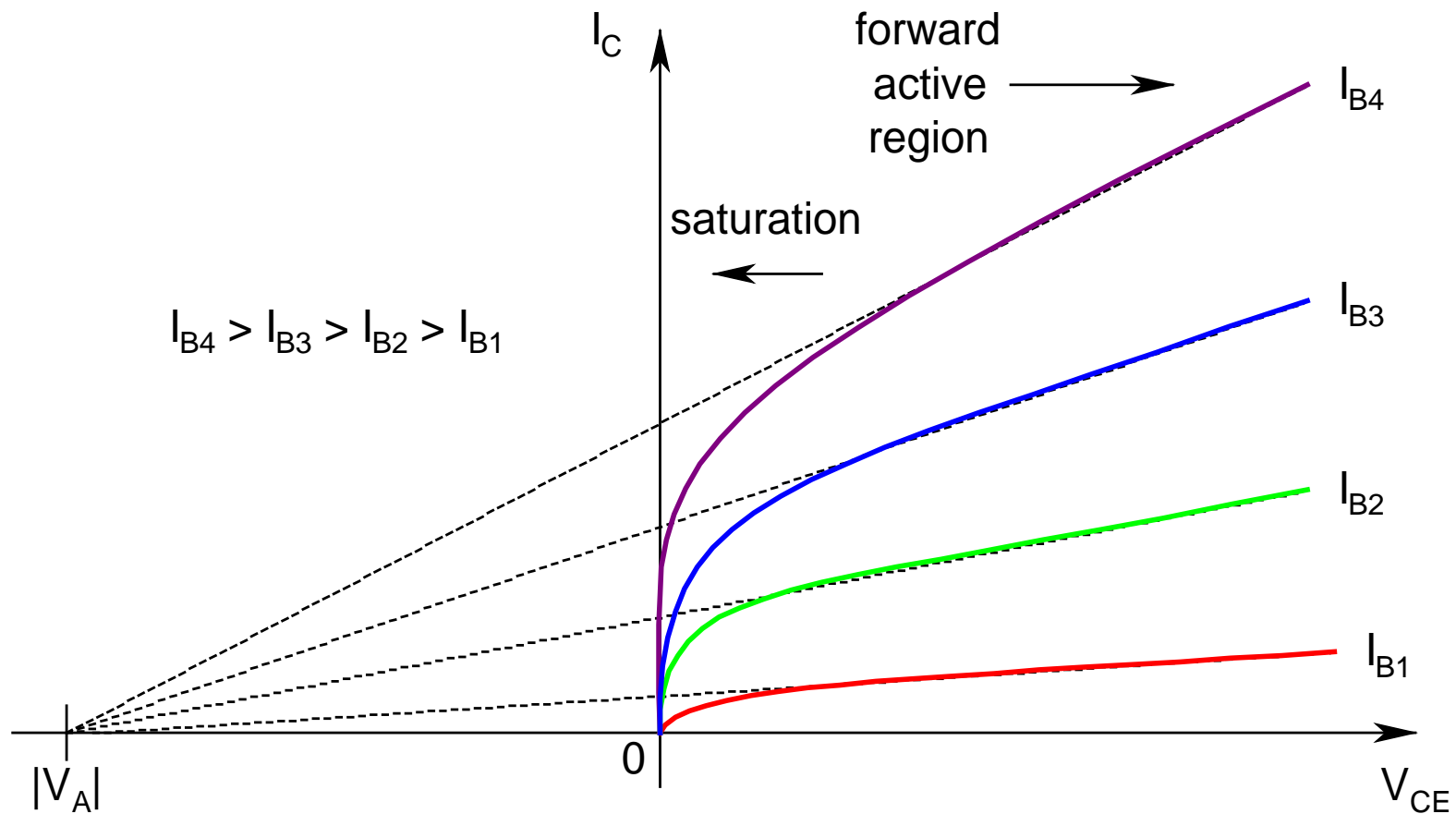

**All characteristics merge at  $|V_A|$  in the negative  $V_{CE}$  axis**

**Note:** If  $V_A \rightarrow \infty$ , all characteristics become horizontal in the FA region

# IEEE Notational Convention

- *Pure DC quantities:*
  - *Capital letter with capital subscript* (e.g.,  $V_{BE}$ )
- *Pure ac quantities:*
  - *Small-case letter with small-case subscript* (e.g.,  $v_{be}$ )
- *Instantaneous (DC + ac) quantities:*
  - Either *capital letter with small-case subscript* (e.g.,  $V_{be}$ ) or *small-case letter with capital subscript* (e.g.,  $v_{BE}$ )

# Small-Signal Model

- The *electrical equivalent* of the BJT at the *DC bias point*
- Basically an *electrical network*, having *passive and active elements*
- To obtain this model, *DC analysis* is needed, since the *information* regarding the *Q-point* ( $I_C$ ,  $V_{CE}$ ) is necessary
- *This model for npn and pnp BJT is same*