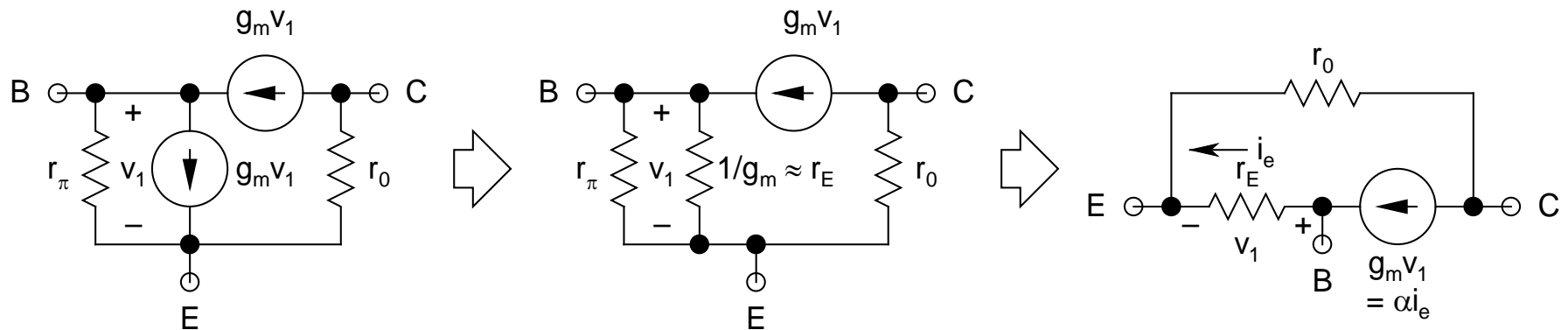
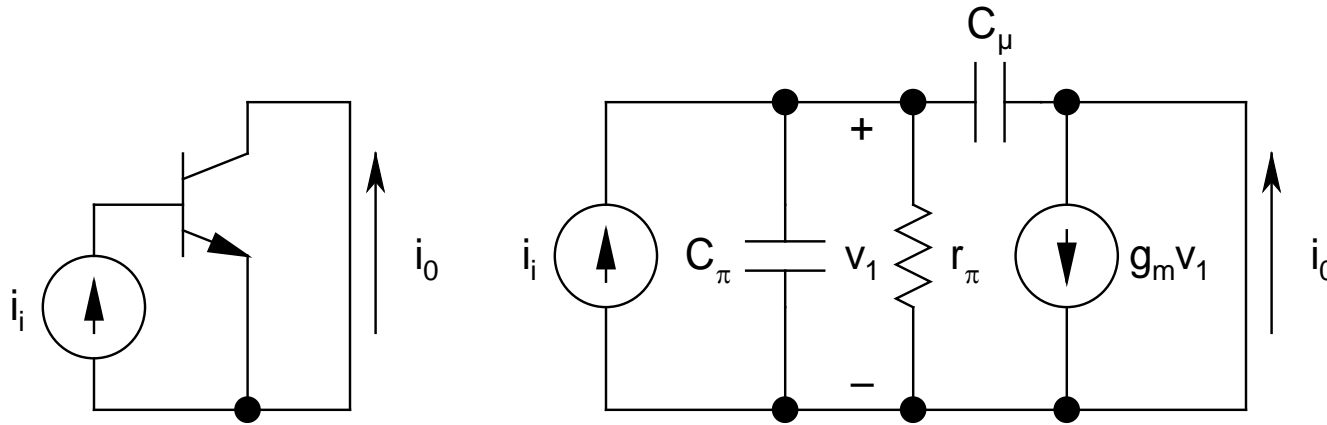


- *This model is appropriate when the ac input is applied to base*
- *When the ac input is applied to the emitter, then need to draw this circuit in a slightly different way*



Frequency Specifications of BJTs

- *Four important characteristic frequencies:*
 - *Beta Cutoff Frequency* (f_{β})
 - *Unity Gain Cutoff Frequency* (f_T)
 - *Alpha Cutoff Frequency* (f_{α})
 - *Maximum Operable Frequency* (f_{\max})



- $i_o \approx g_m v_1$ (*neglecting reverse transmission through C_μ*)
- $v_1 = i_i Z_{eq}$

$$Z_{eq} = \frac{r_\pi}{1 + s r_\pi (C_\pi + C_\mu)} \quad (s = j\omega)$$

- Thus:

$$\beta(j\omega) = \frac{i_o(j\omega)}{i_i(j\omega)} = \frac{\beta_0}{1 + j\omega/\omega_\beta}$$

$\beta_0 (= g_m r_\pi)$: *Low-frequency short-circuit common-emitter current gain*

$$\omega_\beta = \frac{g_m}{\beta_0 (C_\pi + C_\mu)}$$

- $f_\beta [= \omega_\beta/(2\pi)]$: *Beta Cutoff Frequency*
- At $f = f_\beta$, $\beta = \beta_0/\sqrt{2}$

- For $f \gg f_\beta$:

$$\beta(j\omega) \simeq \frac{g_m}{j\omega(C_\pi + C_\mu)}$$

- At $\omega = \omega_T = g_m/(C_\pi + C_\mu)$, $|\beta| = 1$
- $f_T [= \omega_T/(2\pi)]$: **Unity Gain Cutoff Frequency** (also known as **Unity Gain Bandwidth**)
- **Note**: $f_T = \beta_0 f_\beta$
- $f_T > f_\beta$, and their spacing depends on β_0

