

ESC201T: Introduction to Electronics


Users Online : 26

discussion Quiz-3

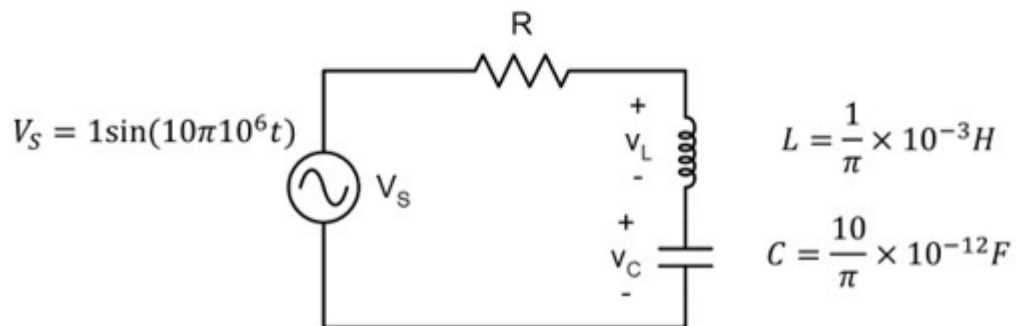Q.1

ESC201T : Introduction to Electronics
Discussion Quiz 3 (7/10/2020)

Q. Determine the minimum value of resistance (in Ω) required to obtain magnitude of capacitor voltage (v_c) larger than 100V.
(Give answer only as an integer)



Your answer:

10

Score: Will be uploaded after end date.