FEEDBACK, STABILITY, & COMPENSATION

Feedback

- Connection between input and output either directly through a wire, or through some circuit elements
 - ⇒ Input and output gets coupled
 - ⇒ Any change in either of them, affects the overall behavior
- 2 Types:
 - > Negative
 - > Positive


- Negative Feedback:
 - > Output fed back to input in such a way that it reduces net input
 - \Rightarrow Causes a reduction in the output
 - > Known as *Degenerative Feedback*
- Positive Feedback:
 - > Output fed back to input in such a way that it increases net input
 - \Rightarrow Causes an increase in the output
 - > Known as *Regenerative Feedback*

- Properties of Negative Feedback:
 - > Reduction in gain
 - ⇒ Improvement in bandwidth

 (Due to constant GBP)
 - > Tailoring of input and output resistances
 - > Desensitization of gain
 - Gain becomes almost independent of the properties of the active device
 - ➤ Minimization of frequency and phase distortion

- > Reduction in nonlinear distortion
 - By suppression of harmonics present in the output
- > Reduction of noise
- > If not properly designed, can have problem of stability
- Properties of Positive Feedback:
 - > Inherently unstable
 - Due to its regenerative nature
 - This property can be effectively utilized in the design of oscillators, which do not need any input

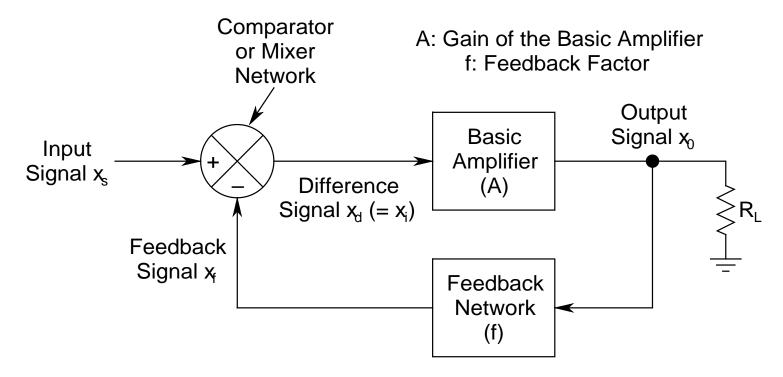• Mathematical Foundation of Negative Feedback:



Block Schematic of a Negative Feedback System

> 3 Main Blocks:

- The Basic Amplifier (Gain A)
- The Feedback Network (Feedback Factor f)
- The Mixer (note the negative sign)
- > Defining Relations:
 - Input Signal x_s
 - Output Signal $x_0 = Ax_i$
 - *Feedback Signal* $x_f = fx_0$
 - *Difference Signal* $x_d = x_i = x_s x_f$
- **Gain with feedback**: $A_f = x_0/x_s$

> Thus:

$$A_{f} = \frac{X_{0}}{X_{s}} = \frac{X_{0}}{X_{i}} \frac{X_{i}}{X_{s}} = A \frac{X_{s} - X_{f}}{X_{s}} = A \left(1 - \frac{X_{f}}{X_{s}}\right)$$
$$= A \left(1 - \frac{X_{f}}{X_{0}} \frac{X_{0}}{X_{s}}\right) = A \left(1 - fA_{f}\right)$$

➤ Gives the *fundamental expression* for *negative feedback*:

$$A_f = \frac{A}{1 + fA}$$

• Some Definitions:

- \succ Loop Gain (L) = fA
- \triangleright Return Difference (D) = 1 + L
- $ightharpoonup Amount of Feedback (N) = 20 log_{10}D (dB)$
- Positive Feedback:
 - > Output fed back to the input through the mixer, but now with a positive sign
 - ⇒ Feedback signal gets added to the input signal

> Show that under this condition:

$$A_{f}(j\omega) = \frac{A(j\omega)}{1 - f(j\omega)A(j\omega)} = \frac{A(j\omega)}{1 - L(j\omega)}$$

- This is a *general expression*, taking both A and f as *frequency dependent*
- \triangleright Note: As $L \rightarrow 1, A_f \rightarrow \infty$
 - Implies that output is possible even without any input
 - This is the *basic principle of oscillation*

- Conditions for Oscillation:
 - Barkhausen's Criteria:
 - L becoming unity implies that the signal has completely regenerated itself while traversing once through the loop
 - ⇒ There is no need for any input any more, since the loop has become self-sustained!
 - > Since A and f are frequency dependent, hence, there may exist a frequency ω_0 , at which:

$$L(j\omega_0) = f(j\omega_0)A(j\omega_0) = 1$$

- Since ω_0 is a *particular frequency*, for which *this condition holds*, hence, the output will be a *pure sinusoid* of *this frequency*
 - Similar to *picking out* f₀ only from a *Fourier Spectrum*
 - This phenomenon is known as *Sinusoidal Oscillation*
- Serman physicist *Heinrich Georg Barkhausen* summed this up by *two conditions*, came to be known as the *Barkhausen's Criteria*:
 - 1. $|L(j\omega_0)| = 1$ and
 - 2. $\angle L(j\omega_0) = 0^{\circ}$

- > Barkhausen's Criteria in words:
 - For a feedback system to oscillate, the magnitude of the loop gain must at least be unity, and the total phase shift around the loop should be 0° or 360°
- ➤ If these criteria are satisfied exactly, then the oscillations would go on forever, and can be stopped only by shutting the power off for the system
- ➤ However, for *practical circuits*, the *exact conditions for oscillations* are *very difficult to achieve*

- ➤ If |L| becomes *slightly less than 1*, but ∠ L is *exactly 0°*, then with *each pass around the loop*, the *amplitude of oscillation* would keep on *going down*, and eventually, it will *die down* on its own
 - Thus, under this condition, sustained sinusoidal oscillation won't be achieved
- ➤ On the other hand, if |L| becomes *slightly* larger than unity, but ∠ L is exactly 0°, then with each pass around the loop, the amplitude of the signal will keep on growing
 - Will eventually get limited by the nonlinearities present in the circuit

Stability

- 2 Types of Systems:
 - > Stable
 - > Unstable
- Stable System:
 - Any transient disturbance would result in a response that will die down with time
 - The system will be able to get rid of the disturbance on its own

• Unstable System:

- Any transient disturbance would result in a response that will persist or even blow up with time
 - Eventually gets limited by the nonlinearities of the system
- ➤ Positive feedback systems are inherently unstable
 - They are designed as such, e.g., oscillators
- > Negative feedback systems are inherently stable

- However, there may be situations when they may become unstable and break out into spontaneous oscillations
- Potentially dangerous situation, and the system should be protected against it
- How does a negative feedback system become unstable?
 - > Write the *loop gain* expression in *polar form*:

$$L(j\omega) = f(j\omega)A(j\omega) = |f(j\omega)A(j\omega)| \exp[j\phi(\omega)]$$

 $\phi(\omega)$: Frequency dependent phase of the system

- Consider a *particular frequency* ω_x , at which $\phi(\omega_x) = 180^\circ$
- ightharpoonup At ω_x , L would be a *real number* with *negative sign*
 - ⇒ The feedback turns positive at this frequency
- \triangleright 3 conditions may arise at ω_x :
 - $\blacksquare |L| < 1:$
 - $A_f(j\omega_x) > A(j\omega_x)$, but the *system will be stable*
 - |L| = 1:
 - $A_f(jω_x)$ → ∞, and output will appear without any input ⇒ Oscillator

- |L| > 1:
 - $A_f(j\omega_x) < A(j\omega_x)$, but the *output will oscillate with* gradually increasing amplitude, and will eventually get limited by the nonlinearities present in the system
- Thus, for a negative feedback system to turn into a positive feedback one, the loop gain (L = fA) being equal to or less than -1 is a sufficient and necessary condition
- For this to happen, the magnitude of the loop gain (L) should be equal to or greater than unity, and the total phase around the loop should be 180°

The Complex Frequency & The s-Plane

- Needed to understand the concept of *stability* of a system
- s-Plane: Complex Frequency Plane
- Consider a *sinusoidal signal* with an *exponential envelope*:

$$v(t) = V_{M}[\cos(\omega t + \phi)] \exp(\sigma t)$$
$$V_{M}: Amplitude$$

- φ: *Phase*
- σ: Coefficient of the exponential enevelope, having unit of time inverse (similar to frequency)
- For positive σ , the signal will keep on growing with time
- For *negative* σ , the signal would *decay* exponentially all the way to zero

• 3 interesting scenarios:

1.
$$\sigma = \omega = 0$$
:
 $\Rightarrow v(t) = V_{M} \cos \phi$
 $\Rightarrow DC signal (constant)$

2.
$$\sigma = 0$$
:

$$v(t) = V_{M}[\cos(\omega t + \phi)]$$

- ⇒ Normal ac signal
- 3. $\omega = 0$:

$$v(t) = [V_M \cos \phi] \exp(\sigma t)$$

 \Rightarrow Exponential signal (increasing/decreasing with time for positive/negative σ)

• A normal *sinusoidal voltage* v(t), having *angular frequency* ω and *phase* ϕ , can be represented in *polar form* as:

$$v(t) = V_{M} \exp[j(\omega t + \phi)] \qquad (1)$$

- Comparing Eq.(1) with *scenario 3*, we note that their *functional forms* are the *same*
 - \Rightarrow σ can be thought of as a *frequency*, and is referred to as the *neper frequency*, with unit of *nepers/sec*
 - ➤ However, this definition is *not much used*

- Note also that the *comparison* of the two expressions show that σ is actually an *imaginary number*
 - > This needs further *exploration*
- Eq.(1) can be written in *polar form* as:

$$v(t) = (V_{M}/2)[exp{j(\omega t + \phi)} + exp{-j(\omega t + \phi)}]$$

$$= [(V_{M}/2)exp(j\phi)]exp(j\omega t)$$

$$+ [(V_{M}/2)exp(-j\phi)]exp(-j\omega t)$$

$$= Aexp(s_{1}t) + Bexp(s_{2}t) \qquad (2)$$

- $s_1 = j\omega$ and $s_2 = -j\omega$
- $A = (V_M/2)\exp(j\phi)$ and $B = (V_M/2)\exp(-j\phi)$
- \Rightarrow s_1 and s_2 as well as A and B are complex conjugates
- ⇒ The 2 terms of Eq.(2) are also *complex* conjugates, with their sum being a real number
- Similarly, a *sinusoidal signal* with an *exponential envelope* can be expressed by:

$$v(t) = [(V_{M}/2)\exp(j\phi)]\exp[(\sigma + j\omega)t]$$

$$+ [(V_{M}/2)\exp(-j\phi)]\exp[(\sigma - j\omega)t]$$

$$= A\exp(s_{1}t) + B\exp(s_{2}t) \qquad (3)$$

• *Matching coefficients* of Eq.(3), we get a *complex pair of frequencies*:


$$s_1 = (\sigma + j\omega)$$
 and $s_2 = (\sigma - j\omega)$
which are also *complex conjugates*

- Thus, *sinusoidal signals* having *complex envelopes*, can be expressed in terms of a *complex frequency* s
- s has both real and imaginary parts (σand jwrespectively)

• s is defined by:

$$s = \sigma \pm j\omega$$

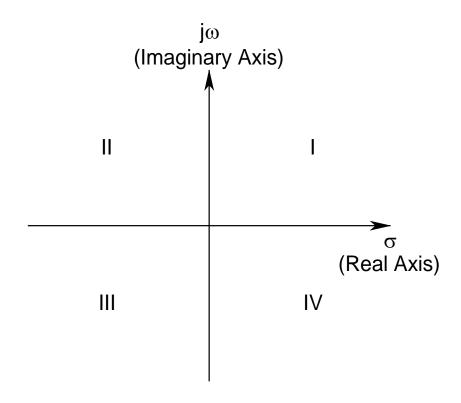- σ: **Real part** dictates the **exponential rise/fall** of the signal
- ω: *Imaginary part actual angular frequency*, describes the *sinusoidal variation* of the signal
- s is represented in a *graphical form* as a 2D plane, with σ plotted along the x-axis (known as the real axis), and ω plotted along the y-axis (known as the imaginary axis)




The Complex Frequency Plane (s-Plane)


- Poles of a transfer function can lie anywhere on this plane
- If $\sigma = 0$, poles lie on the jwaxis
 - ⇒ Perfect sinusoidal response
- If $\omega = 0$, poles lie on the σ axis
 - \Rightarrow Pure exponential response
- If a pole has both real and imaginary parts, then the response would be either an exponentially increasing or decreasing sinusoid

- Pole Location & Stability:
 - > Locations of the poles in the s-plane governs the stability of the system
 - > We will consider 3 cases:
 - Complex conjugate poles without any real part
 - Complex conjugate poles with negative real part
 - Complex conjugate poles with positive real part

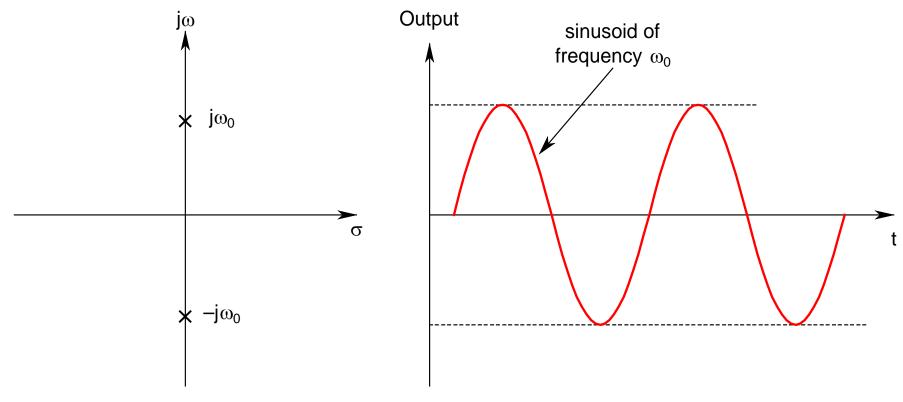- > Complex conjugate poles $s_1 (= j\omega_0)$ and $s_2 (= -j\omega_0)$, without any real part:
 - ⇒ Undamped sinusoidal response
 - ⇒ Perfectly stable system




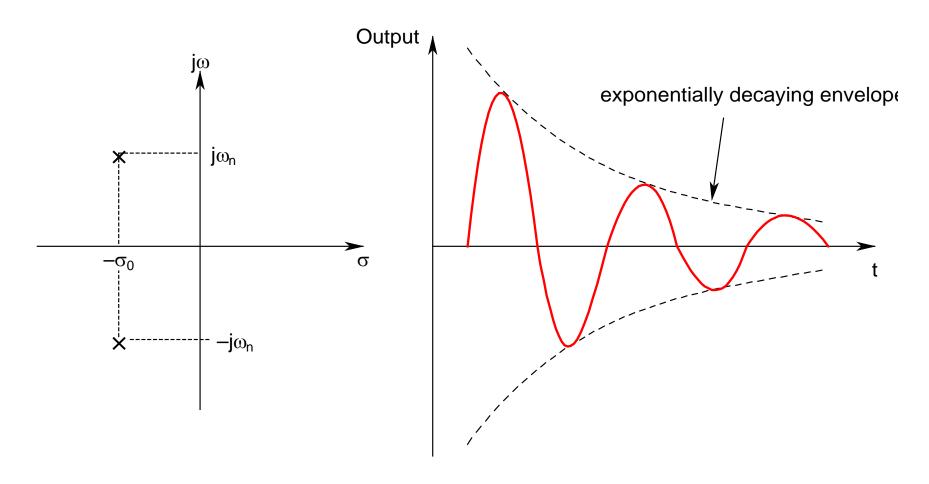- > Complex conjugate poles $[s_1 = (\sigma_0 + j\omega_n)]$ and $s_2 = (\sigma_0 j\omega_n)$, with negative real part $(\sigma_0 + j\omega_n)$:
 - Poles lie in the left-half plane (LHP Quadrants II and III)
 - Response to any transient disturbance will be sinusoidal, but with an exponentially decaying envelope
 - Such systems also are stable or well-behaved



Response to Transient Disturbance of a System Having Poles in the LHP (Stable System)

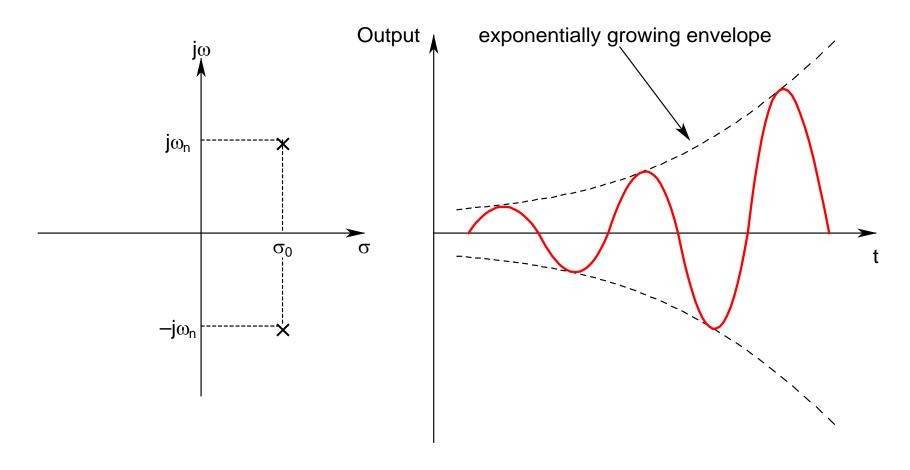- ► Complex conjugate poles $[s_1 = (\sigma_0 + j\omega_n)]$ and $s_2 = (\sigma_0 j\omega_n)$, with positive real part $(\sigma_0 + j\omega_n)$:
 - Poles lie in the right-half plane (RHP Quadrants I and IV)
 - Response to any transient disturbance will still be sinusoidal, but now with an exponentially rising envelope
 - The system now is NOT well-behaved, rather illbehaved, and an unstable system



Response to Transient Disturbance of a System Having Poles in the RHP (Unstable System)

Transfer Function & Stability

- There is a *strong correlation* between the *transfer function* and *stability* of a system
- Single-Pole System:
 - > Transfer function with a negative real pole at ω_p :

$$A(j\omega) = \frac{A_0}{1 + j\omega/\omega_p}$$

A₀: Low-Frequency Gain

- ➤ Now, assume that the *system* is *connected* in a *feedback loop*, with the *feedback network* having *feedback factor* f
 - \Rightarrow The *closed-loop transfer function*:


$$A_f = \frac{A_{f0}}{1 + j\omega/\omega_{pf}}$$

$$A_{f0} = A_0/(1 + fA_0) \text{ and } \omega_{pf} = \omega_p(1 + fA_0)$$

The gain with feedback reduces by the same amount as the bandwidth gets increased, keeping the GBP constant

- Thus, the *new pole frequency* is D (the *return difference*) times the *old pole frequency*
 - \Rightarrow It shifts *left* along the σ axis in the s-plane, and remains on the LHP without any imaginary component
 - ⇒ The system remains stable even with feedback
- ➤ Also, the *phase* of the system *can never fall* below -90°
- ➤ Here, of course we are assuming a *passive* feedback network, i.e., f is a real number

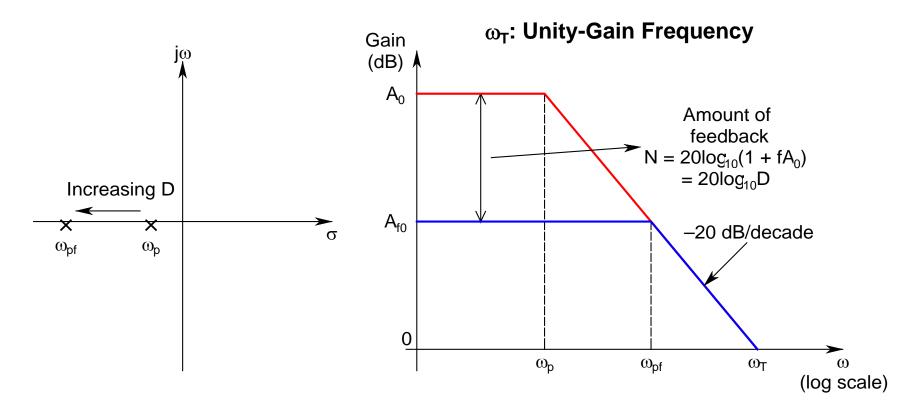- > Thus, f does not add any phase to the system
- > Hence, Barkhausen's criteria can never be satisfied for this case
- > Also, the *pole can never enter the RHP*
- > Thus, we *conclude*:
 - A system with *single-pole transfer function* is *Unconditionally Stable*, i.e., it will *remain stable* for *values of f* all the way *up to unity* (i.e., *the entire output fed back to the input*)



Movement of the Pole for a Single-Pole System Under Negative Feedback and the Bode Plot of the Gain

• Two-Pole System:

> Transfer Function:

$$A(s) = \frac{A_0}{(1 + j\omega/\omega_{p1})(1 + j\omega/\omega_{p2})}$$

A₀: Low-Frequency Gain

- ω_{p1} , ω_{p2} : Two negative real poles, lying on the σ axis, with $\omega_{p2} > \omega_{p1}$
- Now, with *passive feedback* with *feedback* factor f, the *locations* of the *closed-loop poles* can be found from: 1 + fA(s) = 0

> Thus:


$$s^2 + (\omega_{p1} + \omega_{p2})s + (1 + fA_0)\omega_{p1}\omega_{p2} = 0$$

> Solution gives the locations of the two closed-loop poles:

$$s_{1}, s_{2} = -\frac{\omega_{p1} + \omega_{p2}}{2} \pm \frac{1}{2} \sqrt{(\omega_{p1} + \omega_{p2})^{2} - 4(1 + fA_{0})\omega_{p1}\omega_{p2}}$$

- With increase in feedback, the second term reduces
 - \Rightarrow s_1 and s_2 start to move towards each other along the σ axis
- > Eventually, at a *particular feedback*, the *second term would vanish*

- > At this point, the two poles will merge at $(\omega_{p1} + \omega_{p2})/2$
- ➤ With further increase in feedback, the second term becomes imaginary, while the first term remains constant
 - ⇒ The poles remain complex conjugates
- Even for f all the way up to unity, when the entire output is fed back to the input, the poles remain in the LHP and can never enter RHP
 - ⇒ The system remains unconditionally stable

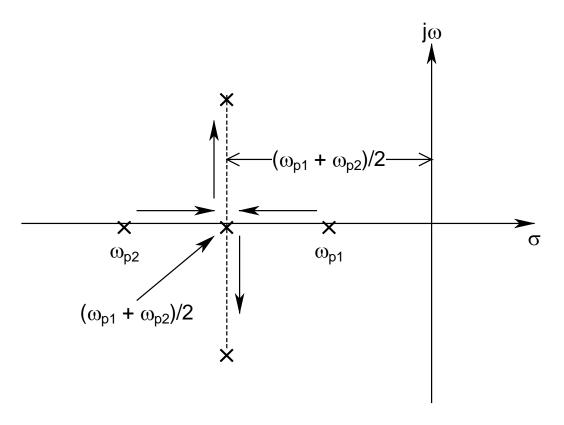

Movement of the Poles for a Two-Pole System Under Negative Feedback With Increasing D


- ➤ Also, for a two-pole system, the phase reaches

 -180° only when the frequency becomes
 infinite (mathematically)
 - ⇒ There is no physically achievable frequency when this can happen
 - ⇒ *Unconditional Stability*
- System With Three (or More) Poles:
 - > Actual mathematical analysis quite tedious
 - ➤ It can be shown that as the *amount of* feedback (D) is increased:
 - The highest frequency pole (ω_{p3}) moves outward along the $-\sigma$ -axis

- The other two poles $(\omega_{p1} \text{ and } \omega_{p2})$ move towards each other (similar to a two-pole system)
- As *D* is increased further, these two poles
 eventually merge, and then start having imaginary
 components
- Their real part also keeps on changing with D, keeping the nature of complex conjugacy intact, and moves right in the s-plane
- The path traced out by these poles is known as the root locus
- For a particular value of D, this root locus intersects the imaginary axis of the s-plane at two symmetric points

- Under this condition, sustained sinusoidal oscillation can be achieved, since it now has a complex conjugate pair of poles without any real part $(\omega_{p3}$ will be so large that it will be inconsequential)
- With further increase in D, the root locus enters the RHP with the poles now having positive real part
 - ⇒ Potentially dangerous situation in terms of stability
- In terms of phase, the total can be -270°
 - \Rightarrow There exists a particular value of f, for which the phase will become -180°


- Under this condition, if the magnitude of the loop gain is exactly unity, then the system will break out into spontaneous oscillation, however, the amplitude will be controlled
 - \Rightarrow Sustained sinusoidal oscillation
- This particular value of f is known as the critical feedback factor (f_{crit}) for oscillation
 - \Leftrightarrow For $f < f_{crit}$, the *system will be stable*
 - For $f > f_{crit}$, the *system will be unstable*
- Thus, the system is *NOT Unconditionally Stable*, but *stable only till a specific value of f*
 - * Known as *Conditionally Stable System*

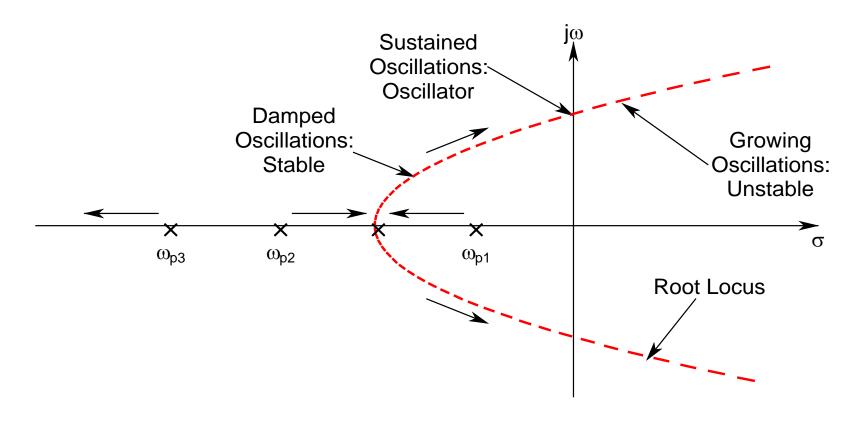

Root Locus of the Poles of a Three-Pole System as D is Increased

Stability Study Using Bode Plot

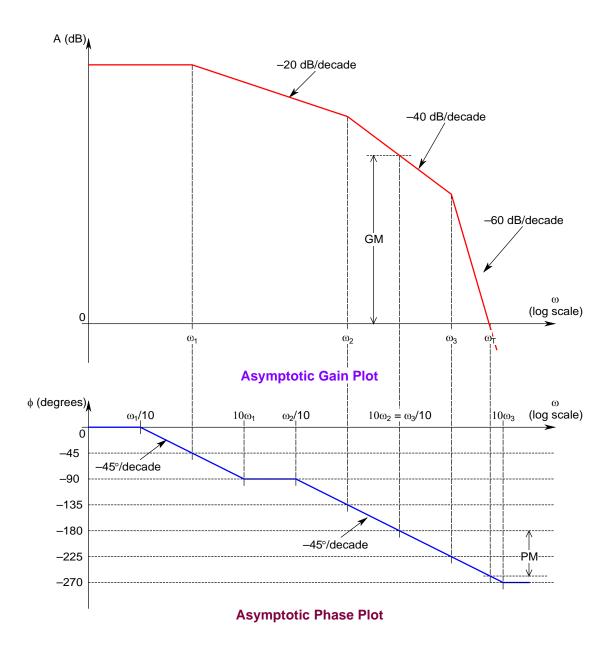- The *most convenient* and the *most useful*
- Recall: Single- and Two-Pole Systems are unconditionally stable
- Consider a *Three-Pole System*, with the *pole frequencies* at ω_1 , ω_2 , and ω_3 , with $\omega_3 = 100\omega_2$, and $\omega_2 > 100\omega_1$
- *Note*: A = L *if* f = 1 (100% feedback)
- Refer to the next slide (**Bode Plot**)



Aloke Dutta/EE/IIT Kanpur

• Profile of A:

- \triangleright Remains constant at its low-frequency value for $ω ≤ ω_1$
- \succ Then drops @ 20 dB/decade till ω_2
- \succ Followed by a drop @ 40 dB/decade till ω_3
- > Then drops @ 60 dB/decade
- Finally crosses 0 dB at ω (= ω_T : unity-gain cutoff frequency) slightly less than $10\omega_3$
- Profile of ϕ :
 - \triangleright Remains zero till $\omega_1/10$
 - > Then drops @ 45 %decade

- \triangleright Reaches -90° at $10\omega_1$
- > Stays constant at -90° till $\omega_2/10^{\circ}$
- \triangleright Then starts to drop again @ 45 %decade till $10\omega_3$
- ► Reaches –180° at $10\omega_2$ (= $\omega_3/10$) and –270° at $10\omega_3$
- Gain Margin (GM) and Phase Margin (PM):
 - > Extremely important terms with regard to stability of a system
 - From the sign and magnitude of these terms, the stability of the system can be predicted

- $ightharpoonup GM = A (dB) (when \phi = -180^{\circ})$
- $PM = 180^{\circ} |\phi| (when A = 0 dB)$
- ➤ In our example, *GM is positive* (as shown in the figure)
- This is *potentially a dangerous situation*, and characterizes a *highly unstable system*
 - For positive GM, with each pass around the loop, the output amplitude will keep on growing
- > On the contrary, if GM were negative, with each pass around the loop, the output amplitude would have decreased

- The system would have come out of any unwanted oscillations
- The GM dictates the maximum amount of feedback that can be allowed for the system to remain stable
- For an unconditionally stable system, GM must be negative
 - \Rightarrow A must be negative when $\phi = -180^{\circ}$
- ➤ With regard to phase, when A crossed 0 dB, \$\phi\$ is close to -270°
 - \Rightarrow PM is negative, with a value of \sim -90°

- This also implies that when ϕ crossed -180° , A of the system was greater than unity (0 dB)
 - A potentially dangerous situation in terms of stability
- Therefore, for an unconditionally stable system, PM must be positive
- The two conditions with regard to GM and PM are actually correlated
- > Rule of Thumb:
 - For a stable system, GM ~ -10 dB and PM ~ 45° are generally good enough

Compensation

• Basic Idea:


- To tailor the gain characteristic of a system, having three or more poles, such that it would be stable for any value of the feedback factor f, all the way up to unity (referred to as the unity feedback system, where the entire output is fed back to the input)
- ➤ After compensation, the system will become either conditionally (f < 1) or unconditionally stable (f = 1)

- Two widely used methods:
 - **▶** Dominant Pole Compensation (DPC)
 - ➤ Pole Zero Compensation (PZC)
- Dominant Pole Compensation (DPC):
 - This technique introduces a *dominant pole* (*DP*) into the system
 - ➤ Also known as *Miller Compensation Scheme*
 - ➤ This *DP* is chosen such that the *compensated* gain characteristic meets the *first pole* of the uncompensated system at 0 dB, with a slope of -20 dB/decade

This will make the system *unconditionally stable*, i.e., the *stability* of the system will be *independent* of the *amount of feedback*
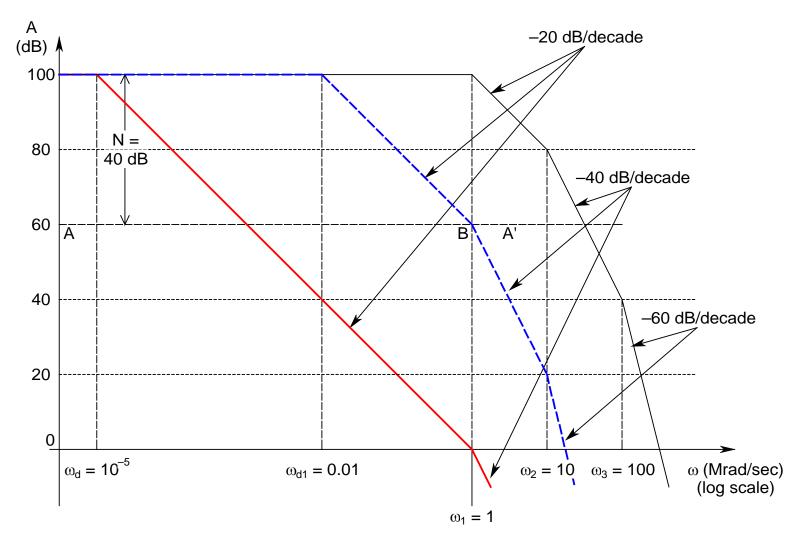
> Example:

- Assume A = 10^5 (100 dB), $\omega_1 = 1$ Mrad/sec, $\omega_2 = 10$ Mrad/sec, $\omega_3 = 100$ Mrad/sec
- Refer to the slide on the next page
- For *unconditional stability*:
 - * Refer to the *red line*
 - ❖ The *compensated transfer function* should meet the *first* pole (ω_1) of the uncompensated system at A = 0 dB with a slope of −20 dB/decade



Normal Line: Open-loop system

Red Line: Compensated system for unconditional stability
Blue Line: Compensated system with conditional stability
(till a feedback of 40 dB)

- * To construct the *compensation characteristic*, *start at* ω_1 and *go back 5 decades* (= 100/20)
- **The Example 2** Ends up at the DP frequency (ω_d) of 10 rad/sec
- Note that in between ω_d and ω_1 , the system behaves as if it has a single-pole transfer function
- ❖ The total phase of the system at ω_1 will be −135°[−90° due to the pole at ω_d , and −45° due to the pole at ω_1 (since ω_2 is ten times away from ω_1 , the phase due to ω_2 is yet to start at this point)]
- ❖ Thus, the *PM of the compensated system will be 45°*
- ❖ This implies a *stable system*, since the *PM is positive*
- * Note that if ω_2 and ω_1 were closer than 10 times, the PM would have been less than 45°, but still positive, and thus, would have retained the stable nature of the system

- ❖ Note that in order to achieve *unconditional stability* of the system, the *bandwidth* has *reduced drastically* from *1 Mrad/sec* to only *10 rad/sec*!
- **This is the most severe limitation of the DPC technique**


• For conditional stability:

- ❖ The previous compensation scheme ensured system stability for f all the way up to unity (corresponding to the amount of feedback of 100 dB, i.e., the entire output is fed back to the input)
- ❖ In some cases, it may be an *overkill*, if it is known *a priori* that the *entire output* will *NOT* be *fed back* to the *input*, *rather only a part of it*
- ❖ This is what is known as *conditional stability*
- ❖ Suppose that the *maximum amount of feedback* that the system would have is *40 dB*


- \clubsuit For this system to be *stable*, the *DP frequency need not be* at ω_d , but at a higher value
- ❖ To construct the *compensation characteristic* of this system, draw a *horizontal line* AA', corresponding to the *amount of feedback* (40 dB in our example \Rightarrow $A_f = 60$ dB)
- From the *intersection point* (B) of this *line* with the *first* pole (ω_1) , go back 2 decades (40/20), to get the new dominant pole ω_{d1} at 10 krad/sec (shown by the blue line)
- ❖ This compensation scheme protects the system from any stability issues only till a maximum feedback of 40 dB, by ensuring that from 0 to 40 dB of feedback, no other pole will be encountered, apart from ω_{dI}
- ❖ Note the *tremendous bandwidth improvement* of 1000 times (from 10 rad/sec for unconditional stability to 10 krad/sec for conditional stability till a feedback of 40 dB)

> Technique:

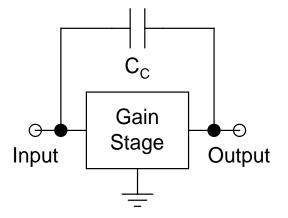- Simplest way: Attach
 a capacitor between
 the input and output
 of the gain stage
 (similar to Miller
 Capacitor)
- This capacitor is labeled as the Compensation
 Capacitor (C_C)



Schematic

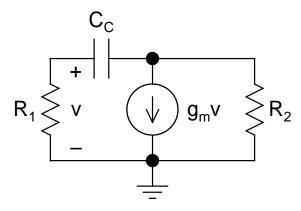

Equivalent Circuit

■ **By inspection**, the equivalent circuit can be identified as a **Three-Legged Creature**:

$$\Rightarrow R_C^0 = R_1 + R_2 + g_m R_1 R_2$$

 $R_1 = Effective total resistance on the left of <math>C_C$ $R_2 = Effective total resistance on the right of <math>C_C$

 $g_{m} = Transconductance of the gain stage$

■ Thus:

$$\omega_{\rm d} = 1 / \left(R_{\rm C}^{0} C_{\rm C} \right)$$

• From a knowledge of ω_d , we can find C_C

- Pole Zero Compensation (PZC):
 - ➤ In the *DPC technique*, we observed a *drastic* reduction in *bandwidth* after compensation
 - > PZC technique alleviates this problem to some extent
 - > Novelty of this technique:
 - It adds both a pole and a zero to the open-loop transfer function, with the added zero canceling the first pole of the uncompensated system

Consider a three-pole uncompensated transfer function:

$$A(s)\Big|_{\text{uncompensated}} = \frac{A_0}{(1+s/\omega_1)(1+s/\omega_2)(1+s/\omega_3)}$$


A₀: Low-Frequency Gain

 $\omega_1, \omega_2, \omega_3$: **Pole Frequencies** $(\omega_3 > \omega_2 > \omega_1)$

➤ After adding the network for PZC, the compensated transfer function will be:

$$A(s)\Big|_{\text{compensated}} = \frac{A_0 (1 + s/\omega_z)}{(1 + s/\omega_p)(1 + s/\omega_1)(1 + s/\omega_2)(1 + s/\omega_3)}$$

- ω_z : added zero, and ω_p : added pole
- \triangleright By design, ω_z is made equal to ω_1
 - \Rightarrow They cancel each other
- Thus, the *compensated transfer function* still has *three poles*, but the *first pole gets shifted* from ω_1 to ω_p
- The procedure for finding ω_p is the same as that for the DPC technique
- ➤ We take the *same example* as that considered for the *DPC technique*
- > Refer to the next slide

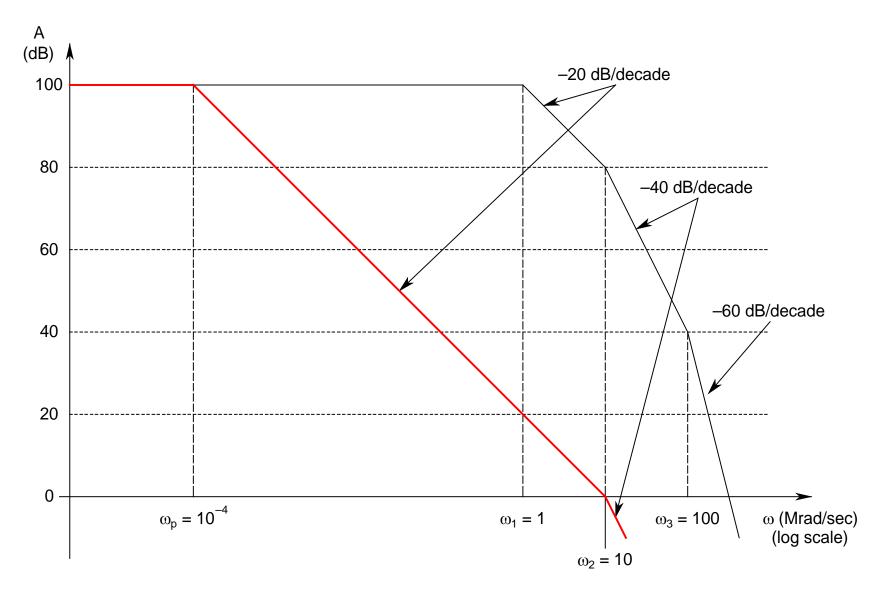

Normal Line: Open-loop system


Red Line: Compensated system for unconditional stability

- \succ Here, the *added zero* (ω_z) *cancels* the *first pole* (ω_1)
- Thus, we now start from ω_2 and go back 5 decades to find ω_p , which comes out to be 100 rad/sec (refer to the red line)
- The compensated system will be unconditionally stable with PM of 45 ° (since ω_3 is ten times away from ω_2)
- The increase in bandwidth, as compared to *DPC*, is 10 times (from 10 rad/sec to 100 rad/sec: equal to the ratio of ω_2 and ω_1)


> Technique:

- Just attach a resistor R_C
 with the compensation
 capacitor C_C
- Put this R_C-C_C network
 between the input and
 output of the gain stage
- Show that the transfer function of the compensated system is of the form:

$$A(s)\Big|_{compensated} \propto \frac{1+s(R_C-1/g_m)C_C}{1+s(R_C+R_2)C_C}$$

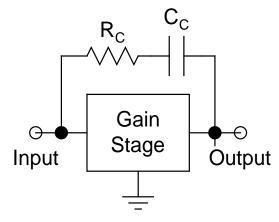

Schematic

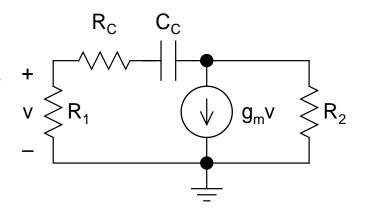

Equivalent Circuit

Here

$$\omega_{z} = 1/[(R_{C} - 1/g_{m})C_{C}]$$

 $\omega_{p} = 1/[(R_{C} + R_{2})C_{C}]$

- Choose R_C and C_C such that
 - $\bullet \omega_z$ is equal to ω_I (the first pole of the uncompensated system)
 - $\bullet \omega_p$ is as found from the example given