

BIASING

- To find the *DC operating point* (*bias point*, *Q-point*)
- Has to *precede ac analysis*, since *small-signal parameters depend on the bias point*
- For *diodes*: (I_D , V_D)
- For *BJTs*: (I_C , V_{CE})
- For *MOSFETs*: (I_D , V_{DS})
- Also, $P_D = V_D \times I_D$ (*Diodes*), $V_{CE} \times I_C$ (*BJTs*), and $V_{DS} \times I_D$ (*MOSFETs*)

- *DC power dissipated in a circuit* = (*Supply Voltage*) \times (*Supply Current*)
- Circuits may be *biased* by *single supply* (*positive/negative and ground*) or *dual supply* (*positive and negative*)
- Devices should be *properly biased* and *ideally* should be under the *best biasing* (BB)
- Also, need *voltage references* to provide *fixed DC voltages* at some *circuit nodes*

- *Two types:*

- *Discrete Stage Biasing:*

- Uses *power supplies* and *resistors* along with the *active devices*
- Used for *discrete circuits* assembled in *breadboards*
- Also known as *passive biasing*

- *IC (Integrated Circuit) Stage Biasing:*

- *Avoids resistors* as much as possible and *uses transistors* as *biasing elements*
- Used for *IC stages*
- Also known as *active biasing*

Discrete Stage Biasing: BJT

- Will be using *quick estimate* ($V_{BE} = 0.7 \text{ V}$)
- *FA mode of operation* with $V_{CE} \geq 0.2 \text{ V}$
- *Error of $\pm 5\text{-}10\%$ perfectly acceptable*
- *Common Schemes:*
 - *Fixed Resistor Bias*
 - *Emitter Feedback Bias*
 - *Collector Feedback Bias*
 - *Voltage Divider (or 4-Resistor) Bias*

- **Fixed Resistor Bias:**

- $I_B = (V_{CC} - V_{BE})/R_B$

- $I_C = \beta I_B$

- $I_E = (\beta + 1)I_B \approx I_C$


- $V_{CE} = V_{CC} - I_C R_C$

- For BB, $V_{CE} = V_{CC}/2$

- P_D (*circuit*) = $V_{CC} \times I_E$

- **Note:** *Need β to find the operating point*

 - The *simplest biasing circuit*, but has *severe β dependence*




- ***Emitter Feedback Bias:***

- *While writing KVL, never take CE or BC loops, since V_{CE} and V_{BC} are not known*

- *Consider only BE loops with $V_{BE} = 0.7\text{ V}$*

- $V_{CC} = I_B R_B + V_{BE} + I_E R_E$
 
$$\Rightarrow I_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1) R_E}$$



- $I_C = \beta I_B$
- $V_{CE} = V_{CC} - I_C R_C - I_E R_E \approx V_{CC} - I_C (R_C + R_E)$
- $P_D = V_{CC} \times I_E$
- This is a **3-element output branch**, with $V_{CE} = V_{CC}/3$ for **BB**
- **Rest $2V_{CC}/3$ drops across R_C and R_E , with the ratio typically chosen to be 2:1** (reason later!)
- Circuit is **very robust** since R_E provides **negative feedback**
- Also, has **better β insensitivity**

- **Collector Feedback Bias:**

- $V_{CC} = I_E(R_C + R_E) + I_B R_B + V_{BE}$

$$\Rightarrow I_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1)(R_C + R_E)}$$


- $I_C = \beta I_B$

- $V_{CE} = V_{CC} - I_E(R_C + R_E)$

- $P_D = V_{CC} \times I_E$

- This circuit also provides

better β insensitivity

 

- ***Voltage Divider (or 4-Resistor) Bias:***


- *The best: Extremely robust and versatile*

- If properly designed, *almost β independent*

- If $I_1 \geq 10I_B$, $I_1 \approx I_2$

$$\Rightarrow V_B \approx \frac{R_2}{R_1 + R_2} V_{CC}$$
 
$$\Rightarrow V_E = V_B - V_{BE} \text{ and } I_C \approx I_E = V_E / R_E$$



- **Example:** Let $V_{CC} = 5 \text{ V}$, $R_1 = 40 \text{ k}\Omega$, $R_2 = 10 \text{ k}\Omega$, $R_C = 2 \text{ k}\Omega$, and $R_E = 300 \Omega$
 - **Quick estimate:** Assume $\beta \geq 100$
 - $\Rightarrow V_B = 1 \text{ V}$, $V_E = 0.3 \text{ V}$, $I_C \approx I_E = 1 \text{ mA}$, $V_{CE} = 2.7 \text{ V}$, and $P_D = 5.5 \text{ mW}$
 - \Rightarrow Done! Piece of cake, isn't it?
 - $I_1 = 100 \mu\text{A}$ and $I_B \leq 10 \mu\text{A}$ (for $\beta \geq 100$):
Assumption of $I_1 \geq 10I_B$ validated
 - Actually, *as I_1 and β go down*, this *analysis becomes more and more inaccurate!*

- **Exact Analysis:**

- *Sufficiently more complicated*

- *Open the base lead and*


- Thevenize the left branch*

$$\Rightarrow V_B = \frac{R_2}{R_1 + R_2} V_{CC} = 1 \text{ V}$$

$$R_B = R_1 \parallel R_2 = 8 \text{ k}\Omega$$

- Also, $V_B = I_B R_B + V_{BE} + I_E R_E$

 
$$\Rightarrow I_B = \frac{V_B - V_{BE}}{R_B + (\beta + 1) R_E}$$



- Gives:
 - $I_B = 7.83 \mu\text{A}$, $I_C = 0.78 \text{ mA}$, and $V_{CE} = 3.2 \text{ V}$ for $\beta = 100$ (*quite off from quick estimate!*)
 - $I_B = 3.6 \mu\text{A}$, $I_C = 0.9 \text{ mA}$, and $V_{CE} = 2.93 \text{ V}$ for $\beta = 250$ (*within $\pm 10\%$ error band*)
- Thus, *as $\beta \uparrow$, accuracy of quick estimate \uparrow*
- Also, *as $R_B \downarrow$, accuracy \uparrow*
- *R_B should not be too small, since $P_D \uparrow\uparrow$*
- Thus, there are *various design constraints*

Discrete Stage Biasing: MOSFET

 - *Almost universally biased using 4-Resistor Bias*
- *Significantly more complicated than BJT biasing, since there is no quick estimate*
- *Also, body effect and CLM complicate matters*



- **No I_G** \Rightarrow *R_1 - R_2 combination provides a perfect voltage division*

$$\Rightarrow V_G = \frac{R_2}{R_1 + R_2} V_{DD}$$

- $V_S = I_D R_S$ and $V_D = V_{DD} - I_D R_D$

$$\Rightarrow I_D = \frac{k_N}{2} (V_G - I_D R_S - V_{TN})^2 \times \\ \left(1 + \lambda [V_{DD} - I_D (R_S + R_D)] \right)$$

- Also:

$$V_{\text{TN}} = V_{\text{TN0}} + \gamma \left(\sqrt{2\phi_F + I_D R_S - V_B} - \sqrt{2\phi_F} \right)$$

- *Extremely intimidating!*
- *I_D equation becomes cubic!*
- *Thus, bias calculation including all higher order effects is pretty tedious, and almost impossible for hand analysis*
- *Need to make approximations!*

- Assume $\lambda V_{DS} < 0.1$:

$$\Rightarrow I_D = \frac{k_N}{2} (V_G - I_D R_S - V_{TN})^2$$

- *Even then it's quite complicated, since V_{TN} has a square root dependence on I_D*
- *Tie B and S together* $\Rightarrow V_{SB} = 0$ and $V_{TN} = V_{TN0}$

➤ *Note that it can't be done always!*

$$\Rightarrow I_D = \frac{k_N}{2} (V_G - I_D R_S - V_{TN0})^2$$

- *Even now, it's a quadratic equation in I_D*
- *However, much easier to solve than earlier cases*
- *No further simplification possible!*
- *Solving, we will get 2 values of I_D : one will be the correct one, while the other one will be unphysical*
- *2 values of I_D will give 2 different values of V_{GS} : one $> V_{TN0}$ and the other $< V_{TN0}$*

- *Obviously, I_D for $V_{GS} < V_{TN0}$ is completely meaningless, since the device is off under that condition*
- Compute $V_{DS} [= V_{DD} - I_D(R_S + R_D)]$
 - *Should be $> V_{GT}$ (saturation mode)*
 - *For BB, $V_{DS} = V_{DD}/3$*
- $P_D = V_{DD} \times (I_D + I_1) \quad [I_1 = V_{DD}/(R_1 + R_2)]$
- *Here, no constraints on R_1 and R_2 , and they can be made as large as physically possible to reduce I_1 , and thus P_D*

IC Stage Biasing

- *Avoids resistors as much as possible*
 - *Resistors take up very large area on IC chips, which is at a premium*
- *Uses transistors as biasing elements*
 - *Much more compact than resistors, and area consumption is almost negligible as compared to resistors*
- Also known as *active biasing*

- **Parameters:**

- **Output Current I_0**

- *As per specification*

- **Output Resistance R_0**

- $R_0 = \Delta V_0 / \Delta I_0 = dV_0 / dI_0 = v_0 / i_0$ (**ac**)
- *As large as possible - ideally infinite*

- **Minimum Allowed Output Voltage $V_{0,min}$**

- *As small as possible - ideally zero*
- **Dictated by:**
 - ❖ **For BJT:** $V_{CE(min)} = V_{CE(SS)} = 0.2 \text{ V}$
 - ❖ **For MOSFET:** $V_{DS(min)} = V_{GT(min)} = 80 \text{ mV}$

- *I_0 should be independent of power supply and temperature*
 - *Temperature and Supply Independent Biasing*
- *Should use minimum number of circuit elements*
 - *Economization of space*
- *Should not affect frequency response*
- It is *almost impossible to satisfy all these constraints simultaneously*
 - *Look for optimization*

Current Sources/Sinks

- Also known as *Current Mirrors* (CM)
- Can be used for *biasing* as well as *load elements* (known as *active load*)
- Designed based on *required specifications*
- *Two sources of errors:*
 - *Systematic: Even when devices are matched*
 - *Random: When there is a random mismatch between devices*

- *Simple npn CM:*

- Q_1 has its *B and C shorted*

- *Can never saturate* ($V_{BC} = 0$)
- Known as *diode-connected BJT*


- Q_1 and Q_2 have *same V_{BE}*

- $I_{REF} = \text{Reference Current}$
 $= (V_{CC} - V_{BE})/R$

- $I_0 = \text{Output Current} = I_{C2}$

- $V_0 = \text{Output Voltage}$

 - *Variable, depends on the load connected to it*



➤ *General Analysis:*

$$I_{\text{REF}} = I_{\text{C1}} + I_{\text{B1}} + I_{\text{B2}} = I_{\text{C1}} \left(1 + \frac{1}{\beta_1} \right) + \frac{I_{\text{C2}}}{\beta_2}$$

➤ Now:

$$V_{\text{BE}} = V_{\text{T}} \ln \left(\frac{I_{\text{C2}}}{I_{\text{S2}}} \right) = V_{\text{T}} \ln \left(\frac{I_{\text{C1}}}{I_{\text{S1}}} \right)$$

$$\Rightarrow I_{\text{C2}} = K I_{\text{C1}} \quad (K = I_{\text{S2}}/I_{\text{S1}})$$

➤ Thus:

$$I_{\text{REF}} = I_{\text{C2}} \left[\frac{1}{\beta_2} + \frac{1}{K} \left(1 + \frac{1}{\beta_1} \right) \right]$$

➤ ***Finally:***

$$I_0 = I_{C2} = \frac{I_{REF}}{\frac{1}{\beta_2} + \frac{1}{K} \left(1 + \frac{1}{\beta_1} \right)}$$

- This is the ***exact expression*** of I_0 , ***without making any assumptions/approximations whatsoever***
- The ***only assumption*** so far is that we have ***neglected Early effect***, which we would include soon

➤ Now, we *make approximations/assumptions*:

1. $\beta_1 = \beta_2 = \beta$:

$$\Rightarrow I_0 = \frac{KI_{\text{REF}}}{1 + \frac{1+K}{\beta}}$$

2. $I_{S1} = I_{S2} = I_S$ ($K = 1$):


$$\Rightarrow I_0 = \frac{I_{\text{REF}}}{1 + 2/\beta}$$

3. And finally $\beta \gg 2$:

$$\Rightarrow I_0 = I_{\text{REF}} \Rightarrow \text{Current Mirror!}$$

- For this to happen, Q_1 and Q_2 must have *same β ($\gg 2$)*, and *same I_S*
- If two BJTs have *same β , I_S , and V_A* , they are known as a *matched pair*
- If $I_{S1} \neq I_{S2}$ and/or $\beta_1 \neq \beta_2$, then $I_0 \neq I_{REF}$
 - Leads to *random error (process induced)*
- If $\beta_1 = \beta_2$, but $I_{S1} \neq I_{S2}$, then $I_0 = KI_{REF}$
 - *K or $1/K$ can only be integers*
 - *I_0 and I_{REF} become integer multiples of each other*

- **Multi-Emitter BJT:**

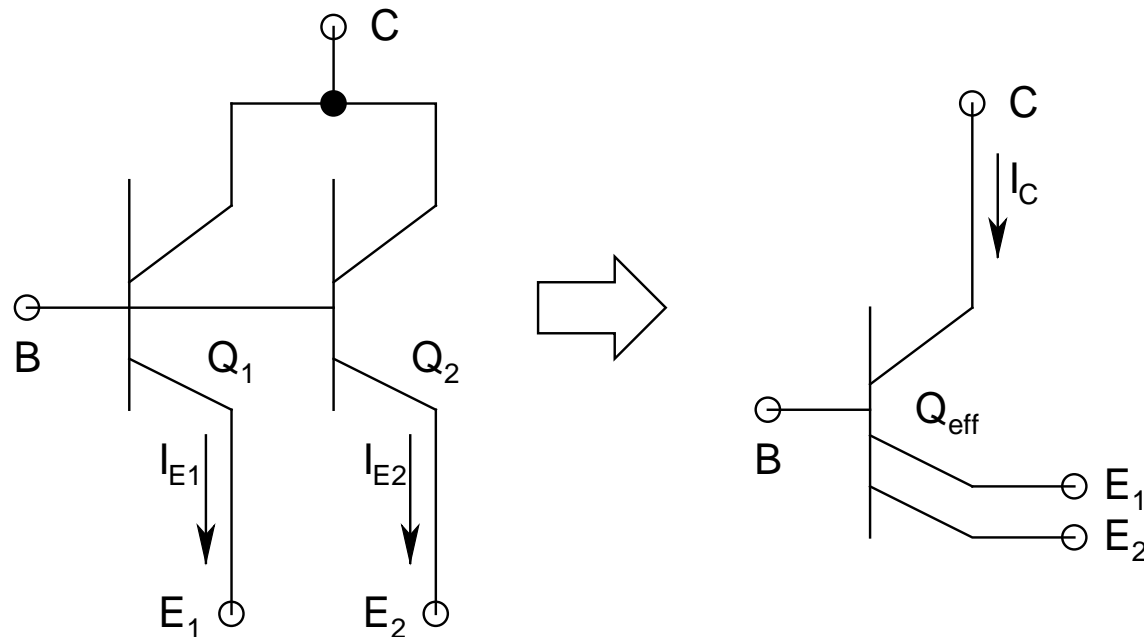

➤ $I_{S1} = I_{S2} \Rightarrow I_{E1} = I_{E2} = I_E \Rightarrow I_C \approx 2I_E$

- *This does not imply that $\alpha = 2$, since there are two emitters*

- **Systematic Error:**

- *Even if Q_1 and Q_2 are perfectly matched and $\beta \gg 2$, still I_0 may not equal I_{REF} !*


- **Recall:**

$$I_C = I_S[\exp(V_{BE}/V_T)](1 + V_{CE}/V_A)$$

- **Thus:**

$$\frac{I_{C2}}{I_{C1}} = \frac{I_0}{I_{C1}} = \frac{1 + V_{CE2}/V_A}{1 + V_{CE1}/V_A} = \frac{1 + V_0/V_A}{1 + V_{BE}/V_A}$$

 - Therefore, *$I_0 = I_{C1}$ only when $V_0 = V_{BE}$*



$$V_{0,min} = V_{CE2(SS)} = 0.2 \text{ V}$$

- *Simple npn CM:*

- Q_1 has its *B and C shorted*

- *Can never saturate* ($V_{BC} = 0$)
- Known as *diode-connected BJT*


- Q_1 and Q_2 have *same V_{BE}*

- $I_{REF} = \text{Reference Current}$
 $= (V_{CC} - V_{BE})/R$

- $I_0 = \text{Output Current} = I_{C2}$


- $V_0 = \text{Output Voltage}$

 - *Variable, depends on the load connected to it*



- **Output Resistance R_o :**

➤ First, *investigate Q_1*

 

- The *small-signal equivalent* consists simply of r_E , which is the same as that for a **diode**
- Hence the name *diode-connected BJT*

- *Algorithm to find R_0 :*
 - *Short all independent DC/ac voltage sources*
 - *Open all independent DC/ac current sources*
 - *Replace the active device by its low-frequency hybrid- π model*
 - *Excite the output terminal by a test voltage source (ac) v_t*
 - *Find the current (ac) i_t drawn from v_t*
 - *Then, $R_0 = v_t/i_t$*

- *For the complete circuit:*

- *Left part of the circuit has no source*


$$\Rightarrow v_2 = 0$$

$$\Rightarrow g_{m2}v_2 = 0$$

- Thus, $R_0 = v_t/i_t = r_{02} = V_{A2}/I_0$

- For a *good current source*, R_0 should be as large as possible (ideally infinite)

 $\Rightarrow V_{A2}$ should be as large as possible and/or I_0 should be as small as possible



- **Simple NMOS CM:**

- $V_{GS1} = V_{GS2} = V_{GS}$


- M_1 has its ***D and G***
shorted $\Rightarrow V_{GD1} = 0$

\Rightarrow ***always in saturation,***

since $V_{DS1} > V_{GT1}$

\Rightarrow Known as ***diode-***
connected MOSFET

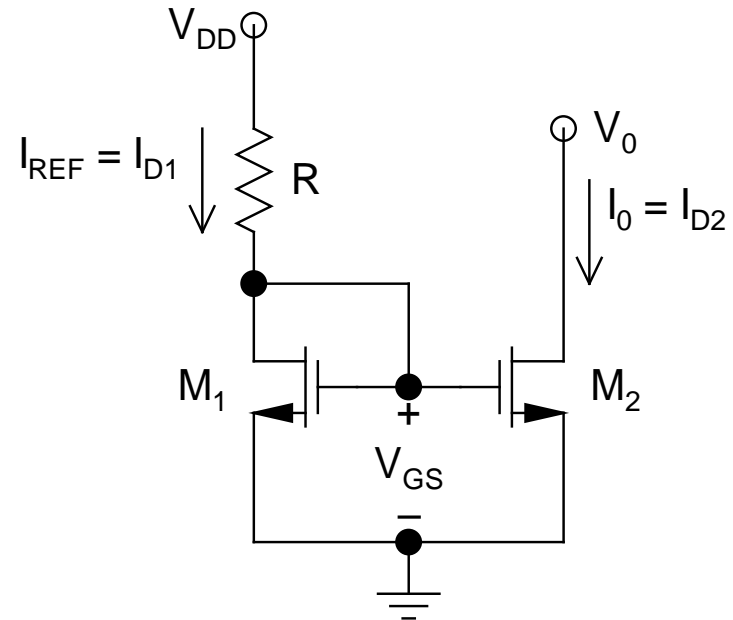- Even though $I_G = 0$, the analysis is slightly more cumbersome than simple BJT CM



- *In general, for NMOS (PMOS), the B terminal is always connected to the most negative (positive) potential available in the circuit to ensure that SB and DB junctions never get forward biased*
- *Both M_1 and M_2 have their B terminals grounded $\Rightarrow V_{SB1} = V_{SB2} = 0$*
 - $V_{TN1} = V_{TN01}$ and $V_{TN2} = V_{TN02}$
- Thus:

$$I_{REF} = I_{D1} = \frac{k'_{N1}}{2} \left(\frac{W}{L} \right)_1 (V_{GS} - V_{TN01})^2$$

- For a *given V_{DD} and R* , the equation has *2 unknowns*: I_{D1} and V_{GS}
- Need *another equation* for *unique solution*, which is the *load line equation*:
$$I_{D1} = (V_{DD} - V_{GS})/R$$
- *Simultaneous solution* of these *two equations* would give a *unique solution* for I_{D1} and V_{GS}
 - *Caution: 2 roots, out of which, one will be unphysical*
- So far, we have *neglected CLM*, which we would include soon!

➤ Now:

$$V_{GS} = V_{TN01} + \sqrt{\frac{2I_{REF}}{k'_{N1} (W/L)_1}} = V_{TN02} + \sqrt{\frac{2I_0}{k'_{N2} (W/L)_2}}$$

➤ Thus:

$$I_0 = \frac{k'_{N2} (W/L)_2}{2} \left[(V_{TN01} - V_{TN02}) + \sqrt{\frac{2I_{REF}}{k'_{N1} (W/L)_1}} \right]^2$$

➤ This is the *exact expression* of I_0 , *without making any assumptions/approximations whatsoever*

➤ Now, if $V_{TN01} = V_{TN02} = V_{TN0}$, and

$$k'_{N1} = k'_{N2} = k'_N :$$

$$I_0 = \frac{(W/L)_2}{(W/L)_1} I_{REF}$$

➤ *Very similar* to BJT CM, but with a *big exception*:

- *In BJT CM, this ratio could only be an integer*
- *In MOS CM, no such restriction exists: $(W/L)_2$ can be $>$, $=$, or $<$ $(W/L)_1 \Rightarrow$ any arbitrary current ratio can be obtained*

- Finally, if $(W/L)_2 = (W/L)_1$:
 $I_0 = I_{REF} \Rightarrow \text{Current Mirror!}$
- Two MOSFETs are deemed to constitute a *matched pair*, if they have *same* V_{TN0} , γ , ϕ_F , λ , and k'_N
 - Note that all of these are *process parameters*
 - *(W/L) is NOT a process parameter*, since it's under *designer's control*
 - *If (W/L)s are also same, then the pair is known as perfectly matched*

- **Systematic Error:**

- Even if M_1 and M_2 are *perfectly matched*, still I_0 *may not equal* I_{REF} !


- Recall:

$$I_D = \frac{k_N}{2} V_{GT}^2 (1 + \lambda V_{DS})$$

- Thus:


$$\frac{I_0}{I_{REF}} = \frac{1 + \lambda V_{DS2}}{1 + \lambda V_{DS1}} = \frac{1 + \lambda V_0}{1 + \lambda V_{GS}}$$

 - Therefore, **$I_0 = I_{REF}$ only when $V_0 = V_{GS}$**



- **Output Resistance R_o :**

➤ First, *investigate M_1*

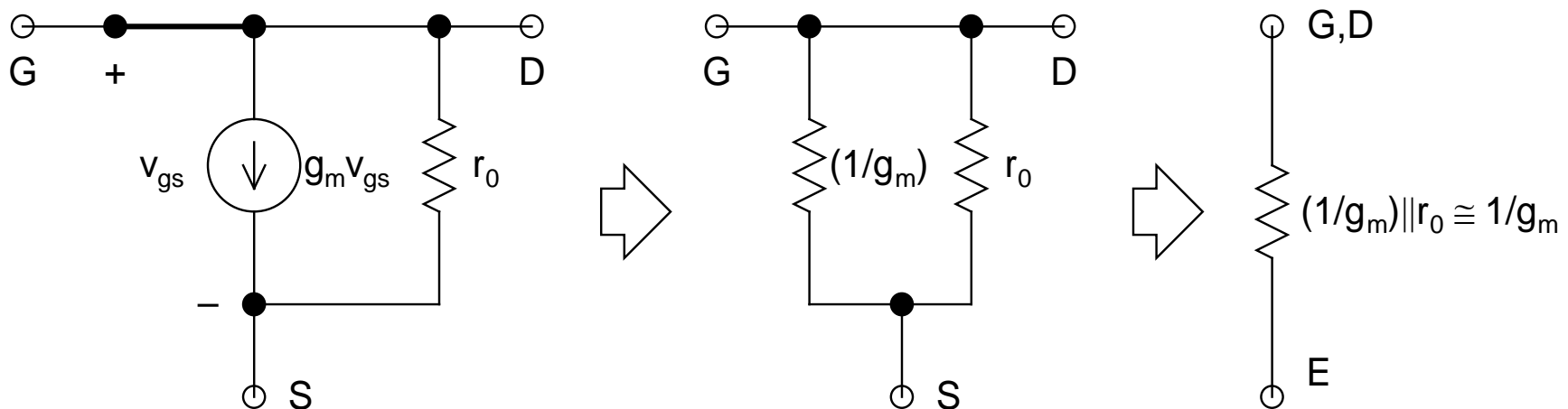

- The *small-signal equivalent* consists simply of $1/g_m$, which is similar to r_D for *diodes*
- Hence the name *diode-connected MOSFET*

- *For the complete circuit:*

- *Left part of the circuit has no source*


$$\Rightarrow v_2 = 0$$

$$\Rightarrow g_{m2}v_2 = 0$$

- Thus, $R_0 = v_t/i_t = r_{02} = 1/(\lambda I_0)$

- For a *good current source*, R_0 should be as large as possible (*ideally infinite*)

 $\Rightarrow \lambda$ should be as small as possible and/or I_0 should be as small as possible



- *Golden Rule for Calculation of R_o :*

- For a *BJT* (or *MOSFET*):

- With E (or S) *grounded*
- *No electrical connection (feedback)* between C (or D) and B (or G)
- *Looking from* the C (or D)
 - ❖ *The only resistance seen will be the output resistance of the BJT (or MOSFET)*

- ***npn Current Repeater:***


- *Uses multi-emitter BJTs*

- *Maximum number of emitters = 4*

- *All emitters tied together*

- *All Q s have same V_{BE}*

- $I_{REF} = (V_{CC} - V_{BE})/R$

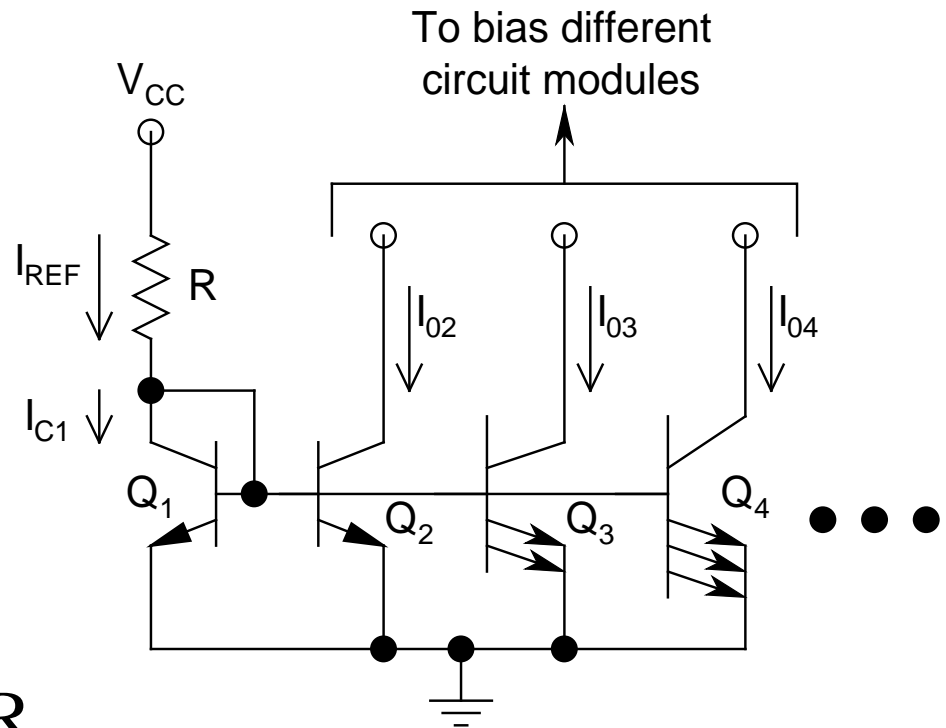


➤ *Neglecting I_B :*

$$I_{02} = I_{REF}, I_{03} = 2I_{REF}, I_{04} = 3I_{REF}, \dots$$

➤ *Limitations:*

- *Output current can never be a non-integer ratio of $I_{REF} \Rightarrow$ no arbitrary scaling possible*
- *Loading Problem:*
 - ❖ *I_{REF} not only supplies I_{C1} , but I_B s of all the Q s*
 - ❖ *As more Q s are added, I_B s will keep on increasing*
 - ❖ *I_{C1} starts to depart significantly from I_{REF}*
 - ❖ *It's not I_{REF} that's mirrored, it's I_{C1}*
 - ❖ *A reduction in I_{C1} will affect all output currents*
 - ❖ *Hence, this circuit is not very popular*

- *NMOS Current Repeater:*

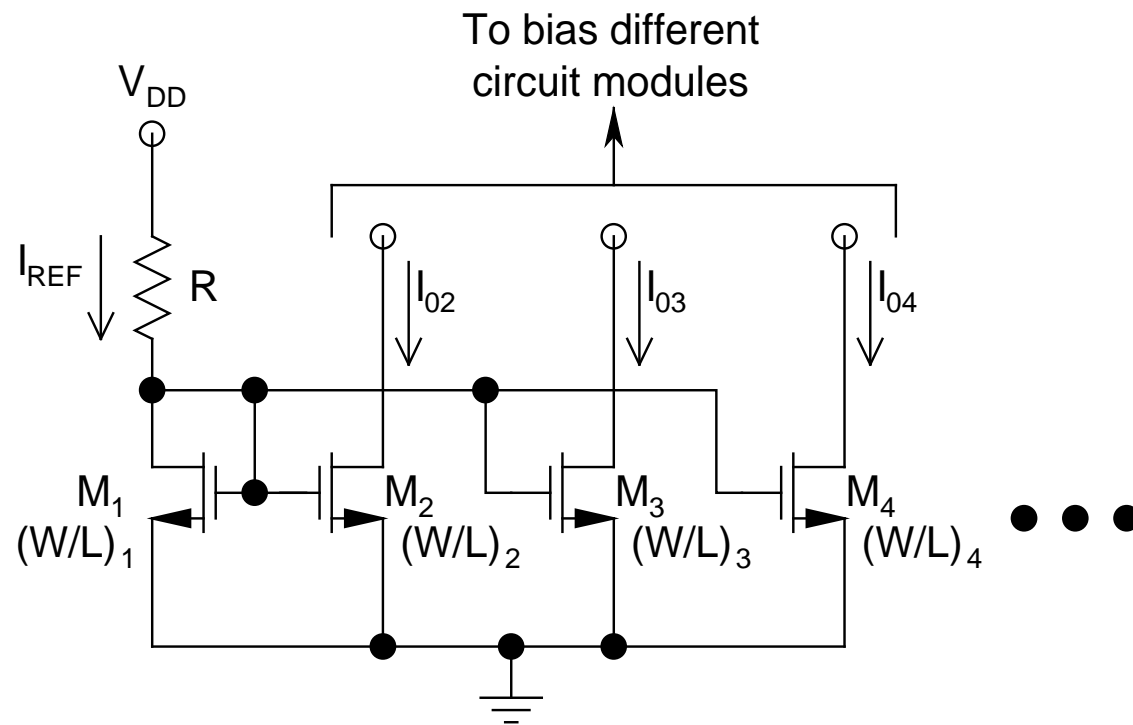

➤ $I_{\text{REF}} = I_{\text{D1}} = (V_{\text{DD}} - V_{\text{GS}})/R$

$$I_{\text{D1}} = \frac{k'_N}{2} \left(\frac{W}{L} \right)_1 V_{\text{GT}}^2 \quad (\text{assuming } \lambda V_{\text{DS}} < 0.1)$$

➤ *All M s have same V_{GS} and are matched*

$$\Rightarrow I_{\text{oi}} = \frac{(W/L)_i}{(W/L)_1} I_{\text{REF}} \quad (i = 2, 3, 4, \dots)$$

➤ *Tremendous flexibility*

❖ *Any arbitrary current ratio can be obtained*

❖ *No loading effect*

❖ *Highly popular and universal choice*

- ***More on W/L Ratio:***

- ***Generally, in technology, W/L is kept between 0.01 and 100***

- ***The ideal ratio is between 0.02 and 50***

- ***Minimum Feature Size*** (MFS):

- ***Minimum dimension that can be resolved in an IC chip***

- ❖ ***Has gone down from 10s of μm in 80s to a few nm now!***

- ***For $W/L > 1$ (or < 1), L (or W) is chosen equal to MFS***

- ***Yields minimum possible device area ($W \times L$)***

- *npn CM With Better β Insensitivity:*

- $I_{REF} = (V_{CC} - 2V_{BE})/R$

- Neglecting I_{B3} :


$$I_{C1} = I_{REF}$$

- *If Q_1 and Q_2 are matched:*

$$I_0 = I_{C2} = I_{C1} = I_{REF}$$

\Rightarrow *Simple CM*

 - *The actual advantage of the circuit lies elsewhere!*



➤ First, assume ***R_B is absent***

$$\Rightarrow I_{E3} = I_{B1} + I_{B2} = I_{C1}/\beta_1 + I_{C2}/\beta_2 = 2I_0/\beta_1$$

(assuming $\beta_1 = \beta_2$)

$$\Rightarrow I_{B3} = \frac{I_{E3}}{\beta_3 + 1} = \frac{2I_0}{\beta_1(\beta_3 + 1)}$$

$$I_{REF} = I_{C1} + I_{B3} = I_0 \left[1 + \frac{2}{\beta_1(\beta_3 + 1)} \right]$$

$$\Rightarrow I_0 = \frac{I_{REF}}{1 + \frac{2}{\beta_1(\beta_3 + 1)}}$$

➤ Now, if $\beta_1 = \beta_3 = \beta$, and $\beta \gg 1$:

$$I_0 \approx I_{\text{REF}}(1 - 2/\beta^2)$$

➤ Compare with that of simple CM:

$$I_0 \approx I_{\text{REF}}(1 - 2/\beta)$$

➤ *The advantage is obvious!*

➤ *Further Insights:*

❖ $I_{\text{E3}} (= I_{\text{B1}} + I_{\text{B2}}) \sim \text{few } 10\text{s of } \mu\text{A}$

❖ *At such a low current, β drops significantly from its nominal value*

❖ *Thus, full advantage of the circuit can't be exploited*

- *Here comes the role of R_B :*
- *It drains a constant current ($= V_{BE}/R_B$), which gets added to ($I_{B1} + I_{B2}$), and **boosts** I_{E3} (and, thus, I_{C3})*
 - *Thus, β_3 gets pulled up to its nominal value*
 - *This resistor has a special name: **Keep Alive**, since it keeps Q_3 alive!*
- *However, it creates some issues as well:*
- *Additional power drain due to the additional current flowing through R_B*
 - *If $I_{E3} \uparrow$, so would I_{B3}*
 $\Rightarrow I_{C1}$ may depart from I_{REF}
 - *Design optimization needed*

➤ *Now, for R_0 :*

- *Looking at C_2*
- *E_2 grounded*
- *No connection between C_2 and B_2 (no feedback)*
- *Therefore, by inspection:*

$$R_0 = r_{02} = V_{A2}/I_0$$

➤ *Also, by inspection:*

$$V_{0,\min} = V_{CE2}(\text{SS}) = 0.2 \text{ V}$$

➤ *There is no MOS counterpart for this circuit for obvious reasons!*

- ***npn Ratioed CM:***

- *Q_1 - Q_2 matched pair*

- *Neglecting all I_B , $I_{E1} = I_{C1} = I_{REF}$, and $I_{E2} = I_{C2} = I_0$*


- $I_{REF} = (V_{CC} - 2V_{BE})/(R + R_1)$

- ***KVL around Q_1 - Q_2 BE loop:***

$$V_{BE1} + I_{REF}R_1 = V_{BE2} + I_0R_2$$

$$\Rightarrow I_0 = (I_{REF}R_1 + \Delta V_{BE})/R_2$$
 
$$\begin{aligned}\Delta V_{BE} &= V_{BE1} - V_{BE2} \\ &= V_T \ln(I_{REF}/I_0)\end{aligned}$$



➤ *Note the \ln dependence:*

- *For $I_{REF}/I_0 = 2$, $\Delta V_{BE} = 18 \text{ mV}$*

- *For $I_{REF}/I_0 = 10$, $\Delta V_{BE} = 60 \text{ mV}$*

$\Rightarrow \Delta V_{BE}$ can be neglected if $I_{REF}R_1 > 10\Delta V_{BE}$

$\Rightarrow I_0 = (R_1/R_2)I_{REF}$ (*Ratioed Mirror*)

➤ *Thus, by tinkering R_1 and R_2 , any ratio between I_0 and I_{REF} can be obtained*

- *Tremendous advantage*


- ❖ *Widely used*

➤ *By inspection:*

$$V_{0,\min} = V_{CE2}(\text{SS}) + I_0 R_2 = 0.2 + I_0 R_2$$

➤ **Calculation of R_0 :**

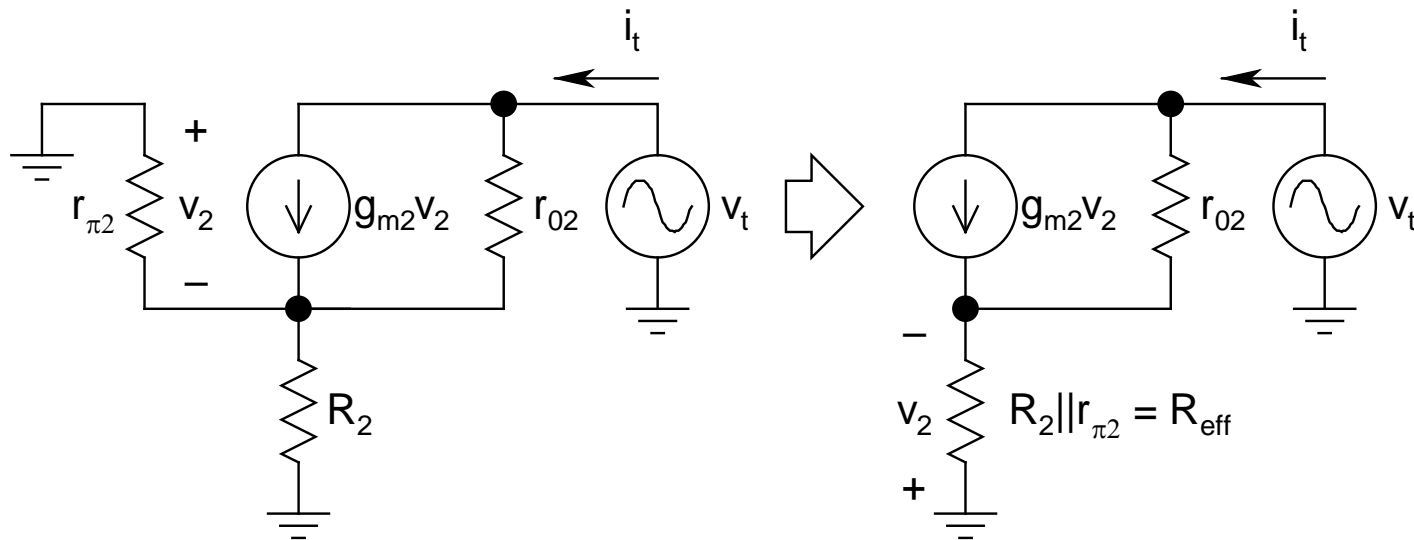- *Golden Rule can't be used since emitter of Q_2 is not grounded (R_2 present there)*
- *Needs analysis*
 - ⇒ *Leads to a module that is frequently encountered*
- *Base of Q_1 - Q_2 at a fixed DC potential ⇒ **ac ground***



$$\begin{aligned} i_t &= g_{m2} v_2 + (v_t + v_2)/r_{02} \\ &= v_t/r_{02} + (g_{m2} + 1/r_{02}) v_2 \simeq v_t/r_{02} + g_{m2} v_2 \end{aligned}$$

$$v_2 = -i_t R_{\text{eff}}$$

$$\Rightarrow i_t = v_t/r_{02} - g_{m2} R_{\text{eff}} i_t$$

$$\Rightarrow R_0 = v_t/i_t = r_{02}(1 + g_{m2} R_{\text{eff}})$$

➤ This is a ***Golden Equation***, which would be *used frequently*

- *Carefully note the topology that produces this result*

➤ ***Exercise***: *Reverse v_2 and show that the expression for R_0 remains invariant*

- If $r_{\pi 2} \gg R_2$, $R_0 = r_{02}(1 + g_{m2}R_2)$
- If $R_2 \gg r_{\pi 2}$, $R_0 \approx \beta_2 r_{02}$ (since $\beta = g_m r_{\pi} \gg 1$)
- *Under the second condition, the circuit produces enormously large value of $R_0 \sim 10s$ of $M\Omega$ or greater*
 - *Almost approaches a constant current source!*
- *It's good to check the relative values of R_2 and $r_{\pi 2}$ before using either of the equations*
- *This circuit does not have any MOS counterpart for obvious reasons!*

- *Cascode Current Source:*
 - *The best and most widely used*
 - *Almost universal choice for biasing IC stages*
 - *Produces extremely high R_0*
 - *Original cascode needs higher values of $V_{0,min}$*
 - *Modified cascode gets rid of this problem and pushes $V_{0,min}$ down*
 - *The topology is basically two simple CMs stacked one upon the other*
 - *Both npn and NMOS implementations exist*

- *npn Cascode:*

- *All Q s are perfectly matched*


- *Neglecting I_B and V_A :*

$$I_0 = I_{REF} = (V_{CC} - 2V_{BE})/R$$

- Show that if *I_B can't be neglected*, but *all Q s have same β* :

$$I_0 = \frac{I_{REF}}{1 + (4\beta + 2)/\beta^2}$$

 - Thus, *β immunity is not that pronounced*



➤ *All Q s operate with the same V_{BE}*

$$\Rightarrow V_{B1} = V_{B2} = V_{BE}, V_{B3} = V_{B4} = 2V_{BE}$$

$$\Rightarrow V_{E4} = V_{C2} = V_{BE}$$

$$\Rightarrow V_{BE2} = V_{CE2}$$


$$\Rightarrow Q_2 \text{ can never saturate, but } Q_4 \text{ can!}$$

$$\Rightarrow V_{0,\min} = V_{BE} + V_{CE4}(\text{SS}) = 0.7 + 0.2 = 0.9 \text{ V}$$

➤ *The output voltage swing is sacrificed quite a bit!*

➤ *However, the main advantage of this circuit is enormously large R_0*

➤ *Calculation of R_o :*

 

Exact Equivalent

- *Q_1 and Q_3 diode-connected $\Rightarrow r_{E1}$ and r_{E3}*

- Note that to a *first-order estimate*, *bases of Q_1 - Q_2 and Q_3 - Q_4* can be considered to be at a *fixed DC potential*, and thus, *ac ground*

$$\Rightarrow v_2 = 0 \Rightarrow g_{m2}v_2 = 0$$

\Rightarrow Leads to the *simplified equivalent* (looks familiar?)

- *By inspection:*


$$R_0 \approx r_{o4}(1 + g_{m4}r_{\pi4})$$

$$\approx \beta_4 r_{o4}$$

(*assuming $r_{o2} \gg r_{\pi4}$*)


- *Actual analysis gives:*
 
$$R_0 = \beta_4 r_{o4}/2 \text{ (large error!)}$$



Simplified Equivalent

➤ *Calculation of R_o :*

 


Exact Equivalent

- *Q_1 and Q_3 diode-connected $\Rightarrow r_{E1}$ and r_{E3}*

➤ ***Simplification:***

 - *Bases of Q_1 - Q_2 and Q_3 - Q_4 can be approximated to be at ac ground (a first-order estimate)*




Equivalent after First-Order Simplification

- $\Rightarrow v_2 = 0 \Rightarrow g_{m2}v_2 = 0$
 \Rightarrow Leads to the *simplified equivalent* (looks familiar?)

- *By inspection:*
 $R_0 \approx r_{o4}(1 + g_{m4}r_{\pi4})$
 $\approx \beta_4 r_{o4}$
(assuming $r_{o2} \gg r_{\pi4}$)

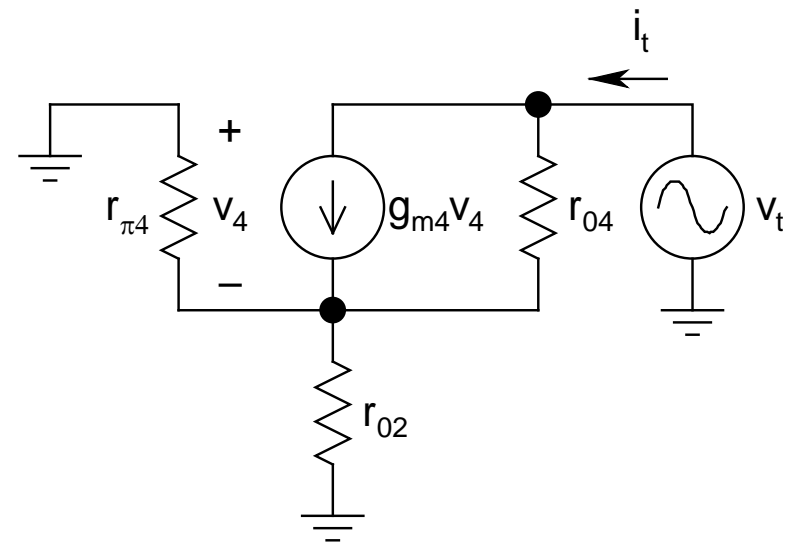
- *Actual analysis gives:*
 $R_0 = \beta_4 r_{o4}/2$ (*large error!*)



Simplified Equivalent

- **NMOS Cascode:**

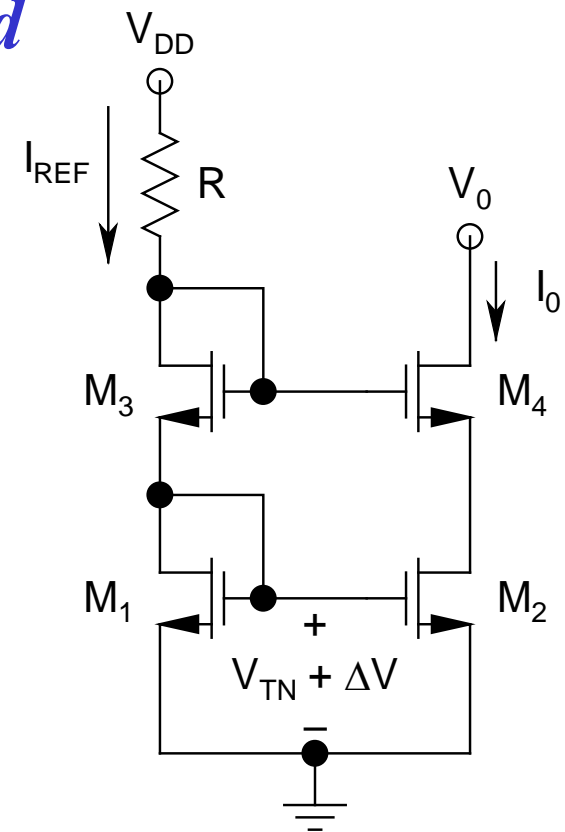- *All Ms perfectly matched*
- *All bodies connected to ground*
 - *M_1 - M_2 does not have body effect, but M_3 - M_4 does!*
 - *Makes hand analysis quite tedious*
 - ⇒ *Neglect body effect*
- *All Ms operate with same V_{GS}*
- Define $\Delta V = V_{GS} - V_{TN} = V_{GT}$
 - $\Delta V =$ *Gate Overdrive*



➤ *The reference current:*

$$I_{\text{REF}} = \frac{V_{\text{DD}} - 2V_{\text{GS}}}{R} = \frac{k_{\text{N}}}{2} V_{\text{GT}}^2 \quad (\text{neglecting } \lambda)$$

➤ *V_{GS} and I_{REF} can be found $\Rightarrow I_0 = I_{\text{REF}}$*

➤ $V_{\text{G1}} = V_{\text{G2}} = V_{\text{GS}} = V_{\text{TN}} + \Delta V$

➤ $V_{\text{G3}} = V_{\text{G4}} = 2V_{\text{GS}} = 2(V_{\text{TN}} + \Delta V)$


➤ $V_{\text{S4}} = V_{\text{D2}} = V_{\text{TN}} + \Delta V$

$$\Rightarrow V_{\text{GS2}} = V_{\text{DS2}}$$


$\Rightarrow M_2$ *can never enter linear region*

$$\Rightarrow V_{0,\text{min}} = V_{\text{DS2}} + V_{\text{DS4}} = V_{\text{TN}} + 2\Delta V$$

- *This can be quite significant, since V_{TN} is added to ΔV*
 - *Assuming $\Delta V \sim 0.1\text{ V}$ and $V_{TN} \sim 0.7\text{ V}$, $V_{0,min} \sim 0.8\text{ V}$, which is very large*
 - *This is one of the drawbacks of this simple cascode circuit (modified cascode doesn't have this problem)*
- *If V_0 drops below $(V_{TN} + 2\Delta V)$, first M_4 enters linear region, and circuit performance starts to get affected*
- *For further drop in V_0 , M_2 also enters linear region, and the current mirror collapses!*

 

➤ *Calculation of R_o :*

 

Exact Equivalent

- *M_1 and M_3 diode-connected* $\Rightarrow 1/g_{m1}$ and $1/g_{m3}$

- *The left part of the circuit has no source*

$$\Rightarrow v_2 = 0 \Rightarrow g_{m2}v_2 = 0$$


\Rightarrow *Leads to the simplified equivalent* (now should look very familiar!)

- *By inspection:*

$$R_0 \approx r_{o4}(1 + g_{m4}r_{o2})$$

$$\approx g_{m4}r_{o2}r_{o4}$$

- *Can be huge!*

 

Simplified Equivalent


- **Double Cascode:**

- *Can be implemented in both BJT & MOS*
- *In npn Double Cascode, another pair Q_5 - Q_6 stacked upon Q_3 - Q_4*
 - *Find $V_{0,min}$ and R_0*
- *In NMOS Double Cascode, another pair M_5 - M_6 stacked upon M_3 - M_4*
 - *Find $V_{0,min}$*
 - $R_0 \approx g_{m6}r_{o6}R_0$ ($R_0 \approx g_{m4}r_{o2}r_{o4}$)
- *Hence, show that double cascode in BJT offers absolutely no advantage in terms of R_0*

- *Low Value Current Source:*
 - *Current thrust: Low-power circuits*
⇒ *Increase in battery life*
 - *If bias current can be reduced from mA to μA , for the same power supply voltage, power drawn reduces by three orders of magnitude!*
 - *Normal CMs can also produce bias current in μA range, however, the required resistance will be huge ⇒ uneconomical for ICs*
 - *Most common: Widlar Current Source*
 - *After its inventor Bob Widlar (father of op-amp)*

- **Widlar Current Source:**

 - *Q_1 - Q_2 matched pair*
- $I_{REF} = (V_{CC} - V_{BE1})/R_1$
- If $I_0 = I_{REF}$, then $V_{BE1} = V_{BE2}$
 - *No drop across R_2 !*
$$\Rightarrow I_0 \neq I_{REF}$$
- *Actually, the difference between V_{BE1} and V_{BE2} drops across R_2*



- *KVL around Q_1 - Q_2 BE loop:*

$$V_{BE1} = V_{BE2} + I_0 R_2$$

$$\Rightarrow I_0 = \frac{V_{BE1} - V_{BE2}}{R_2} = \frac{V_T}{R_2} \ln \left(\frac{I_{REF}}{I_0} \right)$$

(since $I_{S1} = I_{S2}$)

- *Transcendental equation in I_0*
- *If I_0 is known, finding R_2 is absolutely easy!*
- On the other hand, *if R_2 is given, to find I_0 , need to iterate, but the solution will converge rapidly (Why?)*

- *The \ln function compresses a large difference between I_{REF} and I_0 into a small range*
 - For $I_{REF} \sim \text{mA}$, $I_0 \sim \mu\text{A}$, with $R_1 \sim \text{few k}\Omega\text{s}$ and $R_2 \sim \text{few } 10\text{s of k}\Omega$
 \Rightarrow *Significant flexibility!*
- $V_{0,\min} = V_{CE2}(\text{SS}) + I_0 R_2$
 \sim *0.3-0.4 V for practical values of I_0 and R_2*
- *R_0 can be obtained by sheer inspection of the circuit by noting that the base of Q_2 is approximately at ac ground*
- Also, $r_{\pi 2} \gg R_2$ (*Why?*)

➤ Thus,

$$R_0 \approx r_{02}(1 + g_{m2}R_2)$$

➤ **Note:** *To approximate this as $g_{m2}r_{02}R_2$, first make sure that $g_{m2}R_2 \gg 1$ (may not be!)*

➤ **Actual expression:**

$$R_0 \approx r_{02}(1 + g_{m2}R_{\text{eff}}) \text{ with } R_{\text{eff}} = R_2 \parallel r_{\pi 2}$$

➤ *During further simplification, always check the validity of your assumption/approximation*

▪ *Otherwise it may lead to large errors!*

➤ *Counterpart of this circuit in MOS technology does not exist (Why?)*


DC Voltage References

- *Along with current sources/sinks, also need stable and precise DC voltage references*
- *Provides DC bias voltages at specific points of the circuit*
- *Should be independent of power supply and temperature*
- *Can range from $-ve$ to $+ve$ power supplies*
- *On-Chip: Generated within the chip itself*


- *In ICs, diodes are not fabricated as such*
 - *BJTs/MOSFETs are used as diodes by shorting their B/G and C/D terminals*
- *Various Voltage References:*
 - *Single Diode Reference*
 - *Multiple Diode Reference*
 - *V_{BE} (or V_D) Multiplier*
 - *Saturated Transistor*
 - *NMOS Voltage Reference*

- ***Single Diode Reference:***

 - I_{REF} : ***DC Bias Current***
- ***Creates a voltage drop of V_D (or V_{BE}) across the diode of $\sim 0.7\text{ V}$***
- ***Known as V_{BE} (or V_D) Reference***
- ***Precision quite poor***
- ***Thermal tracking poor***




 - **Multiple Diode Reference:**
 - *Putting multiple diodes in series*
 - *DC bias current I_{REF} pushed through them*
 - *Each diode creates a drop of V_D across it*
 - *Has same problems as Single Diode Reference*
 - *Note: n can only be an integer*



- **V_{BE} (or V_D) Multiplier Circuit:**

 - *Previous two circuits provide $V_0 = nV_D$, with n being an integer ≥ 1*
- *For any arbitrary value of n (≥ 1), this circuit becomes useful*
- *Immensely popular because of its simplicity and effectiveness*
- *Biased by a DC current source I_{REF}*



➤ *Neglecting base current:*

$$V_{BE} = \frac{R_2}{R_1 + R_2} V_0$$

$$\Rightarrow V_0 = \left(1 + \frac{R_1}{R_2}\right) V_{BE}$$

$\Rightarrow V_{BE}$ *Multiplier* with *multiplication factor* $(1 + R_1/R_2)$

➤ *Any arbitrary ratio of R_1 and R_2 can be used, but the multiplication factor is always ≥ 1*

- *Least possible $V_0 = V_{BE}$ [$R_1 = 0$ (short-circuit) and $R_2 \rightarrow \infty$ (open-circuit)]*
 \Rightarrow *Diode-Connected BJT*
- *Has excellent thermal tracking, since TC_F of R_1 and R_2 cancel each other, but the TC_F of V_{BE} remains*
- *So far, we have got voltage references having $V_0 \geq V_{BE}$*
- *How to have a voltage reference having $V_0 < V_{BE}$?*

- ***Saturated Transistor:***

- *Neglecting base current:*

$$V_0 = V_{BE} - I_{REF}R$$


- *Note: V_0 is actually V_{CE} ,*

- which is $< V_{BE}$*


- \Rightarrow *Q saturated*

- \Rightarrow *Analysis highly approximate,
since base current can't be
neglected in saturation*

 - *Typical range of $V_0 \sim 0.2-0.7 V$*



 - ***NMOS Voltage Reference:***
 - *Highly popular due to its simplicity and effectiveness*
 - *Can generate n voltage references from $(n + 1)$ MOSFETs*
 - *All MOSFETs diode-connected*
⇒ *Always saturated*
 - *No resistors needed*
 - *All bodies connected to ground*



- *Only for M_1* , $V_{TN1} = V_{TN0}$
- *All other MOSFETs will have body effect*,
e.g., $V_{TN2} = V_{TN0} + \gamma \left(\sqrt{2\phi_F + V_{01}} - \sqrt{2\phi_F} \right)$
- Generally, *all λ s also same*, but *aspect ratios are different*
- $V_{01}, V_{02}, \dots, V_{0n}$ are the *needed reference taps*
- $V_{GS1} = V_{DS1} = V_{01}$, $V_{GS2} = V_{DS2} = V_{02} - V_{01}$,
 $V_{GS3} = V_{DS3} = V_{03} - V_{02}, \dots$
- $V_{SB1} = 0$, $V_{SB2} = V_{01}$, $V_{SB3} = V_{02}, \dots$
- *Same DC current I_{REF} flows through all MOSFETs*

- Assuming that *all MOSFETs* have *same* λ and *same* k'_N :

$$\begin{aligned} I_{REF} &= \frac{k'_N}{2} \left(\frac{W}{L} \right)_1 (V_{01} - V_{TN1})^2 (1 + \lambda V_{01}) \\ &= \frac{k'_N}{2} \left(\frac{W}{L} \right)_2 (V_{02} - V_{01} - V_{TN2})^2 [1 + \lambda (V_{02} - V_{01})] \end{aligned}$$

...

- *First I_{REF} needs to be found by ensuring that the circuit dissipates least DC power*
- *Then, all (W/L) s can be calculated*

- *Choice depends on several design paradigms*
- $P_D = V_{DD} \times I_{REF}$
 \Rightarrow *For minimum P_D , I_{REF} should be minimum*
- *Need to pick up a reference MOSFET to start the design process*
- *Area of a MOSFET* $= W \times L$
- *For minimum area, $W = L = MFS$*
 - ***MFS**: Minimum Feature Size (that is allowed by the technology)*
- Pick the *reference MOSFET* by choosing its $(W/L) = 1$, and having the *least* $V_{GT}^2 (1 + \lambda V_{DS})$

- *This will yield minimum P_D*
- *Once the reference MOSFET is chosen, I_{REF} becomes known, and (W/L) s of all other MOSFETs can be calculated*
- *Total area taken up by the circuit:*

$$\sum_n (W \times L)_n$$
- *Care: No dimension can be $< MFS$*
- *Then what to do if $(W/L) < 1$?*