

In the BiMOS (combination of BJT and MOS) cascode current source shown in the figure, M_1 - M_2 is a *perfectly matched pair*, and so is Q_3 - Q_4 .

Neglect DC base current, and assume that $\lambda V_{DS} \ll 1$.

Data: for M₁-M₂: $V_{TN0} = 0.7$ V, $k'_N = 40$ μ A/V², $\gamma = 0.4$ V^{1/2}, $2\phi_F = 0.6$ V;

for Q₃-Q₄: $\beta = 100$, $V_A = 100$ V.

- Show that $R_0 \approx \beta r_{04}$. Clearly highlight all the assumptions made in arriving at this result. 5
- Choose the values of I_{REF} , R , and (W/L) of M_1 - M_2 , in order to have R_0 and $V_{0,min}$ of $1\text{ G}\Omega$ and 1 V respectively. 7
- What is the most critical parameter and what should be its value for the assumption made in the derivation of R_0 [part a)] to hold? An error band of 5% is acceptable. 3

