

## DC Biasing of the Main Branches

- $Q_{10}$ - $Q_{11}$ - $R_4$  *combination* is a *Widlar current source*:

$$\Rightarrow V_T \ln(I_{REF}/I_{C10}) = I_{C10} R_4$$

$$\Rightarrow I_{C10} = (V_T/R_4) \ln(I_{REF}/I_{C10})$$

*Solution* of this *transcendental equation*:

$$I_{C10} = 19 \mu A = I_{C9}$$

- $Q_{12}$ - $Q_{13}$  another *mirror*:


$$\Rightarrow I_{C13} = I_{C12} = I_{REF} = 733.3 \mu A$$

- $Q_{13}$  is a *special transistor*, having *split collectors* (A and B), with their *area ratios* 1:3

$$\Rightarrow I_{C13A} = 183.3 \mu A \text{ and } I_{C13B} = 550 \mu A$$

➤ **DC Biasing of the Input Stage:**

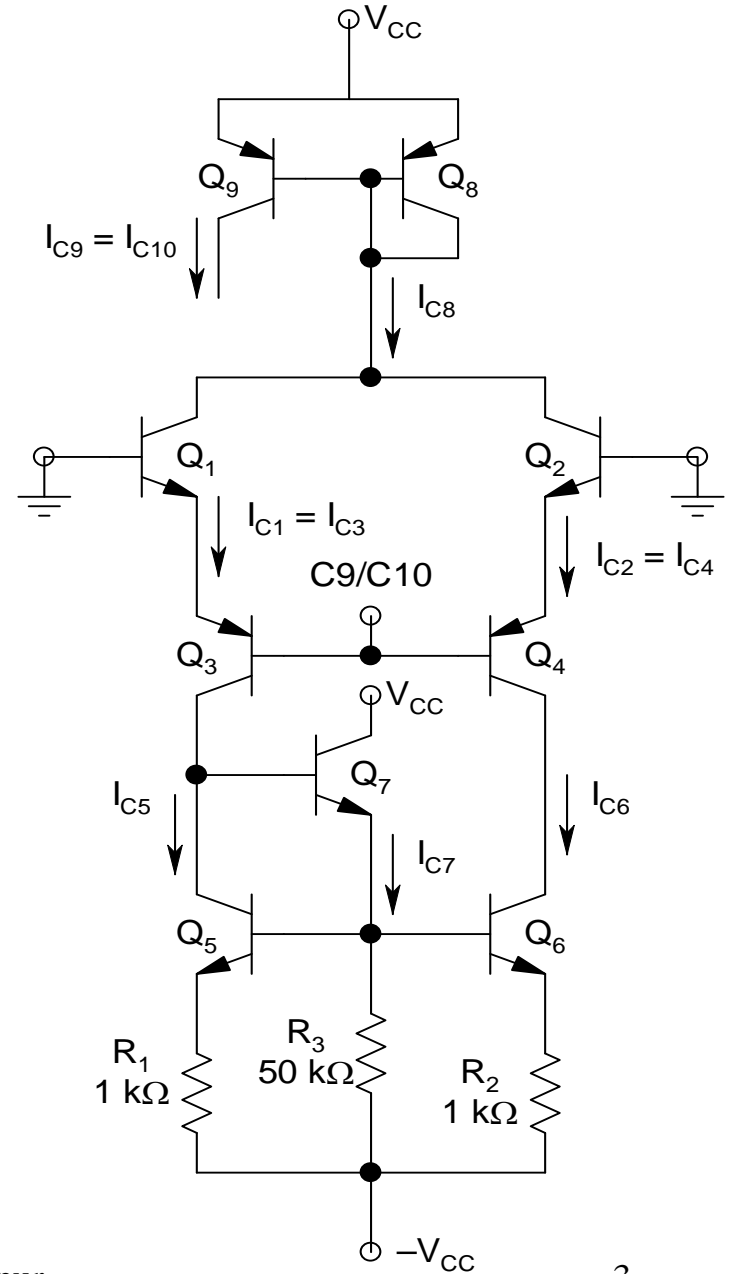- $Q_8$ - $Q_9$  form a *current mirror*:  
 $\Rightarrow I_{C8} = I_{C9} = I_{C10} = 19 \mu A$
- This is the *bias current* for the *DA*:  
 $\Rightarrow I_{C1} = I_{C2} = I_{C3} = I_{C4}$   
 $= I_{C5} = I_{C6} = I_{C8}/2$   
 $= 9.5 \mu A$   
 $I_{C5} = I_{C6}$  (*since  $R_1 = R_2$* )



- *Calculation* of  $I_{C7}$  little more *involved*
  - ❖ *Neglecting base currents*,  $I_{C7} \approx I_{R3}$
  - ❖ Assuming  $I_{S5} = 1 \text{ fA}$ :
$$V_{BE5} = V_T \ln(I_{C5}/I_{S5}) = 597.3 \text{ mV}$$
  - ❖ The *drop* across  $R_3$ :
$$V_{R3} = V_{BE5} + I_{C5}R_1 = 606.8 \text{ mV}$$
$$\Rightarrow I_{C7} \approx I_{R3} = V_{R3}/R_3 = 12.1 \text{ } \mu\text{A}$$

## ➤ *DC Biasing of the Gain Stage:*


- $I_{C17} = I_{C13B} = 550 \mu\text{A}$
- This is a *large current* and the *base current may not be negligible*

- Assuming  $\beta_{17} = 200$ :  
 $I_{B17} = I_{C17} / \beta_{17} = 2.75 \mu\text{A}$
- Assuming  $I_{S17} = 1 \text{ fA}$ , the *base voltage* of  $Q_{17}$ , *w.r.t.*

*the negative power supply* ( $-V_{CC}$ ):

$$V_{B17} \text{ (w.r.t. } -V_{CC}) \approx V_T \ln(I_{C17}/I_{S17}) + I_{C17} R_8$$

$$= 757.9 \text{ mV}$$

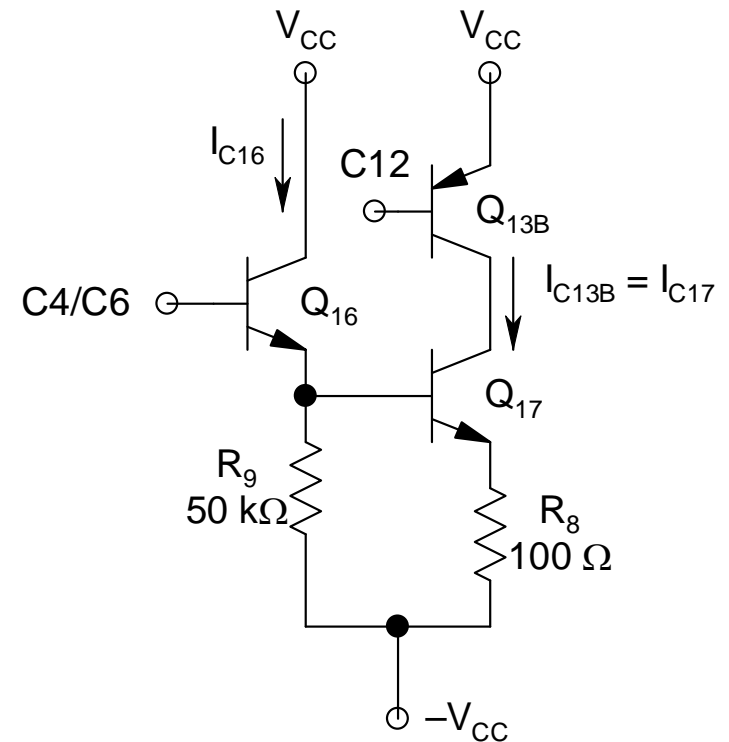


- Thus:

$$I_{R9} = V_{B17}/R_9 \\ = 15.16 \mu A$$

$$\Rightarrow I_{C16} = I_{R9} + I_{B17} \\ = 17.9 \mu A$$

➤ *Finally, the output stage:*

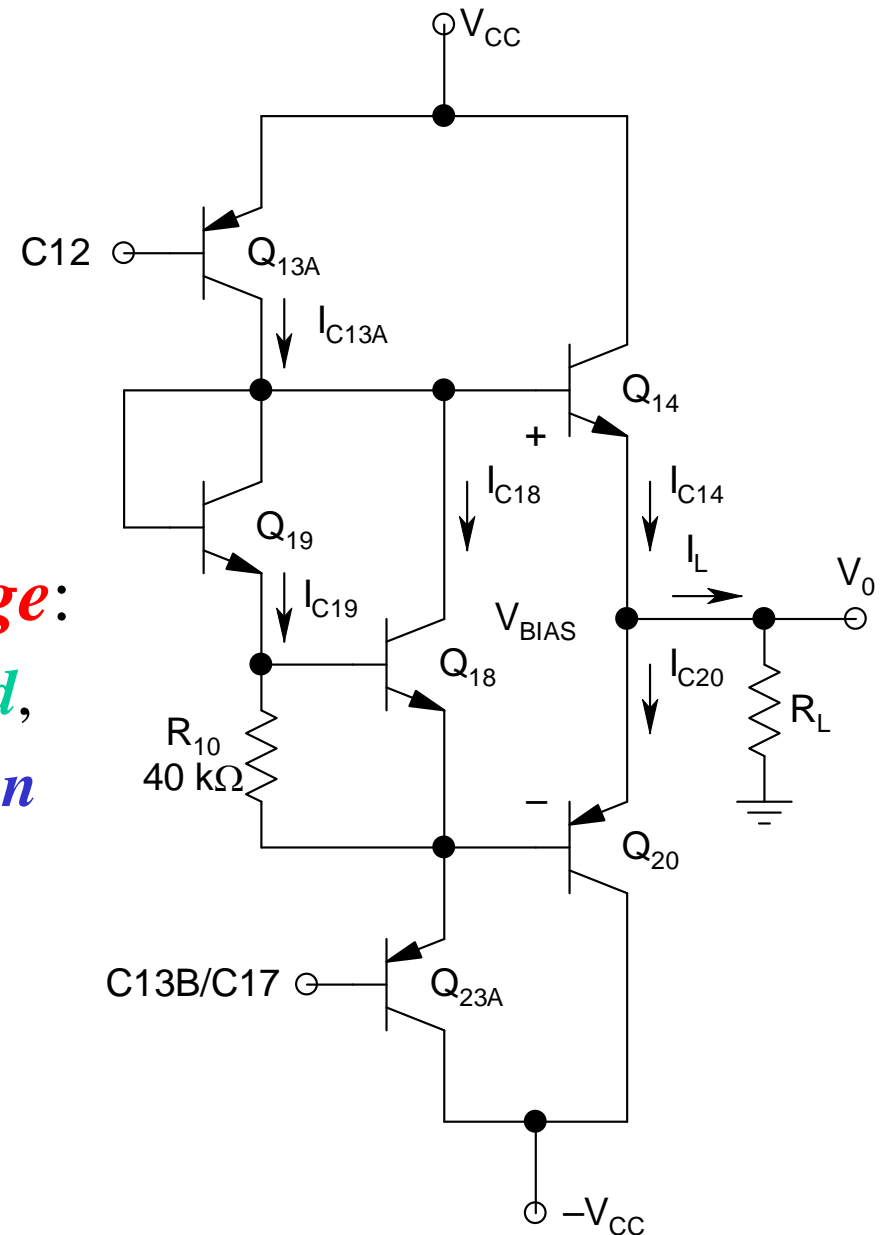- $Q_{15}$ - $Q_{21}$ - $R_6$ - $R_7$  *neglected*, since these are *protection devices*, and *come into play* only during *accidental short-circuiting of the output*



- To find the *idling current*,  $R_L$  is *removed*, thus making  $I_L = 0$   
 $\Rightarrow$  *Standby (Idling) Current*  $= I_{C14} = I_{C20}$
- $Q_{18}$ - $Q_{19}$ - $R_{10}$  is an *extremely cleverly and innovatively designed block*
  - ❖ It produces a *prebias voltage*  $V_{BIAS}$  (*close to  $2V_\gamma$* ) *between the bases of  $Q_{14}$  and  $Q_{20}$*
  - ❖ At the same time, it *reduces the standby power dissipation of the output branch*
- $I_{C13A} = 183.3 \mu A$ , and *splits* into  $Q_{18}$ - $Q_{19}$  combination
- Assuming  $V_{BE18} = 0.7 V$  and for the time being, *neglecting*  $I_{B18}$ :  

$$I_{C19} \approx I_{R10} = V_{BE18}/R_{10} = 17.5 \mu A$$

- Thus:

$$I_{C18} = I_{C13A} - I_{C19} = 165.8 \mu A \text{ (*neglecting } I_{B19}*)}$$

- Since  $I_{C18}$  is *pretty high*, we need to now *fine tune* our analysis by *including  $I_{B18}$*

- Assuming  $I_{S18} = 1 \text{ fA}$  and  $\beta = 200$ :

$$\begin{aligned} I_{C19} &= I_{B18} + I_{R10} = I_{C18}/\beta_{18} + (V_T/R_{10})\ln(I_{C18}/I_{S18}) \\ &= 17.6 \mu A \end{aligned}$$

- This is *sufficiently close* to our *initial estimate* of  $17.5 \mu A$

- Thus:

$$I_{C18} = I_{C13A} - I_{C19} = 165.7 \mu A$$

which is *almost same* as our *original estimate*



- $V_{\text{BIAS}} = V_{\text{BE18}} + V_{\text{BE19}} = V_{\text{BE14}} + V_{\text{EB20}}$   
 $\Rightarrow V_T \ln(I_{\text{C18}}/I_{\text{S18}}) + V_T \ln(I_{\text{C19}}/I_{\text{S19}})$   
 $= V_T \ln(I_{\text{C14}}/I_{\text{S14}}) + V_T \ln(I_{\text{C20}}/I_{\text{S20}})$
- Since  $I_L = 0$ :*  

$$\Rightarrow I_{\text{C14}} = I_{\text{C20}} = \sqrt{\frac{I_{\text{S14}} I_{\text{S20}}}{I_{\text{S18}} I_{\text{S19}}}} \sqrt{I_{\text{C18}} I_{\text{C19}}}$$
- The *sizes* of the *output transistors* are typically *much larger* than the other devices, to be able to *supply large current to the load without overheating*
- Assuming  $I_{\text{S14}} = I_{\text{S20}} = 4I_{\text{S18}} = 4I_{\text{S19}}$ :  
 $I_{\text{C14}} = I_{\text{C20}} = 216 \mu\text{A}$
- Thus, the *idling (standby) power dissipation* of the *output branch* =  $(30 \text{ V}) \times (216 \mu\text{A}) = 6.5 \text{ mW}$