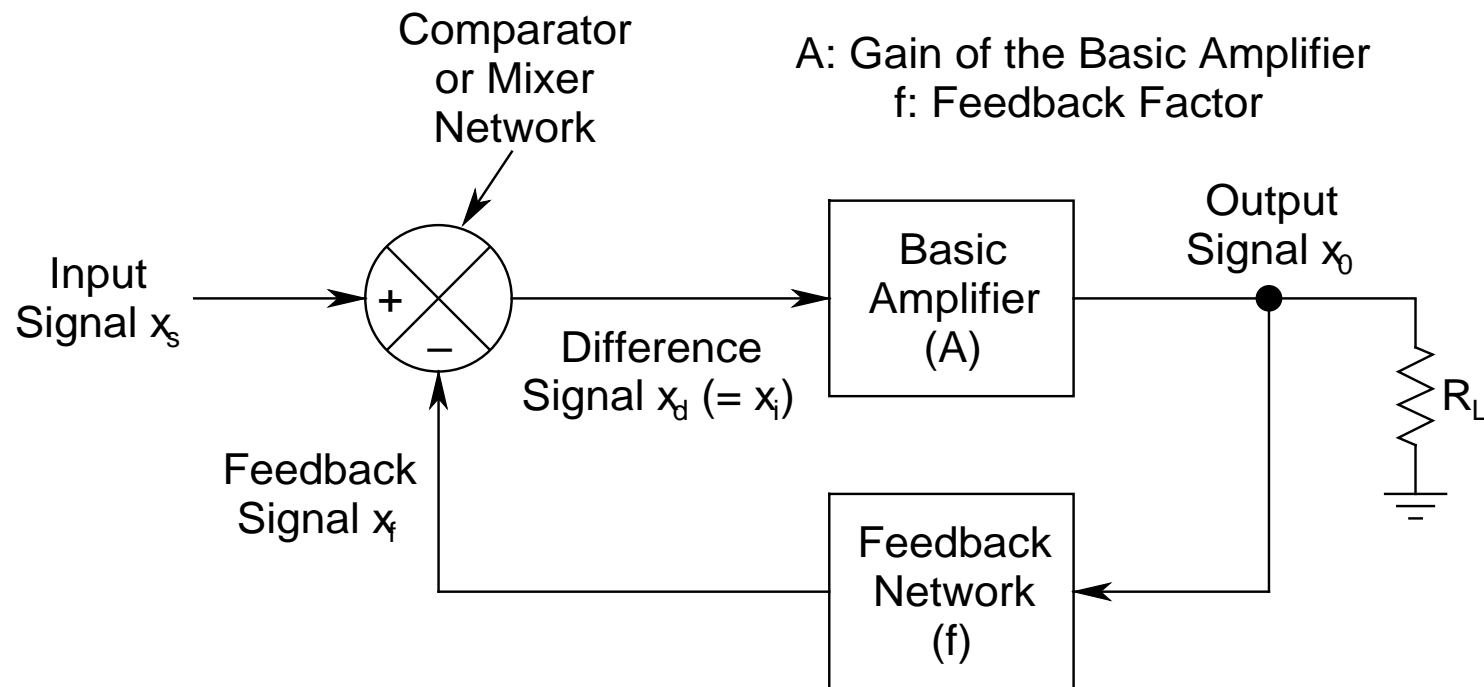


- Mathematical Foundation of Negative Feedback:***



**Block Schematic of a Negative Feedback System**

➤ **3 Main Blocks:**

- **The Basic Amplifier** (Gain  $A$ )
- **The Feedback Network** (Feedback Factor  $f$ )
- **The Mixer** (note the negative sign)

➤ **Defining Relations:**

- **Input Signal**  $x_s$
- **Output Signal**  $x_o = Ax_i$
- **Feedback Signal**  $x_f = fx_o$
- **Difference Signal**  $x_d = x_i = x_s - x_f$

➤ **Gain with feedback:**  $A_f = x_o/x_s$

➤ Thus:

$$\begin{aligned} A_f &= \frac{X_0}{X_s} = \frac{X_0}{X_i} \frac{X_i}{X_s} = A \frac{X_s - X_f}{X_s} = A \left( 1 - \frac{X_f}{X_s} \right) \\ &= A \left( 1 - \frac{X_f}{X_0} \frac{X_0}{X_s} \right) = A (1 - fA_f) \end{aligned}$$

➤ Gives the *fundamental expression* for *negative feedback*:

$$A_f = \frac{A}{1 + fA}$$

- *Some Definitions:*

- *Loop Gain* (L) = fA

- *Return Difference* (D) = 1 + L

- *Amount of Feedback* (N) =  $20 \log_{10} D$  (dB)

- *Positive Feedback:*

- *Output fed back to the input through the mixer, but now with a positive sign*

- ⇒ *Feedback signal gets added to the input signal*