

Basic Fundamentals

- ***Charge*** (q):
 - Elementary charge particle: ***electron***
 - Has a negative charge of magnitude
 $q = 1.6 \times 10^{-19}$ Coulomb (C)
- ***Voltage*** (V) (also referred to as ***potential***):
 - Work done (or energy spent) to move a unit charge between two points
 - (work done)/(unit charge) $\Rightarrow 1 \text{ V} = 1 \text{ J/1 C}$
 - Also, known as the ***potential difference*** (p.d.) between two points, expressed in Volt


- For charges to flow between two points in a closed circuit, a p.d. must exist between these two points
- *Scalar* quantity: always measured with respect to some reference
 - If the reference is not explicitly specified, then it is taken to be *ground* (zero volt)
 - Example:
 - V_A - potential of point A with respect to ground
 - V_{AB} - potential of point A with respect to potential of point B
- All circuits must have a *reference* point
 - If the reference point is not explicitly shown, then any node can be taken as a reference point

- ***Actual Ground and Reference Ground:***
 - Ground provides a return path for the current
 - Earth is considered to be an infinite source/sink of charge
 - ***Zero resistance*** => can absorb unlimited amount of current without changing its potential
 - Power supply in your homes have a ground connection, so does all big electrical and electronic appliances
 - 3-pin plugs: Live, Neutral, and Ground
 - 2-pin: Only Live and Neutral (floating ground)
 - Lightning arrester is a classic example of an actual ground

- Small and portable appliances (cell-phones, ipods, etc.) do not have actual ground
 - They have something known as *floating ground* (also referred to as *chassis ground*)
 - Typically a metal plate running at the periphery of the PCB
- Floating ground apparatus are dangerous, since they may give electric shocks
- Another example is electrostatic discharge (lightning is also an electrostatic discharge)
 - On a dry day, we may get shock upon touching a metal object (like door-knob) => electrostatic discharge
- The equipments that you will be using in the lab will all have *actual ground*

- ***Kirchhoff's Voltage Law:***

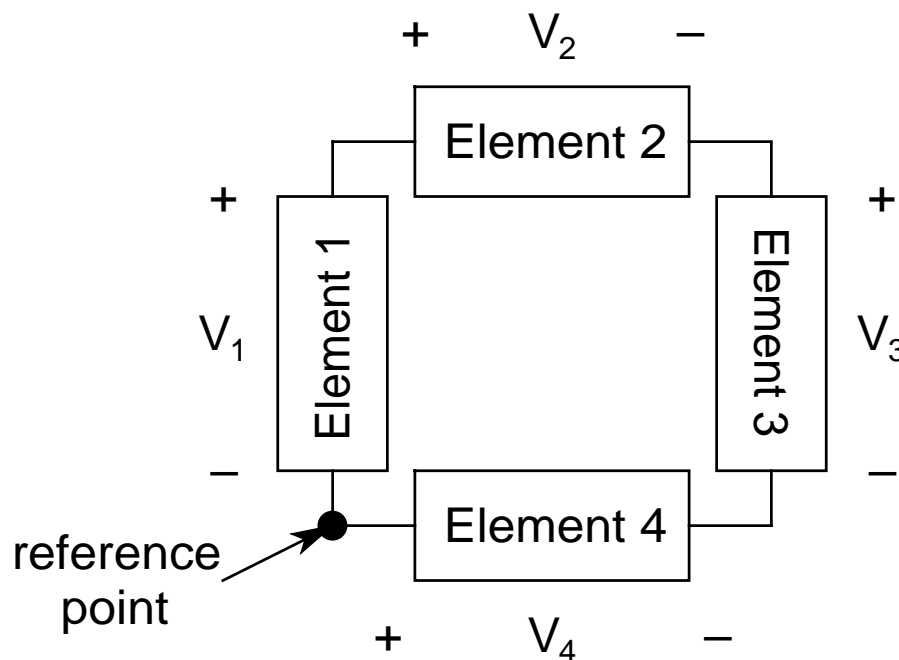
- Net voltage around a closed circuit must be zero
- Origin: ***Law of energy conservation:***
 - Total energy generated in a circuit must equal total energy dissipated in the circuit



$$V_1 - V_2 - V_3 + V_4 = 0$$


Take care of the polarities
of the potentials while
applying this law

- ***Current (I):***
 - Measure of charge transport
 - Defined as incremental charge change with respect to incremental time change
 - Expressed as: $i = \Delta q / \Delta t$ (Coulomb/sec = Ampere)
 - In the limit, as $\Delta t \rightarrow 0$, $i = dq/dt$ (differential form)
 - If dq/dt is constant \Rightarrow ***direct current*** (dc)
 - If dq/dt exists \Rightarrow ***alternating current*** (ac)
 - Note: 1 A of current implies about 10^{19} electrons flowing per second through a cross-sectional area

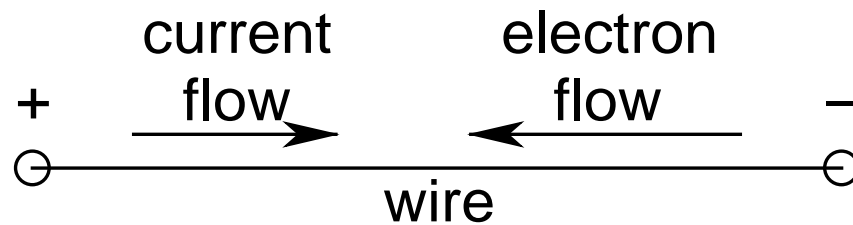

- By convention, positive direction of current is defined as the direction of flow of positive charges
 - Electrons flow opposite to the direction of current flow
- Electrons always move from lower potential to higher potential (attractive for them)
 - Actual flow of current from higher potential to lower potential

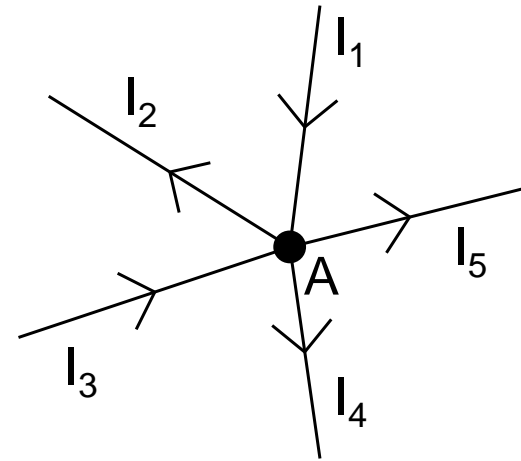- For current to flow, the circuit must be closed
- ***Kirchhoff's Current Law*** (KCL):
 - Sum of currents at a node must be zero
 - Origin: Law of charge conservation:
 - In a closed circuit, no charge is lost
- States that:
 - the sum of currents flowing into a node must equal the sum of currents flowing out of the node



At node A:


$$I_1 + I_3 = I_2 + I_4 + I_5$$

- ***Power (P):***
 - Defined as work done per unit time
 - Thus, $P = (\text{work done})/(\text{unit charge}) \times (\text{unit charge})/(\text{unit time}) = \text{voltage} \times \text{current} = VI$
 - Unit of P is Joules/sec or Watt (W)
 - In an element, if the current flows from:
 - lower to higher potential, then that element is ***generating power***
 - higher to lower potential, then that element is ***absorbing or dissipating power***
 - Within an electric circuit, the total power generated must equal the total power dissipated

- ***Ohm's Law, Resistance, & Conductance:***
 - Fundamental principle of electric circuit
 - Relates the current (I) that flows through a resistor under an applied p.d. of V
 - $V = IR$, with R being the resistance of the resistor
 - Thus, resistors are ***linear*** elements
 - Alternate form: $I = GV$, with G being the ***conductance*** of the resistor
 - Note that $G = 1/R$
 - Current always flows from higher to lower potential
 - The unit of resistance is Ohm (Ω), while that of conductance is Mho (\mathfrak{U})


- **Resistance (R):**

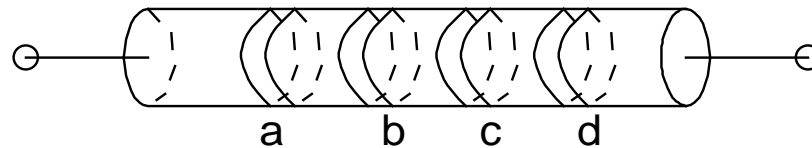- Typically cylindrical, having length l and radius r , with cross-sectional area $A = \pi r^2$
- Expressed as: $R = \rho l/A$, where $\rho = \textit{resistivity}$ ($\Omega\text{-cm}$) = $1/\sigma$, with $\sigma = \textit{conductivity}$ ($\Omega\text{-cm}$)⁻¹
- Usually, nichrome wires wound around a base with an insulating material, bonded with resin



- Resistor value: $R = ab \times 10^c \pm d\%$


- ***Resistor Color Code:***
 - ***B B Roy of Great Britain has a Very Good Wife***
 - BBROYGBVGW: Black (0), Brown (1), Red (2), Orange (3), Yellow (4), Green (5), Blue (6), Violet (7), Gray (8), White (9)
 - Band d is tolerance band: Violet - 0.1%, Blue - 0.25%, Green - 0.5%, Brown - 1%, Red - 2%, Gold - 5%, Silver - 10%, None - 20%
 - Example: brown black brown gold - 100 Ω with $\pm 5\%$ tolerance, blue gray yellow - 680 k Ω with $\pm 20\%$ tolerance

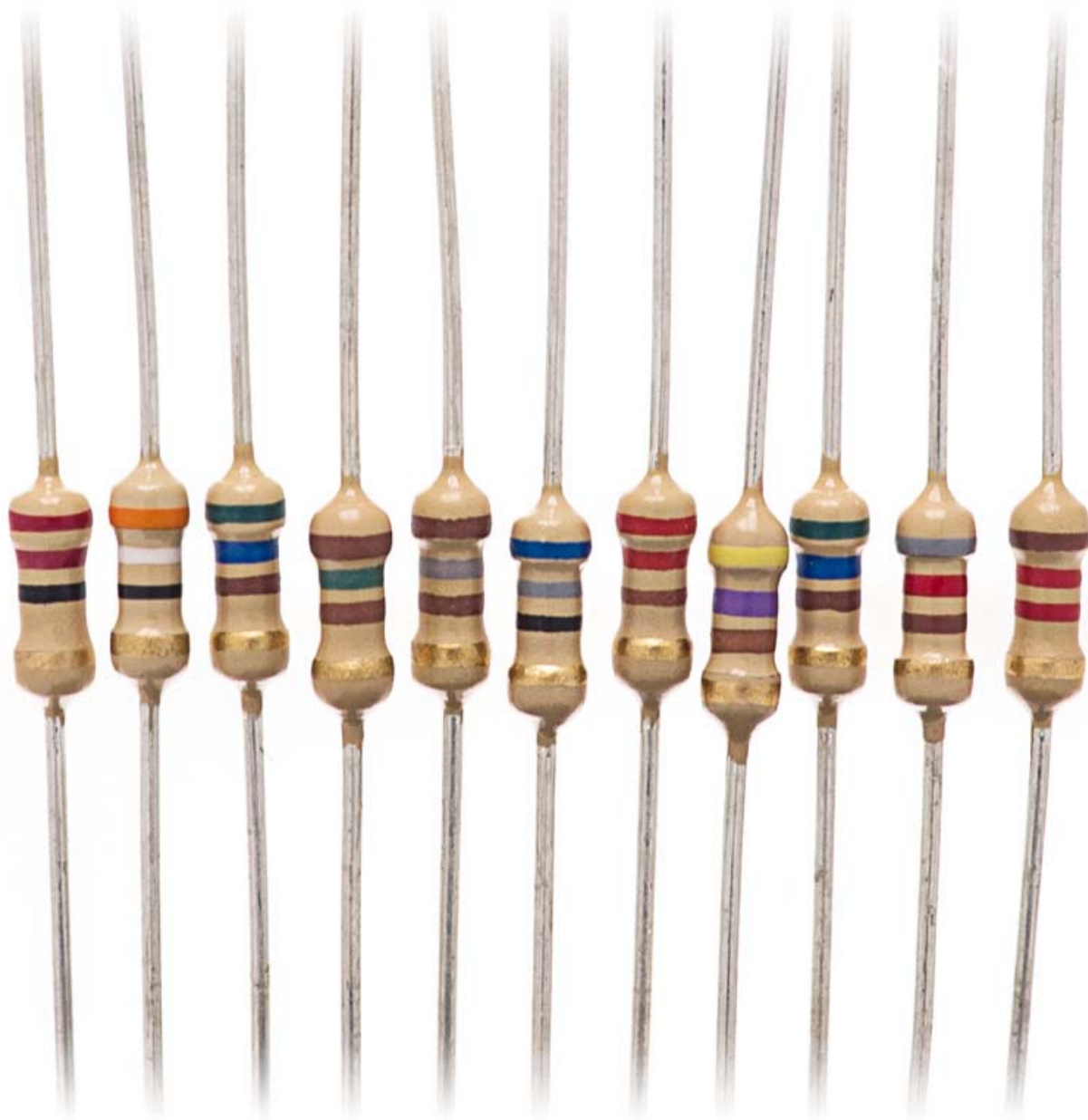

- ***Resistor Temperature & Power Ratings:***
 - Power dissipated in a resistor = $VI = V^2/R = I^2R$
 - Causes a rise in temperature of the resistor due to ***Joule heating***
 - Causes a change in the resistor value, determined by its ***temperature coefficient*** (TCF)
 - $TCF = \alpha = (1/R)(dR/dT)$, expressed in /K or /°C
 - $R = R_{nom}[1 + \alpha(T - T_{nom})]$, where T_{nom} is the nominal temperature, and R_{nom} is the value of the resistance at T_{nom}

- Resistors should be able to effectively dissipate the generated heat, otherwise, they may burn out
- Resistors have *safe power ratings*
- Common power ratings: 1/8 W, 1/4 W, 1/2 W, 1 W, and 2 W
- Resistors having power rating of more than 2 W are referred to as *high-power resistors*
- In power electronics applications, the power rating of resistors may even be kW or more

- *Series Combination of Resistors:*

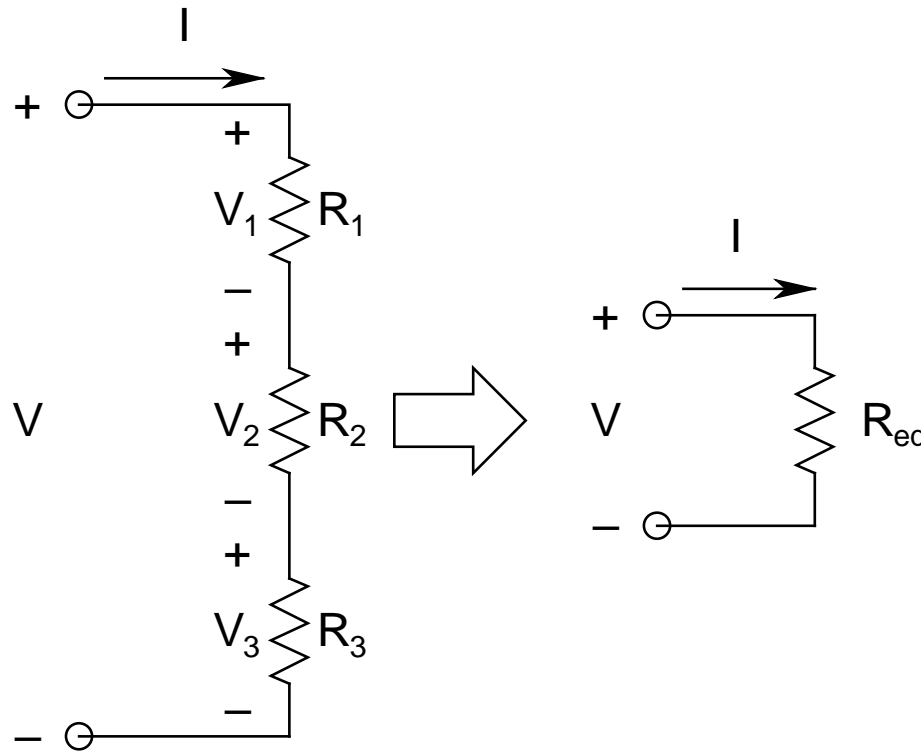


$$\begin{aligned} V &= V_1 + V_2 + V_3 \\ &= I(R_1 + R_2 + R_3) \\ &= IR_{eq} \\ \Rightarrow R_{eq} &= R_1 + R_2 + R_3 \end{aligned}$$

Largest R
dominates

- Note that all resistors are dissipating power, supplied by the source $\Rightarrow VI = I^2R_{eq}$

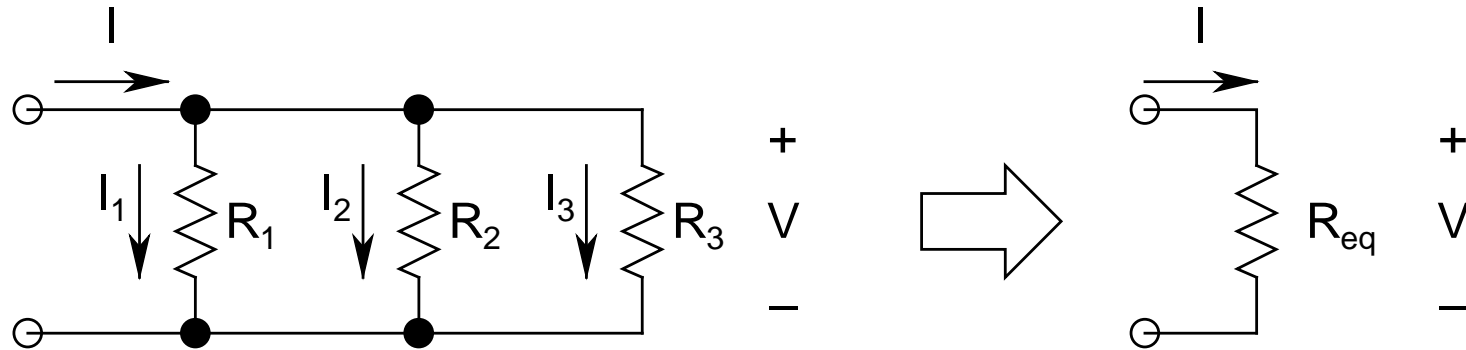- ***Parallel Combination of Resistors:***



$$I = I_1 + I_2 + I_3 = \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) V = \frac{V}{R_{eq}}$$


$$\Rightarrow R_{eq} = R_1 \parallel R_2 \parallel R_3 = \left(R_1^{-1} + R_2^{-1} + R_3^{-1} \right)^{-1}$$

$$= \left(G_1 + G_2 + G_3 \right)^{-1}$$

Smallest R
(highest G)
Dominates

- Note: Resistances in parallel is equivalent to conductances in series

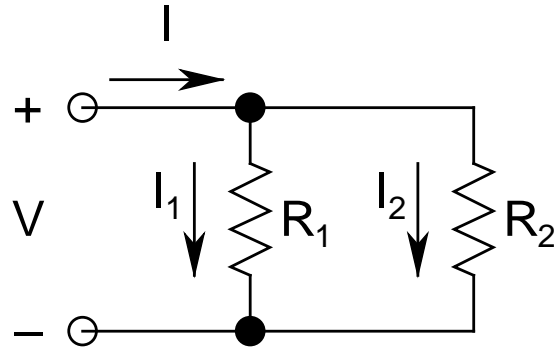- ***Current Branching between Two Parallel Resistors:***




$$V = IR_{eq}, \quad R_{eq} = R_1 \parallel R_2 = \frac{R_1 R_2}{R_1 + R_2}$$

$$I_1 = \frac{V}{R_1} = \frac{R_2}{R_1 + R_2} I, \quad \text{and} \quad I_2 = \frac{R_1}{R_1 + R_2} I$$

- Extremely important relation
 - If $R_2 \gg R_1$, then $I_1 \approx I$, and $I_2 \approx 0$
 - If $R_1 \gg R_2$, then $I_2 \approx I$, and $I_1 \approx 0$
 - If $R_1 = R_2$, then $I_1 = I_2 = I/2$ (equal split)
- The larger resistor carries lesser current, since the voltage drop across both of them is same

- ***Sources:***
 - Elements that supply power (or energy)
 - Voltage and Current
 - Independent and Dependent
- ***Notational Convention*** (IEEE Standard):
 - Capital letter with capital suffix - pure DC
 - Example: V_S
 - Small-case letter with small-case suffix - pure ac
 - Example: i_a
 - Capital letter with small-case suffix, or small-case letter with capital suffix - instantaneous
 - Example: I_s or v_A



- ***Independent Voltage Source:***

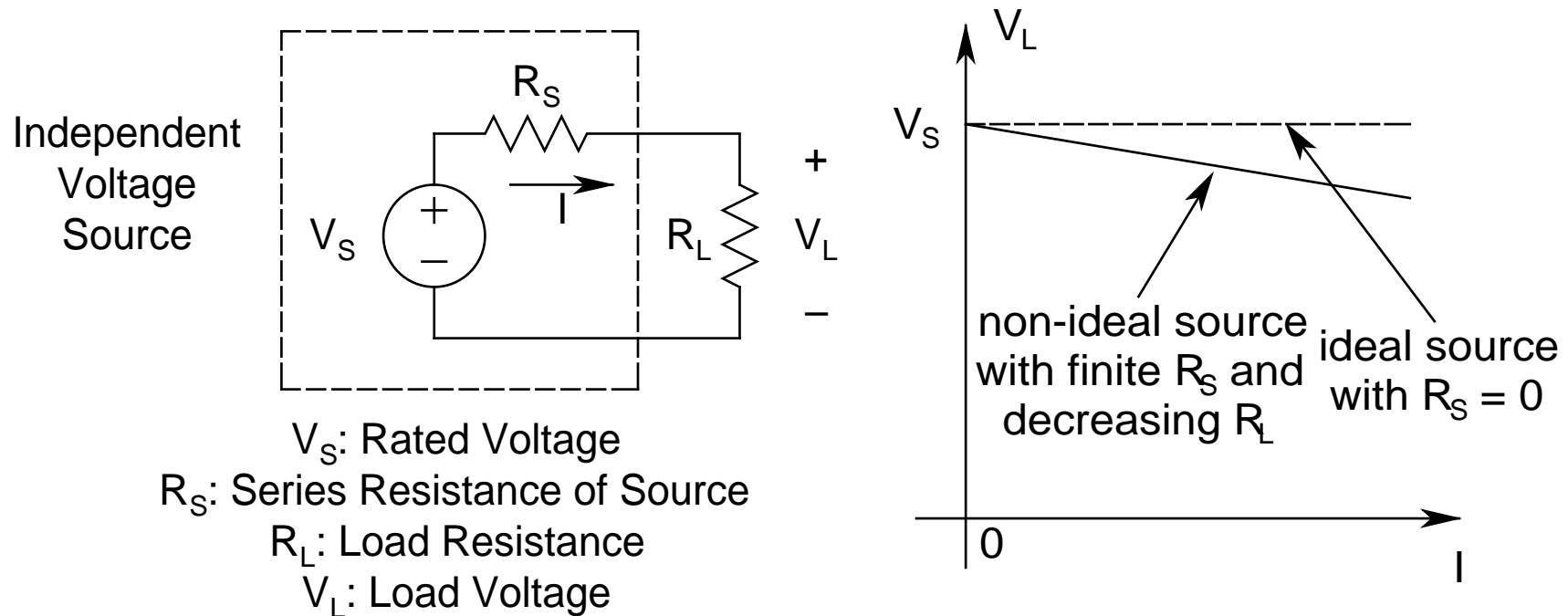

$$I = \frac{V_S}{R_S + R_L}, V_L = IR_L = \frac{R_L}{R_S + R_L} V_S$$

- For $V_L = V_S$, R_S must be zero - an important requirement for a good voltage source
 - Known as *Ideal Voltage Source* \Rightarrow *lossless*
- For finite R_S , V_L will drop with decreasing R_L
 - Known as *loading effect*
- Practical voltage sources have series resistance of the order of a few $k\Omega$
- For well designed sources, it may be less than $100\ \Omega$
- Effect of loading becomes more and more pronounced as R_L and R_S start to become comparable


- ***Independent Current Source:***

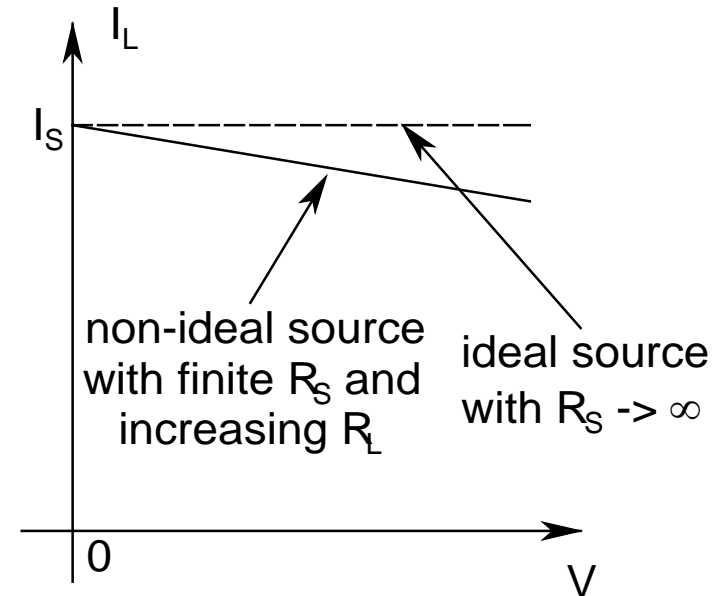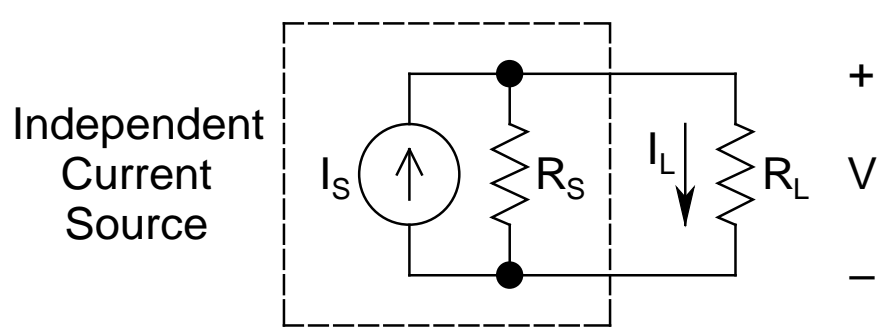

$$I_L = \frac{R_S}{R_S + R_L} I_S, \quad V = I_L R_L = \frac{R_S R_L}{R_S + R_L} I_S$$

- For $I_L = I_S$, R_S must be infinite - an important requirement for a good current source
 - Known as *Ideal Current Source* \Rightarrow *lossless*
- For finite R_S , I_L will drop with increasing R_L
 - Known as *loading effect*
- Practical current sources have shunt resistance of the order of a few hundreds of $k\Omega$
- For well designed sources, it may be even greater than $1\text{ M}\Omega$
- Effect of loading becomes more and more pronounced as R_L and R_S start to become comparable

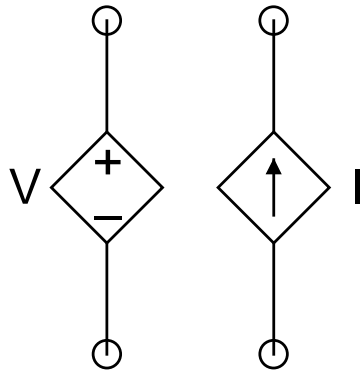- ***Dependent (or Controlled) Sources:***




Source voltage (current) dependent on another voltage (current) somewhere else in the circuit

Note the diamond shape, which distinguishes these from independent sources (round)

– Four possibilities:



- ***VCVS*** (Voltage-Controlled Voltage Source)
 - $V = A_v V_x$, A_v : ***voltage gain***, V_x : controlling voltage
- ***VCCS*** (Voltage-Controlled Current Source)
 - $I = G_m V_x$, G_m : ***transconductance***
- ***CCCS*** (Current-Controlled Current Source)
 - $I = A_i I_x$, A_i : ***current gain***, I_x : controlling current
- ***CCVS*** (Current-Controlled Voltage Source)
 - $V = R_m I_x$, R_m : ***transresistance***

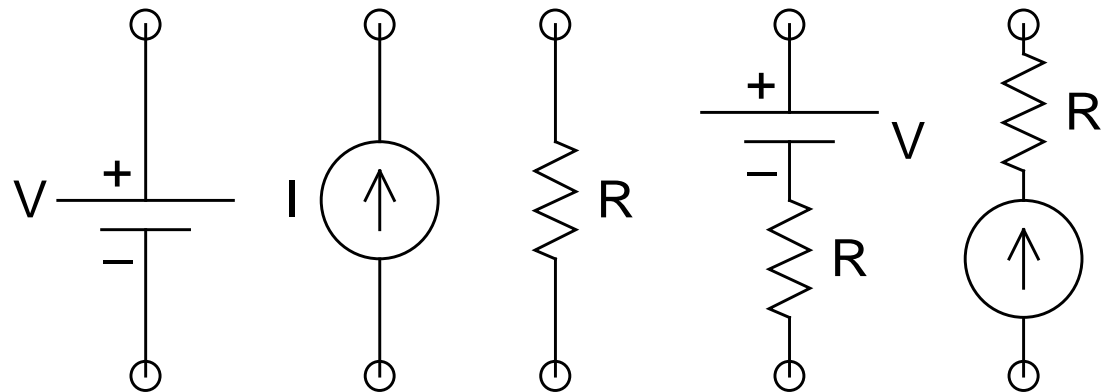- ***Electrical Network:***
 - Connection of elements to form a closed path through which current flows
- ***Branch:***
 - Any portion of a circuit with two terminals connected to it
 - May contain one or more circuit elements



- ***Node***:

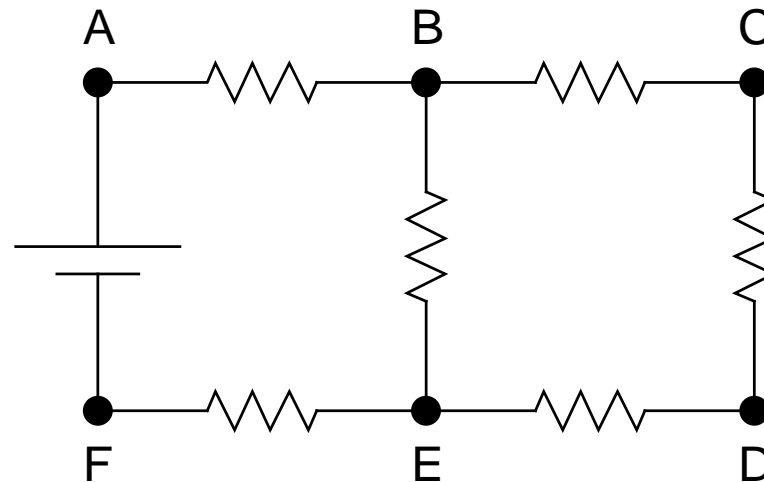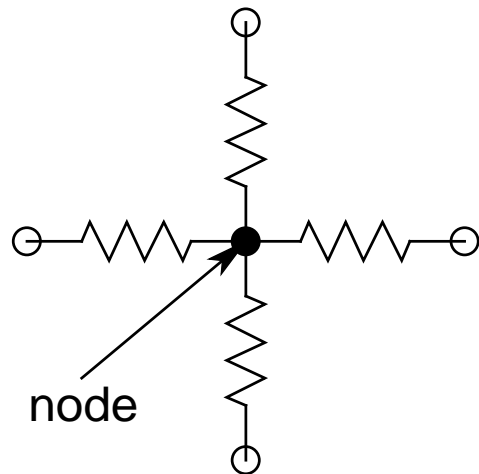
- Junction point of two or more branches
- Junction point of only two branches is also known as ***trivial node***



A, B, C, D, E, F: Nodes
A, C, D, F: Trivial Nodes


- ***Supernode:***

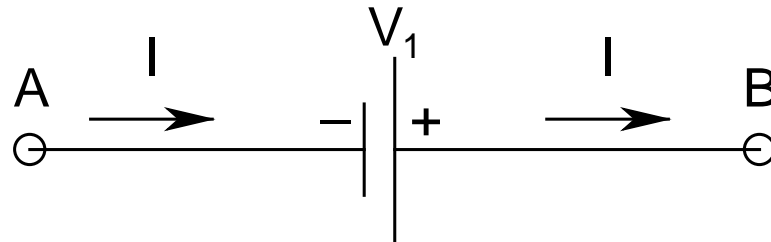- 2 nodes connected by a dc voltage source is denoted as a ***supernode***
- Voltages at the two nodes of a supernode are not independent, e.g., $V_B = V_A + V_1$



- Important condition for a supernode:
 - At any supernode, net current entering = net current leaving

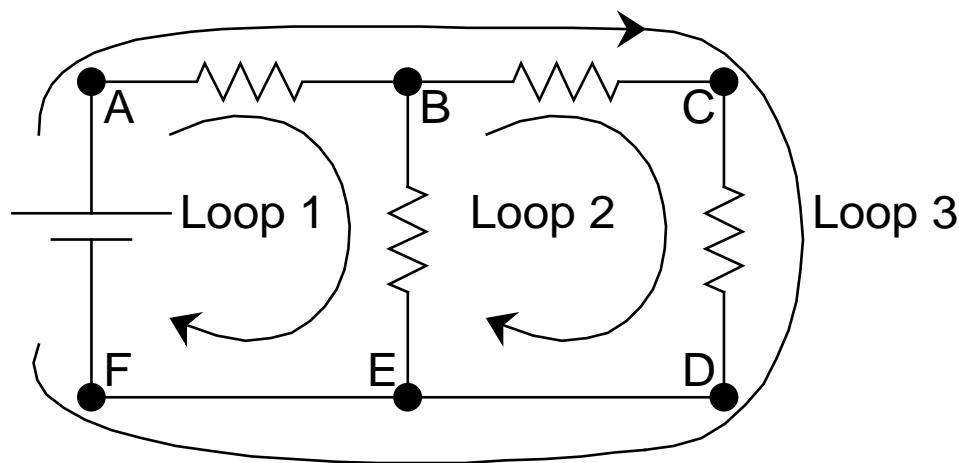- **Loop:**
 - Closed connection of branches
 - Different loops in the same circuit may include some of the same elements or branches
- **Mesh:**
 - A loop that does not contain other loops



Loops 1 and 2 are meshes,
but Loop 3 is not a mesh,
since it includes Loops 1 and 2

- ***Measuring Instruments:***

- ***Ohmmeter:***

- Measures the resistance of a resistor
 - The resistance is put across the two terminals of the instrument, which injects a small current (I) through the resistor, and measures the voltage (V) dropped across it => then $R = V/I$
 - The meter is calibrated to show the output in terms of the ohmic value of the resistor

– *Voltmeter:*



- Measures the voltage (or potential) dropped across any element in the circuit
- Always put in *parallel* to the two nodes across which the potential is to be measured
- To prevent loading caused by this instrument, it has *extremely high resistance*
- Never put a voltmeter in series with any element in a circuit, since due to the high resistance of this instrument, that branch will immediately become open-circuited

– *Ammeter*:

- Measures the current flowing through any branch in a network
- Always put in *series* with the branch through which the current flow is to be measured
- To prevent loading caused by this instrument, it has *negligible resistance*
- Never put an ammeter in parallel with any element in a circuit, since due to the extremely small resistance of this instrument, a huge amount of current will flow through this instrument and burn it

– ***Wattmeter:***

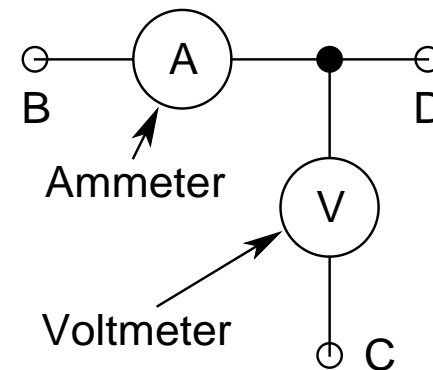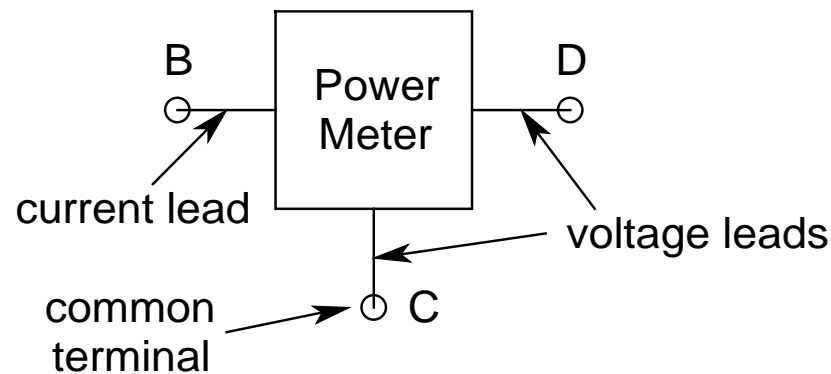- Also known as ***Power Meter***
- Measures the power consumed by a branch



- Involves both current (I) and voltage (V) measurements, and then performs a multiplication of the two in order to get the power