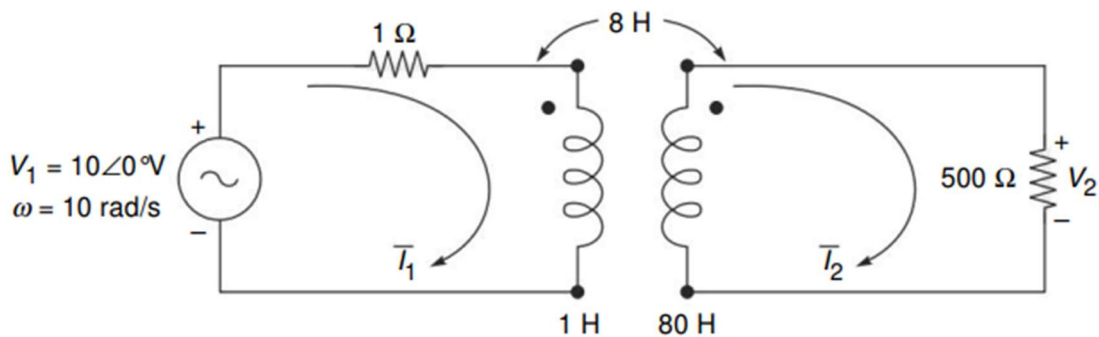


Tutorial 8

1. For the magnetic circuit shown in the Figure below, find the magnitude of V_2 / V_1 i.e. $|V_2 / V_1|$.



Solⁿ: Writing the mesh equations, for these two meshes, we get,

$$[1 + j10 \times 1] \bar{I}_1 - j10 \times 8 \bar{I}_2 = 10 \angle 0^\circ \quad (\text{Mesh 1})$$

$$(1 + j10) \bar{I}_1 - j80 \bar{I}_2 = 10 \angle 0^\circ \quad \text{--- (1)}$$

$$-j10 \times 8 \bar{I}_1 + (500 + j10 \times 80) \bar{I}_2 = 0 \quad (\text{Mesh 2})$$

$$\text{or } j80 \bar{I}_1 - (500 + j800) \bar{I}_2 = 0 \quad \text{--- (2)}$$

from eqⁿ (2), we get,

$$\bar{I}_1 = \left(\frac{500 + j800}{j80} \right) \bar{I}_2 = (10 - j6.25) \bar{I}_2 \quad \text{--- (3)}$$

Substituting eqⁿ (3) in eqⁿ (1), we get.


$$[(1 + j10)(10 - j6.25) - j80] \bar{I}_2 = 10 \angle 0^\circ$$

$$\bar{I}_2 = 0.135 \angle -10.7^\circ \text{ A}$$

$$\bar{V}_2 = 500 \bar{I}_2 = 68 \angle -10.7^\circ \text{ V.}$$

$$\frac{\bar{V}_2}{\bar{V}_1} = 6.8 \angle -10.7^\circ$$

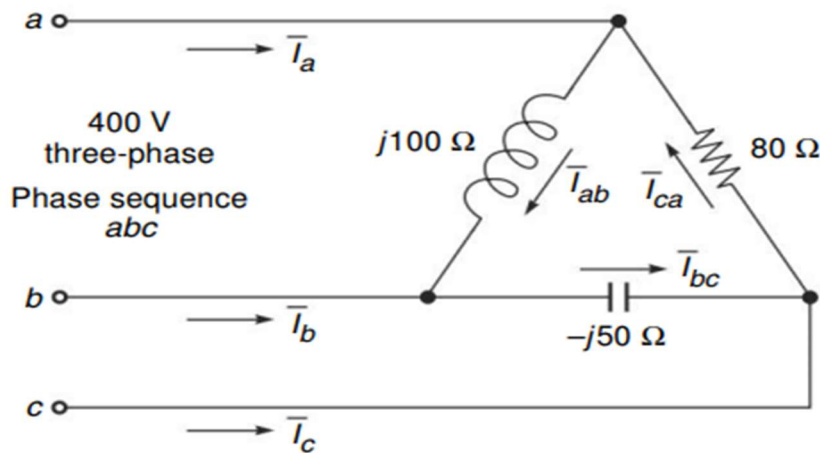2. In an unbalanced delta-connected load shown in the figure below, find the magnitude of line current I_c .



$$\begin{aligned} \bar{V}_{ab} &= 400 \angle 0^\circ, \quad \bar{V}_{bc} = 400 \angle -120^\circ, \quad \bar{V}_{ca} = 400 \angle -240^\circ \\ \bar{I}_{ab} &= \frac{400 \angle 0^\circ}{j100} = -j4 \text{ A.} \\ \bar{I}_{bc} &= \frac{400 \angle -120^\circ}{-j50} = -8 \angle -30^\circ \text{ A.} \\ &= 6.928 - j4 \text{ A.} \\ \bar{I}_{ca} &= \frac{400 \angle -240^\circ}{80} = 5 \angle -240^\circ \text{ A} \\ &= -2.5 + j4.33 \end{aligned}$$

$$\bar{I}_a = \bar{I}_{ab} - \bar{I}_{ca} = (-j4) - (-2.5 + j4.33)$$

$$\bar{I}_a = 2.5 + j0.33 = 2.522 \angle 7.5^\circ \text{ A}$$

$$\bar{I}_b = \bar{I}_{bc} - \bar{I}_{ab} = (6.928 - j4) - (-j4)$$


$$\bar{I}_b = 6.928 \angle 0^\circ \text{ A.}$$

$$\begin{aligned} \bar{I}_c &= \bar{I}_{ca} - \bar{I}_{bc} = (-2.5 + j4.33) \\ &\quad - (6.928 - j4) \end{aligned}$$


$$\bar{I}_c = -9.428 + j8.33 = 12.581 \angle 138.5^\circ \text{ A.}$$

$$\bar{I}_c = 12.581 \angle 138.5^\circ \text{ A}$$

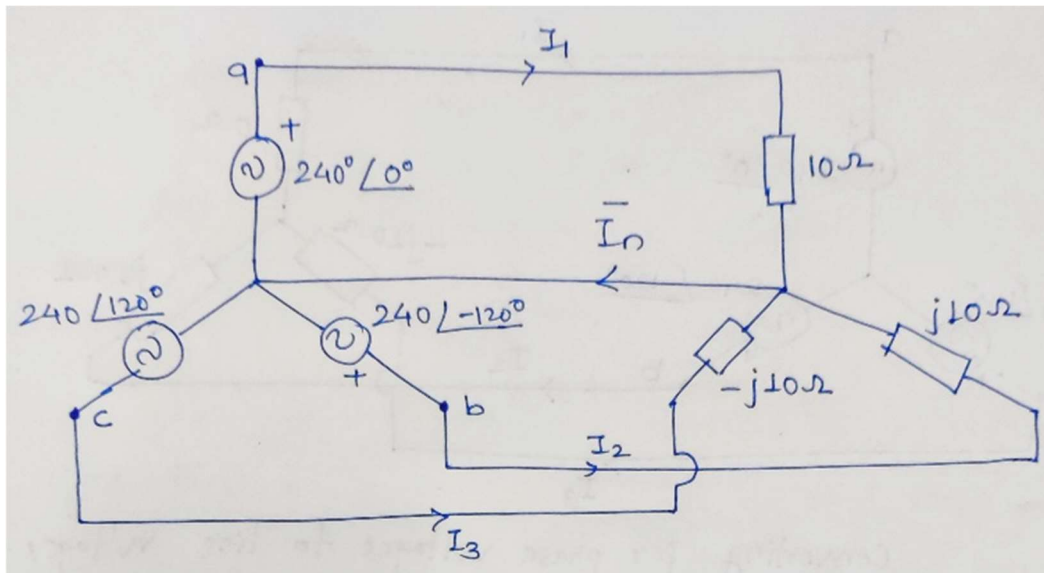3. For the circuit shown below, find the magnitude of neutral current (I_n) flowing in Amperes.



Solution -

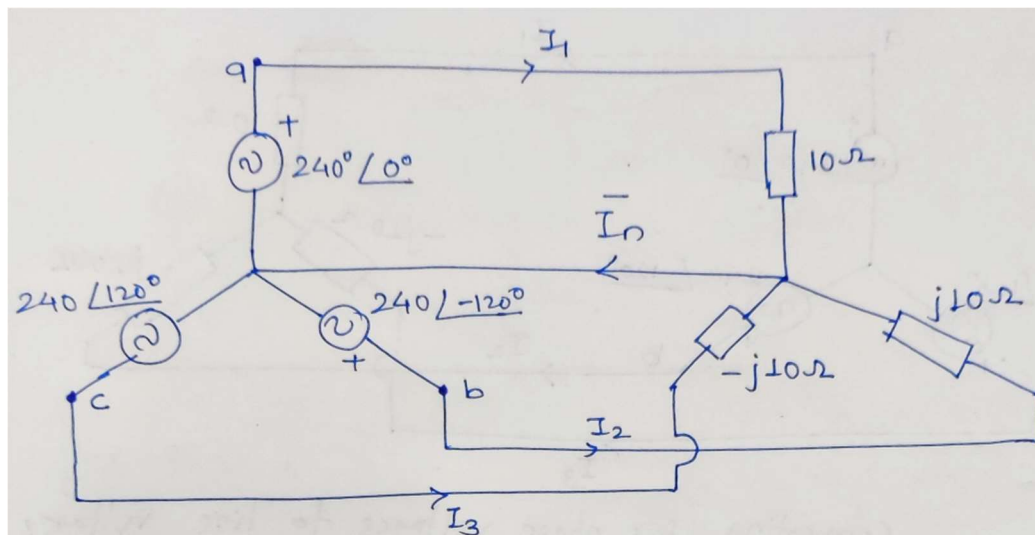

$$\bar{I}_1 = \frac{240 \angle 0^\circ}{10} = 24 \text{ Amp}$$

$$\bar{I}_2 = \frac{240 \angle -120^\circ}{j10} = (-20.785 + j12) \text{ Amp}$$

$$\bar{I}_3 = \frac{240 \angle 120^\circ}{-j10} = (-20.785 - j12) \text{ Amp}$$

$$\bar{I}_n = \bar{I}_1 + \bar{I}_2 + \bar{I}_3 = -17.56 \text{ Amp}$$

4. The two-wattmeter method produces wattmeter readings $P_1 = 1560 \text{ W}$, $P_2 = 2100 \text{ W}$, when connected to a Delta connected load. The Line-Line voltage of the supply is 220 V . Calculate the magnitude of phase impedance of the load in ohms.

Given, $P_1 = 1560 \text{ Watts}$, $P_2 = 2100 \text{ Watts}$

So, avg real power $P = P_1 + P_2 = 3660 \text{ Watts}$

Avg reactive power $\Rightarrow Q = \sqrt{3} (P_2 - P_1) = 935.3 \text{ VAR}$

pf. angle, $\phi = \tan^{-1} (Q/P) = 14.33^\circ$

$\therefore \text{p.f.} = \cos \phi = 0.9689$

Consider, Z_p as per phase Impedance

\therefore per phase active power $= \frac{P}{3} = 1220 \text{ Watts}$


$\therefore \frac{P}{3} = V_{ph} \cdot I_{ph} \cdot \cos \phi$

$$I_{ph} = \frac{1220}{220 \times 0.9689} = 5.723 \angle -14.33^\circ \text{ Amp}$$


$$\therefore Z_p = \frac{220}{5.723 \angle -14.33^\circ} = 38.44 \angle 14.33^\circ \Omega$$

$$Z_p = (37.24 + j9.51) \Omega$$

5. A 3-phase 3-wire system of 400 V (line-to-line) has impedances, $Z_A = (20 - j20) \Omega$, $Z_B = (50 + j0) \Omega$ and $Z_C = (30 + j52) \Omega$, as shown in the figure below. Neglecting impedances of the lines connecting source to load (i.e. A-A', B-B' and C-C'), calculate the magnitude of voltage difference between O and O' ($|V_{OO'}|$). Phase sequence is ABC.

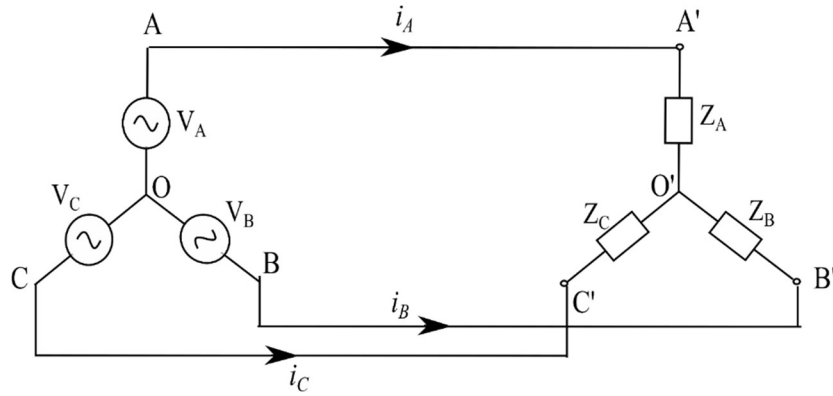

Solution

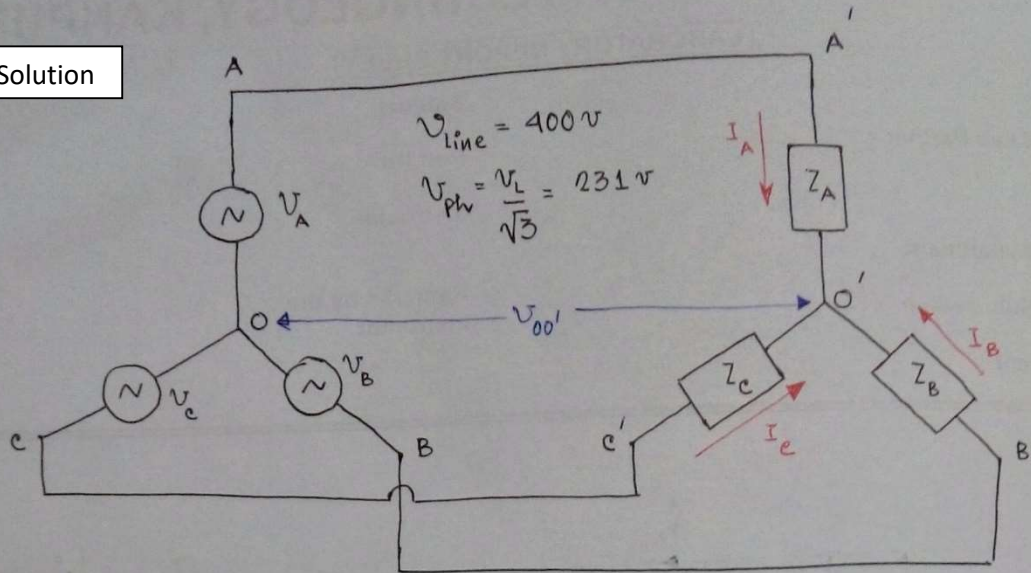

$$V_{OA} + V_{AO'} + V_{O'O} = 0 \Rightarrow V_{OO'} = V_{OA} + V_{AO'}$$

$$= V_A - I_A Z_A$$

Similarly, for 'B' & 'C' phases

$$V_{OO'} = V_B - I_B Z_B ; \quad V_{OO'} = V_C - I_C Z_C$$


$$I_A = \frac{V_A - V_{OO'}}{Z_A} ; \quad I_B = \frac{V_B - V_{OO'}}{Z_B} ; \quad I_C = \frac{V_C - V_{OO'}}{Z_C}$$

$$I_A + I_B + I_C = 0 \Rightarrow \frac{V_A - V_{OO'}}{Z_A} + \frac{V_B - V_{OO'}}{Z_B} + \frac{V_C - V_{OO'}}{Z_C} = 0$$

$$V_{OO'} = \frac{\frac{V_A}{Z_A} + \frac{V_B}{Z_B} + \frac{V_C}{Z_C}}{\frac{1}{Z_A} + \frac{1}{Z_B} + \frac{1}{Z_C}} = \frac{\frac{231 \angle 0^\circ}{(20 - j20)} + \frac{231 \angle -120^\circ}{50} + \frac{231 \angle 120^\circ}{(30 + j52)}}{\frac{1}{20 - j20} + \frac{1}{50} + \frac{1}{30 + j52}} \text{ V}$$

$$= 136.92 \angle 32.37^\circ \text{ V}$$

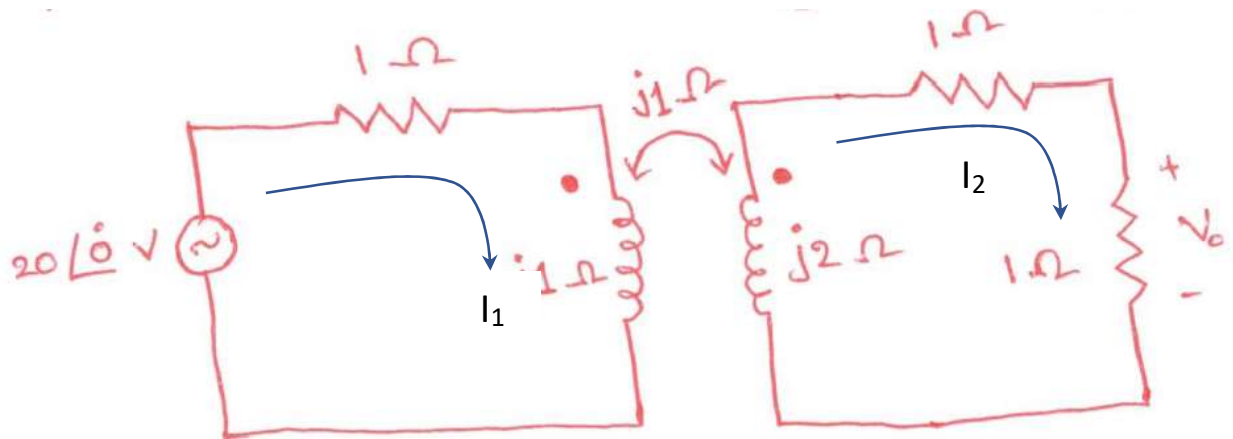6. Consider the coupled circuit shown in the figure below –



Find the magnitude of the voltage V_0 .

Solution -

Mesh-1 : $20\angle 0^\circ - 1I_1 - j1I_1 + j1I_2 = 0$
 $I_1(1+j) - jI_2 = 20\angle 0^\circ$ ——— (1)

Mesh-2 : $-j2I_2 - 1I_2 + 1I_2 + j1I_1 = 0$
 $-j1I_1 + I_2(2+j2) = 0$ ——— (2)

Solving eq (1) & (2), we get

$$I_2 = 4.85 \angle 14^\circ \text{ A}$$

voltage, V_0 is, $V_0 = I_2(1) = 4.85 \angle 14^\circ \text{ V}$