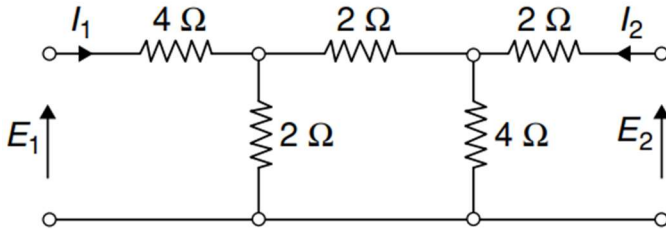


Tutorial 6

1. The h-parameters for a 2- port network are defined by -

$$\begin{bmatrix} E_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ E_2 \end{bmatrix}.$$


For the 2-port network shown in the figure below, the value of h_{12} is given by:




The h-parameter is

$$h_{12} = \left. \frac{E_1}{E_2} \right|_{I_1=0}$$

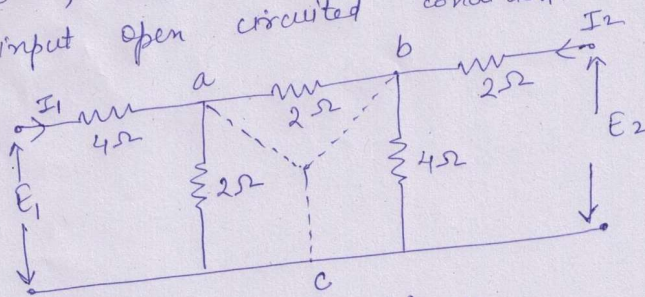where, h_{12} is ratio of E_1 and E_2 for the input open circuited condition.



Using Δ -Y transformation:-

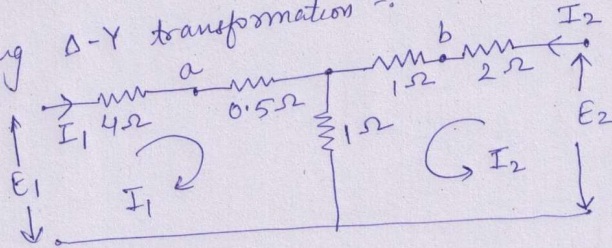

$$E_1 = (4 + 0.5)I_1 + 1(I_1 + I_2) = 5.5I_1 + I_2 \quad \text{--- (1)}$$

$$E_2 = (2 + 1)I_2 + 1(I_1 + I_2) = I_1 + 4I_2 \quad \text{--- (2)}$$

Substituting $I_1 = 0$ in eq^{ns} (1) and (2), we



get,

$$E_1 = I_2$$

$$E_2 = 4I_2$$

$$h_{12} = \left. \frac{E_1}{E_2} \right|_{I_1=0} = \underline{\underline{0.25}}$$

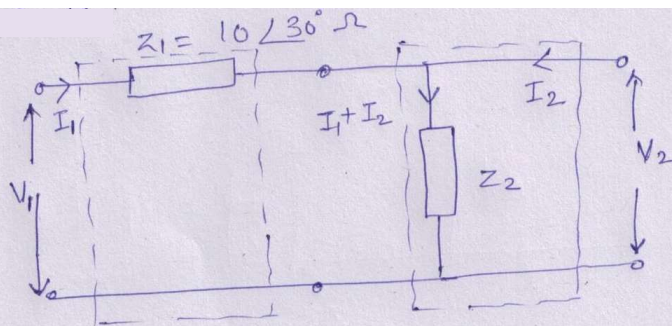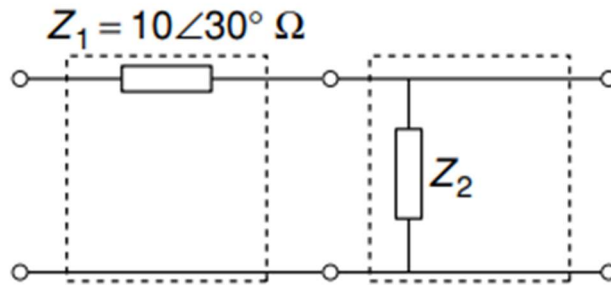2. Two networks are connected in cascade as shown in the figure. With the usual notations, the equivalent A, B, C, and D constants are obtained. Given that, $C = 0.025 \angle 45^\circ$, the value of Z_2 is -



$$V_1 = AV_2 + BI_2$$

$$I_1 = CV_2 + DI_2$$

$$V_2 = Z_2(I_1 + I_2) \quad \text{--- (1)}$$

$$C = \left. \frac{I_1}{V_2} \right|_{I_2=0}$$


substituting $I_2=0$, in eqⁿ (1), we get,

$$V_2 = I_1 Z_2$$

$$\Rightarrow Z_2 = \left. \frac{V_2}{I_1} \right|_{I_2=0} = \frac{1}{C} = \frac{1}{0.025 \angle 45^\circ}$$

$$Z_2 = 40 \angle -45^\circ \Omega$$

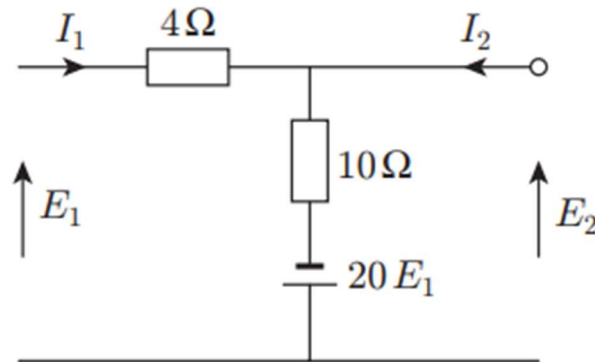3. Consider a 2-port network given in the figure below. The voltage source in the middle is a dependent voltage source having value $20E_1$. The Z parameters, Z_{11} and Z_{21} , for the network are -



from the given N/W,

$$E_1 = 4I_1 + 10(I_1 + I_2) - 20E_1$$

$$21E_1 = 14I_1 + 10I_2 \quad \text{--- (1)}$$

$$E_2 = 10(I_1 + I_2) - 20E_1$$

$$E_2 + 20E_1 = 10I_1 + 10I_2 \quad \text{--- (2)}$$

from (1), $Z_{11} = \frac{E_1}{I_1} = \frac{14}{21} \Big|_{I_2=0}$


from (2), $E_2 = 10I_1 - \frac{14}{21} \times 20I_1 \Big|_{I_2=0}$

$$= \frac{210I_1 - 280I_1}{21} = -\frac{70}{21} I_1 \Big|_{I_2=0}$$

$$\frac{E_2}{I_1} = Z_{21} = -\frac{70}{21}$$

$$\boxed{Z_{11} = \frac{14}{21}, \quad Z_{21} = -\frac{70}{21}}$$

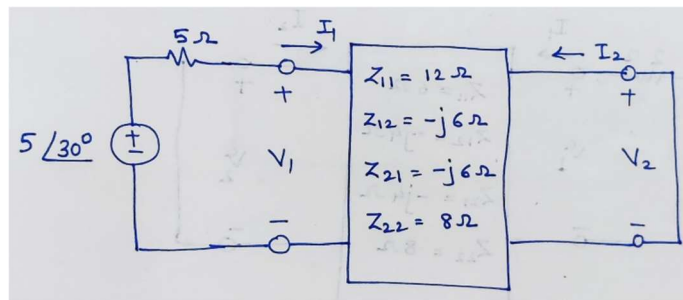4. For the circuit shown in the figure below, the possible combinations of currents I_1 and I_2 in mA are given below-




- I. $232.55 \angle 30^\circ, 116.27 \angle 120^\circ$
- II. $232.55 \angle 30^\circ, 174.42 \angle 120^\circ$
- III. $398.66 \angle 60^\circ, 116.27 \angle 150^\circ$
- IV. $398.66 \angle 60^\circ, 174.42 \angle 150^\circ$

Out of the above possible combinations, the correct option is -

$V_1 = Z_{11} I_1 + Z_{12} I_2$ & $V_2 = Z_{21} I_1 + Z_{22} I_2$
 $5 \angle 30^\circ - 5 I_1 = 12 I_1 + (-j6) \cdot j 0.75 I_1$ $0 = Z_{21} I_1 + Z_{22} I_2$
 $5 \angle 30^\circ = 17 I_1 + (-j6)(j 0.75) I_1$ $I_2 = -\frac{Z_{21}}{Z_{22}} I_1$
 $5 \angle 30^\circ = 17 I_1 + 4.5 I_1$ $I_2 = \frac{-(-j6)}{8} I_1 = j 0.75 I_1$
 $5 \angle 30^\circ = 21.5 I_1$
 $I_1 = 232.55 \angle 30^\circ \text{ mA}$
 $\& I_2 = 174.42 \angle 120^\circ \text{ mA}$

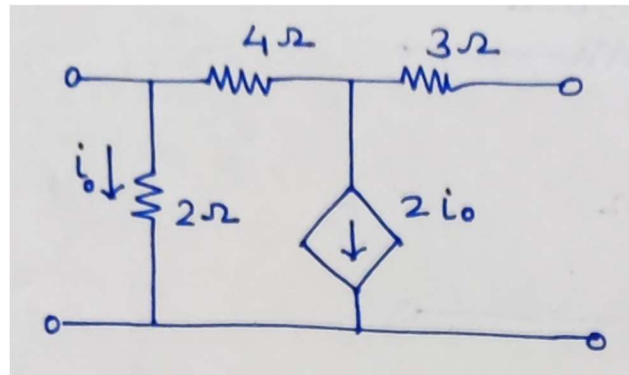5. For the circuit shown below, find the short circuit input and output admittances, respectively, in S.



Solution -

Short circuit input admittance, $y_{11} = \frac{I_1}{V_1}$

Short circuit output admittance, $y_{22} = \frac{I_2}{V_2}$

for $y_{11} \Rightarrow$ short circuit port 2, $V_2 = 0$

for $y_{22} \Rightarrow V_1 = 0$

$i_o = \frac{V_1}{2}$

At node 1

$$I_1 = i_o + \frac{V_1 - V_b}{4}$$

$$I_1 = \frac{V_1}{2} + \frac{V_1}{4} - \frac{V_b}{4}$$

$$I_1 = \frac{3V_1}{4} - \frac{V_b}{4}$$

$$I_1 = \frac{3V_1}{4} + \frac{9V_1}{4 \times 7}$$

$$I_1 = \frac{15}{14} V_1$$

$\therefore y_{11} = \frac{I_1}{V_1} = \frac{15}{14} \text{ S}$

At node 2

$$\frac{V_1 - V_b}{4} = 2i_o + \frac{V_b}{3}$$

$$\frac{V_1}{4} - \frac{V_b}{4} = 2 \times \frac{V_1}{2} + \frac{V_b}{3}$$

$$-\frac{V_b}{4} - \frac{V_b}{3} = \frac{3V_1}{4}$$

$$7\frac{V_b}{12} = -\frac{3V_1}{4}$$


$$V_b = -\frac{9V_1}{7}$$

$i_o = 0, \therefore 2i_o = 0$

$\therefore V_2 = 7 I_2$

$\therefore y_{22} = \frac{I_2}{V_2} = \frac{1}{7} \text{ S}$

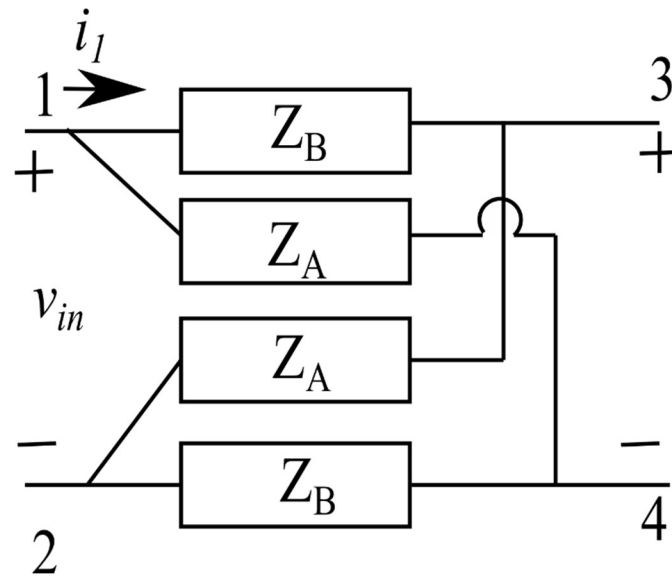6. For the lattice network shown in the figure below, $Z_A = j2\Omega$ and $Z_B = 2\Omega$, find out the transfer impedance $\frac{v_{34}}{i_1}$



Handwritten solution for the lattice network problem:

The circuit diagram shows the lattice network with impedances Z_A and Z_B . The input voltage is v_{in} and the input current is i_1 . The output voltage is v_{34} .

The voltage equations are:

$$v_{34} = v_3 - v_4$$

$$= v_{in} \cdot \frac{Z_A}{Z_A + Z_B} - v_{in} \cdot \frac{Z_B}{Z_A + Z_B}$$

$$= v_{in} \left[\frac{Z_A - Z_B}{Z_A + Z_B} \right]$$

The input current is given by:

$$i_1 = \frac{v_{in}}{(Z_A + Z_B)/2}$$

Therefore, the transfer impedance is:

$$\therefore \frac{v_{34}}{i_1} = \frac{(Z_A - Z_B)}{2} = \frac{j2 - 2}{2} = (-1 + j) \Omega \quad (\text{Ans})$$