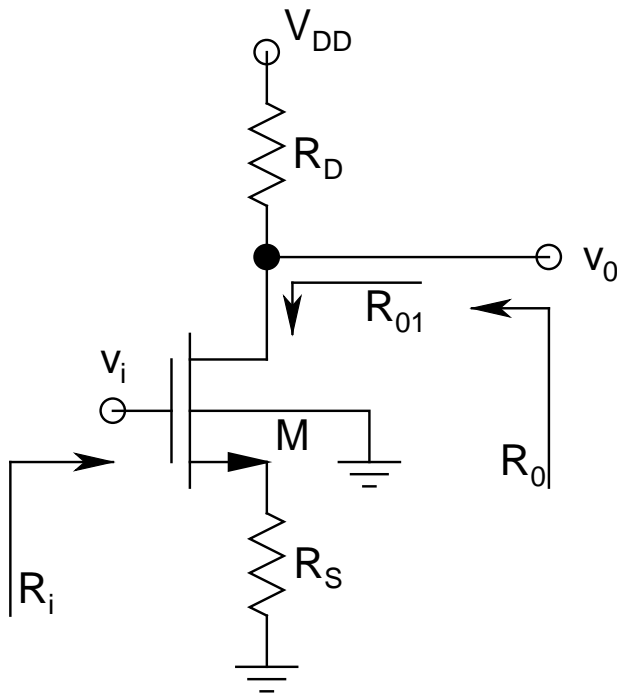



- $(1 + g_m R_E)$ is known as the ***Degeneration Factor***
- R_i can also be written as:
$$R_i \approx r_\pi + \beta R_E = r_\pi (1 + g_m R_E)$$
Thus, $R_i \uparrow$ by the ***Degeneration Factor*** as compared to the ***CE stage***
- ***Interesting to note that the loss in gain is returned by this circuit to its R_i by the same factor!***

- *Why do we sacrifice gain?*
 - Later on, we will see that this *sacrifice in gain* leads to a *commensurate increase in the bandwidth* of the circuit
- *For a given DC bias point*, the *gain-bandwidth product (GBP) of a circuit remains constant* (will be explored later)
- This is one of the *famous paradoxes* of analog circuits:
 - *To increase gain, sacrifice bandwidth, and vice versa*

- **Common-Source (Degeneration) [CS(D)]:**



ac Schematic

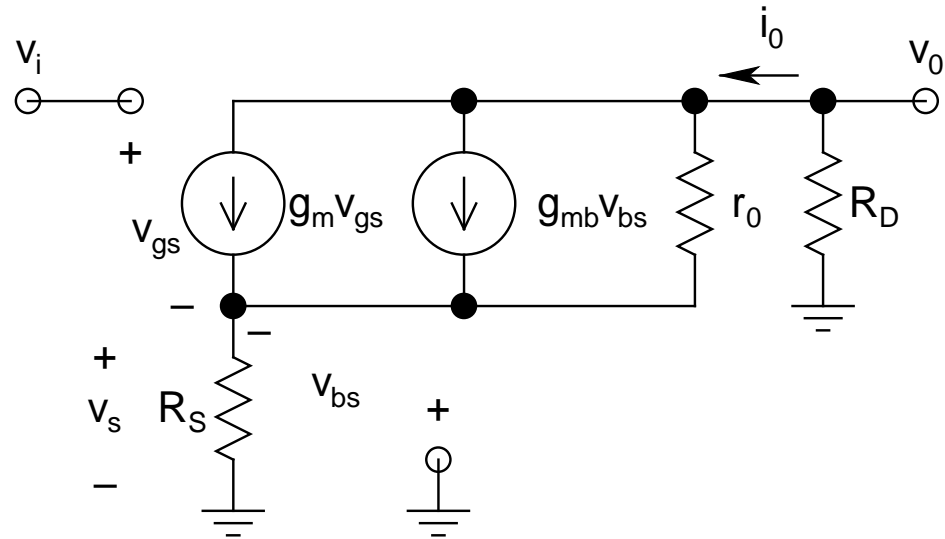

ac Low-Frequency Equivalent

➤ *Defining Relations:*

$$V_0 = -i_0 R_D$$

$$i_0 = g_m V_{gs} + g_{mb} V_{bs} + (V_0 - V_s)/r_0$$

$$V_s = i_0 R_S$$

$$V_{gs} = V_i - V_s$$

$$V_{bs} = -V_s$$

$$\Rightarrow A_v = \frac{V_0}{V_i} = -\frac{g_m R_D}{1 + (g_m + g_{mb}) R_S + (R_S + R_D)/r_0}$$

➤ Pretty *complicated* expression, however, *simplifications* can be made

- Generally, $(R_S + R_D)/r_0$ can be *neglected*:

$$\Rightarrow A_v = \frac{V_o}{V_i} \simeq -\frac{g_m R_D}{1 + (g_m + g_{mb}) R_S}$$

- *Neglect body effect*:

$$\Rightarrow A_v \simeq -\frac{g_m R_D}{1 + g_m R_S} = -\frac{R_D}{1/g_m + R_S}$$


- Again, *remarkable similarity with CE(D) stage*

- *Golden Observation*:


- *MOS stages, in absence of body effect, is absolutely similar to BJT stages, with r_E replaced by $1/g_m$, and both β and $r_\pi \rightarrow \infty$*

- Note that here the *Degeneracy Factor* is $(1 + g_m R_S)$
- $R_i \rightarrow \infty$
- $R_0 = R_{01} \parallel R_D$
 $R_{01} = r_o[1 + (g_m + g_{mb})R_S]$ (*Show!*)
- Again *gain is sacrificed* in order to *improve the bandwidth* by the *same amount*
- The complexity of analysis of this circuit is slightly more than the others encountered so far

- **Common-Base (CB):**

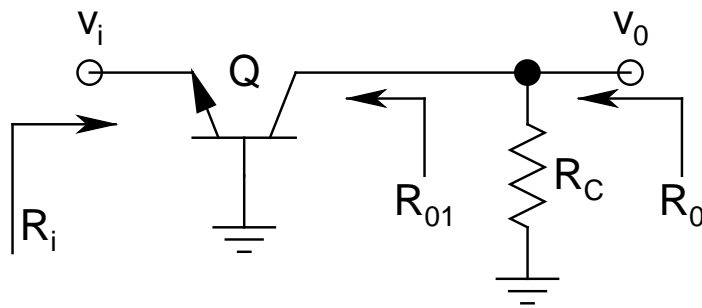

ac Schematic

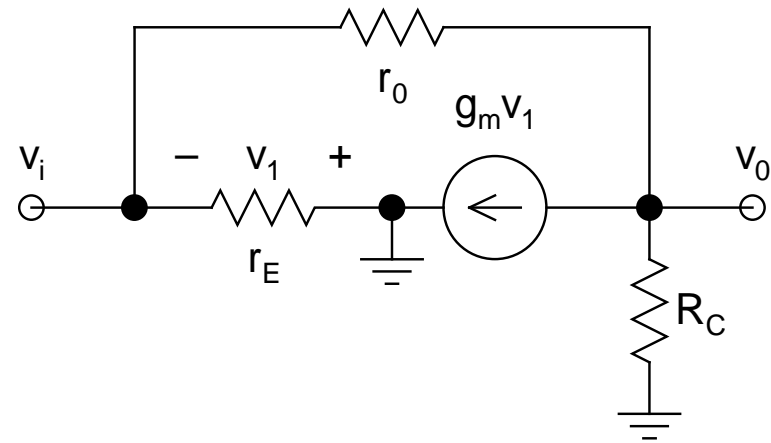

ac Low-Frequency Equivalent

- Note that the *alternate hybrid- π model* appropriate for *CB circuit* has been used
- *r_0 appears between input and output*