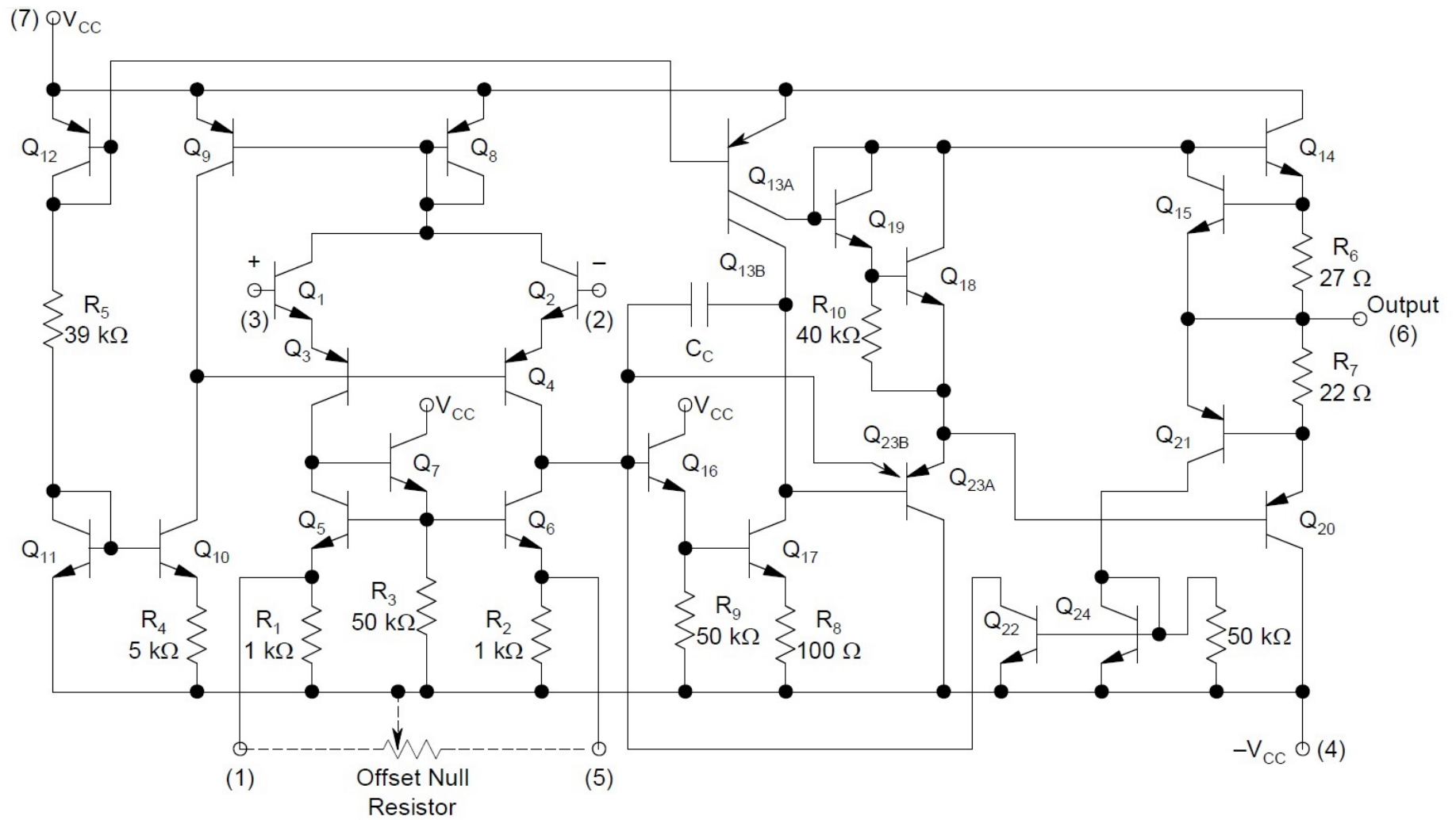


- $V_1$ ,  $V_2$ , and  $V_0$  are measured *w.r.t. ground*, but  $V_i$  is a *floating signal* (*difference* between  $V_1$  and  $V_2$ )
- The *controlled source* in the *MacroModel* is *VCVS*
- For  $V_1 > (<) V_2$ ,  $V_0$  is *positive* (*negative*)
- *Typical values for 741 op-amp*:
  - $A_{VOL} \sim 10^5$  (*100 dB*),  $R_i > 1\text{ M}\Omega$ ,  $R_o < 100\ \Omega$ ,  
CMRR  $\sim 80\text{-}100\text{ dB}$ ,  $V_{S+}$  and  $V_{S-}$ :  $\pm 3\text{ V to } \pm 15\text{ V}$

- *Uncompensated bandwidth* typically *larger than 1 MHz*
- Such a *large gain* and *high bandwidth* system will be prone to *oscillations* (*instability*)
- Need adequate *compensation*
  - *Compensated bandwidth* drops to about *5-10 Hz*
- *History of 741 Op-Amp:*
  - In *1965*, *Bob Widlar* (remember *Widlar current source*?) of *Fairchild Semiconductors* (now defunct) first came up with the design of a *monolithic* (*single substrate IC*) *op-amp*

- Named it  $\mu A$  709 ( $\mu A$  was the *trademark* of *Fairchild Semiconductors*)
- Almost immediately thereafter, *a number of improvements* were made on the *original architecture*, and  $\mu A$  741 evolved
- It became so *popular* that *the term 741* became a *legend*
- *All subsequent op-amp designs continued to be called 741!*
- *Initial design* of course was based on *bipolar technology*, since at that time, *MOSFETs were not even there!*

- In *late 70s*, *JFET version* of op-amps came into existence, followed by the *MOSFET version* in the *80s*
- The *design pedagogy* of the *original version* is a *real beauty*
- So many *brilliant innovations* were *incorporated* in the *design*, that it is a *learner's paradise*!
- In this chapter, we will do a *detailed analysis* of the *bipolar version* of the *741 op-amp*
- So, sit tight and enjoy! :)



The schematic of the 741 bipolar op-amp (the pin numbers of the 741 chip is shown in parantheses).

- *Steps of the Analysis:*

- First, we need to do the *DC analysis*
- For this, we need to find the *reference branch*
- This branch should be from *rail-to-rail* (i.e., *between the two power supplies*)
- It should encounter only *base-emitter junctions* and *resistors*
  - ⇒ The branch  $Q_{11}$ - $Q_{12}$ - $R_5$  is our *reference branch*
- *The DC current flowing through this branch fixes the DC bias current of all other branches*