





2) Contd. or  $U_a = \frac{U_{s1} \alpha (1-\alpha)}{\alpha(1-\alpha) + 1 - \alpha + \alpha} \& U_b = \frac{U_{s2} \sigma (1-\sigma)}{\sigma - \sigma^2 + 1}$

$$= \frac{U_{s1} \alpha (1-\alpha)}{\alpha - \alpha^2 + 1}$$

or  $U_{o2} = U_{s1} \frac{\alpha(1-\alpha)(1-2\alpha)}{\alpha(1-\alpha)(\alpha - \alpha^2 + 1)} + U_{s2} \frac{\sigma(1-\sigma)(1-2\sigma)}{\sigma(1-\sigma)(\sigma - \sigma^2 + 1)}$

$$= \frac{1-2\alpha}{\alpha - \alpha^2 + 1} U_{s1} + \frac{1-2\sigma}{\sigma - \sigma^2 + 1} U_{s2}$$

(b)  $\alpha = \sigma = 1$ .  $U_{o2} = -(U_{s1} + U_{s2}) \Rightarrow$  Inverted Summing Amplifier.

(c)  $\alpha = \sigma = 0$ .  $U_{o2} = U_{s1} + U_{s2} \Rightarrow$  Non-inverted Summing Amplifier.

3)  $U_+ = 4.02 \times \frac{99k}{10.1k + 99k} = 3.65V$

$U_- \cong 3.65V \therefore \frac{U_1 - 3.65}{9.9k} = \frac{3.65 - U_o}{101k} \approx i_- = 0$

or  $U_o = 3.65 - \frac{(U_1 - 3.65) \times 101}{9.9}$

$$= 3.65 - (3.98 - 3.65) \times \frac{101}{9.9} = 3.65 - 3.37$$

$$= +0.283V$$

Ideally  $U_o^{\text{ideal}} = -10(U_1 - U_2) = -10(3.98 - 4.02)$

$$= +0.4V \quad (\text{when the resistors are matched to } 100k\Omega \& 10k\Omega)$$

$\therefore \text{Error } 0.4 - 0.283 = \underline{0.117V}$

4) Ideal OpAmp  $\therefore U_- = U_+$  for all.

$\therefore U_b = U_1 = 4.99V$  and  $U_c = U_2 = 5.01V$

$\therefore U_a = U_b + 4.9k \times \frac{U_b - U_c}{200}$

$$= 4.99 + 24.5(4.99 - 5.01)$$

$$= 4.5V$$

and  $U_d = U_c - 4.9k \times \frac{U_b - U_c}{200} = 5.01 - 24.5(4.99 - 5.01)$

$$= 5.5V$$

$\therefore U_f = U_d \times \frac{9.99k}{9.99k + 10.01k} = 2.748V \cong U_e$

Same current from  $U_a$  node to  $U_d$  node



4. Contd.)  $\therefore \frac{V_a - V_e}{9.99k} = \frac{V_e - V_o}{10.01k}$

or  $\frac{4.5 - 2.748}{9.99} = \frac{2.748 - V_o}{10.01}$  or  $V_o = 2.748 - 1.755$

or  $V_o = 0.992 \approx 1V$

$V_{cm} = \frac{V_a + V_d}{2} = \frac{4.5 + 5.5}{2} = 5V$

$V_{dm} = \frac{V_a - V_d}{2} = \frac{4.5 - 5.5}{2} = -1V$

N.B. No gain in the 1st Stage

$\therefore \pm \frac{V_{dm}}{2}$  are the two inputs

$\therefore V_a = -0.5V$  &  $V_d = +0.5V$

Again  $V_e \approx V_f = 0.5 \times \frac{9.99k}{10.01k + 9.99k} = 0.24975V$

&  $\frac{V_a - V_e}{9.99k} = \frac{V_e - V_{odm}}{10.01k}$  or  $\frac{-0.5 - 0.24975}{9.99} = \frac{0.24975 - V_{odm}}{10.01}$

or  $V_{odm} = 0.24975 + 0.74975 \times \frac{10.01}{9.99} = 1.001V$

for  $V_{cm} \Rightarrow V_f = V_e = 5 \times \frac{9.99k}{10.01k + 9.99k} = 2.4975V$

$\therefore \frac{V_a - V_e}{9.99k} = \frac{V_e - V_{ocm}}{10.01k} \Rightarrow \frac{5 - 2.4975}{9.99} = \frac{2.4975 - V_{ocm}}{10.01}$


or  $V_{ocm} = 2.4975 - \frac{(5 - 2.4975) \times 10.01}{9.99} = -0.0100$

$\therefore A_{dm} = \frac{1.001}{4.99 - 5.01} = -\frac{1.001}{0.02} = -50.05 \approx -50$

$A_{cm} = \frac{-0.01}{5} = -0.002$

$\therefore CMRR = \left| \frac{A_{dm}}{A_{cm}} \right| = \frac{-50}{-0.002} = 2.5 \times 10^4$

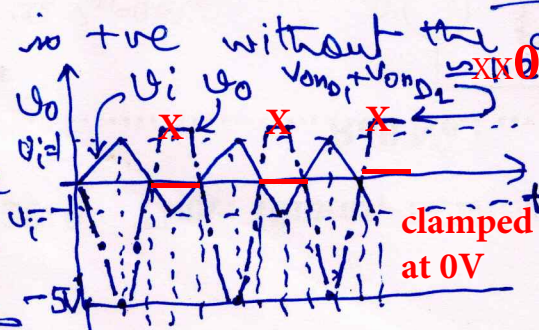5) As the input voltage  $V_i$  is +ve without the diodes  $D_1$ ,  $V_o$  is -ve  $\therefore D_2$  is off.  $\therefore$  If  $D_1$  is put in it will also be off  $\therefore V_o$  is -ve and continues to go down to  $-5V$  when  $V_i$  is  $1V$ . Again when  $V_i$  is +ve but reduces to  $0V$ ,  $V_o$  is negative and reaches  $0V$ .



For  $V_i$  -ve  $V_o \rightarrow +ve$  but the diodes can conduct only when  $V_o$  reaches  $V_{on1} + V_{on2}$  giving down  $D_2$



6.) Assuming that the Zener diodes each have a forward bias cut-in voltage  $V_{on} \approx 0.6V$  and each breaks down at  $4.3V$  in the reverse bias.  $V_o$  is within  $\pm (4.3 + 0.6)V$  irrespective of  $V_{CC}$  &  $V_{EE}$ . (both  $> |4.3 + 0.6|V$ ). Output clamped. (Note: the  $220\Omega$  resistor is necessary only to limit current through the Zeners or current flow through the Zeners to supply to any suitable load, if connected).

When  $V_o$  is clamped at the upper level  $V_o = 4.9V$ .

$$\therefore V_{+|High} = 4.9 \times \frac{4.3k}{39k + 4.3k} = 0.4866 \approx 0.487V (V_{IH})$$

Similarly when  $V_o$  is clamped at the lower level  $V_o = -4.9V$  or  $V_{+|Low} = -4.9 \times \frac{4.3}{39 + 4.3} = -0.487V (V_{IL})$ .

$$\therefore \text{Hysteresis Width} = 0.487 - (-0.487) = 0.974V.$$

7.) By superposition: For 0101

$$V_o = (0) \times \left[ -\frac{R}{2R} V_{REF} \right] + (1) \times \left[ -\frac{R}{4R} V_{REF} \right] + (0) \times \left[ -\frac{R}{8R} V_{REF} \right] + (1) \times \left[ \frac{R}{16R} V_{REF} \right]$$

$$= 3 \times \left\{ 0 \times \left(-\frac{1}{2}\right) + 1 \times \left(-\frac{1}{4}\right) + 0 \times \left(-\frac{1}{8}\right) + 1 \times \left(-\frac{1}{16}\right) \right\}$$

$$= -3 \times \left( \frac{1}{4} + \frac{1}{16} \right)$$

$$= -0.9375V.$$

possible  
digital  
combinations  
are

$b_1$	$b_2$	$b_3$	$b_4$	$V_o (V)$
0	0	0	0	0
0	0	0	1	$-0.0625 \times 3$
0	0	1	0	$-0.125 \times 3$
0	0	1	1	$-0.1875 \times 3$
0	1	0	0	$-0.25 \times 3$
0	1	0	1	$-0.9375$
0	1	1	0	$-0.375 \times 3$
0	1	1	1	$-0.4375 \times 3$
1	0	0	0	$-0.5 \times 3$
1	0	0	1	$-0.5625 \times 3$
1	0	1	0	$-0.625 \times 3$
1	0	1	1	$-0.6875 \times 3$
1	1	0	0	$-0.75 \times 3$
1	1	0	1	$-0.8125 \times 3$
1	1	1	0	$-0.875 \times 3$
1	1	1	1	$-0.9375 \times 3$

The value of the digital quantization is the smallest increment that the DAC can make and a smoother conversion to analog is not possible.

Check and see that each step is  $0.0625 \times 3 = 0.1875V$

This is the quantization error.



8.) Let's assume that the circuit had been switch off for a long time  $\therefore V_c(0^-) = 0$  and  $V_o(0^-) = 0$ .

Note: The  $+V_{cc} = 12V$ , and  $-V_{EE} = 0V$ .

$\therefore V_o$  can only swing between  $+12$  and  $0V$ .  
When the circuit has been switched on,  $V_c$  cannot change instantaneously and so does  $V_o$ .

$$\therefore \text{for } V_o = 0, V_+ = \frac{12 \times (6.8k \parallel 24k)}{6.8k + (6.8k \parallel 24k)} = \frac{12 \times 5.3}{6.8 + 5.3} = 5.255V$$

Now when the capacitor slowly gets charged, at one point in time  $V_-$  will reach the  $V_+$  voltage, when the output will swing to  $+12V$ . To find  $V_+$  now, use superposition for  $V_o = 12V$ .

$$\therefore V_+ = \underbrace{5.255}_{\substack{\downarrow \\ \text{due to the } +12V \text{ supply at the input}}} + \frac{12 \times (6.8k \parallel 6.8k)}{24k + (6.8k \parallel 6.8k)} \quad \leftarrow \text{due to } V_o = 12V$$

$$= 5.255 + \frac{12 \times 3.4k}{24k + 3.4k} = 6.744V \approx 6.74V$$

(If you approximate earlier you would get  $6.75V$ .)

$$\therefore V_c(t) = V_c(\infty) - (V_c(\infty) - V_c(0^+))e^{-t/\tau}$$

$$\text{where } \tau = RC = 6.2k \times 0.33\mu F = 2.05ms$$

$$\text{For } V_+ = 5.255 \rightarrow V_c(\infty) = 0, V_c(0^+) = 6.74V$$

$$\therefore 5.255 = 0 - (0 - 6.74)e^{-t_1/2.05ms}$$

$$\text{or } t_1 = -2.05ms \times \ln\left(\frac{5.255}{6.74}\right) = 0.51ms$$

$$\text{Similarly for } V_+ = 6.74V, V_c(\infty) = 12V, V_c(0^+) = 5.255V$$

$$\text{or } 6.74 = 12 - (12 - 5.255)e^{-t_2/2.05ms}$$

$$\therefore t_2 = 2.05ms \times \ln\left(\frac{12 - 6.74}{12 - 5.255}\right) = 0.5098ms \approx 0.51ms$$

$$\therefore \text{Switching times are } t_1 = T/2 = t_2 = 0.51ms$$

$$\therefore \text{frequency of oscillation} = f_o = \frac{1}{t_1 + t_2} = \underline{\underline{980.4Hz}}$$

b) Here when  $V_o$  is at  $0$  at switch on  $V_+ = 0$ .

$\therefore V_o$  does not get a chance to change state.  $\therefore$  The circuit does not oscillate

$$\therefore f_o = 0$$



9.) For the closed loop gain to be real (i), as required for oscillation, the closed loop gain has to be equal to be unity (ii) for stability in the oscillator output.

$$\therefore (i) \omega_0 L = \frac{1}{\omega_0 C} \text{ or } f_0 = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{0.01\mu\text{F} \times 10\text{m}}} = 15.915\text{kHz}$$

At resonance  $Z$  of  $(Z_L || Z_C) \gg R$  (tank circuit).

$$\therefore Z_L || Z_C \gg 15\text{k}\Omega. \text{ let } (Z_L || Z_C)_{\text{real}} \cong 10 \times 15\text{k}\Omega$$

Note: that the feedback is at the non-inverting terminal. much larger.

$$\therefore \text{Loop gain is } \left(1 + \frac{100\text{k}}{5\text{k}}\right) = 21.$$

$$\text{Now the feed back is } \frac{(1-\sigma)R || [Z_L || Z_C]_{\text{real}}}{[(1-\sigma)R || [Z_L || Z_C]_{\text{real}} + \sigma R} \cong \frac{(1-\sigma)R}{(1-\sigma)R + \sigma R}$$

$$\cong \frac{(1-\sigma)R}{R} \text{ since } (Z_L || Z_C)_{\text{real}} \gg R.$$

$$= \alpha \text{ where } \alpha = 1 - \sigma$$

$\therefore$  For oscillations to sustain

$$\therefore \text{Closed loop gain} \cong 21 \times \alpha \geq 1 \text{ for oscillation to sustain.}$$

$$\text{or } \alpha_{\min} = \frac{1}{21} = 0.04762$$

$$\therefore R_{\min} \cong 15\text{k} \times 0.04762 = 0.714\text{k}\Omega = 714.3\Omega$$

