
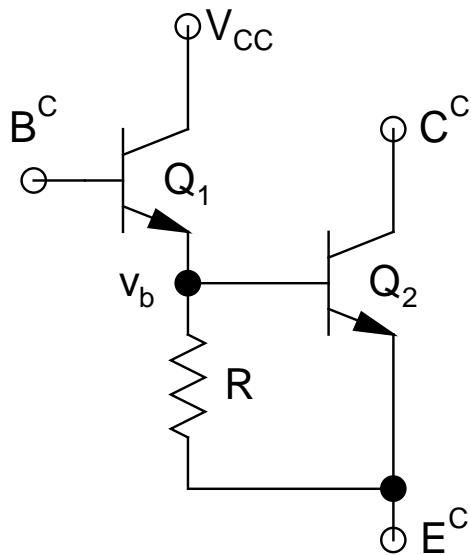


➤ *Need to jack up  $\beta_1$*

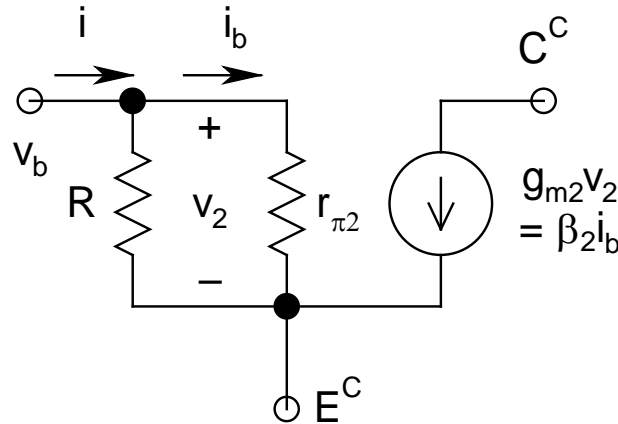
❖ *How about using a keep-alive resistor?*



**Darlington with  
Keep-Alive Resistor R**



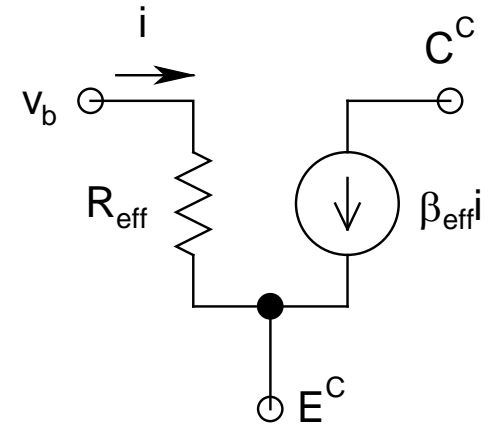**ac Midband Equivalent  
of  $Q_2$ -R Combination**



**Simplified Equivalent  
of  $Q_2$ -R Combination**

- ***R drains a constant DC current of  $\sim 0.7/R$***
- ***This current is supplied by  $Q_1$ , along with  $I_{B2}$***   
 $\Rightarrow I_{C1} \uparrow \Rightarrow \beta_1 \uparrow$
- ***However, this technique also changes  $\beta_2$***
- ***Analysis:***

$$i_b = Ri/(R + r_{\pi 2})$$


$$\begin{aligned} \Rightarrow i_c &= \beta_2 i_b = \beta_2 Ri/(R + r_{\pi 2}) = g_{m2} r_{\pi 2} Ri/(R + r_{\pi 2}) \\ &= g_{m2} (R \parallel r_{\pi 2}) i = g_{m2} R_{\text{eff}} i = \beta_{\text{eff}} i \end{aligned}$$

$$\beta_{\text{eff}} = g_{m2} R_{\text{eff}} < \beta_2 \quad (R_{\text{eff}} = R \parallel r_{\pi 2})$$

- ***Note:**  $r_{E2, \text{eff}} = R_{\text{eff}}/\beta_{\text{eff}} = 1/g_{m2} = r_{E2}$  (**unchanged**)*

- *npn Cascode:*

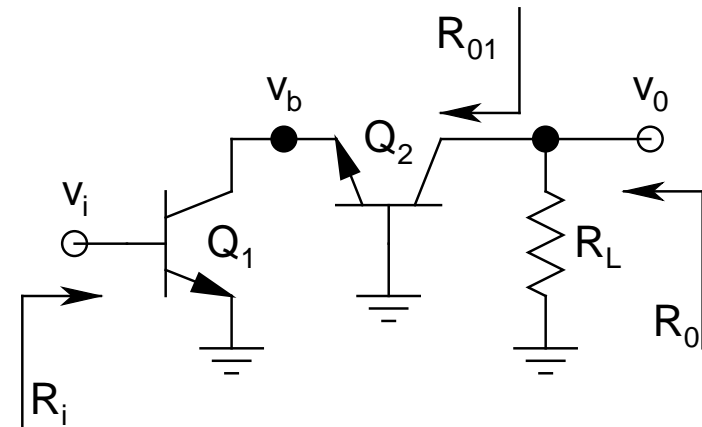- *CE*, followed by *CB*
- Known as *Wideband Amplifier*, due to its *superior frequency response characteristic*



**ac Schematic**

- *Generally, both  $Q_1$  and  $Q_2$  are biased with the same  $I_C$*
- *Assuming  $Q_1$ - $Q_2$  have same  $\beta$ :*

$$r_{E1} = r_{E2} = r_E \text{ and } r_{\pi1} = r_{\pi2} = r_{\pi}$$

- *This circuit can be analyzed by inspection*
- $R_i = r_{\pi 1}$
- $v_o/v_b = +g_{m2}R_L = R_L/r_{E2}$  (**CB Stage**)
- $v_b/v_i = -r_{E2}/r_{E1} = -1$ 
  - *CE Stage with  $R_i$  of  $Q_2 (= r_{E2})$  as its load*
- Thus,  $A_v = v_o/v_i = -R_L/r_{E2}$
- *Note that  $A_v$  is same as that for a CE stage, however, the bandwidth of this circuit is far superior than a CE stage*