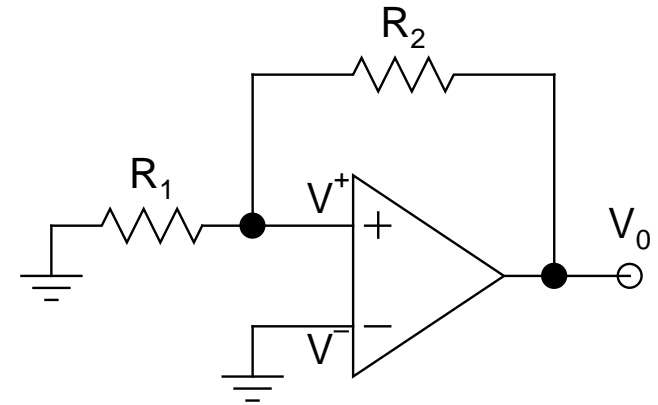


- **Closed-Loop: *Positive Feedback*:**
 - Connection between output and **non-inverting** terminal of the OA
 - Analysis technique for such circuits needs special care and attention:
 - **Concept of Virtual Ground and Summing Point Constraint can't be applied anymore**
 - **Applications:**
 - *Schmitt Trigger*
 - *Waveform Generation (Square- and Triangular-Wave)*
 - *Oscillators (Wein-Bridge and Phase-Shift)*

Concept of Positive Feedback: Metastability:

- * Circuit looks remarkably similar to an inverting amplifier, but it's not, since the output is fed back to the *non-inverting* terminal



- * Also, the **circuit doesn't have any input signal source**
- * The output V_0 should be *zero*, if the OA were assumed to be *ideal* (i.e., *without any offset voltage*)
- * Now, suppose that the output V_0 picks up some *positive noise signal*

- * This would be fed back to the *non-inverting* terminal of the OA through the voltage divider action of R_1 and R_2
- * With the *inverting terminal grounded*, this would *increase the differential input voltage* of the OA, which would result in a *greater output*
- * This would cause *more fraction* of the output fed back to the input, causing an *even greater output*
- * This process *repeats*, and the output *grows* to be eventually *limited* by the *saturation voltage* V_{SAT^+}

- * The process described is called *signal regeneration*
- * Similarly, if V_o picked up a *negative noise signal*, then the output would eventually *saturate* to V_{SAT^-}
- * Once this happens, it is *impossible* to bring the system out of it, i.e., V_o *would get stuck at $\pm V_{SAT}$* , **unless the power supply to the OA is turned off!**
- * Thus, the *presumption* that the output of the circuit would be *zero* is **wrong**, since the chance of the output *picking up noise signals*, and thus the output eventually *saturating* to $\pm V_{SAT}$ is almost a cinch

- * Hence, such a state (i.e., $V_o = 0$) is known as a *metastable state* for the circuit
- * **Metastable**: A state of precarious stability
- * The circuit is known as a **bistable** circuit, since the output can stay at either of $\pm V_{SAT}$ for an indefinite time, until and unless it's *forced* to switch state
- * This *forced transition* is known as *external triggering*
- * The circuit shown has *no such provision*
- * A circuit, known as **Schmitt Trigger**, has this *triggering mechanism* built-in

Schmitt Trigger:

* Named after the inventor ***Otto H.***


Schmitt (in 1934)

* Note the signal V_R applied at the ***inverting*** input and the ***positive feedback*** (output fed back to the ***non-inverting*** terminal)

$\Rightarrow V_R$ is the ***trigger signal*** that creates change of state


* Assume ***negative*** $V_R \Rightarrow V_0$ would ***saturate*** to V_{SAT+}
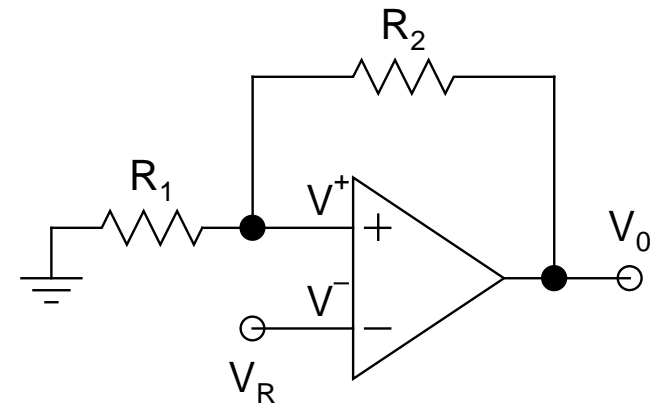
$$\Rightarrow V^+ = f' V_{SAT+}, \text{ where } f' = \text{feedback factor} = \frac{R_1}{R_1 + R_2}$$




- * Now, if V_R is *increased*, i.e., it's made *less negative*, then *zero*, and then *positive*, output can't change state till V^- becomes *greater* than V^+ , which is at fV_{SAT^+}
- * Once this happens, the output will immediately *toggle* to V_{SAT^-} , and remain there till V_R is reduced *below* fV_{SAT^-} (note that $V^+ = fV_{SAT^-}$ under this condition)
- * Thus, the circuit has *two stable states* at $\pm V_{SAT}$, and is hence known as a **bistable circuit**
- * For a *change of state* at the output, *appropriate trigger signal* (V_R) needs to be applied at the input


- * The value of V_R at which this change of state takes place is known as the ***threshold voltage*** of the **Schmitt Trigger**
- * The ***upper*** one is known as **threshold high** (V_{TH}) and is given by fV_{SAT+} , while the ***lower*** one is known as **threshold low** (V_{TL}) and is given by fV_{SAT-}
- * Note that for values of V_R ***in between*** V_{TL} and V_{TH} , the output is ***indeterminate*** (\because it can be ***either*** of $\pm V_{SAT}$), and depends on ***direction of change*** of V_R
- * $(V_{TH} - V_{TL})$ is known as the **Hysteresis Width (HW)**

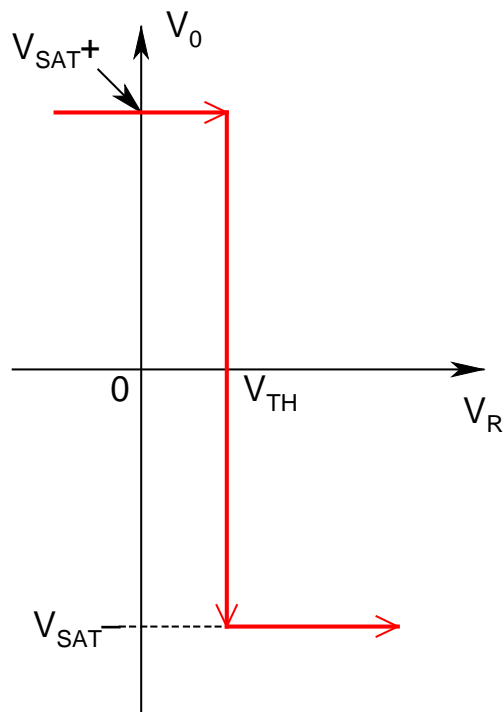

V_R Increasing

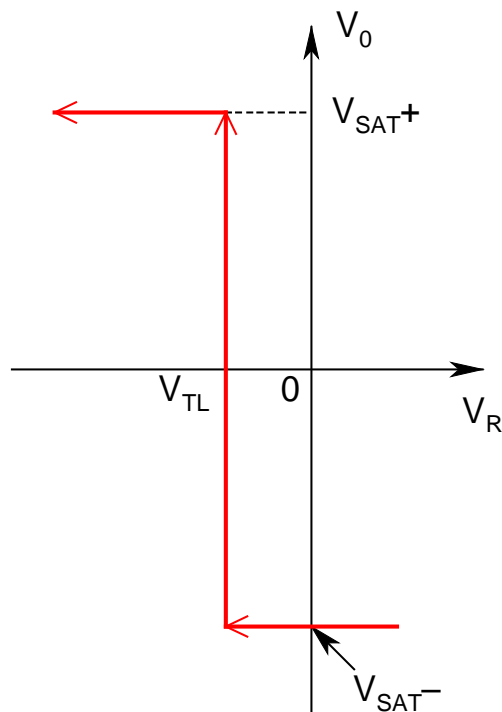

V_R Decreasing

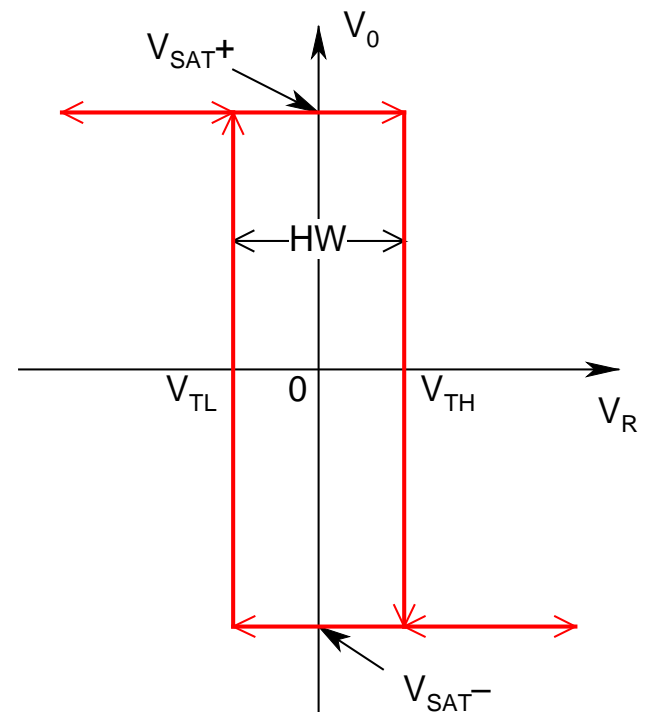

Overall VTC

- * The region bound by HW is known as the **dead zone** or **forbidden zone**
- * Note for $V_R > V_{TH}$, the output remains at V_{SAT^-} , while for $V_R < V_{TL}$, the output remains at V_{SAT^+}
 \Rightarrow Circuit known as **Inverting Schmitt Trigger**
- * Note that the *hysteresis characteristic* is absolutely *symmetric around zero*, i.e., $|V_{TL}| = V_{TH}$, since $|V_{SAT^-}| = V_{SAT^+}$, and f' is a constant
- * However, it is **not necessary** for a Schmitt Trigger to be always symmetric: there are ways to make it *asymmetric*

- * Since the *direction of change* of V_R has a profound impact on the outcome of the circuit, hence, this type of circuits is also known as *directional circuit*
- * Note that once the circuit has reached one of the *stable states*, V_R can be safely *grounded*, since it has *no impact* on the circuit any more
- * *For example*, if V_R becomes greater than V_{TH} , thus causing a change of state at the output from V_{SAT^+} to V_{SAT^-} , then the only way the output can be switched back to V_{SAT^+} is by reducing V_R below V_{TL}

- * Thus, **grounding** V_R would have absolutely ***no effect*** on the circuit once a ***transition*** has been achieved
- * Therefore, these circuits are considered to have a ***memory effect***, i.e., by observing the ***output*** at any given instant of time, the ***last input*** applied to the circuit can be easily assessed
- * Also, for values of V_R ***between*** V_{TL} and V_{TH} , the output could ***either*** be V_{SAT^+} or V_{SAT^-} , which would depend on the ***last input signal*** V_R that caused the ***transition*** — again it is a ***memory action***


Schmitt Trigger as an Effective Noise Suppressor:

* ***Recall:*** A ***comparator*** with $V_R = 0$ acts as a ***zero-crossing detector***

⇒ As soon as the input ***crosses zero***, the output ***changes state***

⇒ Thus, if there is ***noise*** present during the ***zero crossings*** of the input, then an absolutely ***unusable*** output results

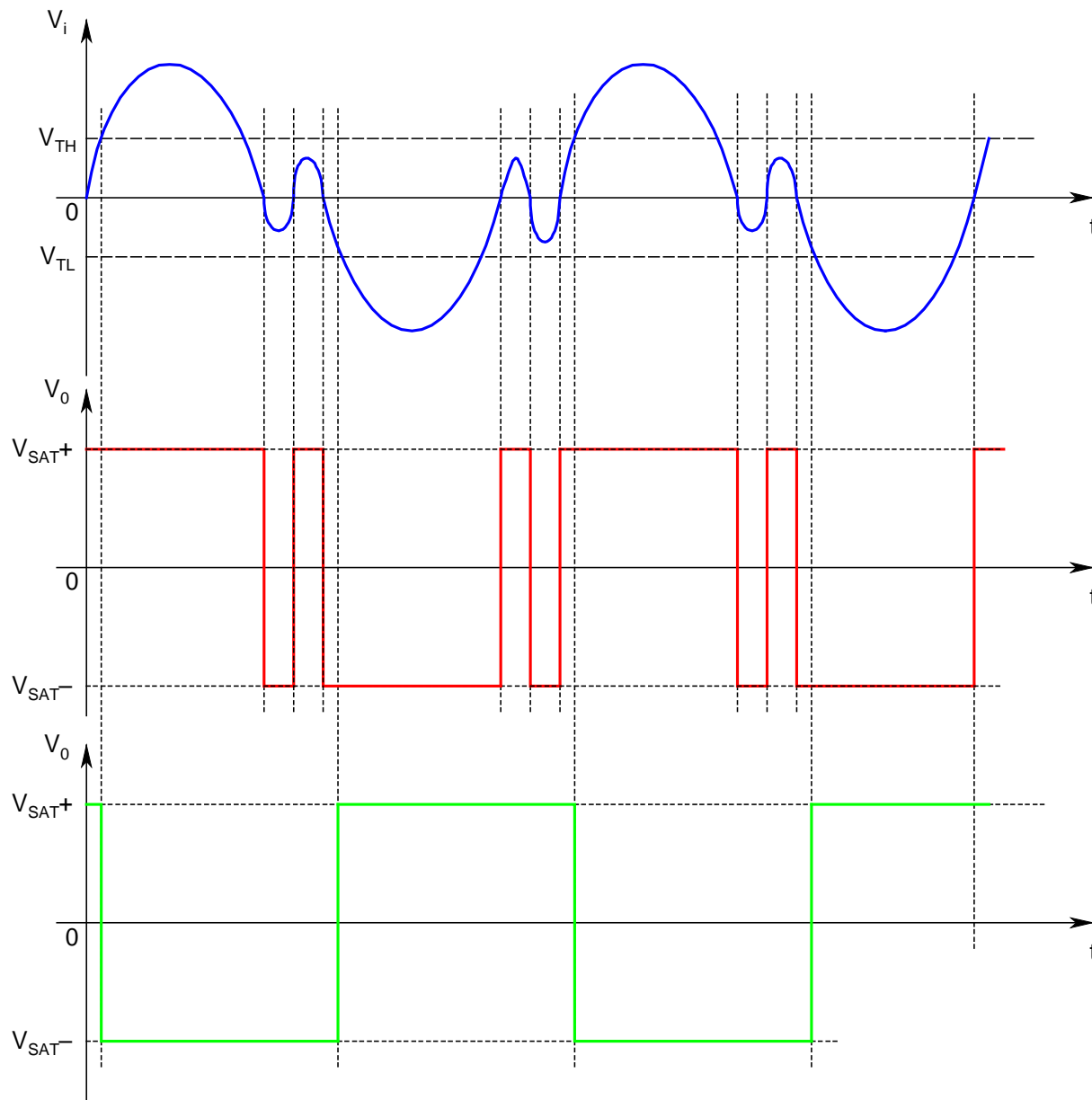* Now, if the same signal is applied in place of V_R to a ***Schmitt Trigger***, then the output will ***change state*** only when the signal ***crosses*** V_{TH} or V_{TL}



Input signal with
noisy zero crossings

Output obtained from a
non-inverting comparator
with $V_R = 0$: Totally
unusable with lots
of undesirable spikes

Output obtained from
an inverting Schmitt
Trigger: Absolutely clean



Non-Inverting Schmitt Trigger:

* Using *superposition*:

$$V^+ = \frac{R_2}{R_1 + R_2} V_R + \frac{R_1}{R_1 + R_2} V_0 \quad (1)$$

* Note that $V^- = 0$ (ground)

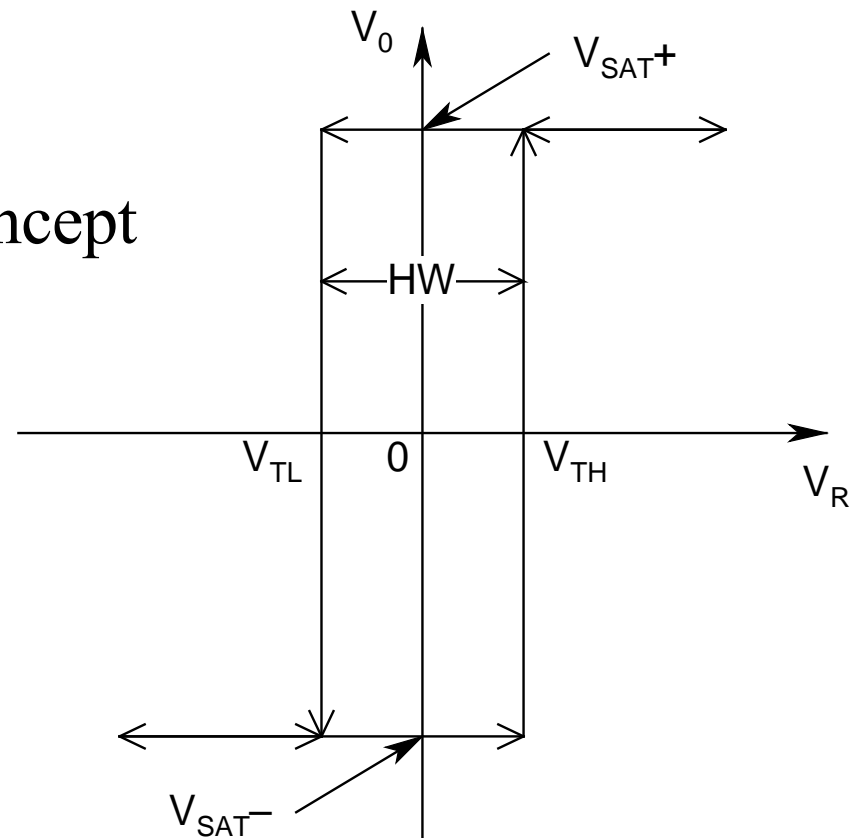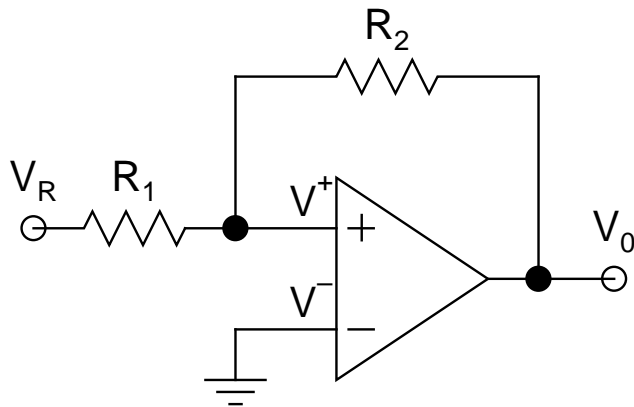* **Caution:** *Virtual Ground* concept cannot be used




- * Due to *positive feedback*, the output V_0 will be at V_{SAT^+} for $V^+ > V^-$, and at V_{SAT^-} for $V^- > V^+$
- * Now, with $V^- = 0$, if V_0 is at V_{SAT^+} , then *no positive value* of V_R can change the state of the output
 - \Rightarrow To switch V_0 to V_{SAT^-} , V^+ must be *pulled below ground* (which is the potential V^-), and from (1), it would be possible only if V_R goes below $-(R_1 / R_2) V_{SAT^+}$
 - \Rightarrow This corresponds to the *threshold low* (V_{TL}) of the circuit

- * Similarly, when V_0 is at V_{SAT^-} , *no negative value* of V_R can change the state of the output
 \Rightarrow To cause a change in the state of the output under this condition, V_R must be *more positive* than $-(R_1 / R_2) V_{SAT^-}$ (*Note: V_{SAT^-} is negative*)
 \Rightarrow This corresponds to the *threshold high* (V_{TH}) of the circuit
- * Thus, $V_{TH} = -f' V_{SAT^-}$, $V_{TL} = -f V_{SAT^+}$, $f' = R_1 / R_2$, and $HW = V_{TH} - V_{TL}$

- * From the VTC, the *non-inverting* behavior is obvious
- * Also, the hysteresis characteristic is *symmetric* around zero, however, as mentioned before, **it need not be**
- * Simplest way to make the hysteresis characteristic *asymmetric* is to attach a *reference voltage* V_I to the inverting terminal of the OA
 - \Rightarrow By properly choosing the *sign* and *magnitude* of V_I , the entire hysteresis characteristic can be *shifted* either to *first and fourth* or to *second and third* quadrants

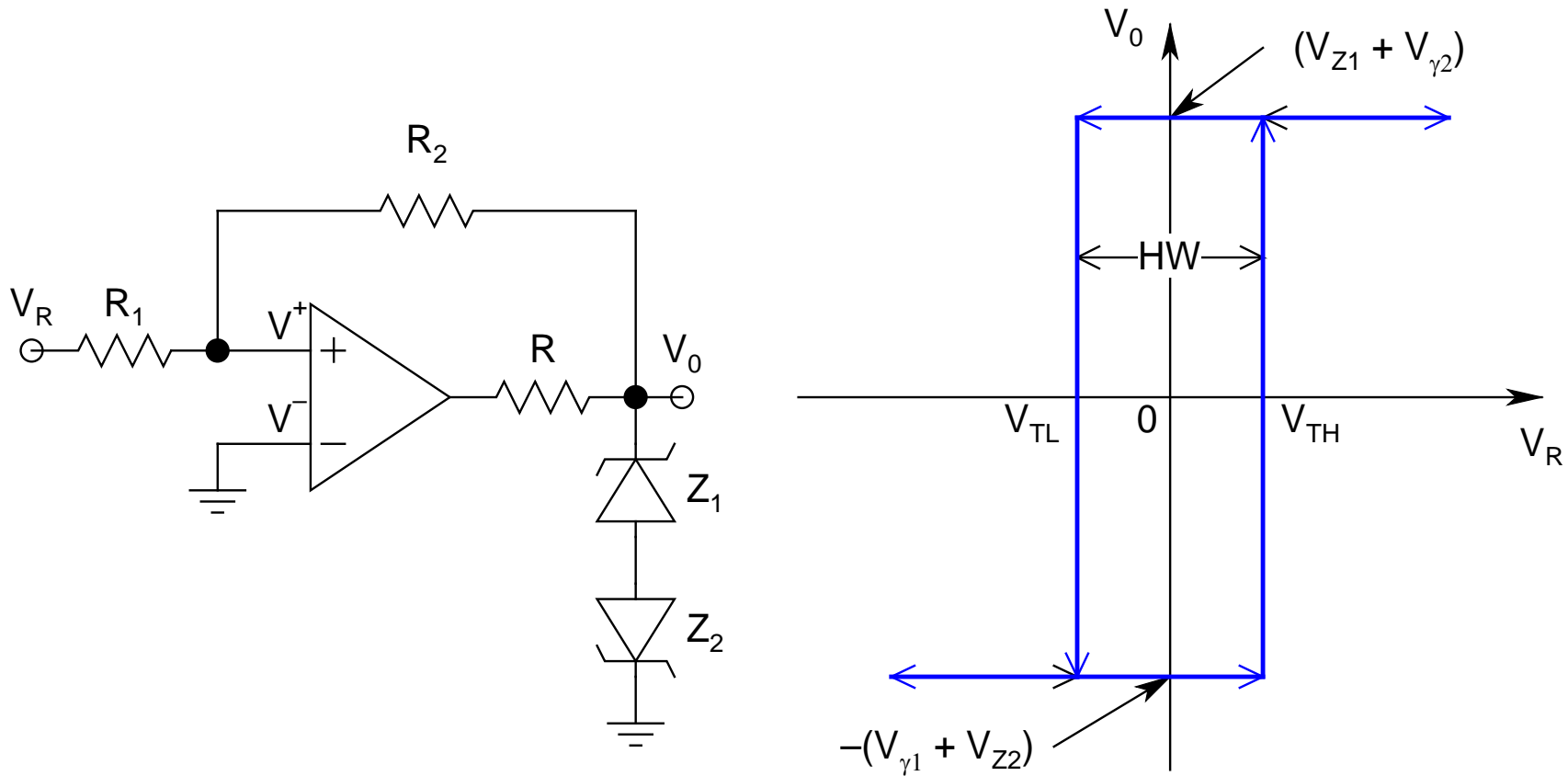Non-Inverting Schmitt Trigger With Output Clamp:



- * By putting a ***Zener diode clamp*** (identify Z_1 - Z_2 as a ***double-anode Zener***) at the output, V_0 can be made to swing between extremes ***other than the saturation voltages***
- * $V_{0,\max} = V_{Z1} + V_{\gamma2}$ (Z_1 under ***breakdown***, Z_2 under ***forward bias***)
- * $V_{0,\min} = -(V_{Z2} + V_{\gamma1})$ (Z_2 under ***breakdown***, Z_1 under ***forward bias***)
- * Quite useful circuit, with the output ***adjustable*** by a proper choice of the ***Zener breakdown voltages*** (it can even be made ***asymmetric***)

Waveform Generation:

- * A very important instrument in the lab is the ***Function Generator***
- * Capable of producing ***sinuoidal***, ***triangular***, and ***square*** waveforms
- * ***Sinusoidal waveforms*** are generated by ***Sinusoidal Oscillators***
- * ***Triangular*** and ***Square waves*** can be generated effectively using ***Schmitt Triggers***

Square-Wave Generation:


- * *Recall:* A *Schmitt trigger* circuit is essentially *bistable*, with both output states (V_{SAT^+} and V_{SAT^-}) being *stable states*, and a *triggering mechanism* is needed for the *change of state* to take place
- * Now, if somehow this *triggering mechanism* can be made *automatic*, then the output waveform would keep on *switching* between its two extremes *periodically*, without any further intervention

- * Thus, under such a condition, none of the output states are *stable states*, since they keep on *changing* with respect to time
- * Such circuits are known as *astable circuits*, since they do have *two output states*, however, **none of them are stable states**
- * An extremely popular *square-wave generator* circuit uses only three resistors and a capacitor, along with an OA

* **Note:** The circuit has *both* positive and negative feedback

* Due to the *positive feedback* present in the circuit, irrespective of the *negative feedback*, V_0 would be *saturated* at either V_{SAT^+} or V_{SAT^-} , depending on whether V^+ is greater than or less than V^- , respectively

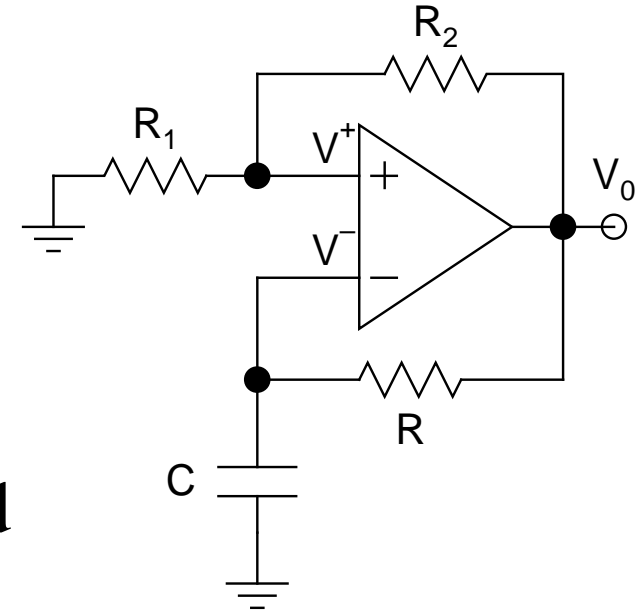
* Assume that at time $t = 0$, the capacitor is completely discharged, i.e., $V^- = 0$



- * Thus, for the result to be **consistent**, V_0 must be at $V_{SAT^+} \Rightarrow V^+ = f'V_{SAT^+} (> 0)$, with $f' = R_1/(R_1 + R_2)$
- * Now, for $t > 0$, C would start to **charge** through R, V^- would **rise**, attempting to reach its **final** maximum value of V_{SAT^+}
- * However, **this won't happen**, \because as soon as V^- **rises** above V^+ , which is at a constant potential of $f'V_{SAT^+}$, the output would **change state** to V_{SAT^-}
- * **Note:** $f'V_{SAT^+}$ is the **threshold high** (V_{TH}) of this circuit
- * Thus, V^+ would now become equal to $f'V_{SAT^-}$

- * The capacitor also would now start to *discharge* towards V_{SAT^-}
- * Similar to the previous situation, it won't be able to *discharge* all the way down to V_{SAT^-} , since as soon as V^- would *fall* below $f^+V_{SAT^-}$, the output would again *toggle* to V_{SAT^+}
- * *Note:* $f^+V_{SAT^-}$ is the *threshold low* (V_{TL}) of the circuit
- * These two processes of capacitor *charging* and *discharging* would continue *ad infinitum* and a *square wave* will be produced at the output, ranging between $\pm V_{SAT}$

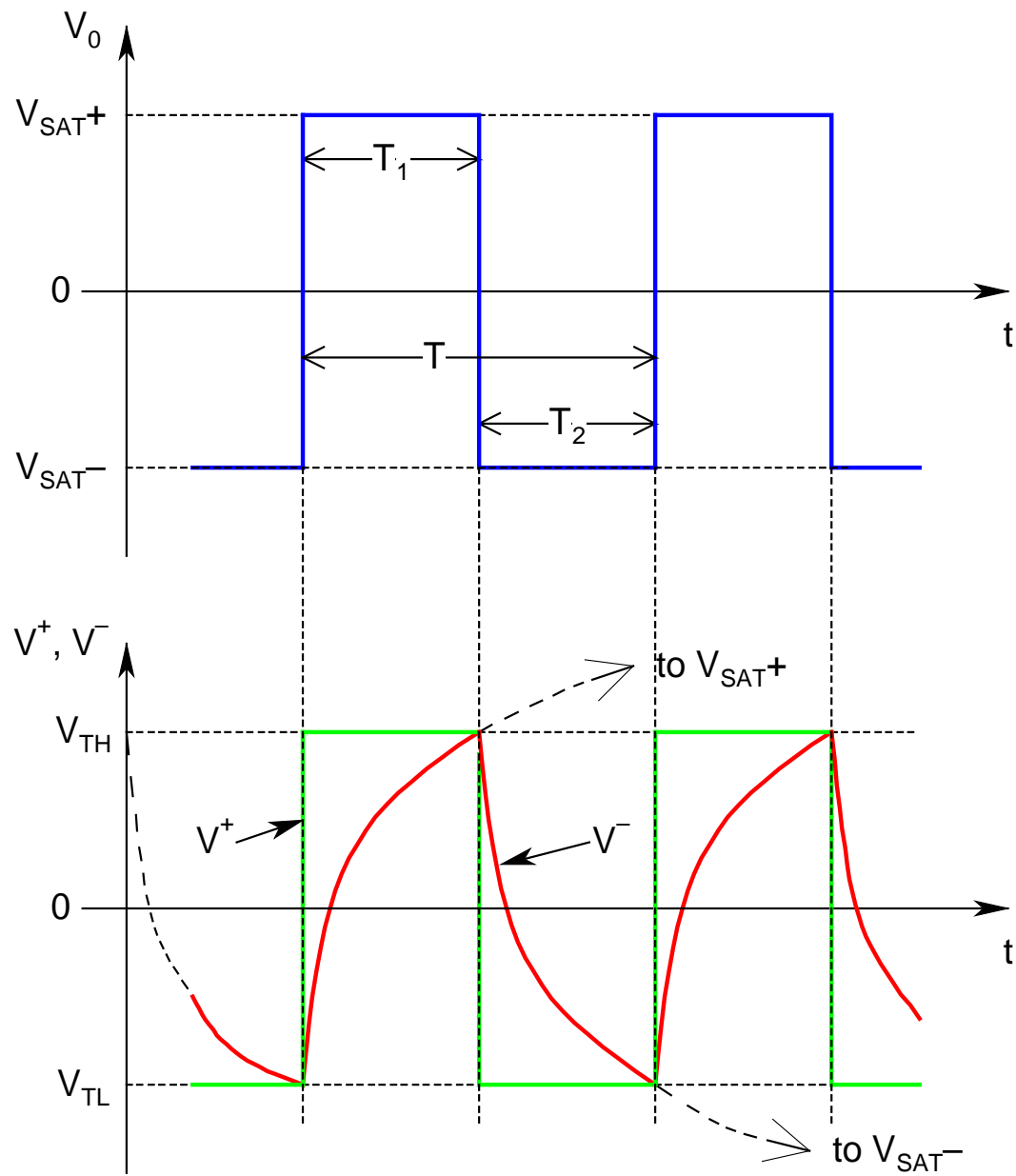- * Note that the circuit does not need *any source*: as soon as the *power supply* to the circuit is turned on, the *oscillations* would start, and a *square wave* will appear at the output
- * Refer to the figure on the next page:
 - T_1 : *On* (or *High*) *Time*
 - T_2 : *Off* (or *Low*) *Time*
 - $T (= T_1 + T_2)$: *Time Period*
 - $f (= 1/T)$: *Frequency*
 - $\delta (= T_1/T)$: *Duty Cycle*



Evaluation of T_1 and T_2 :

- * Use the familiar expression for *capacitor charging/discharging*:

$$v_c(t) = v_c(\infty) + [v_c(0) - v_c(\infty)] \exp(-t/\tau)$$

- * Note that the *time constant* $\tau = RC$

- * **For T_1 :** $v_c(0) = V_{TL}$, $v_c(\infty) = V_{SAT^+}$, and $v_c(T_1) = V_{TH}$

$$\Rightarrow T_1 = \tau \ln \left[\frac{1 - f V_{SAT^-} / V_{SAT^+}}{1 - f'} \right] = \tau \ln \left[\frac{1 + f'}{1 - f'} \right]$$

where we have assumed that $V_{SAT^+} = -V_{SAT^-}$

* **For T_2 :** $v_c(0) = V_{TH}$, $v_c(\infty) = V_{SAT^-}$, and $v_c(T_2) = V_{TL}$

$$\Rightarrow T_2 = \tau \ln \left[\frac{1 - f V_{SAT^+} / V_{SAT^-}}{1 - f'} \right] = \tau \ln \left[\frac{1 + f'}{1 - f'} \right]$$

where again we have assumed that $V_{SAT^+} = -V_{SAT^-}$

* Note that for *symmetric* saturation voltages, the on and off times are same, resulting in a **50%** duty cycle square wave


* **Frequency:**

$$f = \frac{1}{T} = \frac{1}{T_1 + T_2} = \frac{1}{2T_1} = \left(2\tau \ln \left[\frac{1 + f'}{1 - f'} \right] \right)^{-1}$$

- * Note that the output swings between $\pm V_{\text{SAT}}$
- * In order to obtain other swings, a ***double-anode Zener*** can be connected at the output
- * Also, the ***breakdown voltages*** of the Zeners can be chosen to be ***unequal***, which would produce different values of ***positive and negative amplitudes***, as well as ***duty cycle*** other than 50%
 - \Rightarrow Significant ***waveshaping***
- * ***Exercise:*** Assume that the positive and negative saturation voltages are V_1 and $-V_2$, find T_1 and T_2

Triangular-Wave Generation:

- * Note that with regard to the *square-wave* generator circuit, if τ is made *very large*, and/or f' is made *very small*, then the voltage waveform across the capacitor will be approximately *linear*, since it will traverse only a *very small part* of the exponential characteristic \Rightarrow ***Triangular-Wave Generation***
- * However, there is a much simpler way to generate triangular waves, which is basically a *non-inverting Schmitt Trigger* (with *symmetric* values of V_{TL} and V_{TH}) followed by an *integrator*

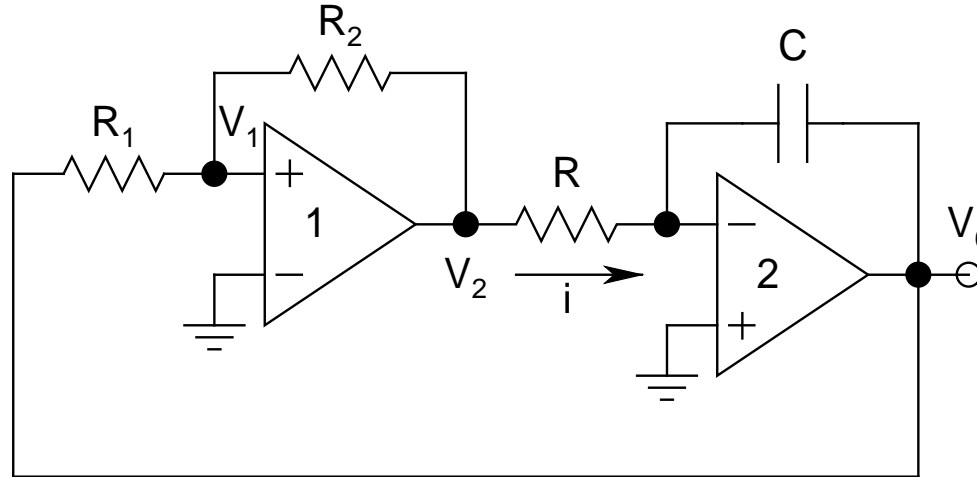


- * Identify OA1 as a *non-inverting Schmitt Trigger* with symmetric threshold, and OA2 as an *integrator*
- * Due to *positive feedback* present in OA1, V_2 will always be either at V_{SAT^+} or V_{SAT^-} , depending on whether V_1 is greater than or less than zero, respectively

- * Note also that OA2 is under *negative feedback*
 \Rightarrow Concept of *virtual ground* can be applied, and the *inverting terminal* of OA2 is effectively *ground*
- * Assume that at some arbitrary time, the capacitor was completely discharged (i.e., $V_0 = 0$), and V_2 is at V_{SAT^+}
- * This would push a *constant current* $i = V_{SAT^+} / R$ through R , which would flow through the capacitor as well
- * Note that it is a case of *constant current charging* of a capacitor, which will lead to a *linear* change in voltage across it

- * Thus, $dV_0/dt = -i/C = -V_{SAT^+}/(RC)$
 $\Rightarrow V_0$ *decreases linearly* with time, producing a
ramp waveform, with a slope of $-V_{SAT^+}/(RC)$
- * Note that V_0 is fed back to the *Schmitt trigger* as
its input, which has a *threshold low* $V_{TL} = -f'V_{SAT^+}$,
with $f' = R_1/R_2$
- * \therefore As soon as V_0 falls below V_{TL} , the *Schmitt Trigger*
would get *triggered*, and V_2 would *toggle* to V_{SAT^-}
- * This would immediately *change the sign* of the current
 i , however, if the saturation voltages are *symmetric*,
then its *magnitude* would remain the *same*

- * Now, C would start to ***discharge*** with this constant current, and V_0 would increase ***linearly*** with time, with a slope of $-V_{SAT^-}/(RC)$
- * It would rise all the way to the ***threshold high*** V_{TH} ($= -fV_{SAT^-}$), and again a ***change of state*** would take place, with V_2 ***swinging back*** to V_{SAT^+}
- * This sequence of events would keep on ***repeating*** itself, and at the output, we would get a clear ***triangular*** waveform, swinging between V_{TL} and V_{TH}

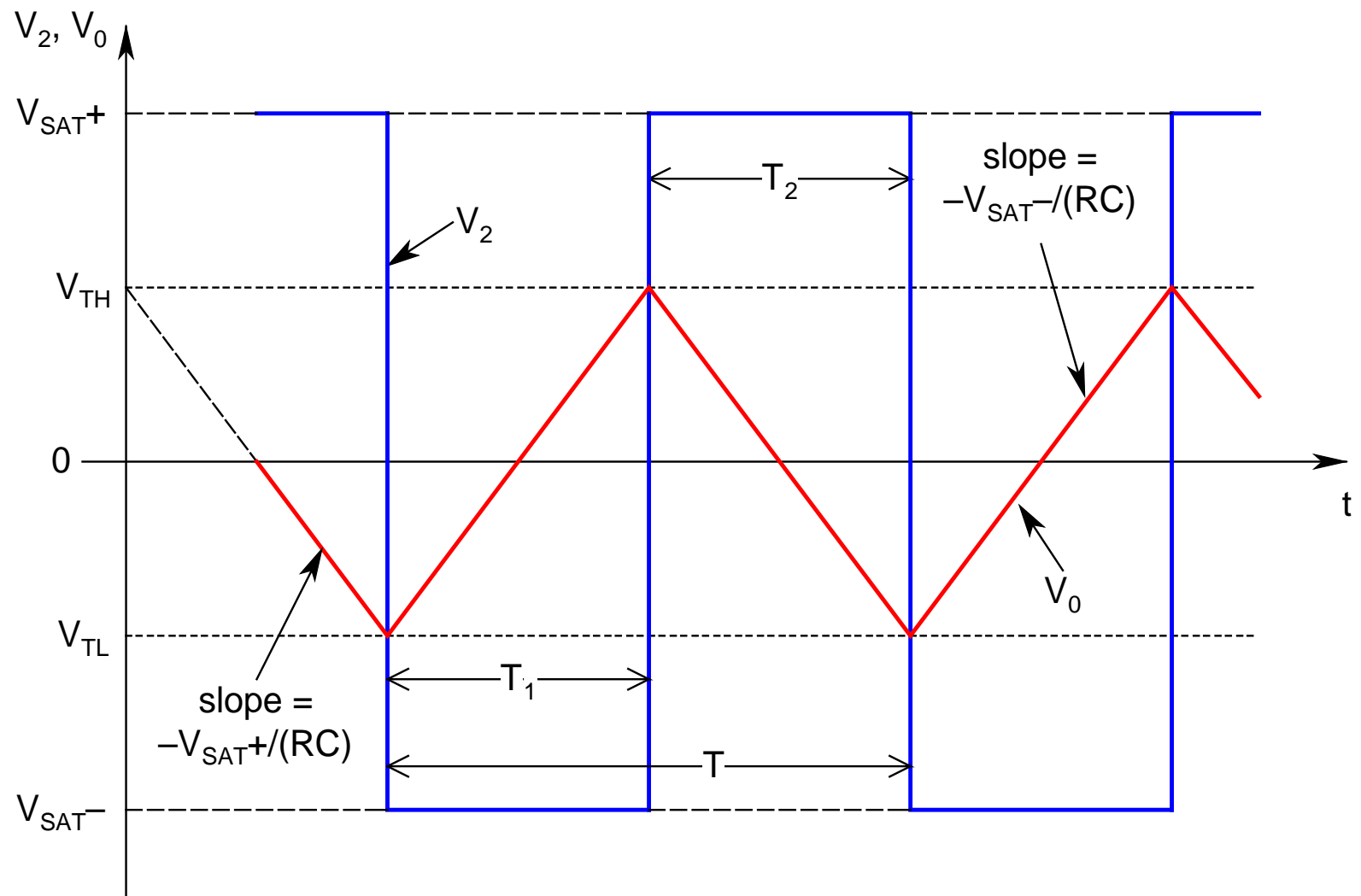

- * **Note:** When $V_2 = V_{SAT^+}$, V_0 *decreases linearly* from V_{TH} to V_{TL} with a slope of $-V_{SAT^+}/(RC)$
- * On the other hand, when $V_2 = V_{SAT^-}$, V_0 *increases linearly* from V_{TL} to V_{TH} with a slope of $-V_{SAT^-}/(RC)$
- * Thus, *positive ramp time duration:*

$$\frac{V_{TH} - V_{TL}}{T_1} = -\frac{V_{SAT^-}}{RC} \quad \Rightarrow \quad T_1 = RC \times \left(\frac{V_{TH} - V_{TL}}{-V_{SAT^-}} \right)$$

- * Similarly, *negative ramp time duration:*


$$\frac{V_{TL} - V_{TH}}{T_2} = -\frac{V_{SAT^+}}{RC} \quad \Rightarrow \quad T_2 = RC \times \left(\frac{V_{TH} - V_{TL}}{V_{SAT^+}} \right)$$

- * **Note:** For symmetric saturation voltages, a **50%** duty cycle triangular waveform results
- * **Time Period** $T = T_1 + T_2$
- * **Oscillation Frequency** $f = 1/T$
- * Note that this circuit also **does not need any source**
 - As soon as the **power supply** is turned on, the **oscillations** would start, and would continue **ad infinitum** till the **power supply** is turned off

Sinusoidal Oscillators:

- * *Note:* The *square- and triangular-wave generator circuits* discussed earlier *do not need any source*
 - As soon as the *power supply* to the circuit is turned on, the *oscillations* start, and continue till the *power supply* is turned off
 - These circuits are also known as *oscillators*
- * However, generating *sinusoidal oscillations* is a totally different ball game
- * *Sinusoidal Oscillators* achieve this task

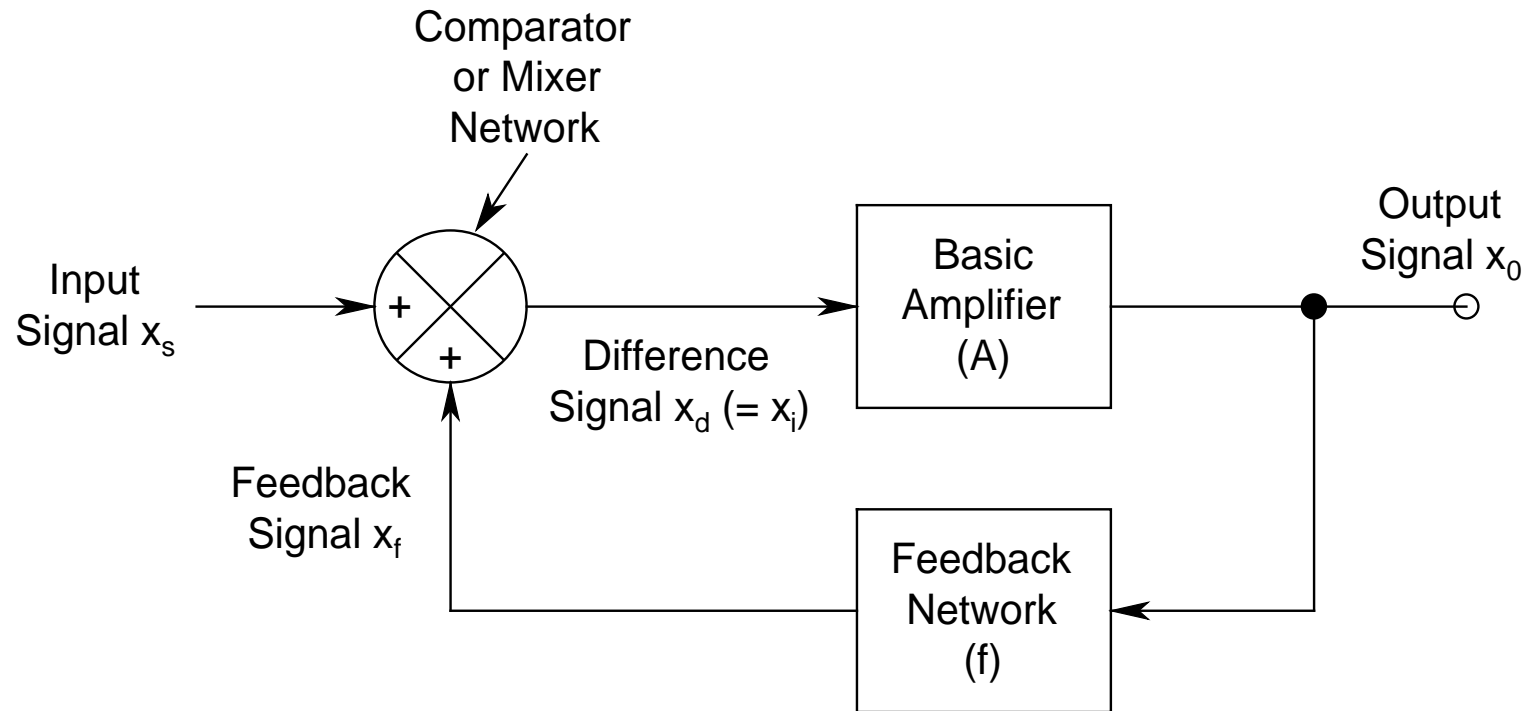Concept of Oscillation : Positive Feedback:



A: Gain of the Basic Amplifier

f: Feedback Factor of the Feedback Network

$$x_0 = Ax_i, x_f = fx_0, x_i = x_d = x_s + x_f$$

* *Gain with feedback:*

$$\begin{aligned} A_f &= \frac{X_o}{X_s} = \frac{X_o}{X_i} \frac{X_i}{X_s} = A \frac{X_s + X_f}{X_s} = A \left(1 + \frac{X_f}{X_s} \right) \\ &= A \left(1 + \frac{X_f}{X_o} \frac{X_o}{X_s} \right) = A (1 + fA_f) \\ \Rightarrow A_f &= \frac{A}{1 - fA} \end{aligned}$$

- * An extremely interesting relation: **If $fA \rightarrow 1$, $A_f \rightarrow \infty$, and output appears without any input!**
- * This is what *oscillators* are all about: Make fA [known as the *Loop Gain* (L)] approach *unity*!

Conditions for Oscillation : Barkhausen's Criteria:

- * Note that both f and A are *functions of frequency* (ω)
- * Therefore, there may be a *certain frequency* (ω_0), at which: $L(j\omega_0) = f(j\omega_0) A(j\omega_0) = 1$
- * Note that at this frequency (ω_0), the *gain* of the system would be *infinite*, and the signal will *self-regenerate*, without the need for any external input
- * Thus, ω_0 becomes the *oscillation frequency*
- * **Also, since this oscillation happens only for a particular frequency (ω_0), hence, a pure sinusoidal waveform results**

* German physicist *Heinrich Georg Barkhausen* summarized this condition into two criteria, which came to be known as **Barkhausen's Criteria**:

- $|L(j\omega_0)| = 1$ and $\angle L(j\omega_0) = 0^\circ$

* Barkhausen's Criteria in words:

- **For a positive feedback system to oscillate, the magnitude of the loop gain must at least be unity, and the total phase shift around the loop should be 0° (or 360°)**


- * Note that once the oscillations start, it cannot be stopped without turning the power supply off
- * At ω_0 , if $|L| < 1$, then with each pass around the loop, the *amplitude* of the output signal would keep on *decreasing*, and eventually, it will *die down* on its own \Rightarrow **Under this condition, sustained sinusoidal oscillation is impossible to achieve**
- * On the other hand, at ω_0 , if $|L| > 1$, then with each pass around the loop, the output signal would keep on *increasing*, and will eventually get *limited* by the power supply voltages \Rightarrow **Creates distorted output**

- * $|L|$ *exactly equal to unity is a risky proposition, since component values drift with age and temperature*
- * Practical oscillator circuits operate with $|L|$ *slightly greater than unity*, which lets the oscillations *build up*, and then control it using *automatic gain control* (AGC) circuit
- * Two very popular OA-based *sinusoidal oscillators*:
 - **Wien-Bridge Oscillator**
 - **Phase-Shift Oscillator**

Wien-Brige Oscillator:

- * Identify that the circuit has ***both positive and negative feedback***
- * Identify that the ***non-inverting terminal*** with a potential of V_x is the ***positive feedback node***
- * In the absence of the positive feedback, the circuit is simply a ***non-inverting amplifier***, with the gain (A) given by:
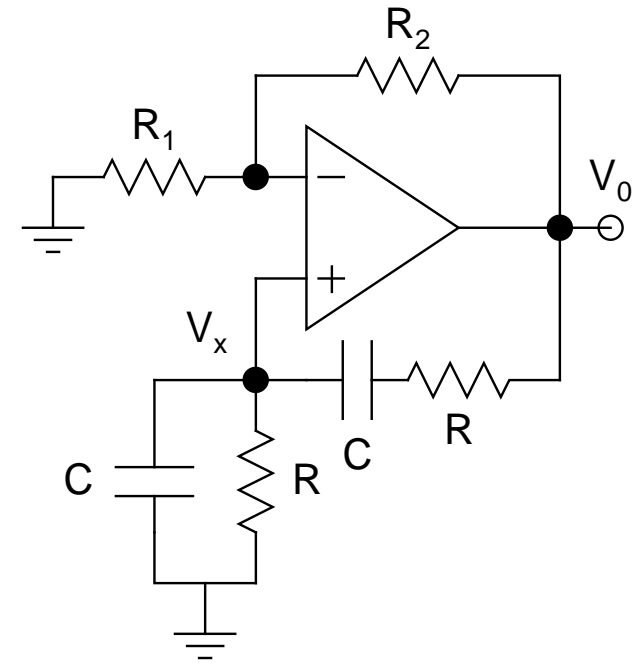
$$A = \frac{V_0}{V_x} = 1 + \frac{R_2}{R_1}$$



* ***Impedance*** of series RC circuit:

$$Z_1 = R + 1/(j\omega C)$$

* ***Impedance*** of parallel RC circuit:

$$Z_2 = R \parallel \left(\frac{1}{j\omega C} \right) = \frac{R}{1 + j\omega RC}$$

* Thus, the ***feedback factor***:

$$f = \frac{V_x}{V_0} = \frac{Z_2}{Z_1 + Z_2} = \frac{1}{3 + j[\omega RC - 1/(\omega RC)]}$$

* Hence, the ***loop gain***:

$$L = fA = \frac{1 + R_2/R_1}{3 + j[\omega RC - 1/(\omega RC)]}$$

*** *For sustained sinusoidal oscillations, Barkhausen's criteria must be satisfied***

\Rightarrow L must be a real number with zero phase angle

\Rightarrow The imaginary part of L must vanish

\Rightarrow Gives the *oscillation frequency* $\omega_0 = 1/(RC)$

*** Also, $|L|$ must equal unity**

$\Rightarrow R_2/R_1 = 2$


*** Actually, R_2/R_1 is made *slightly larger than 2* to take care of the drift of component values with temperature and age \Rightarrow *Amplitude builds up and eventually gets controlled by the AGC circuit***

Phase-Shift Oscillator:

- * Interesting to note that the circuit uses *negative feedback* with the non-inverting terminal grounded
- * Thus, the circuit is simply an *inverting amplifier*, with the gain (A) of the *basic amplifier* given by:

$$A = \frac{V_0}{V_x} = -\frac{R_1}{R}$$

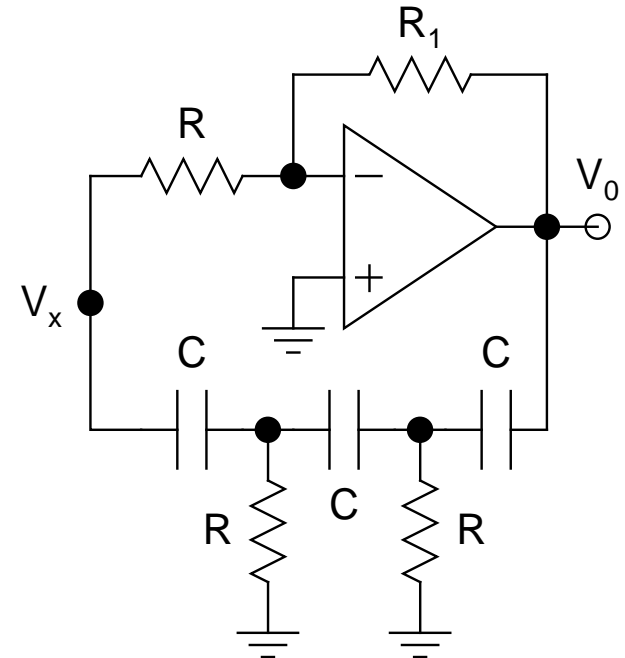- * **Note the negative sign in front, which implies 180° phase shift between V_x and V_0**



- * *Note also that the feedback path consists of three RC-sections*
- * **If each of these sections contribute a phase shift of 60° , then the total phase shift of the feedback path will be 180° , which would result in 0° phase shift for the loop gain (L)**
- * The *feedback factor* (f):

$$f = \frac{V_x}{V_0} = \frac{(\omega RC)^3}{\omega RC \left[(\omega RC)^2 - 5 \right] + j \left[1 - 6(\omega RC)^2 \right]}$$

*** Now, for L to be real, the imaginary part of f must vanish at the oscillation frequency ω_0**

$$\Rightarrow \omega_0 = \frac{1}{RC\sqrt{6}}$$

*** At ω_0 , $f = -1/29$**

*** This negative sign, implying a phase shift of 180° , coupled with the phase shift of 180° of A, makes the total phase of L to be 0°**

\Rightarrow *One part of Barkhausen's criteria satisfied*

* L at ω_0 :

$$L = fA = \left(-\frac{1}{29}\right) \times \left(-\frac{R_1}{R}\right) = \frac{R_1}{29R}$$

which should be slightly larger than unity

* Thus, **R_1** should be made slightly larger than **$29R$**

* This would *initiate the oscillations*, which will *tend to blow up*

\Rightarrow **Amplitude needs to be controlled by AGC circuit**

* Typical *oscillation frequency* for both these oscillators \sim *tens of Hz to hundreds of kHz*